ELECTRONICS TODAY INTERNATIONAL Dec. 1980 61.60*NZ\$1.75

GOLD DETECTOR

Can discriminate 'trash' from 'treasure'

BUILD A pH METER

Keep your pool or fish tank healthy; lots of other uses etc. **Voltage Regulators**-circuits and techniques

Learn BASIC

Pot core coil design


Hi-Fi Reviews:

Marantz ST500 FM/AM tuner

PAS-30 loudspeakers from G.R.D.

Will de l'Inter

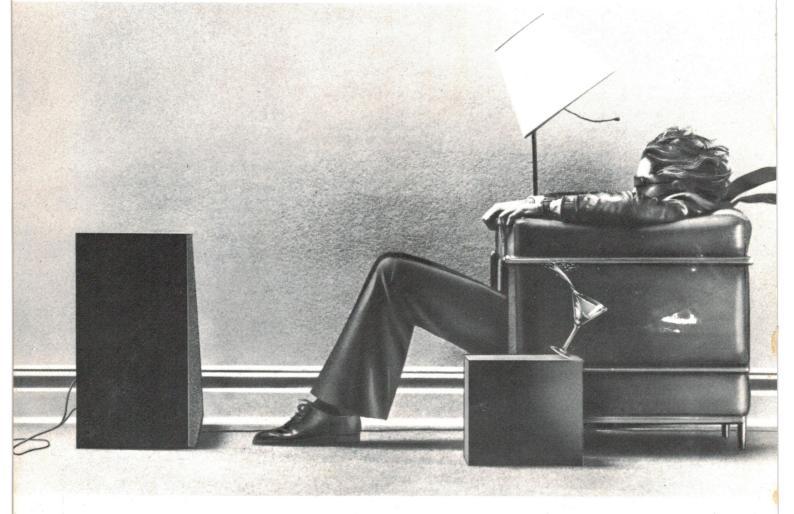AFTER 500 PLAYS OUR HIGH FIDELITY TAPE STILL DELIVERS HIGH FIDELIT



If your old favourites don't sound as good as they used to, the problem could be your recording tape.

Some tapes show their age more than others. And when a tape ages prematurely, the music on it does too.

What can happen is, the oxide particles that are bound onto tape


loosen and fall off, taking some of your music with them.
At Maxell, we've developed a binding process that helps to prevent this. When oxide particles are bound onto our tape, they stay put. And so does your music.

So even after a Maxell recording is 500 plays old, you'll swear it's not a play over five.

HAGEMEYER

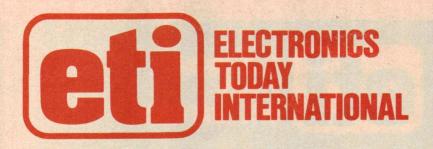For further information on Maxell Tapes write to Maxell Advisory Service, P.O. Box 307, North Ryde, N.S.W. 2113





QUICK INDEX

FEATURES:

16 pH — the Acid Test

104 Back Door into BASIC

114 Matrox Video Boards Reviewed

121 Micros Invade the Communications World

101 Win a ZX80 Computer & Software

87 Special Offer: C10 Data Cassettes

SOUND SECTION:

135 Sound News

150 The Craft of the Speaker Box Maker

156 Marantz ST500 FM/AM tuner review

168 G.R.D. PAS30 Loudspeakers reviewed

138 Mail Order 'Disco Lite'

PROJECTS & TECHNICAL

23 572: Digital pH Meter

39 1500: Discriminating Metal Detector

57 597: Emergency Lighting Unit

65 Lab Notes: Voltage Regulators

74 Designing Potcore Inductors

52 Short Circuits: Thermatic Fan Controller

80 Ideas For Experimenters

85 Shoparound

145 PC Board Patterns

WE HAVE RECEIVED quite a few enquiries over the past six months or so concerning projects which have appeared in the British edition of ETI, which have not subsequently appeared in the Australian edition of ETI. Indeed, some callers have become quite irate, despite our explanations! Firstly, we should put readers in the picture about our relationship with the overseas editions of ETI.

ETI originated in Australia in 1971 under Modern Magazines and a British edition was started by us a year later. German, Dutch and Canadian editions followed in 1976 and 1977. There was a French edition produced for a while but that was sold and has since been converted to a hi-fi magazine.

Australia's ownership and interests in the overseas editions were sold by the previous owners of Modern Magazines in June 1978. Since that date the overseas editions have been autonomous, although some material is exchanged between the various editions. The majority of projects originated by ETI Australia are re-published in the overseas editions. Almost all the projects in the Canadian edition, for example, are taken from ETI Australia.

The UK edition of ETI is not available in Australia — nor ours in the UK — owing to pre-existing agreements. However, it seems that, by one means or another, some Australian readers have become aware of projects published in the British edition but not published in ETI Australia.

Naturally, we exchange copies of each issue with the overseas editions. *Every* project originated overseas we consider for republication here — and we do that with a great deal of care: we consider the usefulness and possible popularity of the project, whether we have done something similar in the past, are the techniques new and/or interesting, what about component availability? The latter is particularly important. That's generally the reason why we don't (can't!) republish a project from an overseas edition. So many components, particularly ICs, available in Europe are just not available here. Often we consider finding some other way around this problem, but it generally means re-designing the project and in so many cases, because of the special devices used, the re-design is either impossible or the project becomes too expensive to the end user — you. We often go to great lengths, and spend considerable time, trying to find sources of components for would-be popular projects from our overseas editions. Sometimes we're successful, sometimes not.

Those projects we do take from overseas editions we build up in our own laboratory and completely test out. Sometimes we have to modify pc boards to suit locally available components (relays, cases, meters etc) and the text is generally rewritten and additional material included. In fact, we once so changed a project that we'd taken from the UK edition that they accidentally re-published it some months after their original project appeared!

If you come to hear about a project that one of our overseas editions has done, but which has not appeared in ETI Australia, rest assured we've looked at it closely and we're either preparing it for publication or it's been shelved until special components can be obtained.

The best wishes of the season to all our readers and advertisers.




Rogh Dann

Roger Harrison Editor

advertisers

A.P. Products	3, 17
Air New Zealand	3, 17
Ampec Electronics	: 18
Audio Engineers	. 18 152 170
Aust. Guarantee Corp	170
All Electronic Components Applied Technology	119
Applied Technology	119
A&R Soanar	100
Auditec Aust.	124
Audio Kits	174
Audio Kits	. 68
Amscat Systems	. 68
Autotron Aust.	. 48
Advanced Electronic Systems	154
Barratt Lighting	3:4
Bose Australia	103
Belle Lumiere	163 123 174
Belle Lumiere Bright Star Crystals Box Hill Tech. Consolidated Marketing 30, 31, C&K Electronics	. 64 173 120
Box Hill Tech	173
Consolidated Marketing 30, 31,	, 120
C.I.S.A	. 22
Computerland in Melbourne	126
CPI	125
Computer Imports	. 84
Commodore Aust	. 92
Chadwick Audio	. 92
Cooper Tools	. 94
Computer Country	110
Compucom	103 173
Dick Smith 36.37.56.62 68 70	0.81
96,109,112,113, 118,129,166	.167
Cleftronics	. 82
David East	. 29
Delsound	
D.J. Gillin	174
Daneva Control	. 88
Ellistronics Wholesale	8. 79
Electro-Voice	148
Electronic Agencies	. 60
Emona 68, 108,	127
Electrocraft	154
Edible Electronics	110
Energy Control	173
Energy Control	173
Energy Control Ferguson Transformers Freedman Electronics John F. Rose	173
Energy Control	173
Energy Control	173 . 54 153 . 33 147
Energy Control	173 . 54 153 . 33 147 179 134
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust Hitachi Ltd. Looky Video	173 . 54 153 . 33 147 179 134
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust Hitachi Ltd. Looky Video	173 . 54 153 . 33 147 179 134 143
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hidachi Sales Aust. Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust.	173 .54 153 .33 147 179 134 .29
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust. Maruni Corp. Maruni Corp.	173 . 54 153 . 33 147 179 134 143
Energy Control Ferguson Transformers. Freedman Electronics John F. Rose Jaycar Hagemeyer	173 . 54 153 . 33 147 179 134 6 140 139 28
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Litachi Sales Aust Hitachi Ltd Looky Video McWilliams Wines Marantz Aust Maruni Corp. Microtrix Micro 80	173 . 54 153 . 33 147 179 134 . 29 6 139 28
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Litachi Sales Aust Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust Maruni Corp. Microtrix Microt 80 Mensa Computers Marangay	173 . 54 153 . 33 147 179 134 143
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Litachi Sales Aust Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust Maruni Corp. Microtrix Microt 80 Mensa Computers Marangay	173 . 54 153 . 33 147 179 134 143
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 11, Microtrix, Micro 80 Mensa Computers Magnavox McGills Newsagency	173 . 54 153 . 33 147 179 134 143
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 11, Microtrix. Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House	173 153 147 173 147 134 149 140 139 140 161 107
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 11, Microtrix. Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House	173 153 147 173 147 134 149 140 139 140 161 107
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust Maruni Corp. Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design National Panasonic	173 153 147 173 147 134 149 140 139 140 161 107
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 11, Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi	173 153 147 173 147 134 149 140 139 140 161 107
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 11, Microtrix, Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Nothopont Hi Fi Philips Industries Pre Pak.	173 153 147 173 147 134 149 140 139 140 161 107
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 11, Microtrix, Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Nothopont Hi Fi Philips Industries Pre Pak.	173 153 147 173 147 134 149 140 139 140 161 107
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust. Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust. Maruni Corp. Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways	173 153 147 173 147 134 149 140 139 140 161 107
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 11, Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving 50.51.	173 . 534 . 147 . 179 . 143 . 28 . 28 . 161 . 139 . 180 . 147 . 139 . 147 . 139 . 147 . 139 . 147 . 139 . 147 . 147 . 157 . 157
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust. Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust. Maruni Corp. Microtrix. Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Rod Irving Rod Irving Rod Oparts Rod Irving Rod Irving Rod Oparts	173 . 153 . 143 . 143 . 140 . 14
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust. Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust. Maruni Corp. Microtrix. Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Rod Irving Rod Irving Rod Oparts Rod Irving Rod Irving Rod Oparts	173 .543 .143 .293 .288 .996 .161 .127 .110 .138 .147 .159 .159 .151 .111 .143
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 11, Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving. 50, 51, Radio Parts Radio Pespatch Resco P/L Stuart Alexander	173.1543.147.1343.1447.1329.99.1611127.1555.151111.147.1555.1551.1551
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust Maruni Corp. Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic A'Asia National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Radio Despatch Radio Despatch Radio Despatch Resco P/L Stuart Alexander Sony Australia 131	173431 1437 13431 1439 1439 1439 1439 1439 1439 143
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust Maruni Corp. Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic A'Asia National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Radio Despatch Radio Despatch Radio Despatch Resco P/L Stuart Alexander Sony Australia 131	173431 1437 13431 1439 1439 1439 1439 1439 1439 143
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust Maruni Corp. Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic A'Asia National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Radio Despatch Radio Despatch Radio Despatch Resco P/L Stuart Alexander Sony Australia 131	173431 1437 13431 1439 1439 1439 1439 1439 1439 143
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust Maruni Corp. Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic A'Asia National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Radio Despatch Radio Despatch Radio Despatch Resco P/L Stuart Alexander Sony Australia 131	173431 1437 13431 1439 1439 1439 1439 1439 1439 143
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust Maruni Corp. Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic A'Asia National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Radio Despatch Radio Despatch Radio Despatch Resco P/L Stuart Alexander Sony Australia 131	173431 1437 13431 1439 1439 1439 1439 1439 1439 143
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust Maruni Corp. Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic A'Asia National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Radio Despatch Radio Despatch Radio Despatch Resco P/L Stuart Alexander Sony Australia 131	1754334 177943434 11398 11320 11320 11487 11554 11111 11320 11479 11554
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust. Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust. Maruni Corp. Microrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic A'Asia National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Radio Despatch Radio Despatch Resco P/L Stuart Alexander Sony Australia Spectrum Lighting ME Sons House Sansul Speetronics Sevien Lighting	1754334 177943434 11398 11320 11320 11487 11554 11111 11320 11479 11554
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 111, Microtrix. Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving 50, 51, Radio Parts Radio Despatch Resco P/L Stuart Alexander Sony Australia. 131, Spectrum Lighting SM Electronics 102, Systems Automation 88 Sansul Speedy Communications Sevien Lighting S.I. Microcomputers Scone I abovatories	1754334 177943434 11398 11320 11320 11487 11554 11111 11320 11479 11554
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 111, Microtrix. Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving 50, 51, Radio Parts Radio Despatch Resco P/L Stuart Alexander Sony Australia. 131, Spectrum Lighting SM Electronics 102, Systems Automation 88 Sansul Speedy Communications Sevien Lighting S.I. Microcomputers Scone I abovatories	1754334 177943434 11398 11320 11320 11487 11554 11111 11320 11479 11554
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 111, Microtrix. Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving 50, 51, Radio Parts Radio Despatch Resco P/L Stuart Alexander Sony Australia. 131, Spectrum Lighting SM Electronics 102, Systems Automation 88 Sansul Speedy Communications Sevien Lighting S.I. Microcomputers Scone I abovatories	1754334 177943434 11398 11320 11320 11487 11554 11111 11320 11479 11554
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 111, Microtrix. Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving 50, 51, Radio Parts Radio Despatch Resco P/L Stuart Alexander Sony Australia. 131, Spectrum Lighting SM Electronics 102, Systems Automation 88 Sansui Speedy Communications Sevlen Lighting S.I. Microcomputers Scope Laboratories Small Bus. Computers Starcross Scientific Software Source.	17543371179 11439311439311439311631311631311631311631311631316313
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust. Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust. Maruni Corp. Microrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Radio Despatch Radio Despatch Resco P/L Stuart Alexander Sony Australia Spectrum Lighting SM Electronics Systems Automation Sevlen Lighting SM Electronics Sevlen Lighting SN-L Microcomputers Scope Laboratories Small Bus. Computers Starcross Scientific Software Source T.C.T. Micro Design	17543-1479 11433-1479 11433-1479 11439-11439 11439 11439-11439 114
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer. 2. Hitachi Sales Aust. Hitachi Ltd. 142, Looky Video McWilliams Wines Marantz Aust. Maruni Corp. 11, Microtrix. Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic A'Asia National Pana	17543-1479 11433-1479 11433-1479 11439-11439 11439 11439-11439 114
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust. Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust. Maruni Corp. Microrix. Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic A'Asia National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Radio Despatch Radio Despatch Resco P/L Stuart Alexander Sony Australia. Spectrum Lighting SM Electronics Systems Automations Sevien Lighting S.I. Microcomputers Seven Lighting S.I. Microcomputers Scope Laboratories Small Bus, Computers Starcross Scientific Software Source. T.C.T. Micro Design The Bulletin Tasman Electronics The Logic Shop	173 153 147 179 143 128 161 110 128 161 110 173 110 173 110 173 110 110 110 110 110 110 110 110 110 11
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust. Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust. Maruni Corp. Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic A'Asia National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Radio Parts Radio Despatch Resco P/L Stuart Alexander Sony Australia. Spectrum Lighting SM Electronics Sevien Lighting SM Electronics Sevien Lighting SI. Microcomputers Scope Laboratories Small Bus, Computers Starcross Scientific Software Source. T.C.T. Micro Design The Bulletin Tasman Electronics The Logic Shop T. A.A. R.C.	173 153 147 179 143 128 161 110 128 161 110 173 110 173 110 173 110 110 110 110 110 110 110 110 110 11
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust. Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust. Maruni Corp. Microrix. Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic Northpoint Hi Fi Philips Industries Pre Pak. Plessey Qantas Airways Rod Irving Radio Despatch Radio Despatch Radio Despatch Resco P/L Stuart Alexander Sony Australia. Spectrum Lighting SM Electronics Systems Automations Sevlen Lighting S.I. Microcomputers Scope Laboratories Small Bus. Computers Starcross Scientific Software Source T.C.T. Micro Design The Bulletin Tasman Electronics The Logic Shop T.A.A.R.C. University Graham Inst.	173 153 147 179 143 128 161 110 128 161 110 173 110 173 110 173 110 110 110 110 110 110 110 110 110 11
Energy Control Ferguson Transformers Freedman Electronics John F. Rose Jaycar Hagemeyer Hitachi Sales Aust. Hitachi Ltd. Looky Video McWilliams Wines Marantz Aust. Maruni Corp. Microtrix Micro 80 Mensa Computers Magnavox McGills Newsagency Micro Pro Design Microcomputer House National Panasonic A'Asia National Panasonic Northpoint Hi Fi Philips Industries Pre Pak Plessey Qantas Airways Rod Irving Radio Parts Radio Despatch Resco P/L Stuart Alexander Sony Australia. Spectrum Lighting SM Electronics Sevien Lighting SM Electronics Sevien Lighting SI. Microcomputers Scope Laboratories Small Bus, Computers Starcross Scientific Software Source. T.C.T. Micro Design The Bulletin Tasman Electronics The Logic Shop T. A.A. R.C.	17543.1533.1479.1143.2.60113.288.16171.070113.288.188.16171.070113.288.16171.070113.288.16171.070113.288.16171.070113.288.16171.07011



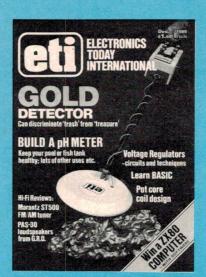

COVER

We don't think we're making extravagant claims for our super new metal detector. It really can tell precious metals from old iron! Photo, gold nugget and cover design by the inimitable Ivy Hansen.

features

pH — THE ACID TEST

16

Most people know that pH is an index of acidity and alkalinity, but what exactly is it and how can we measure it? This article answers these questions and talks about fascinating applications of the pH concept.

1500: SUPER METAL DETECTOR

Truly an excellent metal detector — it features three T/R modes of operation plus VLF, variable ground balance control and variable discrimination control.

BACK DOOR INTO BASIC

104

The first in a series of articles that will explain the basics of BASIC programming, using the familiar pocket calculator as a starting point.



MATROX VIDEO BOARDS REVIEWED

114

Two stackable video boards from Matrox of Canada give a steady, flicker-free display with lots of flexibility. This article discusses their merits and deficiencies.

news

NEWS DIGEST

TV transmissions by Technical College; Room temperature superconductivity; Venusian surface mapped by orbiter; Video noise reducer, etc.

PRINTOUT

90

The 8th World Computer Congress in Melbourne; Review of the Sinclair ZX80; Software contest results; Sorcerer hints and programs, etc.

COMMUNICATIONS NEWS

Six metres "buried"; National VHF Field Day; ETI's callsign.

SHORTWAVE LOGGINGS

130

India woos DXers; Summer nights good for African signals; Iceland comes in well.



CONTEST — WIN A ZX80 PORTABLE MICROCOMPUTER

You could win one of the world's cutest micros and six packs of software in this easy-to-enter competition.

projects



572: DIGITAL PH METER

At last! An inexpensive and accurate pH meter. It uses an Australian-made probe and shows pH units on a liquid crystal display.

597: EMERGENCY LIGHTING UNIT 57

No more fumbling around in the dark! If the mains power fails, this simple, reliable unit automatically switches on a small lamp.

LAB NOTES — VOLTAGE REGULATORS

Everything you're ever likely to need to know about voltage regulation, from simple zeners to sophisticated three terminal regulator circuits.

DESIGNING POTCORE INDUCTORS 74

Ferrite potcores have many advantages for small inductors and transformers. This article describes a simple method of designing coils for low frequency applications.

SERIES 3000 COMPACT AMPLIFIER OVERLAY DIAGRAM

In last month's issue, this wasn't printed very clearly, so we're repeating it before we get deluged with complaints!

sound

SOUND NEWS

Sansui's feedforward amplifiers; Rega Planar 2 released; TEAC diversify, etc.

THE CRAFT OF THE SPEAKER BOX MAKER 150

There's more to making a speaker box than just slapping a few bits of wood together. We look at Chadwick Audio's operation.



MARANTZ ST500 COMPUTER STEREO TUNER

A high fidelity FM tuner with all the latest station search and memory facilities. Our reviewer found it "a real delight".

156

121

G.R.D. PAS 30 LOUDSPEAKERS 168

Danish drivers in Australian enclosures add up to value for money in a smallish speaker system.

general

MICROS INVADE THE COMMUNICATIONS WORLD

Radio communications equipment is more versatile, easier to operate and service, thanks to the influence of microprocessor technology.

SHOPAROUND 85

IDEAS FOR EXPERIMENTERS 80

Mods to the ETI-152 Capacitance Meter; LED chasers; A 'no hands' organ.

SHORT CIRCUITS 32

Thermatic fan controller for a vehicle

SPECIAL OFFER C10 DATA CASSETTES 87

Save up to 20% on quality data cassettes for your home computer.

IONOSPHERIC PREDICTIONS 128

ELECTRONICS BOOKS FROM ETI 164

Beginners' books, data books, circuit books etc.

'DISCO LITE' MAIL ORDER OFFER


And now — the gadget you've been waiting for! It's a three-in-one light controller. Just the thing for parties, mood lighting, night light and just about anything you can think up.

PC BOARD PATTERNS	145
MINI-MART	146
KITS FOR PROJECTS	176
ETI SERVICES	177
DREGS	178

next month

PERMOSTAT ANTI-STATIC RECORD CARE KIT

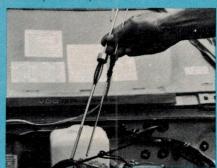Record care products are legion and many claims are made as to their efficacy. Permostat is claimed to "... permanently remove static electricity from a gramophone record". And what's more, without adverse effect. Louis Challis explores this claim and comes up with a surprise!



OIL TEMPERATURE METER FOR YOUR CAR

Featuring a linear LED readout, like most of our recent vehicle projects, this instrument employs a readily available dipstick probe. No car should be without one . . .



VIDEO DISC

What is it, what's inside the machines, where is it all going to end? Your questions answered. A fascinating rundown on this new consumer technology which will be upon us before you can say "National Panasonic, Philips, Pioneer, Kenwood, Magnavox, IVC."

150W MOSFET POWER AMPLIFIER MODULE

Would you believe less than 0.0008% distortion at 1kHz—and unconditionally stable? And that's conservative! This brilliant design forms the basis of our Series 5000 state-of-the-art stereo hi-fi system. If you've always wanted a really good hi-jfi amp, this is it. Don't miss it!

Although these articles are in an advanced state of preparation, circumstances may affect the final content. However, we will make every attempt to include all features mentioned here.



Quality $\star \star \star \star$ Price \star

Those who believe that a one star price will invariably dictate a similar result have obviously still to experience the union of Traminer and Rhine Riesling. **mewilliam's**

SUME E EFFECTS LICHTING ALLYOUR REOUIREMENTS AUSTRALIA WIDE

300w 240V SEALED BEAM LANTERN

PAR



The PAR 56 — we brought this amazing lantern to Australia, and our version is the one that others try to copy. With a 2,000 hour life lamp, what could be more economical?

Look at these features:

- Large lamp rotating knob.
- New "easy glide" rotating assembly.
 Pole focus hook.
- New, hi strength colour runners.

To celebrate the end of the year, our agents are now offering very attractive deals on Par 56 lanterns — go and talk turkey NOW with your local Barratt Lighting Agent. The price will surprise you. Options: 4 door barndoor, colour wheel.

STAGE LIGHTING COURSE

The only intensive stage lighting course that covers all aspects of Stage and Effects Lighting. To be held on Saturday 17th and Sunday 18th January, 1981, at Barratt Lighting in Sydney. Cost is \$25.00 including notes, refreshments, and a night out on the

Saturday night. To enrol, contact Barratt Lighting now. Hurry, numbers are limited.

DIMMERS



The new Ceitex Dimmer Rack -12 channels, 2000 watts per channel in 3 x 4 way modules. This dimmer rack uses Flakey iron toriods for RF suppression — inter-ference with audio systems is virtually non-existant. The Ceitex rack will drive either positive or negative control dimmer control desks - thus almost any dimmer control desk now available, will mate the Ceitex rack.

Top level adjustment is a trim pot on the front of each module, making trimming easy. The rack can be housed in any standard equipment rack, or be free standing. It is of very rugged construction. Power requirement to drive this dimmer rack is 3 phase, 30 amps per phase into an internal terminal block. Control connection is a 14 pin cannon twist lock — standard on some dimmer desks. A control cable up to 60 metres (more in some situations) can be used to connect this dimmer rack with a control desk.


JANDS DIMMER DESKS

These mate the Ceitex Rack.

JL 24/8 • 24 channels, 2 presets • 8 scenemasters on Pin Matrix • 3 channel chaser . Flash buttons.

JL 36/12 • 36 channels • 2 presets • 12 scenemasters on Pin Matrix • 3 channel chaser • Flash buttons.

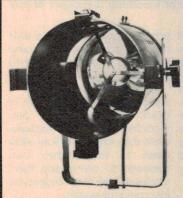We also have other 12 and 24 channel desks!



RAYLIGHT 500 WATT, 240V **VERY TIGHT BEAM**

Rock Industries think this is the brightest 500 watt lantern on the world market - in fact, we would love to be proven wrong! The Raylight is a fixed beam lantern used mainly by Rock bands where extremely high in-

tensity is needed. LAMP: 500 watts, 240V, A1/244.

LANTERN HOUSING: Same can as the PAR 64 sealed beam lantern

APPLICATION: Where very high intensity, tight-beam lighting is required.

CHRISTMAS SPECIAL OSCILITES \$39

The Osilite — a 3 channel chaser (sequencer). Variable rate • 450 watts per channel • Normal or shadow chase. Cheapest chase in Australia.

> ALL THE BEST FOR 1981!

DELTALIGHT IS COMING!

SYDNEY: Ceitex 2/33 College St, Gladesville (02) 896-2900 WOLLONGONG: Trilogy Electronics 40 Princes Hwy, Fairy Meadow (042) 83-1219

NEWCASTLE: Your Move Lighting 37a Beaumont St, Hamilton (049) 69-3560 BRISBANE: Harvey Theatrical Lighting 21 Crosby Rd, Albion (07) 262-4622 BRISBANE: Rave Light & Sound 95 Bridge Rd, Fortitude Valley (07) 52-3310 GOLD COAST: Rave Audio Visual 2388 Gold Coast Hwy, Mermaid Beach (075) 38-3331

MELBOURNE: Clearlight Shows 17 Alex Ave, Moorabbin (03) 553-1446

MELBOURNE: Lighting Corporation 131 Brighton St, Richmond (03) 429-5122

Also available Australia-wide at Strand Rank Electronic outlets

ADELAIDE: Hiwatt Lighting 37 Angus St, Nth Adelaide 5006 (08) 212-2033 ADELAIDE: Hiwatt Lighting 37 Angas St, Adelaide 5000 (08) 212-2033 ACT: Topstage Productions 8/14 Kembla St, Fyshwick ACT 2609 (062) 80-4694 PERTH: Stagecraft 1142 Hay St, West Perth 6005 (09) 321-9363. PERTH: Kosmic Sound 1074 Albany Hwy, Bentley (09) 361-8981 HOBART: Good Oil Sound 310 Liverpool St. Hobart (002) 23-5151

Distributed by

Telex AA25298

III U LTD.

140 Myrtle Street, Chippendale, NSW 2008.

NOW OPEN: New One-Stop Lighting Shop Showroom. All products ex-stock.

New Phone No. (02) 698-8499

digest

College TV transmissions

A six week experiment in educational TV broadcasting was recently completed by Box Hill Technical College in Melbourne.

The programmes concen- months. trated on teaching elec-34 of the UHF band.

picked up in Geelong.

Phase Modulation and Fre- distribution available. Modulation, were line into the studio.

was carried out by members of own pace. the college.

sometime within the next twelve regularly.

Many schools in the area tronics, as a service to local watched the transmissions with amateurs, and were trans- great interest and have already mitted from the college's indicated their desire to become amateur repeater on channel involved in the administration, planning or production of future Transmitter power was programmes. Mr Ron Ritchie, only 10 watts and the broad- the Acting Director of Technical casts were only meant to cover a Education, has also been an insmall area of east Melbourne, terested viewer. He sees the but reception reports indicate experiment as yet another asthat they reached well beyond pect of an enlarging electronic the target area and were even communication and distribution system. As most schools The programmes, which already have television recovered subjects like Oscillo- ceivers, this must be one of the scope Triggering, Oscillators, most cost effective methods of

It would also be relatively broadcast on two evenings each simple to marry a teletext week. A unique feature of the system into the transmissions. transmissions was that students Up to 150 pages of information viewing the programmes could could be modulated onto the 'talk back' to the programme otherwise unused line synch presenters via a direct telephone part of the signal to reinforce. recapitulate or extend the pro-All the work involved in the gramme material. Viewers project, from construction of the would be able to go through the transmitter to scripting and pro- main points of a programme duction of the programmes, they had just watched at their

Such a facility would obvi-At the moment the college is ously improve the effective still assessing the effectiveness dissemination of Technical and of the project. They hope to use Further Education (TAFE) prothe experience gained in this six grammes. With suitable written week experiment as the basis for backup material, it would even producing a longer and perhaps be feasible for people to study continuous series of educa- TAFE courses at home without tional transmissions, beginning having to attend a college



Programmable answering device

The A-100 telephone answering machine from Answerex can be programmed to accept incoming messages of any length.

Considering how flustered price tag, will appeal to a wide and how angry they are when homes. cut off in mid-message, this is certainly a desirable feature, standard cassette, one side of Even when their message time which is professionally preis up, callers encountering the recorded with forty messages, A-100 will not be abruptly while the other is blank to allow disconnected — a recorded users to record their own have run out of time.

The public relations value of incoming messages. these features to a business is obvious, but Answerex are also Answerex expecting that the machine, with Australia, its competitive (less than \$200) Sydney 2000. (02) 357-2527.

some people get when they range of active individuals who speak to an answering machine will want to instal it in their

The A-100 comes with a message warns them when they message to callers and leave whatever time they choose for

> For more details, contact Communications 100 William St.

Electronics courses at Newcastle

Newcastle Technical College is planning a wide range of electronics courses in 1981 for residents of Newcastle and the lower Hunter Valley.

In particular they are offering the Electronics Trades Course in block release format for students living anywhere in NSW. This is a three year course covering analogue and digital techniques for apprentices and others.

Post Trade courses include Television Receiver Servicing,

Semiconductor Electronics, Industrial Electronics, Post Trade Electronics and Industrial Instruments (conversion).

In addition there are a number of attractive special courses, including Two Way Radio, Microprocessor Principles, Servicing of Electronic Musical Instruments, Television Studio Techniques and others.

Full information on any of these courses for 1981 is available from: The Senior Head Teacher, School of Applied Electricity — Electronics Division, Newcastle Technical College, Maitland Road, Tighes Hill, NSW 2297. Phone (049) 61 0461 ext. 367.

Superconductivity at room temperature

A metals researcher at a US Air Force base has accidentally discovered a compound which appears to superconduct at room temperature.

along as a gift.", as he put it.

He was using a four point

Zero resistance, however, is accepted physical theory.

Fred W. Valdiek was experi- not the only property of a supermenting with titanium boride conductor. To properly qualify crystals, deforming them under for this description a material hydrostatic conditions in an must also repel magnetic fields, effort to improve their ductility. a property known as the When he finally achieved this Meissner effect, which is essenaim by making crystals with an tial for any practical applications unusual and highly symmetrical of superconductors. Valdiek is structure, he set about look- setting up a coil to test for the ing at other properties and Meissner effect and he claims to the superconductivity "... came have already seen magnetic repulsion caused by the fields in his electron microscope.

At the moment physicists can probe to test for electrical re- only speculate about the mode sistance and found that in two of conduction in the new directions the resistance was material. General thermodynormal (titanium boride is namic considerations seem to usually a good conductor) but rule out the possibility that in the third direction the resis- electron Cooper pairs are being tance was zero. Nor was this an formed (as happens in low temunrepeatable fluke. Valdiek perature superconductors), but made other crystals using the if conduction is by more exotic same growth and deformation means like exciton interaction techniques and now has about or electron-hole pairs, then fifteen crystals which all exhibit room temperature superconzero resistance in one direction. ductivity does not violate

10 00 CFC

New National video recorder

National Panasonic have recently released their third generation home video recorder, a lightweight model weighing less than 13 kg and incorporating several unique features.

The model NV-7000 is a VHS recorder with a four hour record used, the video head cylinder and playback ability. The video motor being quartz locked to signal to noise ratio is 43 dB and give an accuracy of 99.999%, Double Dolby circuitry gives the according to National. machine an audio S/N ratio of 50 dB.

Four direct drive motors are

The standard model comes with a cable-linked remote control unit that in addition to the auto-edit function which ennormal functions can also be sures used to review or cue at nine between programmes. times normal speed, to play at half or double speed and to dis-recommended retail price of play single frames.

unique to this model are an the heads, which are guaranantenna signal booster and an teed for twelve months.

smooth continuity

NV-7000 has \$1500 and comes with a two Other features claimed to be year warranty on all parts except





New ETI staff members

Pictured here are two new members of our advertising sales staff in Melbourne.

Bill Philpott has just been appointed our Victorian Sales Manager. Bill began his career in the Royal Australian Navy, where he was trained in electronic, electrical and submarine communications theory. On leaving the service in 1976 he worked for four years as a marketing consultant for Computer Technology.

Virginia Salman has also recently been appointed to our Melbourne sales staff. She was formerly secretary to Southern States Executive Manager, Tom Bray, who was so impressed with her abilities that he promoted her to her new position. Virginia, who is tall and athletic, is married with two children. She enjoys playing tennis and riding bicycles, loves music and is very interested in computers.

Laser depth sounder

An airborne laser depth sounder will help ease the burden of hydrographic survey work around Australia's coasts.

was developed by the Defence laborious one. Research Institute at Salisbury, interval by the velocity of light in system. sea water gives the depth.


waves they must be carried on Australia.

The equipment, which is surface vessels, which makes believed to be in advance of any- the task of surveying Australia's thing else in the Western world, vast continental shelf a long and

All measured depths must of SA. Known as WHELADS II it course be accompanied by works by measuring the time in- accurate positional information, terval between the reflection of a and the generation of such data laser beam from the sea surface (accurate to within a few metres) and the bottom. Multiplying this is an essential part of the

Installed in a RAAF Dakota, Conventional acoustic soun- WHELADS II has been tested ders work on a similar principle, over North Queensland waters but because they use sound and is currently on trial off South

MEWS digest

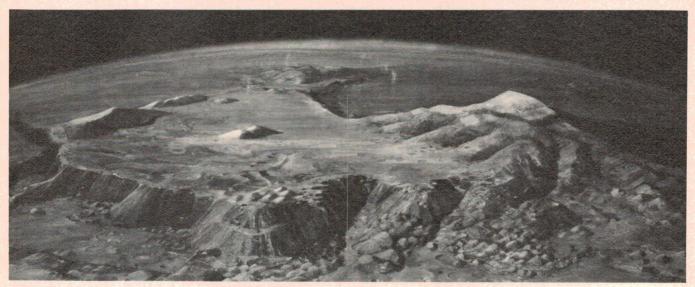

Venusian surface mapped by orbiter radar

The Pioneer Venus craft (see ETI May 1979) has been orbit- is another name for Venus itself. and 10 craft landed in this ing the planet since December 1978 during which time its radar has penetrated the thick clouds of the planet to provide information about large surface features.

By May 18th, 1980 the Orbiter had mapped 93% of the below the reference level. Venusian surface from 73° planet. The work should con-higher than Mount Everest. tinue for a few more years.

work, less than 1% of Venus' which may resemble the corresurface had been detected by sponding areas of low-density powerful Earth-based radar rock on the Earth. techniques.

of Australia, while another, Aph- Aphrodite (centred at 5° South) rodite Terra, is as large as half of Africa.

There is no 'sea level' on Venus, but 60% of the surface consists of relatively flat rolling plains lying at a radial distance of 6050 km from the centre of the planet. This 6050 km radius is used as a reference distance like sea level on the Earth.

The lowlands of Venus may be compared with the oceanic areas of the Earth, but only 16% of the surface lies below the 6050 km radius whereas on Earth nearly two-thirds of the surface is covered by the oceans.

The lowest point is 2.9 km

The highest point, Maxwell North to 63° South latitude, Montes, in Ishtar Terra is missing relatively small circular 10.8 km (35 400 feet) above the regions around each pole of the reference level and is therefore

Only about 8% of the planet's Prior to the Pioneer Orbiter surface is true "highlands"

An international group is The most prominent features naming the surface features on Venus are the highland after mythical goddesses. Ishtar regions which are comparable (centred at 65° North) is named to the continents of the Earth. after the Babylonian goddess of One of these, Ishtar Terra, in the love and war, daughter of the northern hemisphere is the size Moon and sister of the Sun.

figures and still smaller features on the Earth. after famous women who are no cated on a tentative basis.

North which appears to consist equator. of two huge shield-shaped volrunning from 40° North to 50° this South latitude.


face and shaped like the very munications network. Complex wide-based South distance of some data into acceptable images. 2100 km. The Soviet Venera 9

Minor features will be named region and found radioactivity after other mythical female similar to that of volcanic rocks

These Theia Mons (northerly) longer living. However, the and Rhea Mons (Southerly) names have so far been allo- mountains rise to about 4 km above the reference level. Alpha Other major features on Regio is a smaller highland Venus include Beta Regio at 30° region about 25° South of the

When considering the maps canoes larger than the Hawaii- of the Venusian surface, readers Midway chain on the Earth; it is should remember that it would probably situated on a fault line not have been possible to obtain information without modern electronics, space-There are two huge adjoining borne radar and a highly mountains (smooth on the sur- efficient inter-planetary com-Hawaiian vol- data reduction systems were canoes) which cover a North- employed to convert the raw

Brian Dance

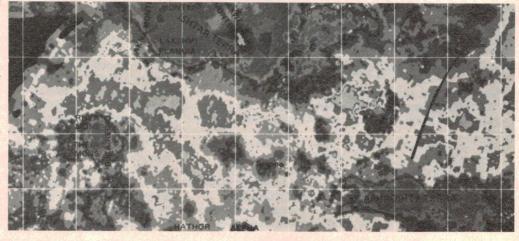



Small Fridge. Big Deal.

Space age breakthrough creates a new line of Koolatron electronic portable refrigerators and food warmers.

You're nicely away on your long-awaited vacation, camping trip or long weekend with the family. You're comfortably cruising in your car, van or rec. vehicle along a busy interstate with few rest stops or restaurants. You guessed it ... the kids want to stop for a snack. But your Koolatron P34 or P34A is full of sandwiches, cold drinks, fried chicken... home made, fresh and cold. The family helps themselves and you've saved valuable vacation time and another expensive restaurant bill.

expensive restaurant bill. You're a commuter, a salesman or a trucker Now with your amazing Koolatron plugged in beside you, you open the lid and instantly fresh food and drinks are at your fingertips. Just for the price of a good cooler and one or two seasons of buying ice, (or about 10 family restaurant meals), all the marvels of home refrigeration are available electronically. An amazing space-age miracle... the thermo-electric solid state module... makes these portable refrigerators possible. possible

These amazing heat pumps have not only gone to the moon, but have provided the breakthrough for Koolatron's portable fridge revolution

THOUSANDS IN USE

THOUSANDS IN USE

Koolatron now has tens of thousands of electronic fridges in use worldwide using these same powerful solid state modules. Built to take it, two of these electronic modules are encased in lough, plastic insulated chests that are designed to be rugged and trouble-free. Nonrusting hinges and latches prevent corrosion in salt water environments. And with only one moving part (a small 12 volt fan) Koolatron's portables seldom see a service depot. Now you can enjoy Koolatron's whole family of electronic portable refrigerators and food warmers that eliminate costly ice and provide "home refrigera." eliminate costly ice and provide "home refrigera-tion" convenience at sane and sensible prices.

THE PERFECT RECREATIONAL FRIDGE

MODEL P34 \$219.00



Holds over 20 kg food or 48 cans or 12 bottles of wine. Refrigerates in air temperatures up to 35°C. Tough ABS case in Sand Beige case in sand beige with non-corroding latches and handle. Large 33 litre capacity. Weighs only 7½ kg when empty. Operates on 12 volts DC with supplied power corre supplied power cord or from optional 240 volt adaptor.

Exterior: 53cm x 41cm x 41cm Interior 41cm x 31cm x 31cm

As a travel fridge Koolatron keeps food As a travel flidge Koolatron Keeps lood and drinks fresh and cold wherever you go. Carry frozen food, medical samples, insulin, dietetic food. Photographers use it for films. Boatowners keep your drinks cold and food fresh without going ashore for hard to get and cumbersome ice. Operate Koolatron up to six cumbersome ice. Operate Koolatron up to six hours from your battery and still start your engine. With the power off, Koolatron keeps everything cold and fresh for many hours in its well insulated case. Imagine dry dependable refrigeration with the size to match your travelling and camping needs. Fits into any boat, van, truck, camper or back seat of your car, Ideal for aeroplanes. Unaffected by motion car. Ideal for aeroplanes. Unaffected by motion or tilting. A natural for drive-in movies, picnics, sporting events. With our optional 240 volt adaptor you'll also find endless uses wherever household current is available... at your weekender... as a bar fridge... in your motel room for a midnight snack or drink... as an office fridge... or beside your pool, Use as auxiliary fridge at your next party. Dazzle your friends with the latest space age technology.

THE ULTIMATE RECREATIONAL MODEL P34A FOOD WARMER \$239.00



The same size, colour, weight and capacity as the P34 but includes food warming features, fully adjustable temperature control and low battery warning indicator

The P34A is our top of the line portable. It heats, it refrigerates and with specially designed electronic circuit control (patent applied for) it allows you to dial a complete applied for) it allows you to dial a complete range of temperatures from very cold to very warm. You wine buffs will find it ideal to keep up to 12 bottles of wine at just the right temperature. In winter take your favourite casserole and hot food for the whole family with you and save on restaurant meals. Mothers can keep baby's formula just right for baby. Low battery indicator warns you when battery needs a recharge and the sensing circuits efficiently control your power consumption to save on battery drain. This is our best of the line recreational fridge and food warmer with all the bells and whistles for the discerning buyer who demands quality, size discerning buyer who demands quality, size and versatility.

WHY IS KOOLATRON BETTER VALUE THAN

WHY IS KOOLATRON BETTER VALUE THAN ANY OTHER PORTABLE FRIDGE?

The full size family of Koolatron portables are specially designed for the serious traveller and outdoors man. They will refrigerate more than 3 times the contents of the Sheen and 4 times the contents of the Electrolux Sunnycool. You can fit more drinks (48 small cans or 12 wine bottles) or more food (20 kg) into your Koolatron than into most other portable fridges, yet Koolatron costs a lot less for it's size At the yet Koolatron costs a lot less for it's size. At the same time it consumes no more power under full load than other smaller units

WE MAKE YOU A PROMISE
If you can find any other 12VDC or gas
operated portable refrigerator that is lighter,
bigger and costs less than Koolatron—we w buy it for you. No questions asked.

ORDER TODAY WITHOUT ANY OBLIGATION AND 21 DAY MONEY BACK GUARANTEE

Simply complete the attached order form or phone collect and we will rush you your Koolatron on our no risk 21 day trial offer. Each unit comes with complete instructions and a written 1 year warranty. In the unlikely event you ever need service we have service centres in all capital cities and overseas. When you receive your Koolatron use it constantly for a full 3 weeks without risk.

weeks without risk.

If you ordered our optional 240 volt adaptor, plug it in, then use your portable immediately as a bar fridge or around the patio or pool. Next plug your fridge into your car or van. Take your family out for a weekend trip. Enjoy fresh home cooked food as you thumb your nose at expensive restaurants and takeaways. If after you have thoroughly tested it, you don't agree that your Koolatron represents a major breakthrough that will save you time money and bother for years to come, send it back for a full refund. You can't lose ... we guarantee it.

So be among the thousands to discover that

So be among the thousands to discover that the ice age is over. Don't waste another dollar on ice ... order your Koolatron without any obligation today



CREDIT CARD HOLDERS - You can phone your order reverse charge

(03) 645 2068

Koolatron Industries 297 Williamstown Road Port Melbourne 3207 409 Sussex Street Sydney 2000

Or use this handy order coupon.

Koolatron INDUSTRIES

297 Williamstown Road, Port Melbourne, 3207 Telex 32571 Send me with full refund privileges:

Koolatron P34 at \$219.00

Koolatron P34A at \$239.00.

Koolatron 240V Adaptor at \$37.50

Please add \$7.50 for handling and delivery per unit No charge for shipping A.C. adaptor if ordered with unit.

I understand that I may return any item undamaged within 21 days and receive a full refund if I am not satisfied.

I enclose my cheque or money order for

or please	Charge It to my
Bankcard	☐ Diners Club
☐ Americ	an Express

A/c Numbe	er
Expiry Dat	
Signature	A HOLD BY THE
Oignature	(necessary to send merchandise

NAME ADDRESS

CODE

ETI 12/80

MEMS digest

Video image processor reduces noise

The Australian company, Dindima, have announced the development of a new method of processing video images to improve the signal-to-noise ratio by 45 dB.


A patent application has been samples the image at 14.5 MHz expected to have applications in 82 s. the fields of medicine, asindustry.

made for the Arlunya TF4000 over a period selected by the digital temporal filter which is operator, ranging from 0.3 s to

The Arlunya TF4000 is tronomy, nuclear physics, and unique in that it can effectively eliminate noise on a real time The instrument stores a video basis. This makes the instruimage on a 512 x 512 picture ment especially useful in the element matrix, applying a noise image processing of X-ray integration algorithm and 256 fluoroscopy where it enables the grey scale levels on an element minimum dosage of radiation by element basis. The processor to be used, for example in the





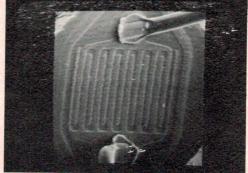

examination of a patient with suspected cancer.

It is hoped that the instrument will have considerable export potential and although it is new it is already being sold in the UK as an image intensifier and noise reduction system for electron microscopy.

Further information can be obtained from Dindima Group Pty Ltd, P.O. Box 106, Vermont,

The same image before and after processing by the TF4000.

Californian power industry backs solar cells

Westinghouse announce that two of the major Californian electric power companies will fund the development of an automatic solar cell production plant.

The plant will produce single crystal silicon ribbon, known as dendritic web, directly from molten silicon. The process yields a long, smooth and pure US\$1 million in its first year of ribbon which, unlike ingots, production, of which Pacific Gas does not need to be sliced, polished and cleaned. This fornia Edison will each provide saves time and avoids wasting expensive high purity silicon.


Solar cells made from dendritic web have already achieved conversion efficiencies approaching 16 per cent and Westinghouse expect that improvements currently underway will take this figure over 18 per cent, which in midday sunshine means a power output around 170 watts per square metre.

Phase one of the project, a pilot facility with a capacity of 50 kilowatts per year, will have operating costs of about and Electric and Southern Cali-\$300 000. Under the agreement, the utilities will receive their first cells later this year to use in their own research and development programmes.

Once the first stage is completed, Westinghouse plan to expand to a fully automated attenuation of 69 dB in six steps 25 000 kilowatt per year production line, which will be the The AT-872 has eight steps of 1, basic module for a full scale 2, 3, 6, 10, 10, 20 and 20 dB for production plant.

Attenuate me baby!

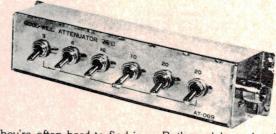RF attenuators are an indispensable instrument in the shack of every true ham and experimenter.



They're often hard to find in fully in Emtronics' George St, tors, models from the Goodwill 220 mm long by 50 mm square. company.

are available in 50 and 75 ohm impedances and are specified to work from dc to 250 MHz.

The AT-069 has a maximum - 3, 6, 10, 10, 20 and 20 dB. a maximum of 72 dB.

Both models can be obtained the shops, but if you look care- with N, BNC or S0239 connecalthough the latter Sydney store you'll find two are favoured. Both measure

Applications include measur-Models AT-069 and AT-872 ing receiver and preamp noise figure, checking or measuring relative antenna gain, reducing front end overload in receivers, providing calibrated steps from a signal generator output, etc.

See Emtronics at 649 George St, Sydney 2000 (P.O. Box K21, Haymarket 2000). (02) 211-0531.





It can happen! Once you start using Hobby-BloxTM, you'll get more joy than ever from electronics.

The 14 modular units in the solderless, Hobby-Blox system allow you to complete projects faster, easier. Help you to move on to more and more sophisticated projects. Faster, easier.

The modules are color-coded and cross indexed. There are terminal, distribution and bus strips. Speaker panels, binding posts...everything you see illustrated here.

And for the beginning nobyset, there are two starter packs. One for integrated circuit projects, the other for those involving discrete components. And each comes with an illustrated booklet describing 10 projects.

If you thought you were into electronics, look out. Once you get into Hobby-Blox, you're hooked for good!

Patents Pending. © A P PRODUCTS INCORPORATED 1980



AP PRODUCTS INCORPORATED 9450 Pineneedle Drive P.O. Box 603 Mentor, Ohio 44060 [216] 354-2101

Free Project-of-the-Month to Hobby-Blox purchasers!

For a free catalog, contact your local HOBBY-BLOX™ dealer:

N.E.T. PTY. LTD. 92 Woodfield Boulevard Caringbah, N.S.W. 2229 TEL: 525-6090 RIFA PTY. LTD. P.O. Box 485 Cross House, 2 Cross Street Hurstville, N.S.W. 2220 TEL: 570-8122

RIFA PTY. LTD. P.O. Box 95 202 Bell Street Preston, Victoria 3072 TEL: [03] 480-1211

AP-58 A

And you thought just for old



New Zealand was geysers.



pH—the acid test

Many chemical and biological systems depend critically on a parameter known as pH. This article explains what pH means, outlines how it is measured and investigates some areas where it is important.

Elaine Ray & William Fisher

THE IMPORTANCE of acids and alkalis is well known, as is the fact that some acids and alkalis are stronger than others — that is, they react more vigourously with other substances. But what is it that makes sulphuric acid, for example, stronger than acetic acid? And how can we quantify their strengths?

Dissociation

All acids have at least one hydrogen atom that tends to break away from the molecule when the acid is dissolved in water. In doing so it leaves behind an electron and becomes a positively charged hydrogen ion. It is these free hydrogen ions that are responsible for the chemical properties of acids, and their relative numbers determine the strength of the acid in question.

For example, acetic acid (CH_3COOH) dissolved in water tends to partly dissociate into positive hydrogen ions (H^+) and negative acetate residues (CH_3COO^-), thus:

CH₃COOH ♦ CH₃COO⁻ +H⁺

and sulphuric acid dissociates almost completely in water into hydrogen ions and sulphate residues thus: $H_2SO_4 \triangleright 2H^+ + SO_4^{--}$

Alkalis are extreme examples of a class of substances known as bases. Bases are like converses of acids. When they are dissolved in water they tend to break up into a negatively charged hydroxyl ion (OH⁻) and a positively charged residue. For example the strong alkali potassium hydroxide (KOH) breaks up thus:

KOH ♦ K+ + OH-

and the weaker base calcium hydroxide (lime) partly breaks up into calcium and

—to page 19 ▶



A high quality portable pH meter with a liquid crystal display that directly indicates the pH of the solution under test.



Until now, you had to buy "professional" solder-less breadboards for your projects and pay "professional" prices. Now there's Hobby-Blox, "professional" prices. Now there's Hobby-Blox, a totally new circuit-building system that's not only economically priced but offers many more advantages to the hobbyist.

At the core of the system are two expandable starter packs, one for discrete component projects, the other for integrated circuit projects. Each comes with a number of Hobby-Blox modules that fit into a tray and an illustrated project booklet. In addition, the system includes 14 separate component packs you can purchase individually—terminal, you can purchase individually—terminal, binding posts, etc.

The Hobby-Blox system is easy to use because the modules are color-keyed and letter/number indexed. It's time-saving, because they're solderless. It's compatible with DIP's of all sizes and a wide variety of discrete components. And you save money, because the parts can be reused again and again.

How far can you go with the Hobby-Blox system? Take a look at the example above. Then you'll know why we say, "your only limit is your own imagination!"


Patents Pending © A P PRODUCTS INCORPORATED 1980



A P PRODUCTS INCORPORATED 1359 West Jackson Street Painesville, Ohio 44077 (216) 354-2101 For a free catalog, contact your local HOBBY-BLOX™ dealer:

N.E.T. PTY, LTD. 92 Woodfield Boulevard Caringbah, N.S.W. 2229 TEL: 525-6090 RIFA PTY, LTD. P.O. Box 485 Cross House, 2 Cross Street Hurstville, N.S. W. 2220 TEL: 570-8122

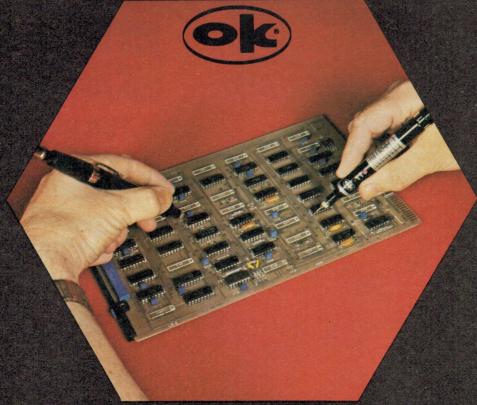RIFA PTY. LTD. P.O. Box 95 202 Bell Street Preston, Victoria 3072 TEL: (03) 480-1211



Digital IC Probe & Logic Pulser

PRB-1 DIGITAL LOGIC PROBE

Compatible with DTL, TTL CMOS, MOS and Microprocessors using a 4 to 15V power supply. Thresholds automatically programmed. Automatic resetting memory. No adjustment required. Visual indication of logic levels, using LED's to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, shirt pocket portable (protective tip cap and removable coil cord).

Automatic threshold resetting • DE to > 50 MHZ

Compatible with all logic families 4-15 VDC • 10 Nsec. pulse response

Supply O.V.P. to ± 70 VDC • 120 K Ω impedance

No switches/no calibration • Automatic pulse stretching to 50 Msec.

Open circuit detection • Automatic resetting memory

Range extended to 15-25 VDC with optional PA-1 adapter PLS-1 LOGIC PULSER

The PLS-1 logic pulser will superimpose a dynamic pulse train (20 pps) or a single pulse onto the circuit node under test. There is no need to unsolder pins or cut printed-circuit traces even when these nodes are being clamped by digital outputs

PLS-1 is a multi-mode, high current pulse generator packaged in a hand-held shirt pocket portable instrument. It can source or sink sufficient current to force saturated output transistors in digital circuits into the opposite logic state.

Signal injection is by means of a pushbutton switch near the probe tip. When the button is depressed, a single high-going or low-going pulse of 2μ sec wide is delivered to the circuit node under test. Pulse polarity is automatic: high nodes are pulsed low and low nodes are pulsed high. Holding the button down delivers a series of pulses of 20 pps to the circuit under test.

High input impedance (off state) 1 meg ohm • Multi mode-single pulses or pulse trains

Low output impedance(active state) 2 ohms • Automatic polarity sensing

Output pulse width 2 μ sec nominal • Automatic current limiting; 7 amps nominal

Input over voltage protection + 50 volts • Automatically programmed output level

Finger tip push button actuated • Circuit powered


Power lead reversal protection \bullet No adjustments required

Multi-family RTL, DTL, TTL, CMOS, MOS and Microprocessors.

AMPEC ELECTRONICS PTY. LTD.

1 Wellington St, Rozelle, 2039. PO Box 132, Rozelle, 2039. Ph (02) 818-1166.

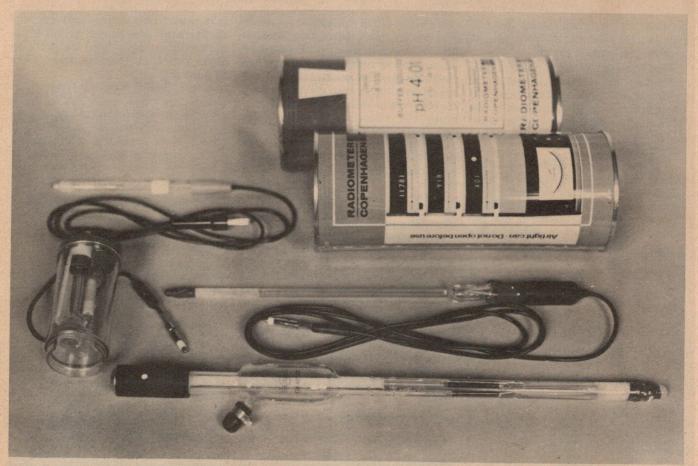Available from: NSW Radio Despatch Service, 211-0191. Applied Technology, 487-2711. David Reid Electronics, 29-6601. Electronics (Distributors), 636-6052. Martin De Launay, 29-5834. VIC: Stewart Electronics, 534-3733. Ellistronics, 602-3282. John Pearce, 528-5240. Ritronics, 489-8131. QLD: N.S. Electronics, 36-5061. WA: Reserve Electronics, 275-2377. Taimac, 328-1988.



pH electrodes are made in a variety of shapes and sizes to suit different applications, at the rear of the picture are two cans of 'buffer solutions' — liquids whose pH does not change much when they are contaminated. Buffer solutions are used to calibrate pH electrodes.

hydroxyl ions, thus:

Ca(OH)₂ ♦ Ca⁺⁺ + 2OH⁻

Bases and acids in the same solution tend to neutralise each other. The free hydrogen ions from the acid combine with the free hydroxyl ions from the base to form molecules of water, thus:

H+ + OH- ♦ H2O

Neutrality and activity

The reaction between hydrogen and hydroxyl ions can also proceed in the other direction — that is, water molecules can break up again into free hydrogen and hydroxyl ions. There is only a slight tendency for this to happen, however. In pure water at room temperature only about one water molecule in ten million dissociates into ions. In other words, the concentration of free hydrogen ions in pure water is one part in ten million. This concentration of hydrogen ions is known as a neutral solution.

If an acid is dissolved in water, the solution will no longer be neutral—there will be more hydrogen ions because of the dissociation of the acid. Dissolved bases will initially result in a

solution that has more hydroxyl ions than neutral water, but these hydroxyl ions will tend to combine with any free hydrogen ions to form H₂O molecules. The net result is that the number of free hydrogen ions in a basic solution is *lower* than in neutral water.

Clearly if we can measure the number of free hydrogen ions in a solution we can find out if it is acidic or basic, and to what extent. Actually what we will be interested in is not the absolute number of hydrogen ions, but their relative numbers, i.e. their concentration.

For reasons of mathematical convenience and logical purity, chemists prefer to work with a quantity known as the *activity* of hydrogen ions. Since the activity is generally proportional to the concentration, the exact distinction between the two terms need not concern us here.

The range of possible values for hydrogen ion activity is very wide, from 10 for the strongest acid solution to 10^{-14} for the strongest alkali. This leads to numbers that are awkward to write and even more awkward to speak (try saying 2.76×10^{-11} quickly!).

The pH notation, which was introduced in 1909 by the Danish chemist S.P.L. Sorensen, makes things a bit easier. It defines pH as the negative logarithm of the hydrogen ion activity, i.e.

pH = - log A (where A is the hydrogen ion activity)

Low values of pH indicate acidity, high values alkalinity. Neutral water is pH7.

pH measurement

The best way to measure the hydrogen ion activity of a solution is to use that solution as part of an electric cell. Before 1937 this was commonly done with a 'hydrogen cell'.

When a platinum electrode is dipped into a solution containing H⁺ ions, the positively charged ions tend to attract negatively charges electrons out of the metal. The higher the activity of the ions, the stronger the attraction of the solution for the electrons.

One way to compare the H⁺ activities of two different solutions is to put an electrode into each solution and join the electrodes with a wire. The solution with the higher activity will exert a greater pull on the electrons and a current will flow through the wire. If the wire is broken, a voltage will appear

tage is a measure of the hydrogen ion activity and hence of the pH.

There are considerable practical and theoretical difficulties involved in the 'hydrogen cell' method of measurement described above. The invention of the 'glass electrode' pH meter in 1937 overcame these difficulties and was a boon to chemists.

A typical glass electrode consists of a porous glass bulb containing a saturated solution of silver chloride (AgCl) in which a silver electrode is immersed. This electrode is connected to one terminal of a voltmeter, whose other

Voltmete Filling Hole Reference Electrolyte From Silver Flectrode Sealed Glass Tube From Reference Electrode Silve Solution Salt Bridge Glass . Membrane

A GLASS ELECTRODE

Above is a cross-sectional diagram of a typical pH electrode or 'probe'. It consists of a glass membrane in the shape of a bulb, inside which is a solution of silver chloride and a silver metal electrode. Around the stem of the probe is a refillable reservoir which contains a reference solution and a reference metal electrode.

The two electrodes are connected to the terminals of a voltmeter, which normally reads a steady voltage. When the probe is immersed in the sample solution, some ions from the sample migrate across the glass membrane and alter the activity of the silver chloride, so that the voltmeter reading alters.

between the two break points. This vol-terminal is wired to another electrode that sits in a reference solution. Because the silver ions in the silver chloride solution tend to suck electrons from one electrode and the positive ions in the reference solution suck electrodes from the other electrode at fixed but different rates, the voltmeter normally reads some steady voltage.

The glass bulb containing the silver chloride is immersed in the solution whose pH is being measured. The hydrogen ions in the latter solution migrate across the glass membrane of the bulb and alter the activity of the silver chloride solution, thereby altering the attraction of the silver chloride solution for the electrons in the silver electrode dipped into it. Consequently, the reading on the voltmeter will alter.

Careful design can result in a glass electrode pH meter which generates a voltage that is linearly proportional to the pH of the solution being tested. (Sometimes this linearity is achieved by putting the test solution in contact with the reference solution as well, via a 'bridge' of some electrically conducting salt).

pH in medicine


The complex chemical interactions that

take place in the human body are very sensitive to changes in pH so the body is constantly trying to keep the pH of its blood within the narrow range from 7.38 to 7.42.

A complicated feedback system, controlled by the endocrine glands, operates to counteract any abnormal deviations in blood pH, which would otherwise be traumatic. For example, after a heavy intake of alcohol, which makes the blood over-acid, the lungs breathe deeper and faster so as to expel carbon dioxide (which makes carbonic acid when it is dissolved in the blood) and the kidneys extract more carbonic acid from the blood and pass it into the bladder where it can do no harm.

Acidosis and alkalosis, which are the medical terms for abnormally low and abnormally high blood pH, are generally indications of serious diseases like diabetes, kidney or lung failure.

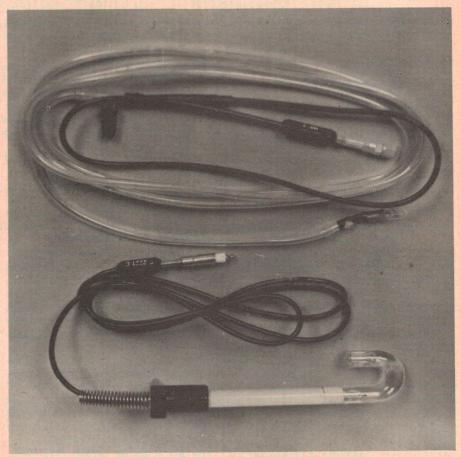Polio victims and others in artificial respirators sometimes suffer from an excessive build-up of carbon dioxide in the blood (because their lungs cannot excrete it). Fortunately this can easily be detected in time for corrective action to be taken by routinely monitoring the blood pH. The amount of blood required for this purpose is quite small — a few



Two special pH probes for medical applications. The upper one is a gastric pH probe, designed to pass through a patient's nose and the lower probe is used for blood analysis.

millilitres, which must be syringed directly to a gas analyser because exposure to the air would alter its pH.

The pH level in the stomach is quite different to that of the blood. The gastric juices are rich in hydrochloric acid and vary from pH 1.5 to 3.5. A hormonal feedback control system normally keeps the gastric pH within bounds, but this system can be upset by abnormal secretion of adrenaline in times of prolonged nervous tension. This is why people who live under a great deal of stress tend to have ulcers caused by gastric over-acidity.

There are also some people who have little or no free hydrochloric acid in their stomachs. This group run a very high risk of developing stomach cancers. Clearly the measurement of gastric pH levels is of considerable medical importance and over the years physicians have developed various methods of doing this. Perhaps the commonest technique nowadays is to pass an electrode through the nose and down the alimentary canal into the stomach, to give a fast and accurate indication.

Soils

Soil acidity or alkalinity is one of the major factors that affect the growth of plants. The pH of a soil is an indication of the extent to which exchange reactions in the soil are preventing nutrients from reaching the roots of plants.

Roughly what happens is this - the fine particles in a soil aggregate into bodies known as colloids, which have an electrical charge distributed over their surface. The water that permeates the soil contains dissolved ions which plants need and which they normally suck up from the solution by capillary action through their roots. However, some of these ions in solution may change places with less valuable ions on the colloid surfaces. Plants can only absorb ions from the aqueous solution surrounding the colloids; they cannot attract them from the colloid surfaces, so the soil is effectively depleted nutritionally.

Plant nutrient ions are commonly attached to the colloids in exchange for hydrogen ions, which pass into solution. Measuring the soil pH obviously gives an indication of the extent to which this has happened.

Plants vary a great deal in the range of pH they will tolerate. Most will flourish somewhere between pH 6 and 8, but some well known plants grow best outside this range. Potatoes and tomatos, for example, like an acid soil with a pH between 5 and 6, while camellias, azaleas and other hardy flowering plants cannot tolerate any degree of acidity and do best in alkaline conditions with a pH between 8 and 9.

Acid soils can be neutralised by adding lime and over-alkaline ones will benefit from a dressing of bone meal or any other source of phosphates. If you want to measure the pH of your own soil, you should first make a ten per cent aqueous solution (i.e. 10 grams of soil in 100 millilitres of water) and measure the pH of that.

Aquariums

Fish are sensitive creatures and won't flourish unless the pH of their environment is correct. Most freshwater fish do best between pH 6.5 and pH 7.5, but goldfish (whether they are cold or warm water types) like their water a little more alkaline, i.e: pH greater than 7.5.

Acidic water in a goldfish tank encourages the growth of fungus and also induces a malady known as 'acid burn',

which makes the fish look as if they have had bites taken out of them. It is advisable to measure the pH of goldfish tanks about once a week, preferably when the water is refreshed.

If you don't have a pH meter you can get some idea of the acidity by inspecting the plants growing in the tank. If they are looking unhealthy, the water is too acid.

Swimming pools

The recommended pH for swimming pool water is between 7.2 and 7.6. In the summer months when pools are in frequent use the pH should be tested every second day and chemicals added if necessary to keep it within bounds.

Over-acid pool water enourages the growth of algae, whose colour depends on the degree of acidity. First to form are green algae, in sheltered areas around steps or ladders. Brown algae that stain the tiles are the next stage, followed by black.



Chlorinated pools should be maintained at a pH between 7.2 and 7.6. An automatic chlorinator is the best method — see the Pool Magic offer on page 35.

. . and now we have

Collet Knobs*

and caps and pointers and figure dials and nut covers ... and they all fit together to form competitively priced, vibration-proof and very satisfying

knob assemblies

Call us NOW! to talk about your requirements . . . from single to O.E.M. custom made quantities.



C&K Electronics (Aust.) Pty Limited

Office 2/6 McFarlane Street Merrylands NSW 2160
PO Box 101 Merrylands 2160 Telephone 682 3144 Telex AA23404
Agents Melb. 598 2333/Adel. 269 2544/Bris. 36 1277/Perth 458 7111

Bringing you the excellence of International Professional components



AUDITEC 1045
OVERLOAD
LINE
10
10
10
10
10
AUDITEC

OVERLOAD

AUDITEC

OVERLOAD

OVERLO

The new AUDITEC 1045 MIC/LINE Pre-Amplifier

- 51/4" rack frame mounting
- Balanced input
- 600 Ohm output
- Input sensitivity from mic to line level
- Input peak level indicator
- Low distortion/low noise performance
- Designed for high quality PA and mixers

SIFAM LTD England

- 1045's can be mixed simply by interconnecting
- Australian designed and manufactured

AUDITEC MAJOR STOCKISTS. VIC: ZEPHYR PRODUCTS, 70 Batesford Rd, Chadstone, 3148. Ph (03) 568-2922. QLD: DELSOUND PTY. LTD., 1 Wickham Terrace, Brisbane, 4000. Phone (07) 229-6155. SA: NEIL MULLER PTY. LTD. 8 Arthur St, Unley, 5061. Ph (08) 272-8011. ACT: MUSIQUE BOUTIQUE, 29-31 Colbee Court, Phillip, 2606. Ph (062) 81-5255. NT: DARWIN COMMUNICATIONS SYSTEMS, 2420 Scriven St, Casuarina, 5792. Ph (089) 85-3184. FAMMER & DAVIES ELECTRONICS, Weber Sales Bld, Fogarty St, Alice Springs, 5750. Ph (011) 52-2967. TAS: STAGE SYSTEMS, 52 Molle St, Hobart, 7000. Ph (002) 34-4009.

OTHER AGENTS, NSW: RAY WALSH SOUND SYSTEMS, 448 Swift Street, Albury, 2640. Phone (060) 21-1502. W.M.R. ELECTRONICS, "Wirra-Willa", Belmont Road, Glenfield, 2167. Phone (02) 605-1203. DAWES SOUND SYSTEMS, 7 Mitchell's Pass, Blaxland, 2774. Phone (047) 39-4421. D.R. HI-F18 ELECTRONICS, 657 Pittwater Road, Dee Why, 2099. Phone (02) 982-7500. LANDERS MUSIC CENTRE PTY. LTD., 302 Summer Street, Orange, 2800. Phone (063) 62-6515. TRILOGY WHOLESALE ELECTRONICS, 40 Princes Highway, Fairy Meadow, 2519. Phone (042) 83-1219. R. ARCHER & SON, 107 Bungaree Road, Wentworthville, 2145. Phone (02) 631-4538. QLD: BUNDABERG HI-F1, 244 George Street, Bundaberg, 4670. Phone (071) 71-3176. KELLER ELECTRONICS, 94 Ellena Street, Maryborough, 4650. Phone (071) 21-4559.

For information on the 1045 and other Auditec products, phone, write or call at AUDITEC AUSTRALIA PTY, LTD.

10 Waitara Avenue, Waitara, NSW 2077 (adjacent to Pacific Highway). Phone (02) 48-4116.

Digital pH meter is simple and accurate

A pH meter has many applications in widely varying fields of interest; in chemical analysis, in soil analysis (gardening!); swimming pool chlorination; care of tropical fish, etc. This project features a 3½-digit liquid crystal display, simple construction and straightforward operation.

Peter Eliot Phil Wait

FROM TIME TO TIME readers write or 'phone us with a project suggestion that, at first sight is attractive and practical, but on further investigation runs into what seems insuperable difficulties — generally with the supply (or lack!) of a critical component.

We first looked at this project in response to a spate of reader enquires. They generally pointed out that a pH meter was something we have never done but there were plenty of commercially available models — generally at prices well beyond the hobbyist or student. The electronics for such a project could be designed in several ways and this seemed to present few problems. So, we went looking for a suitable pH electrode.

That's where it all started to come apart at the seams. Our early efforts turned up imported probes costing in the vicinity of \$100 for the least expensive model. We figured the electronics for an analogue readout instrument (using a moving coil meter) would cost around \$30 or so and for a digital readout instrument around \$40 or so. With probes at three times or more the cost of the electronics, a project started to look decidedly unattractive. It almost fell by the wayside.

However, during a conversation one day with Peter Eliot of the Amalgamated Instrument Company, who make and market a range of digital panel meters and portable digital instruments for industrial applications, the editor enquired where he obtained the pH probes for his digital pH instruments, and what did they cost? Peter was using Australian made probes chiefly because they cost less than half the equivalent imported types, and what's more they were readily avail-

CALIBRATION

1 Sur all controls to mid range
2 Ones relacionds with deliant valuer
3 Adjust STANDARDISE control for correct reading in p417
4 Clean electrode with deliant valuer
5 Adjust SLOPE control for correct reading in p445 buffer solution
solution
6 (Adjust allower leading on p445 buffer solution in from the Buffer endiation.

SLOPE

STANDARDISE

STANDARDISE

TEMPERATURE

ON

POWER

TEMPERATURE

ON

able. Quick as a flash, we were talking to the man from Starcross Scientific, who distribute the range of 'Ionode' probes made in Queensland. A suitable probe was priced at around \$40 so we figured a project would be timely and popular. What's more, having already done much of the required development work, Peter Eliot volunteered to provide

us with a circuit and some material to suit our requirements. With some pc board and packaging work from the project staff, this project is the result.

Principles

An article elsewhere in this issue explains the theory behind the pH index as well as detailing applications of pH

Project 572

measurement in various fields. This discussion is confined to the principles of operation behind this particular instrument.


The pH electrode or probe consists basically of an electric cell which, when immersed in a solution, will generate a voltage proportional to the hydrogen ion activity of that solution. The voltage generated is a measure of the pH of the solution. Measure the voltage generated by the electrode, display it, and you've got a pH meter. Simple enough, but there are a few difficulties.

First problem is the internal (or source) impedance of the pH probe. It is generally around 10⁹ to 10¹⁰ ohms! This means that whatever instrument you use to measure the voltage output of the pH probe needs to have an input impedance at least an order of magnitude (i.e. 10

times) higher.

The second problem that has to be tackled has to do with the "slope" variation with temperature of the pH electrode. The output of an electrode is typically 60 mV per pH unit, i.e: for a change in pH of a solution from, say, 7.5 to 8.5, the probe's output voltage will vary 60 mV. The electrode generates a positive voltage for pH values less than pH 7 and a negative voltage for pH values greater than pH 7. The electrode output is zero at pH 7.

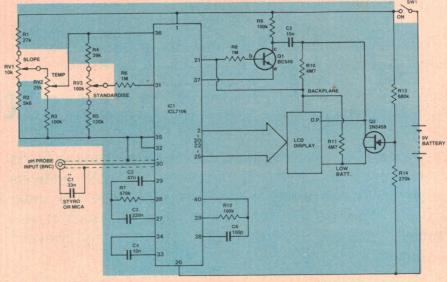If you plot a graph of probe output versus pH, where pH is represented on a log scale, you get a straight line as illustrated by the unbroken line in Figure 1. However, that line is only correct for one temperature. At another temperature, a



PIN 30 DIRECTLY CONNECTED TO SCREENED CABLE
C1CONNECTED BIRECTLY AT BNC CONNECTOR

line having a different "slope", indicating that the probe's nominal "mV per pH unit" output has varied, results as illustrated by the broken line in Figure 1. In general, a probe's sensitivity (mV per pH unit) increases with increasing temperature and vice versa.

The slope of a probe also varies with the age of the unit. Regular calibration checks remove any error that this may bring to the reading.

There are two general ways to correct for slope variations with temperature: by means of a manual control in the circuit, or automatically. For obvious reasons, the first method is the simplest and that's what we've elected to do. Fortuitously, the input impedance of an ICL7106 analogue-to-digital conversion IC is around 10¹¹ to 10¹² ohms which is just what we need, apart from providing an appropriately scaled digital output to drive a display. Consequently, most of the circuitry for the pH meter is contained within two ICs; the ICL7106 and an LAD204 LCD display. The external circuitry is used to provide the appropriate scaling (so that the display reads directly in pH units) as well as slope and temperature compensation controls.

As this is a battery operated instrument, we thought it would be convenient to have some indication of when the battery was getting low. Surprise, surprise — the LCD display we chose incorporates a little "low batt." warning display in the top left hand corner. This is activated with a little extra circuitry once the battery voltage falls below 8.5 volts.

HOW IT WORKS — ETI 572

The instrument employs a single-chip analogue-to-digital (A/D) converter IC, type ICL7106, driving a liquid crystal display. Virtually all of the instrument is contained within the A/D converter chip and display. Operation of the 7106 is explained in a separate box. The reference voltage for the A/D converter is varied by three controls to provide the appropriate 'scaling' of the input so that the instrument reads directly in pH units, corrected for "slope" and temperature variations.

Input to the 7106 is applied between the IN LO pin (30) and COMMON pin (32) as the input is negative-going and we require a display which reads positive. The IN HI pin (31) has a portion of the reference voltage applied to it via a resistive divider involving R4, RV3 and R5. This sets the display to read (positive) 7.00 when the input is zero i.e: when the probe is in a pH 7.00 solution.

The A/D converter reference is developed between pins 35 and 36, derived from a resistive divider pick-off between the positive supply rail and the COMMON pin (32).

Varying the reference voltage by a small amount is used to provide temperature and "slope" compensation. The SLOPE control is part of the reference voltage divider and pro-

vides a 'vernier' control over a reasonable range, so making the control easy to adjust. The TEMPERATURE control forms part of a resistive divider from the wiper of the SLOPE control, RV1. Again, this provides a vernier adjustment. The voltage appearing on the wiper of RV2 is applied to the REF HI input of the 7106. The whole arrangement minimises interaction between the controls.

The internal clock of the 7106 is run at 50 kHz for maximum mains hum rejection, as explained elsewhere. The LCD display is driven by a square wave signal between the backplane and the numeral segments. This is provided by the 7106 from pin 21. The decimal point requires a drive signal in anti-phase to this and Q1 is arranged as an inverter to provide the appropriate drive to the decimal point.

The LOW BATT. indicator is activated by Q2. The gate of this FET is biased by a voltage divider using R13 and R14. When the battery voltage falls below about 8.5 V, Q2 turns on and applies the anti-phase backplane signal (from the decimal point drive) to the LOW BATT, pin on the display.

Hum filtering at the input is provided by a 33n capacitor connected directly across the input socket.

The pH probe

The pH probe we obtained for our instrument comes from Starcross Scien-

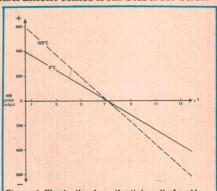


Figure 1. Illustrating how the "slope" of a pH electrode's sensitivity varies with temperature.

tific, P.O.Box 151, Frenchs Forest, NSW 2086. They are available mail order for \$45.70 which includes sales tax and delivery. The probe, designated G101NFE, comes complete with a plastic protector cap, a wetting cap for storage and a comprehensive booklet plus two 200 ml containers of buffer so-

lution, one of pH 6.88, the other pH 4.00. A BNC plug is fitted to the coaxial cable connection. The probe is a "non-flow" or sealed type and will have a long life without needing replenishment of the internal electrolyte.

In addition, Starcross have available accessories such as 100 ml plastic

beakers and plastic wash bottles. They can also supply spear point electrodes suitable for soil analysis.

Construction

The pH meter is housed in a plastic box measuring $150 \times 80 \times 50$ mm, although a 'zippy' box of similar size having an

ABOUT THE 7106

The ICL7106 is manufactured by Intersil of the USA and contains all the circuitry for a digital panel meter employing the 'dual-slope integration' technique all housed in a 40-pin dual-in-line package. It is designed to drive any multiplexed 3½-digit liquid crystal display. A companion chip, the ICL 7107 is designed to drive any suitable 3½-digit LED display.

The internal circuitry of the 7106 can be divided into several areas: firstly there's the precision dual-slope integration type analogue-to-digital converter, then display decoder/driving circuitry and display multiplexing.

The precision dual-slope A/D converter is the most important, so let's take a close look at that.

In this method of A/D conversion the analogue input voltage is first converted to a time period which in turn is converted into a binary number by a timer/counting system. Referring to the block diagram here, and the associated timing diagram, the system commences the measurement when the switch connects the analogue signal input to the integrator which commences to 'ramp up'. At the same time the counter begins. from zero, to count the clock pulses. When a predetermined number of pulses, 1000 with the 7106, appear in the counter, the integrator is electronically switched over to the reference voltage. At this point, the integration capacitor, C, has then charged linearly from the input, rising as a ramp voltage to a level decided by the average input signal value over the counter time period (T). As the switch changes to the reference, the counter is reset to zero and commences counting again. The reference, which is of opposite polarity to the input signal, now causes the charged integration capacitor (C) to ramp downward with a fixed slope. When the output of the integrator reaches the zero threshold the counter is stopped and its contents displayed on the digital readout. The count displayed is the ratio of the counts during the 'downward' ramp (over time 't') to the counts during the upward ramp. Thus, for a limit of 1000 counts during the upward ramp, a direct reading of input voltage is obtained if the reference voltage is chosen appropriately.

The absolute value of the integration capacitor and the clock frequency are of little significance provided they are stable for the duration of the conversion period.

The relatively long analogue-todigital conversion period has an inherent advantage in that it ignores noise. When noise is integrated over an extended period, its amplitude tends to zero. Thus, dual-slope integration results in excellent accuracy.


The 7106 has an on-board clock oscillator, the frequency of which is determined by external RC components - R3 and C4 in the circuit here, connected between pins 38 and 39. The clock frequency has been set to 50 kHz for the pH meter project. The oscillator frequency is divided by four internally to give a clock period of 80 us. As the integration period is 1000 clock periods long, the analogue input is integrated over a period of 80 ms. This results in pretty nearly optimum mains hum rejection as any 50 Hz ripple on the input will be integrated over four cycles and will thus have a dc value approaching zero

Clock input is to pin 40 (TP5 in the circuit here) and the 7106 may be driven from an external clock if so desired. It requires a square wave drive of 5 V amplitude, positive with respect to the **common** pin. For external clock drive the clock RC network (R3-C4) is not required.


The A/D converter reference voltage is developed between pins 35 and 36 (REF LO and REF HI respectively). Pin 35 is set internally to be always 2.8 V lower than the positive supply rail applied to pin 1. The full-scale sensitivity of the 7106 can be 'programmed' by setting the value of the voltage between the REF LO and REF HI pins. For full-scale sensitivity (reading of 1999 on the display) the voltage between pins 35 and 36 should be set to 100 mV, for 1 V sensitivity it should be 500 mV and

Input current drawn by the 7106 is extremely low, typically one picoamp (1 pA or 10⁻¹² amp as it has an input impedance measured in Giga-ohms (10⁹ ohm)! For this reason, the unit can be used to measure voltage sources having a source impedance up to 10¹¹ ohms — making it ideal for application in a pH meter. A useful spin-off from the 7106's high input impedance is that

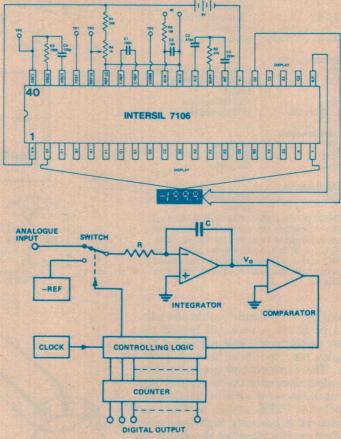only quite small value capacitors are required in parallel with the input to provide good hum rejection. In addition, the input impedance is readily defined by using an appropriate value parallel resistor or simple attenuator on the input.



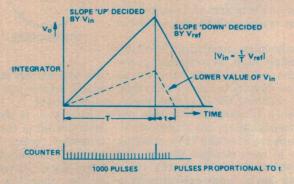Block diagram of the 'dual-slope integration' technique of analogue-to-digital conversion commonly used in digital meters.



Timing diagram for the dual-slope A/D conversion technique.

Project 572

PARTS LIST —	ETI 572
Resistors all 1/2W, 5%	ne Close that with finds
R127k	
R25k6	成功性 四個問題的學
R3, 9, 12 100k	The second second
R439k	
R5 120k	
R6, 81M	
R7	
R13680k	
R14	
114	
Capacitors	
Č133n s	
C247ng	reencap or
polyc	arbonate
C3220n	
polyc	arbonate
C4, 5 10n g	greencap or
polyc C6 100p	ceramic or mica
Со	ceramic of mica
Semiconductors	
Q1 BC54	49, BC109 or similar
Q22N54	
simila	
IC1 ICL7	106 see text
LCD Display LAD	204 see text
Potentiometers	
RV110k1	inear
RV225k1	
RV3 50kl	inear
100000000000000000000000000000000000000	
Miscellaneous	The second second
SW1 SPS	
Switc	
ETI 572 pc board; plastic box 50 mm; battery clip and	
battery; length of 4 mm diar	neter coaxial cable
RG174 or similar — not sh	ielded audio cable:
BNC socket (teflon insulate	
hand); three collett knobs;	
bolts etc.	

aluminium front panel would also suit. The pc board is mounted behind the front panel, positioned such that the display may be viewed through a cutout. The three control potentiometers are also mounted on the front panel. The input connector is a BNC coaxial socket which has PTFE insulation. This was chosen as it has very high insulation resistance. We mounted the socket on one end of the case and it is connected via coaxial cable. The battery was mounted on the bottom of the case, held in place with double-sided adhesive tape.

Since the input impedance of the 7106 is extremely high, as explained previously, the input pin (pin 31) must be connected directly to the coaxial cable, without touching the fibreglass board. To do this a 1.5 mm diameter hole was drilled through the pc board immediately beneath pin 31 of the 7106, allowing the pin to pass straight through the board where the cable to the input connector can be terminated directly to it. If you look at the pc board artwork,


TO PH PROBE INPUT SOLDER LUG BRAID **RG174 COAXIAL** CABLE CENTRE CONDUCTOR _R11. INSULATED WIRE LINK SEE DETAIL Y SW1 POWER BATT RV1 RV2 RV3 10k 25k STANDARDISE TEMPERATURE SLOPE


you will see this drill hole marked by a small square pad with a drill centre marked on it.


First step in the construction is to drill the lid of the case for the potentiometers, power switch and display cutout. This is best done by using the front panel artwork as a template. Scribe around the inside of the cutout, then mark a parallel line about 2 mm

inside this. Drill a series of 3 mm diameter holes using this inside line as the drill centre line, and then pop out the centre of the cutout. Use a flat file to smooth off the edges to the first scribed line.

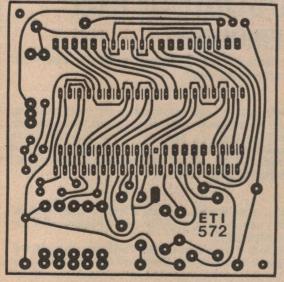Mark the centres of the potentiometer holes and centre punch them. These holes are drilled to 10 mm diameter. The hole for the power switch should be



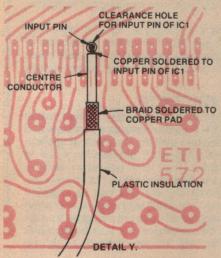

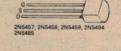

Top right: view of the printed circuit board, showing the liquid crystal display.

Right: showing the rear of the pcb, with connections to the probe and potentiometers.

marked in the same way and drilled to 6 mm diameter. Next, mark and drill the hole for the BNC input socket (also 10 mm diameter).

The front panel transfer should not be attached yet. The pc board is mounted behind the front panel using two countersunk-head bolts and nuts either side of the board to position it. Using the unloaded pc board as a template, mark and drill the holes for the bolts that are to hold it. Countersink the holes on the upper side of the panel.

The pc board may be tackled next. All the smaller components should be mounted first. The capacitors are bent down onto the board so that they will be lower than the display. Capacitors C2, C3, C4 and C5 can be greencap, polycarbonate or mylar capacitors. If you have bought an Intersil ICL7106EV digital panel meter evaluation kit, some of the components may be used in the sonly solder those pins which are acproject. The clock capacitor, C6, can be either an NPO ceramic type or silver


mica. The evaluation kit uses a 100p silver mica type for this capacitor.


Next mount transistor Q1, and the FET Q2, pushing them hard down on the pc board so the tops of their cases will sit below the display (when it is mounted). The FET has an unusual pinout configuration so be extra careful that you insert it the right way round.

Mount the 7106 IC as shown in the overlay diagram, being careful to orient it correctly. Forty pin ICs are very hard to get out again!

We mounted the display directly above the 7106 on two rows of Molex pins. This permits quite a compact pc board and elevates the display somewhat above the surrounding components on the board. It may also be unplugged, which might be necessary as we explain shortly.

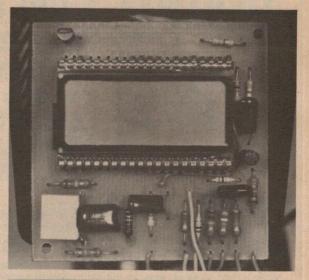Insert the two rows of Molex pins, but tually used. Those pins not having pc



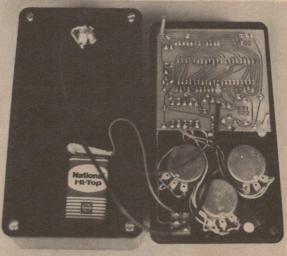

When the pins are in place, bend back the steel connecting strip between the pins with a pair of long-nose pliers until the strip breaks off. The unused pins will come away with it.

Some displays do not have pin 1 designated, but if you turn the display edge-on to the light you should be able to see the numerals faintly. Alternatively, you have a 50-50 chance of getting it right (or wrong — but we're optimists!) if you take a guess

Mount and wire the three potentiometers and the power switch next. Connections are indicated on the wiring diagram. The potentiometer terminals are positioned at odd angles so that they can be fitted in the available space. This necessitates the use of collet knobs so that the pointer can be positioned correctly in relation to the shaft. Some small grub-screw knobs will work, but you may have to shop around. Speaking of Shoparound, see page 85 this issue for board tracks attached are not used. details on where to buy suitable collet



\$100 MICROCOMPUTING WE TAKE S100 SERIOUSLY

Introducing a high quality, cost-effective, locally produced S100 microcomputer system. And we are proud of our achievement!

QUALITY IS BUILT IN

For a system to be of truly high quality, each element must meet exacting standards. We began our system by designing our own 12-slot motherboard, power supply, and cabinet. We then chose a series of S100 boards whose reliability and performance was well-known; added a floppy disc subsystem; and found a VDU with just the right features we wanted. The result was a complete microcomputer system with impressive specifications.

THE BASIS

As the motherboard is the link between all system components, it deserves special attention. We incorporated stateof-the-art design features like true active termination, and microstrip interconnecting lines. Crosstalk between adjacent lines and signal reflections have been largely eliminated for reliable data transfer, even at the high operating speeds of the new microprocessors.

The power supply has been designed for dependable operation and offers substantial scope for expansion. A full 20A at 8 volts and 4A for the other two supplies is sufficient for an entire complement of cards. You may not need all the capabilities now, but its nice to know they're there when you do.

A lot of effort went into producing an aesthetically pleasing case. Constructed of aluminium and only seven inches high, the cabinet is finished in textured beige and brown with a silk-screened front panel. Its appearance makes it equally suitable for the laboratory or office environment. A cooling fan is supplied as standard.

BUT WHAT'S INSIDE?

The heart of the system is the SBC200 by S.D. Systems, a Z-80 based CPU running at 4 MHz. An RS232 I/O port allows connection to a terminal, and a parallel port to a printer. Automatic baud rate selection is provided by virtue of a counter/timer circuit, three channels of which can be used for other functions. Up to 16K of EPROM can be stored on the CPU card, making for a compact system.

The concept of efficient use of components is further demonstrated by the dynamic memory card. One ExpandoRAM 2 can hold up to 64K bytes of RAM, expandable to 256K bytes using the latest chips. The bank select feature allows the use of up to eight boards simultaneously for multiuser applications.

Either single or double density recording is possible with the Versafloppy 2 disc controller. Both eight and five inch drives may be used, in combination if required. Phase locked loop data recovery circuitry ensures data integrity and high relia-

In combination with the Versafloppy 2, our dual eight inch floppy disc subsystem can store up to two megabytes of information. Packaged in a cabinet matching our card cage, it comes complete with double sided drives, power supply, cooling fan and cable.

SO, WHAT DO YOU GET?

The combination of our cabinet, floppy disc system, visual display unit, and three S100 cards produces a complete and very powerful microcomputer system. Its areas of application are numerous, including word processing, small to medium businesses, accounting work, education, and research. And you will be pleasantly surprised at its low cost. But the good news is that any element can be obtained separately. You can start in a small way and expand when the need arises, knowing that all parts are designed to work together perfectly. Further extension will also be possible: multiuser and hard disc systems are currently being developed.

Price for a complete system with 48K memory, 2 megabytes of disc storage, and a Visual 200 VDU is \$4995 plus sales tax if applicable.

SYSTEM PRODUCTS

S100 CARD CAGE

Attractive sprayed aluminium, complete with 12 slot motherboard, cooling fan, and 20A power supply. Fully assembled & tested. \$350 FLOPPY DISC SUBSYSTEM

In a matching cabinet to our card cage, complete with twin double-headed Remex or YE Data drives. Fully assembled & tested with cable. \$1850.

SBC 200 SINGLE BOARD COMPUTER

280 AND SINGLE BUARD COMPUTER
2.80 based 4 MHz microcomputer with 1K RAM and sockets for 8k/16K PROM, synchronous and asynchronous serial I/O port with software programmable baud rate generator, RS232 interface, parallel ports, four channel counter/timer, power-on jump, and vectored interrupt operation. Kit with monitor in 2716 PROM \$350

EXPANDORAM 2 DYAMIC RAM
A single dynamic RAM card that will hold 64K. Expandable to 256K
with the latest chips. Page mode operation allows the use of up to
eight boards for multiuser applications. Supplied with 200 nS 2116's
for 4 MHz operation. Ideal for use with the SBC 200 and Versafloppy
2. Kit 16K \$360, 32K \$440, 46K \$520, 64K \$500

VERSAFLOPPY 2 DISC CONTROLLER

State-of-the-art controller operates with all combinations of drive types in single or double density modes, and has PLL data recovery circuit. Operates with SDOS or CP/M 2.2. Kit \$350

PROM 100 PROM PROGRAMMER
Capable of programming all popular EPROMs such as 2708, 2758, 2716 and 2732. Zero insertion force socket is standard. Kit \$199

VDB 8024 VIDEO DISPLAY BOARD
On-board 2-80 and CRT 5037 controller I/O mapped, 80 x 24 lines plus programmable characters. Kit \$370.

Z-80 STARTER KIT
This is a unique design, especially suitable for education, control applications, experimentation, and for those who want a complete system for the lowest possible outlay. It is a complete microcomputer based on the Z-80 and contains a keyboard and seven segment display, Ideal for evaluting the Z-80 or learning about microprocessors, if provides 1K of memory on board (expandable to 2K); contains a PROM programmer that is suitable for the Z-758 and 2716 EPROM's: includes a cassette interface for the storage and loading of programs; and comes with a powerful monitor (ZBUG) that provides a large number of functions. A wire wrap area allows the addition of custom circuitry, and the provision for two \$100 sockets means expansion is almost limitless. Two bidirectional I/O ports and a counter/timer circuit completes the impressive list of features. Kit \$340.

We strive to present only top quality boards and systems at competitive prices. We can supply all requirements from single S100 boards to complete systems with software. Please write for our catalogue or for specific information on any product.

Prices are tax free; add 15 percent sales tax if applicable. For built and tested prices, add \$50 to kit prices. Mail orders are welcome; add \$3 for postage.

MICROTRIX PO BOX 158 Hurstbridge, Vic., 3099, Ph. (03) 718-2581.

Project 572

knobs. Wire the battery clip and power switch last.

At this stage you can check to see if you have the display inserted the correct way round. Temporarily plug in a battery and turn the unit on. If all is well, you will see numbers come up on the display. If not, no numbers will appear. Unplug the display and reverse it if this is the case.

With all the components mounted, the pc board can now be mounted to the front panel. Adjust the position of the board so that the display sits firmly behind the cutout in the panel, but don't strain the board.

Finally, solder the coaxial cable from the input socket to the pc board as indicated in the accompanying diagram. Make sure that you use good quality coaxial cable such as RG174 (4 mm dia.), not ordinary 'shielded cable' as its insulation resistance is not good enough for this application. Also ensure that the PTFE insulation on the BNC socket is clean and free from flux. If necessary, wash the socket in alcohol.

Terminate one end of the cable on the socket being careful not to leave any flux on the socket's insulation, or heat the coaxial cable insulation too much. Use a good hot iron with a clean tip and solder quickly. Use a large solder lug

under the socket's nut for the braid connection or solder the braid to the edge of the nut. Capacitor C1 mounts directly across the input socket and it must be a styroseal or mica type.

Cut the cable to about 150 mm length and terminate the other end to the input pin of the 7106 as shown in the drawing on page 26. Don't let flux flow down onto the hole in the pc board or allow the solder bead at the joint to touch the board.

Now you can plug in the battery and your pH probe and give the unit a try. If all is well, the front panel artwork can be mounted. Scotchcal panels will be available from the usual suppliers (see ETI October 1980, p. 65).

Using the instrument

Before making a measurement, the instrument should always be 'buffered'. Remove the wetting cap from the probe and attach the plastic protective cap—that little bulb on the end is *very* fragile. Set the TEMPERATURE control to room temperature (say, 25)—the scale on this control is marked in degrees centigrade (°C). Clean the electrode with distilled water if you have used it recently.

You will need two buffer solutions,

one having a pH near 7 and the other a pH near 4. The two most commonly available have a pH of 6.88 and 4.00. Put the probe in the pH 7 solution and adjust the STANDARDISE control for the correct reading according to the marked pH of the buffer. Allow about two minutes or so for the reading to stabilise before finally adjusting the control. Remove the probe and wash it again in distilled water.

Now put the probe in the pH 4 buffer and allow the reading to stabilise. Then adjust the SLOPE control for the correct reading according to the marked pH of the buffer.

Go through the procedure again to ensure correct adjustment. Only then can you take a reading in the solution or solutions to be tested. Wash the probe before making a measurement and between successive measurements.

If the temperature of the solution, or solutions, to be measured differs substantially from the temperature of the buffers, set the TEMPERATURE control to approximately the temperature of the solution to be measured. This control only has a minor effect and its operation is very 'broad'.

There you have it, your own digital pH meter with an Australian-made probe to boot!

THE CARE & FEEDING OF YOUR PH ELECTRODE

To ensure the maximum life and best response from your pH electrode, the following procedures are recommended.

1) When not in use the pH electrode should be stored with its tip soaking in distilled water. It is important that the porous glass membrane and salt bridge are not allowed to dry out. If for some foolish reason this does occur the electrode will require soaking in distilled water for 24 hours before it can next be used.







Store the pH electrode with its tip soaking in distilled water, use the protective shield and rinse with distilled water between measurements.







NEVER clean a pH electrode on a rag, or on your sleeve, or under a running tap.

- For long term storage, cover the glass bulb with a 'wetting cap' containing distilled water. (Note that plastic wetting caps are supplied with the Australian-made lonode pH electrodes).
- 3) When in use, the electrode should be rinsed thoroughly with distilled water (preferably applied with a fine-nozzled wash bottle — see the accompanying illustration) between successive readings and between buffer calibrations.
- 4) If the electrode is used with non-clean or organic solutions the electrode may require extra cleaning from time to time. The most common method used is to soak the electrode for 24 hours in a '0.1 normal' hydrochloric acid solution. Alternatively, simply soaking the electrode in a mild solution of household detergent and distilled water will generally emulsify the contaminants and restore the electrode to normal.
- 5) Always be careful not to touch, scratch or damage the porous glass membrane. It is advisable to use a plastic protector cap as shown in the accompanying illustration. (These are supplied with the lonode electrode).
- Generally, a sluggish response from the electrode will indicate that it needs cleaning.

For troubleshooting other problems it is best to consult the instruction booklet supplied with the electrode or the supplier from whom you purchased the electrode.



Until now, building your own computer could cost you around \$600 — and still leave you with only a bare board for your trouble. The Sinclair ZX80 changes all that. For just \$295 you get everything you need including leads for direct connection to your own cassette recorder and television. The ZX80 really is a complete, powerful full-facility computer matching or surpassing other personal computers costing much more. The ZX80 is programmed in BASIC and you could use it for anything from chess to running a power station.

Two unique and valuable components of the Sinclair ZX80: the Sinclair BASIC interpreter and the Sinclair teach-yourself BASIC manual. The unique Sinclair BASIC interpreter: offers remarkable programming advantages — unique 'one touch' key word entry. The ZX80 eliminates a great deal of tiresome typing, Key words (RUN, PRINT, LIST etc) have their own


single key entry. Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately, preventing entry of long and complicated programs with faults only to discover them when you run.

Excellent string handling capability — takes up to 26 string variables of any length. All strings can undergo all rational tests (e.g. comparison). The ZX80 also has string input to request a line of text; strings do not need to be dimensioned. Up to 26 single dimension arrays. FOR/NEXT loops nested up to 26. Variable names of any length. BASIC language also handles full Boolean arithmatic, conditional expressions, etc.

Exceptionally powerful edit facilities, allows modification of existing program lines. Randomise function, useful for games and secret codes. Timer under program control. PEEK and


POKE enable entry of machine code instructions, USR causes jump to a user's machine language sub-routine. High resolution graphics with 22 standard graphic symbols. The Sinclair teach-yourself-BASIC manual 96 page book free with every kit.

Fewer chips, compact design, volume production means MORE POWER FOR YOUR DOLLAR! The ZX80 owes its low price to its remarkable design; the whole system is packed onto fewer, newer more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system and monitor. And the ZX80's IK byte RAM is roughly equivalent to 4K bytes in a conventional computer because the ZX80's brilliant design packs the RAM so much more tightly. (Key words occupy just a single byte). You can add to the memory via the expansion port, giving a maximum potential of 16K.

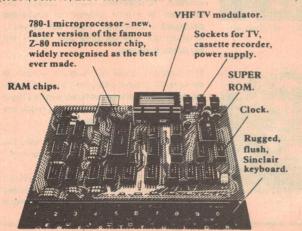

Quantity	Item	Item Price	Total
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price incl. ZX80 BASIC manual, excl. mains adaptor.	\$295.00	
	Mains Adaptor(s) (600Ma at 9V DC nominal unregulated).	\$ 9.50	
	Memory Expansion Board(s) takes up to 3K bytes.	\$ 28.50	
	RAM Memory chips — standard IK bytes capacity.	\$ 10.00	
	Sinclair ZX80 Manual(s) free with every ZX80 computer.	\$ 15.00	TWO
I enclose o	cheque/Bankcard/Diners Club/Amex	TOTAL	19.0

Fantastic new options for Sincleir

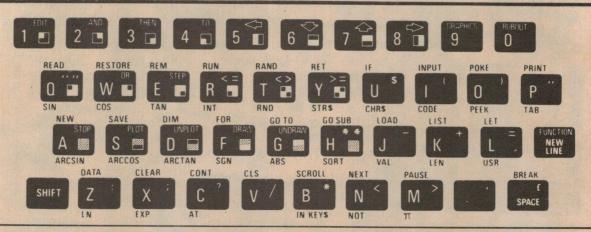

THE CHIP

a drop-in replacement for the existing 4K BASIC ROM, comes with a new keyboard template and a supplementary operating manual. Designed for high-level, full facility computing.

KEY FEATURES INCLUDE —

- Full floating-point arithmetic to 9-digit accuracy.
- Logs, trig, and their inverse functions, graph plotting facility.
- Animated displays using PAUSE n.
- Full set of string-handling facilities.
- n dimensional arrays, cassette LOAD and save with named programmes.

AND ZX80 16K-BYTE RAM PACK

Complete module designed to provide massive add-on memory capacity.

The 16K-BYTE RAM pack can be used for program storage or as a database. Yet it costs up to half the price of competitive additional memory.

Measuring 3 in \times 3 in \times 1.25 in approx., the RAM pack plugs into the existing expansion port on the rear of the Sinclair ZX80 via an edge connector. No additional power supply is needed.

SINCLAIR EQUIPMENT (AUSTRALASIA) PTY. LTD.


308-312 High Street, Kew, Vic., 3101. Tel. 861 6224.

SE3

SERIES 3000 COMPACT STEREO AMPLIFIER

reprint of pc board overlay

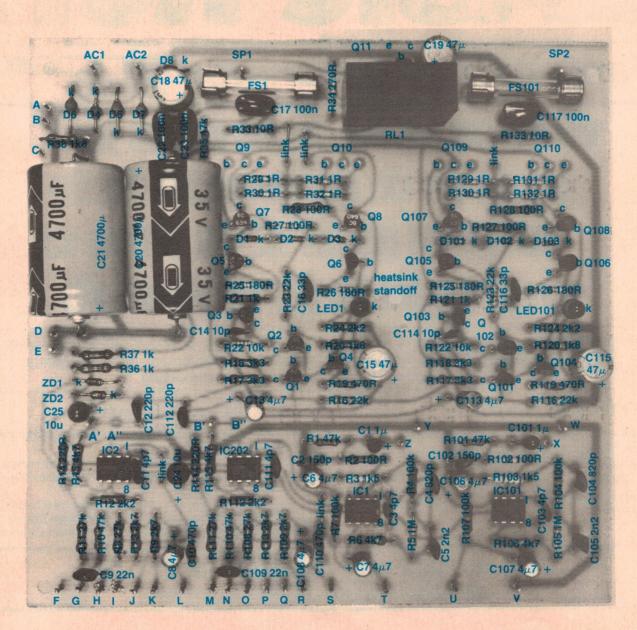Owing to a printer's error, this overlay was not reproduced correctly in last month's issue. In addition, some artwork came off the overlay and this has been corrected here.



OHN F. ROS COMPUTER SERVICES PT

33-35 ATCHISON STREET, ST. LEONARDS, N.S.W. 2065 AUSTRALIA

The NDK S-4000 Wordprocessing Printer

For all bulk wordprocessing applications where reliability, speed and sustained print quality are of prime importance.

The NDK S-4000 is supplied with a heavy duty 16 wire head producing single pass high quality 17 x 16 matrix characters at 75 characters/second for wordprocessing quality and 150 - 200 characters/second

Four fonts (dot matrix, wordprocessing, super/subscript and Katakana) are supplied as standard. Typical scientific, mathematical and currency symbols are included as standard. The fonts can be intermixed as bold faced, enlarged (5 CPI, 17 x 23 matrix), reduced (12 CPI) or normal (10 CPI). Other fonts can be specified by the user. Each dot on the 16 x 16 matrix can be programmed by the host computer to produce special graphic effects (such as Letterheads and trade marks). Full page graphics is possible by controlling ten wires of the printer and executing half-line feeds. John F Rose Computer Services Pty Ltd will be supplying software to enable the user to specify and print special characters for any row/column position. The special patterns can be printed at the rate of 900 dot columns/second at a resolution of 4.7 dots/mm (120 dots per inch) both horizontally and vertically. A horizontal dot resolution of 240 dots per inch can be

produced using half dot timing.

Superscripts and subscripts are produced by the superposition method enabling complicated mathematical formulae to be produced quickly and easily. The subscripts and superscripts are half normal size and the printing pitch is half that of the PICA (see Specification.).

Dot (or Graphics) Mode

The Dot (or Graphics) mode can be entered by software instruction or by pulling the MODE signal pin of the interface low.

Dot Mode by MODE signal

The MODE signal should only be changed between the ACK and DSTB signals. MODE signal changes are limited to 40 times per line. When the MODE is pulled low, the first data byte sent after the change controls print needles 1 to 8 and the second byte controls pins 9 to 16. The third byte controls pins 1 to 8 of the next dot column to be printed and so on. The character mode is re-entered when the MODE signal is

Expanded graphics patterns can be printed vertically in the pitch of 1/12" by using 10 needles and Half line Feeds.

The printer has a built-in test mode and the following STATUS signals are displayed on the control console:

Out of paper

Over-run (no punched hole found)

Sensor Alarm — failure or timing sensor or carriages locked

Head drive Protect — failure of drive circuit of printhead

Motor drive protect

Failure of 30 volt DC supply 6

RAM error

ROM error

Input error (more than 20 software mode changes/line)

Firmware failure

5v supply failure

SPECIFICATIONS

Printing method:

Dot Matrix impact

Printing direction:

Serial printing by 16 wire head Bi-directional printing with logic seeking and 762 mm/second (max.) space skipping function.

136/68

163/81

Printing Characteristics Character Mode (Normal/Enlarged) **Printing Speed** (char/sec) Pitch (CPI)

Line length (char/line) Character Mode (Normal/Enlarged)

Printing Speed (char/sec) Pitch (CPÍ) Line length (char/line)

Regular Mode **Draft Mode** Pica Elite 75/37.5 90/45 Elite Pica 150/75 180/90 10/5 12/6 10/5 12/6

Sub/Superscript Pica Elite 150/75 180/90

136/68 163/81

20/10 24/12 272/136 326/163

Dot Density: Character set: 4.7 dots per mm. 160 codes (JIS c6220, 8 bit) plus special characters. 2 modes (regular and draft) 6 lines per inch or 12 lines per inch

45 lines/second (slew rate 6 lines per inch) 40 ms max. (single feed)

V.F.U.: Ink Ribbon:

Line Feed:

Optical 2 channel (8 bit punched tape) Underwood spool, nylon fabric ribbon 13mm x 27m or 13mm x 11m 4" to 15" inches width continuous paper

Paper: with sprocket holes for tractor feed. Copy: 1 original and 5 copies with 34Kg no carbon paper.

Buffer: Interface:

2 separate line buffers. 8 bit parallel TTL level (Centronics) RS232c Serial interface

2000 hours

MTBF:

7 years (Head life: 100 million characters in regular mode).

The following come as standard and are included in the price shown.

Parallel or RS232c Serial Front or rear paper feed

Adjustable tractors

2 x Form Control Loops & 2 Ribbons. Sound proofed contoured casing

G Ease of maintenance (only 3 major sub-assemblies)

6 months' warranty

\$3,190.00 plus \$390.00 sales tax. The above price is firm for all orders taken before 31/1/81.

NDK S-4000

MATHEMATICS SAMPLE USING STANDARD CHARACTERS

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{RMS} = \sqrt{4KTR(f_2 - f_1)}$$

$$L_1 = 10 \log \frac{1}{80} \times S_m \text{ (dB)}$$


$$L = \int_{0}^{x} \left[\frac{dx_{1}}{d\theta} \right]^{2} + \left[\frac{dy_{1}}{d\theta} \right]^{2} d\theta$$

$$x = \begin{vmatrix} c_{1} & b_{1} \\ c_{2} & b_{2} \end{vmatrix} \div \begin{vmatrix} a_{1} & b_{1} \\ a_{2} & b_{2} \end{vmatrix} = \frac{c_{1}b_{2} - c_{2}b_{1}}{a_{1}b_{2} - a_{2}b_{1}}$$

SEND \$1.00 FOR YOUR COMPREHENSIVE CATALOGUE

TELEPHONE (02) 439 1220 TELEX AA 27901

LIGHTING FOR ENTERTAINMENT

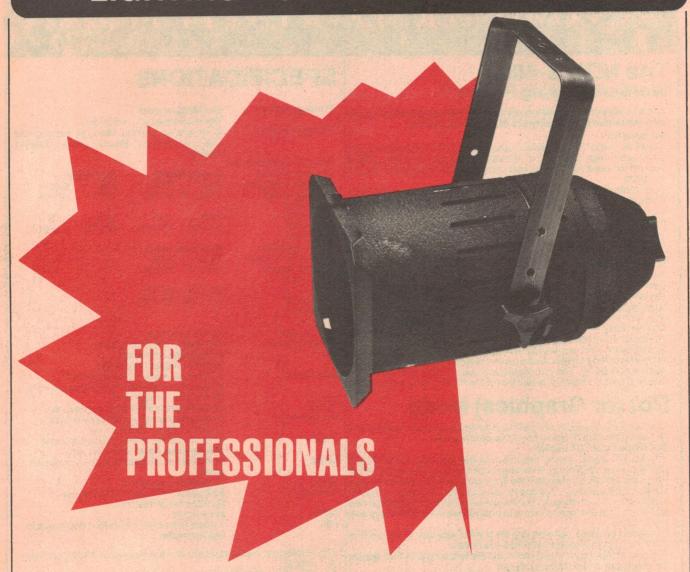

SPECTRUM'S PAR 64 UNIT

This New, Versatile fitting is Top of the Range when it comes to a really professional Lighting Effect. It's compact, extremely light weight, and modular appearance certainly alleviates the hard work previ-

ously experienced when setting up shows with heavy, hard to handle fittings, and can be managed easily without any specialised training.

This unit has been designed to accept PAR 64 lamps which can be alternated to produce a very narrow

spot of light through to a full flood effect.

These lamps are also complemented by the intense colour range available from Rosco.

To implement a variety of colour, quickly and efficiently, easy colour change is imperative. This unit does not require exact colour size as it has no separate old fashioned frame. Its compact design incorporates a built in filter frame which folds away any excess material.


SPECTRUM LIGHTING COMPANY

18 THOMAS STREET, CAVAN, SA, 5094 PHONE (08) 260-2500, A.H. (08) 263-8665

THE PROFESSIONAL LIGHTING EQUIPMENT

CONTROLLER

FILTER

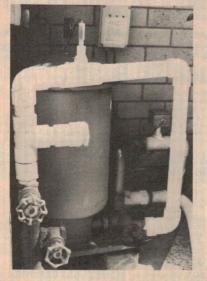

The POOL MAGIC chlorination controller

POOL

For many years municipal swimming pools have used liquid chlorine (sodium hypochlorite) for sanitizing swimming pool water. Liquid chlorine offers many advantages over dry chlorine (calcium hypochlorite) when used in swimming pools. Liquid chlorine is completely soluble and fast-acting. It leaves no residue, eliminating the problem of 'calcium scale' experienced by most pool owners using dry chlorine.

Commercial installations have shown that dosing with chlorine once per day is a very inefficient and uneconomic way of chlorinating a pool. The pool will have a very high chlorine level following dosing. The chlorine level is depleted during the day until virtually no free chlorine exists in the pool when the next day's dose is due.

A much better system is to dose the pool only when it needs chlorine — when the free chlorine level falls below the ideal level. The pool is then maintained at the proper chlorine level all the time. Commercial and municipal pools employ this sytem.

Such a system has now been developed for household and commercial installations. POOL MAGIC provides an efficient and reliable way to dispense liquid chlorine. It employs a sensing device and an electronically-controlled valve to dispense chlorine when the chlorine level falls below that required. The POOL MAGIC system eliminates the need for daily dosing and chlorine testing.

POOL MAGIC employs a probe that measures the oxidation-reduction potential of the pool water. This potential is a measure of the ability of the water to kill bacteria and algae and is proportional to the free chlorine level of the pool. There are three components in the system: a sensing probe which is attached to the return-to-pool line, a solid-state controller and a solenoid injector valve. The latter is mounted on the pool suction line.

You can easily install the POOL MAGIC system yourself or, alternatively, installation can be arranged through chlorine distributors located in major cities and towns.

POOL MAGIC has no external controls. The chlorine level is factory preset. All the customer has to do is turn on the power. POOL MAGIC will operate when the filter and pump are operating. POOL MAGIC is fully Australian made and comes complete with a 12 month warranty. The manufacturers of the POOL MAGIC have agreed to offer these units to ETI readers at a special price for a limited period. The POOL MAGIC equipment normally retails for around \$320 (not including chemicals or installation charges). The POOL MAGIC is offered to ETI readers for:

\$250

(not including chemicals or installation charges) plus \$5.00 packing and delivery charges.

CHEMICALS: For your convenience you can have liquid chlorine home delivered and the supplies will include information on where to get chemicals in your area if you tick the appropriate box in the coupon.

SOLENOID

OPERATED

PUMP

INSTALLATION: The POOL MAGIC is supplied complete with installation instructions and any reasonably handy person can install it for themselves. If you don't wish to install it yourself Starcross will include information on where to contact an installation firm in your area if you tick the appropriate box in the coupon. A nominal charge is made for installation.

If you would like more information about the POOL MAGIC equipment, you can 'phone or write Eddy Joseph at Starcross Pty Ltd, P.O. Box 151, Frenchs Forest, NSW 2086. Phone (02) 451-1346. The special price is only available if you order using the coupon on this page.

NOTE: This offer is made by Starcross Pty Ltd and ETI is acting as a clearing house only. Cheques or money orders should be made payable to POOL MAGIC OFFER and sent, together with this coupon (or a photostat of it) to "Pool Magic Offer", ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011. We will process our order and pass it on to Starcross Pty Ltd who will send you the goods. Please allow up to four weeks for delivery.

NOTE: Offer closes 31 January 1981

-	
	Enclose cheque or money order to total value and mail this coupon to: POOL MAGIC OFFER ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011
	Please send me the POOL MAGIC swimming pool chlorina-
	tion controller priced at \$250 (does not include chemicals or
	installation charges) \$250.00
	Packing and delivery\$5.00
	Please include nearest contact for chemicals
	Please include nearest contact for installation
	TOTAL
	Cheque or money order number
	Signature
	(Please print name and address clearly)
	Name
	Address
	10 10 10 10 10 10 10 10 10 10 10 10 10 1

·····Postcode ·····

PARTS FOR **NEW KITS**

If a kit you want to build is not listed, the parts may be ave Check the Dick Smith Catalogue: or call in to your nearest D

NEW EA MOSFET STEREO AMPLIFIER (See EA December) th's magazines SELECTALOT (See EA December

Cat. H-8384 \$3.00

AC MILLIVOLTMETER (See EA December)

Cat. H-8385 \$2.25

SYSTEM 80/TRS-80 INTERFACE (See EA November) PCB components are stock lines.

ELECTRONIC MUSIC GENERATOR (See EA December)
Implete kit, including instructions ... Cat K-3512\$12.50

B only ... Cat H-8382\$1.90

TRAIN CONTROLLER (See EA November)

Cat H-8381\$1.90

PCB omponents for this kit (including case) are normal s '3000' STEREO AMPLIFIER (See ETI November

H-863157 50 PCB All other components for this project are

MOISTURE INDICATOR (See ETI November)

Cat H-8632 \$1.90 All other components for this project are normal stock lines

EXPANDED SCALE AUTOMOTIVE VOLTMETER (See ETI Sept. Printed Circuit Board LM3914 IC Cat H-8630 \$1.50 Cat Z-6295 \$4.25 und or rectangular, large or small LEDs to suit y

CHASER (See EA August)
Complete kit, including front panel Ca Cat K-3145 \$69.50 Cat H-8379 \$5.95 PCB only

NASA POWER CHOPPER (See EA August)
Short form kit (All components & PCB) ... Cat K-3325 \$16.50
PCB only ... Cat H-8378 \$3.00

Short Form Kit (includes PCB components etc. but no case — build it into your dash hoard)

etc, bu Cat. K-3240 \$24.50

(All other comp

300 WATT AMPLIFIER (See EA June)
Cat H-8376 \$9.95

(Most other components are normal stock lines).

TV CRO ADAPTOR (See EA May)

Cat K-Complete Kit . Cat K-3060 \$29.95 . Cat H-8375 \$3.75

EA's NEW MUSIC GENERATOR

This is a great little kit for the beginner or the experimenter — it uses a very special IC which is pre-programmed with two popular tunes. It plays a complete melody — including chords (not just a few bars as other IC's). It is

intended for novelty or alarm applications: with a suitable amplifier it could be used as a singing doorbell.

ONLY

Cat K-3512

OPENING SOON AT SPRINGVALE

Yes, another Dick Smith branch will be opening early in the new year at Springvale to serve Melbourne's Eastern Suburbs. Watch your local papers for the opening date

CNR DANDENONG ROAD & SPRINGVALE ROAD, SPRINGVALE.



DON'T FORGET: ONLY 3 WEEKS TO CHRISTMAS!!! Need a few ideas for someone into electronics? Go no further than your nearest Dick Smith store!



CLEAN, HEALTHY AIR:

tou must have read press reports about the advantages of negative ions: how they help clean stale air, remove cigarette smoke and dust particles, etc etc.

They're very popular — and huge numbers of customers have been asking for them. We were worried by some reports that they also put out significant levels of dangerous zozone — now we've found an Australian made ion generator that does not emit Dzone. A written test from a leading University proves that it is completely safe.

So now you can have all the advantages of negative ions — and not worry about Ozone.

IDEA FOR LAST MINUTE XMAS ARRIVALS

. \$450

DAD? How many times has Dad come home late, because he'd left his lights on and the battery went flat? Here's a gift he'll really appreciate and it won't break your piggy bank! This light reminder connects easily to his car's electrical system (instructions supplied) and warns him if he leaves the lights on! Have a happy Dad: have a happy Christmas when you give him a

REMEMBER LAST YEAR

We had a very special special each month an Item which was actually BELOW COST? We didn't tell you what it was - you had to find out for yourself (we told you the month after!)

We stopped doing this but it seems we made a very wrong move. So many people have asked to our below cost special each month that every one instated. As we don't want to lose our store yoing to start our special again—next month So from January call into your nearest Dick Smith store and check out our below cost special

Don't try to remember

S139 DIGITAL

3

it - TAPE IT!

When it's important, don't rely on your memory. Tape those important conferences, sales meetings, interviews, etc for later reference. This budget-priced recorder takes standard cassettes, and operates from its cown batteries or external plug-pack adaptor. It features a review button for instant checking of recording. Also has fast forward and pause controls, too. Comes with inbull electret microphone, case & sarphone.

\$4500

ADD-ON DIGITAL DISPLAY KIT IS ALSO

AVAILABLE FOR

CONVERSIONS: Cat D-2861

EXISTING FT-101Z

\$139.00

Just the the shot for amateurs, language students, etc. who have to wear phones for a long period. Lightweight, high quality

40 CHANNEL AM/SSB CB

A NEW ROOK YOUR FIRST COMPUTER.A comprehensive guide to business and personal computing. What it is, how they

perial (and vice

mind training! (Suits

IT'S CU It's called a 'Cutie Phone'!

You've probably seen phones like this one in the movies. Here it is — in Australia! It gives push-button dialling, last number re-dial and folds down when not in use. Great for a bed-side phone, etc.

NOTE: Although this phone connects nes, current regulations do not permit them to be used for this nurnose

unit you can fit anywhere. And it has a 2 speed

Cassettes to suit: Tiny micro cassettes to suit this recorder (up to

\$4750

OR A MICRO CASSETTE

unit you can it anywers. And it has 2 speed motor for start recording time (standard 15 min/ side micro cassettes give either 15 or 30 min/side micro cassettes give either 15 or 30 minutes/side). Tiny size doesn't meen tiny quality: use it anywhere (internal batteries or external supply). Compare our price: single speed equivalents sell for \$79 and more olsowhere!

Cat A-4040

tor With every FT101Z, we're including a digital frequency display kit, normally worth \$137.00, at no extra charge! It's a simple 'drop-in' replacement display, any hom car install it in a hour or as. Full installetion instructions included. You know how and

install it in an hour or so. Full installation instructions are included. You know how good the FT-101Z is: now it is even better: it becomes an FT-101ZD for the same price!

Offer is open strictly while current stocks last: be quick for

ONLY WHILE STOCKS LAST!

YOU PAY: \$775.00

FT-101Z (Cat D-2862): \$775.00 Digital Disp. (D-2861): \$139.00

30 mins/side). Cat C-3360 \$2.95

this bargain.

DISPLAY BON YAESU FT-101Z!!

What a bargain! 10 pieces for less than \$4!! Flat blade, Phillips, range of lengths: all for only



LOOKING FOR SOMETHING A LITTLE DIFFERENT THIS YEAR . .

use their brains? Try this:
'CODEMASTER' It's a game of ntelligence. Using logic and deduction, you have to solve the hidden puzzle.

\$2950



MAJOR DICK SMITH RE-SELLERS:

ellers who stock a large proportion of our range. Ho ertised on these pages

ATHERTON, QLD: Tableland Radio Service
2 Jack Street, Phone 912 017 BENDIGO, Vic: Sumner Electronics 95 Mitchell Street. Phone 431 977 BLACKHEATH, NSW: Goodwin Electronics 123 Station Street. Phone 878 379 BROKEN HILL, NSW: Crystal TV Rentals 66 Crystal Street. Phone 6897 CAIRNS, QLD: Thompson Instrument Services 79-81 McLeod Street, Phone 512 404 COFFS HARBOUR, NSW: Coffs Harbour Electronics 3 Coffs Harbour Plaza, Park Ave. Phone 525 684 DARWIN, NT: Kent Electronics 42 Stuart Highway. Phone 814 749 DUBBO, NSW: Selekta Sound. EAST MAITLAND, NSW: East Maitland Electronics. FAIRY MEADOW, NSW: Trilogy Wholesale Elect. 40 Princes Hwy. Phone 831 219

GERALDTON, WA: KB Electronics & Marine GOSFORD, NSW: Tomorrow's Electronics & Hi Fi 68 William Street. Phone 247 246 HOBART, TAS: Aero Electronics KINGSTON, TAS: Kingston Electronics & Records Channel Court. Phone 296 802 LAUNCESTON, TAS: Advanced Electronics 5a The Quadrant. Phone 317 075 5a The Quadrant, Phone St.
LISMORE, NSW: Decro Electric
Manallan St & Bruxner Hwy. Phone 214 137 MACKAY, OLD: Stevens Electronics 42 Victoria Street, Phone 511 723 MARYBOROUGH, QLD: Keller Electronics 218 Adelaide Street. Phone 214 559 MORUYA, NSW: Coastal Electronics MT GAMBIER, SA: Hutchesson's Communications 5 Elizabeth Street. Phone 256 404

MUSWELLBROOK, NSW: Silicon Chip Electronics NAMBOUR, QLD: Nambour Electronic Shop Shop 4, Lowan House, Ann St. Phone 411 604 NEWCASTLE, NSW: Elektron 2000 181 Wharf Road. Phone 262 644 ORANGE, NSW: M&W Electronics 48 McNamara Street. Phone 626 491 ROCKHAMPTON, QLD: Purely Electronics SOUTHPORT, QLD: Amateur's Paradise
121 Nerang Street. Phone 322 644 TAMWORTH, NSW: Sound Components 78 Brisbane Street, Phone 661 363 TOOWOOMBA, QLD: Hunts Electronics 18 Neil Street. Phone 326 944 TRARALGON, VIC: Power'N'Sound VINCENT, QLD: Tropical TV 249 Fulham Road, Phone 791 421

WAGGA, NSW: Wagga Wholesale Electronics WINDSOR, NSW: Hawkesbury Electronic Centre WODONGA, VIC: A & M Electronics 78a High Street, Phone 244 588 WHYALLA NORRIE, SA: Mellor Enterprises Shop 2 Forsythe Street, Phone 454 764

WOULD YOU LIKE TO BE A DICK SMITH RE-SELLER?

How would you like to join the hundreds of successful Dick Smith re-sellers, spread right across Australia? If you're interested, why not give our wholesale division a call - Sydney (02) 888 3200, 9AM - 5.30PM weekdays It could be the start of something big



(at about 6AM on Thursday, 25 December-as the kids unwrap

their Christmas presents . . .)

Imagine! All those battery operated toys and no batteries to run them. Wouldn't you be

Stock up now with budget Hi-watt batterie from Dick Smith. Far cheaper than most brands, yet they're fresh and ready to go to work immediately. All popular sizes:
UM-1 ('D') size Cat S-3001 30¢ ea

UM-1 ('D') size Cat S-3001 30¢ ea UM-2 ('C') size Cat S-3002 25¢ ea UM-3 ('AA') size Cat S-3003 22¢ ea

ALKALINE BATTERY PACKS

If you prefer, we have famous brand Alkaline
extra-long-life (or extra-heavy-duty!) batteries
available. (Two per pack except 9V type).

AA size Cat S-3280 \$1.39 pack 2
C size Cat S-3282 \$1.69 pack 2
9V size Cat S-3284 \$1.69 pack 2
SY size Cat S-3284 \$1.69 pack 2

CHRISTMAS CAMPING!

who'd be without a torch? But why limit yoursel a plain, ordinary torch! This is a beauty: it's go

UM-10 ('AAA') sizeCat S-3004

ALKALINE BATTERY PACKS

216 size (9V)

GREAT FOR

eCat S-3004 25¢ ea Cat S-3006 45¢ ea



TION! BEWARE OF INFERIOR UNITS WHICH MAY PRODUCE DANGEROUS OZONE.

SO LAST MINUTE WE DIDN'T EVEN HAVE TIME FOR A PIC LIGHTWEIGHT 'PHONES

cord & plug provided. Cat C-4101.A bargain at only \$5.95!

Rushed into our stores – just in time. Top quality 40 channel rig with LED disp., all hardware. (40ch sets not licensable in Aust). D-1712 INCREDIBLE: ONLY \$199.00

GREAT IDEA: JUST \$8.95! METRIC CONVERSION

idea! LCD caculator also gives you instant conversions from

MUM'D LOVE ONE! \$19.95 THE LATEST SYSTEM 80 PROG: RESCUE AT RIGEL

for this one. Really great for mind training! (Suits TRS-80 16K level II also) X-3649

\$6950

 A powerful outdoor spotlight
 A bright, but soft fluorescent light An emergency orange flasher INC MANUAL ONLY \$22.50 \$1495























Incredible! Inside this no size LED package is not only the LED, but a tiny IC chip which makes the LED flash! Just think of the millions of FLASHES! applications for flashing LEDs already: until now you needed external circuitry! Just hook this one up and away it goes

SPECIAL PRICES **AVAILABLE TO** LARGE QUANTITY **BUYERS!**

A 600 MHz DFM UNDER \$200?



Sounds almost impossible to believe? Yes, a beautifully made, ONLY 7 digit 600 MHz digital frequency meter for less than you paid for your 100MHz version last year! \$199 Battery operated, (use Nicads if you like), highly accurate, and Ni-cad batteries (4 req) tiny: fits into one hand! Hurry. Cat S-3300 \$2.05 ea strictly limited stock of this item
- don't say you weren't warned! Cat M-9525 \$9.50

shipment that has gone astray.

What we are trying to say is that, if you're about to drive across to particular line at a Dick Smith store, why not give the store a ring fit

CROPROCESSOR CONTROLLED

Remembers' up to 96 notes-and spaces — so you car compose' your own music and play it back again later!
 Or you can use it as an organ and play a merry tune!
 It is battery operated, so you can take it anywhere!

Liberace, eat your heart out . . .



Seasons Greetings

ALL-CHANNEL

TV ANTENNA

& Melbourne, you're probably finding the old antenna just isn't up to scratch. Fix the problem

yourself at a fraction of commercial installation costs: with a new all-band antenna from Dick Smith.

The big gun for more difficult areas. 75 ohm. Use co-ax or twinlead. Cat L-4030

UHF ANTENNA

Dick Smith and staff wish all our customers and friends the compliments of the season - and hope to be of service to you

again in 1981



Our biggest se 0-2-7-9-10 9-10 reception 6 near fringe areas.

\$3450

You must have seen these around and thought 'Wow'! Imagine: a portable 'phone' you can carry around with you and take calls up to a few hundred feet away from your main phone! Not only that, you can make calls — even re-dial automically! It would have to be the handlest thing since sliced brand, for the home, office, etc price! Save with Dick Smith bargain imports.

It works by radio: the 'master' unit plugs into the phone lines and the power. If a phone call is received, it transmits the call to the pocket-sized 'remote' unit. The master also contains a battery charger for the Ni-cad batteries in the remote unit. You can also 'ring' from the remote unit: push button dialling with last-number re-call

ven though this unit works perfectly with the Australian 'phone system, at present there are no regulations to allow for the testing approval of these units. Users could, therefore, be prosecuted connection or use of this unit.



29.7

PUSH BUTTON KEYPAD 'MASTER' UNIT

REMOTE UNIT

(IN CHARGING



TV HANDBOOK

Almost 600 pages! This is universally regarded as 'the bible' to ANYONE interested in radio and television -ANYWHERE in the world. Lists all stations, their frequencies, etc, reviews gear . . it's got the lot! And it's available right now at a very special price!

WORLD RADIO AMATEUR RADIO CALLBOOKS: ALL AREAS

If you're an amateur (or even an SWL) who's really interested in chasing DX stations, you cannot afford to be without these two: Between them, they list ALL kn

BOOK 1: US CALLS (Cat R-2260 \$15.95 WAS \$21.95

2: FOREIGN CALLS (Cat B-2262 WAS \$20.95 \$14.95



We made a scoop buy of all remaining stocks of the 1978 ARRL H'BOOK at below cost price! Buy now and save: current (1980) cost is near \$16!! Hurry they're selling fast! Cat B-2218

ONLY \$250



standard 300 ohm ribbon, loo. Cat L-4028. \$1995 **CCTV SYSTEM**

FOR UNDER \$400! SECURITY MONITORING HOME, OFFICE

Think of the applications! Extremely simple to set up, light weight and portable (24BV operated). Compare the price of this system with others: and you can still watch TV when it's not

TV Camera: Cat X-1195
12" TV Monitor: Cat X-1198



WOULD YOU LIKE TO WORK WITH US?

Dick Smith Electronics is expanding-if you've been watching your local press you'll probably have noticed this already! Opening new stores requires new staff. Good staff. Electronics enthusiasts who can be trained to become pro-fessional sales people and managers. If you're talented and enthusiastic, we offer good wages and conditions. If you're above average, promotion can be very rapid. (One of our salesmen became general manager three years later!)

No matter what area you live in, if you'd like to work with us, drop us a line. When we open a store in your area, we'll be in touch . . .

Send your application to: The Personnel Manager, Dick Smith Electronics Pty Ltd PO Box 321, North Ryde, NSW 2113

HERE IT IS!

at long last. Dick has his own leboratory oscilloscope. Check it out – feature for centure it compares favourably with others being offered. Dollar for dollar there is simply no comperison! Save with Dick smith quality products for the hobbyist and professional!

Timebase: 10Hz - 100kHz in 4 range Cat 0-1280

BUILDING TIME. In the past, many customers have wanted to buy a particular project case to build **BIG SAVINGS ON DICK'S GENUINE**

SLOTTED ZIPPY BOXES.

More projects have been built in genuine Dick Smith Zippy Boxes than in any other case!!! And since Dick introduced the slotted Zippy box, constructors have really been happy! No more drilling: just make the project board the right size and it simply slots in place! What could be

And now Dick has ordered massive price cuts - for December only - on the three most popular Zippy Boxes. Grab some now and save: you'll never know when you'll need them!

Size Cat No Was **Now** 150x90x50 H-2751 S2.50 **\$1.98** 130x68x41 H-2753 \$1.95 **\$1.59** 83x54x28 H-2755 \$1.50 **\$1.19**



BE SURE YOU ASK FOR GENUINE DICK SMITH ZIPPY BOXES - THEY'RE THE ONES THE MAGS **BUILD PROJECTS IN!**



\$495



In the past, many customers have wanted to duy a particular project case to sund other projects in — maybe to match up with an existing project, or simply because the case was so versatile. We normally couldn't do this: but, once again, we've seen the error of our ways — and released three of our most-asked-for cases to be normal stock lines. While they're intended for specific projects (holes and all!) a simple dress panel on them and they will suit just about anything!

FOR SMALL

A neat folded aluminium case at a A neat folded aluminum case at a bargain price. Originally intended for CDI's, it measures 172 x 125 x 55mm. If you're building a project with any 2N3055's in it. lucky you! The holes are there already!

Cat H-3107



lere's a bargain! This passivated steel case with vinyl covered lid was Or this one: made for the 'Playselling for almost \$11! Suits variety master' amplifiers, size is a of projects; holes suits 'Musicolor' whopping 270 x 250 x 80mm but add your own dress panel and it Holes for pots, switches, terminals but add your own dress panel and it
suits anything! Size is 250 x 200 x etc. Was \$12.50 \$795



FOR LARGE **PROJECTS**

\$095

NSW 145 Parramatta Rd AUBURN 648 0558 613 Princes Hwy BLAKEHURST 546 7744 818 George St BROADWAY 211 3777 531 Pittwater Rd BROOKVALE 93 0441 147 Hume Hwy CHULLORA 642 8922 162 Pacific Hwy GORE HILL 439 5311 30 Grose Street PARRAMATTA 683 1133 125 York Street SYDNEY

WOLLONGONG

290 3377 WA 28 3800

SA

VIC

96 Gladstone St QLD 166 Logan Road 824 Gympie Rd 60 Wright Street 399 Lonsdale St 656 Bridge Road Dandenong Rd

FYSHWICK 80 4944 BURANDA 391 6233 CHERMSIDE 59 6255 ADELAIDE 212 1962 MELBOURNE 67 9834 RICHMOND 428 1614 SPRINGVALE Open soon PERTH 328 6944

414 William St DICK SMITH MAIL ORDER CENTRE:

SERVICE CENTRE: LANE COVE & WATERLOO RDS, NORTH RYDE NSW 2113. PHONE (02) 888 3200. HOURS SAM TO 5PM. MONDAY TO FRIDAY ONLY

COMPUTER HOTLINE

Want to know more about ou computers? Or maybe you're For friendly, helpful information on System 80 or Sprcerer com puters, or on any of our peripherals, phone our Computer Hotline: Monday - Friday, 9 - 5.30 on Sydney (02)

BUYING BY MAIL?

ORDER VALUE: P&P \$2 00 \$3 00 \$50 00 to \$99 99 \$100 or

\$100 or more \$5.50
NOTE These charges apply to goods sent by post in Australia only Large and bulky items cannot be sent by post in Hy you grefer. We will despatch your order by Comet Road Freight to anywhere in Australia for only \$6.00 that's below what it costs us' Large and bulky items are normally sent by Comet unless you specify differently (eg by can't or air you pay freight on delivery)

SHOP HOURS: 9AM TO 5.30PM MONDAY TO FRIDAY; NOON SATURDAY (Brisbane stores half hour earlier). Some stores are open on late shopping nights: please phone your local store to check before coming in!

263 Keira Street

PO Box 321, North Ryde NSW 2113. Phone (02) 888 3200



DAVID EAST COMPONENT CENTRE

has been open for just over 12 months now. I would like to take this opportunity to wish all the readers of ETI magazine a happy Christmas and to thank them for their tremendous support over the past year.

* * * *

Remember, for ideal Christmas gifts at very reasonable prices, come and see us for

- Radio/Cassettes
- Digital Clock Radios
- Novelty Radios

ALSO

A large range of electronic components and accessories.

DAVID EAST COMPONENT CENTRE

33A Regent Street, Kogarah NSW (Opposite Kogarah High School) Phone 588-5172

DO YOU WORK IN ELECTRONICS BUT PREFER IT AS A HOBBY ?



WANT TO GET PAID TO PURSUE THAT HOBBY?

Then we'd like to speak to you. We're looking for someone to join our project design team here at ETI. If you think you have the ability to design projects like you've never seen in ETI then write or phone us now. Age and qualifications are of secondary importance to ability and experience. Pay and working conditions are comparable to or better than generally found in the industry.

Phone, or write to: Roger Harrison, Editor ETI 15 Boundary St Rushcutters Bay NSW 2011 (02)33-4282.

Shop: 418 Bridge Road, Richmond, Vic. Mail: PO Box 347, Richmond, 3121, Vic.

Second hand video recorders and tapes, cheap. Also new.

OSI HARDWARE FOR OHIO COMPUTERS

Superboard II	\$367.00
SII Covers/VDU Stands (plastic)	
RF Modulators 5/9V	
4K RAM (IC's) Kits	cheap
EPROM with single Key Basic and	
Cursor control	\$54.95

OSI SOFTWARE FOR OHIO COMPUTERS

Almost 100 varieties for C1P/SII.
Many available for C2/4P; enquire.
Categories are: Games, Education, Business, Text,
Instructions (Modifications), and Utilities.
K.2 Catalogue, Brief descriptions of all programs,
free hints. New enlarged version. \$3.50 plus \$1.00
P&P.

Example of titles:

Example of titles.	
G33. Grand Prix	\$9.95
G28. Death Ship (2 tapes)	\$18.95
U16. Filename (tape)	\$8.95
U19. Cursor/Editor C2/4	\$11.95
U20. Mini-Assembler	\$9.95
U21. Single Key Basic	\$9.95
Now available blank digital tapes.	
C10 \$1.85 ea. Less for lots of 10 or 100.	

Mail orders allow postage. eg: OSI Software 1 or 2 \$1.00, 3-5 \$1.50, 6-9 \$2.00, 10 or more items \$2.50.

All prices INCLUDE sales tax.

Prices subject to change without notice.

pH ELECTRODES

Complete with buffers

- Combination pH electrode
- Non flow (sealed) type
- Polypropylene body
- Australian made
- Ideal for pH meter kit!

\$38.00

Plus 15 percent sales tax. Plus \$2.00 postage & packing.

Total price incl. tax \$45.70

Price includes ELECTRODE plus:

Electrode plastic protector cap

onace

- Wetting cap for storage
- 200ml buffer pH 6.88
- 200ml buffer pH 4.00
- Comprehensive pH booklet

Accessories available (prices plus 15% tax)

- 100ml plastic beakers \$1.50 ea.
- 250ml plastic (squeeze) wash bottle \$1.50 ea.
- Combination Spear Electrode \$50.00

We also offer a comprehensive range of Australian made electrodes and meters for pH, selective ion, conductivity, dissolved oxygen and temperature for laboratory, field and process control applications.

Trade and Dealer enquiries welcome.

Send orders and enquiries to:



PO Box 151, Frenchs Forest, NSW 2086. Phone (02) 451-1346.



A 'discriminating' metal detector

This metal detector operates just like the 'bought ones' but costs only one-third to one-half as much to build it yourself. It features three 'discriminate' ranges plus VLF operation and includes an 'auto-tune' button.

design: Lee Allen, Altek Instruments, UK

article: Phil Wait

"GOLD FEVER," shrieked the news headlines following the finding of the 27 kg Hand of Faith nugget at Wedderburn in Victoria recently. It was unearthed by a couple of amateur fossickers using a metal detector, just about the most sophisticated tool ever brought to bear in the hunt for gold.

Designs for metal detectors genuinely able to discriminate between 'trash' and 'treasure' have generally been well kept trade secrets. Even the general principles of operation have been veiled in mystery. However, we are indebted to Lee Allen of Altek Instruments of the UK for providing us with the circuit design of this metal detector project via our British edition. The design incorporates all the features and refinements of modern commercially-made instruments and features performance equivalent to units costing two to three times as much.

Principles of operation

This detector employs the basically well-known induction balance technique to detect the presence of a metallic 'target' in the ground, but includes a number of refinements which respond to certain characteristics of the target. The 'search head' contains two coils: an outer coil which is connected to a low frequency oscillator operating somewhere in the range 15 - 20 kHz, and an inner coil which is placed so that it is

transmit coil will be disturbed, and thus the coupling between the transmit and receive coils will be increased. This generally produces an increase in the signal from the receive coil. In simple induction balance detectors, such as the ETI-549 (May 1977), this signal increase is detected and used to gate an audio oscillator on so that a tone is passed to a speaker or headphones.

only very loosely coupled to the outer coil. The latter is connected to the 'receiver' input of the instrument. Being only very loosely coupled, the signal induced in the receiver (inner) coil from the transmit (outer) coil is very small when a target is not in the vicinity of the search head.

That's all quite straightforward, but there are other influences to be taken into account. The ground in which a target is buried can have quite a profound effect on the coils in the search head. Firstly, if the ground is basically non-conducting, then it will have a permeability considerably different to that


When the search head approaches a

metallic target, the target will have a

number of influences on the two coils.

Firstly, the magnetic field pattern of the

Project 1500

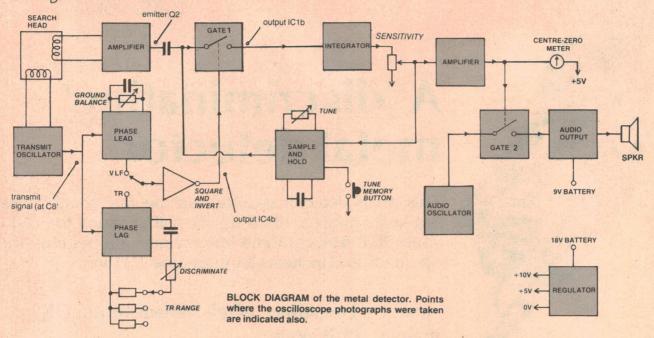

of air. This will affect the coupling between the two coils in the search head, increasing the coupling if the transmit and receive coils are initially set up away from the influence of the ground. You can compensate for this effect by physically varying the position of one coil in relation to the other when the search head is near the ground. However, different soils will have different compositions and thus have different values of permeability—even within quite a small area. The best way to compensate is by electronic means and we'll go into that shortly.

If the soil contains an appreciable amount of iron minerals (maghemite, hematite etc ... often referred to as "iron stone soils"), or mineral salts of one type or another, then it will be partly conducting.

Such soils will have a permeability often greater than basically nonconducting soils, affecting the coupling between the coils in the search head in a similar way to that just explained. Again, as the composition of the soils varies, so will the coupling. Another effect is that of 'eddy currents' induced in the conductive soil. The ac magnetic field of the transmit coil will induce a current in the ground beneath the search head and the eddy current has an effect opposing the permeability effect of the soil - and the whole effect varies in a complex and unpredictable way as you sweep the search head over the ground.

The only way to compensate for these varying, and generally unpredictable effects, is to devise circuitry that 'recognises' the effect.

Permeability effects will vary the phase as well as the amplitude of the signal coupled into the receive coil from the transmit coil while eddy current effects vary the amplitude. Knowing that, one can devise appropriate circuitry to take the effects into account.

However, we need to know how a metallic target affects the phase and amplitude of the receive signal. If the target is ferrous, it will have a much greater effect on the magnetic field of the transmit coil than will the surrounding soil as its permeability is greater and it will bend' or concentrate the field lines to a much greater degree. If the target is non-ferrous it will have a permeability effect opposite to that of ferrous targets, deflecting the field lines, but eddy currents also have some influence.

The eddy current effect in a target depends on the electrical and physical characteristics of the target. Metals which are good conductors will have greater induced eddy currents than metals which have a higher resistivity. It is a fortunate accident of nature that gold and silver are good conductors (low resistivity) while iron (especially if it's oxidised or rusty) is not so good a conductor.

If the target is ring-shaped then the eddy current effect is enhanced, whereas if it's a broken ring or just a peculiarly-shaped mass, the eddy current effect is less pronounced. The 'attitude' or orientation of the target will also affect the eddy current effects. If the main plane of the target object is aligned such that the field lines from the transmit coil cut it at right angles,

then the eddy currents induced will be at a maximum. If the main plane of the target is aligned parallel to the transmit field then the eddy currents induced will be at a minimum. Obviously, the attitude of the target with respect to the transmit coil's field will vary as the head passes over it and the eddy current effect will vary accordingly — it may not be maximum beneath the centre of the search head.

The permeability and eddy current effects combine in the receive coil and the signal varies in phase and amplitude in characteristic ways.

The instrument

The best way to understand how this instrument operates is to look at it in block diagram form. The accompanying diagram shows the basic circuit blocks employed. The transmit oscillator drives the transmit coil in the search head and supplies a signal to two phase control circuit blocks. The signal from the receive head is first amplified and then ac-coupled to the input of a gate (gate 1). This gate is controlled by the output from one or other of the phase control circuits via a block which 'squares up' and inverts the signal. The output gate consists of an ac signal superimposed on a dc level. This passes to an integrator which obtains the average dc level of the composite signal. This is then passed to both a dc amplifier which drives a centre-zero meter, and to a 'sample and hold' circuit. The output of this block provides a dc level to the input of gate 1 which is a measure of the average dc level of the composite signal. The initial dc level applied to the

input of gate 1 is actually established by the tune control. Thus, a dc negative

feedback path is provided.

In addition to meter indication, an audio indication is provided. The output of the dc amplifier driving the meter controls a gate which switches on or off the output of an audio oscillator. This is applied to an audio amplifier and an on-board loudspeaker or headphones.

Power for the audio amplifier is provided by two 9 V batteries in parallel. The rest of the circuitry requires two supply rails at +10 V and +5 V with respect to the common rail (0 V). This is supplied by a regulator from an 18 V source consisting of two 9 V batteries connected in series.


Initially, the instrument is set up in the 'VLF' mode. The search head is held in the air and the tune control adjusted to bring the meter to centre zero. This is done with the tune memory button depressed. This activates the sample and hold circuit, storing the dc level set by the feedback loop in the capacitor of the sample and hold block. Thus, a particular dc level at the output of the integrator corresponding to meter centre zero is set up.

The search head is then lowered to the ground. Naturally, this will upset the coupling between the transmit and receive coils and the output at gate 1 will change. This will change the dc level at the output of the integrator. The ground balance control is then adjusted to bring the meter back to centre zero. What the ground balance circuit does is to provide a signal which leads the phase of the transmit signal and thus leads the phase of the signal induced in the receive coil without the presence of ground. The ground balance control varies the phase of this signal over a range of about four to one. Thus, when you vary the ground balance control, this varies the phase of the signal controlling gate 1, thus varying the average level of the signal passed to the integrator.

The process is then repeated until no change occurs when the search head is lowered to the ground. This establishes a 'normal' condition for the output of the integrator and the sample and hold circuit maintains the appropriate dc level at the input to gate 1 such that the meter remains at centre zero.

If the search head then approaches a metallic object, the amplitude of the signal in the receive coil will vary as the coupling between the coils and the phase of the signal will be altered by the target. This will change the average level of the composite signal out of gate


OSCILLOSCOPE PHOTOGRAPHS

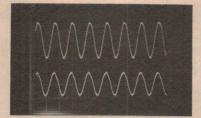


NOTE: As the effect induced by different targets is very, very small, we have had to use fairly large sample targets to show gross effects in order to demonstrate the operation of the instrument

Top trace: transmit signal on C8 (Y-amp 5 V/div, ac-coupled) Bottom trace: received signal on emitter of Q2 (Y-amp 5 V/div ac-coupled). Time base: 50 us/div.

VLF MODE:

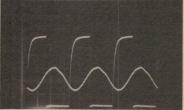


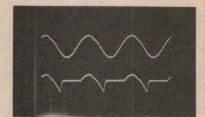Received signal on emitter of Q2 (sine wave) superimposed on output of IC4b. (Both traces 2 V/div, ac-coupled; time base 20 us/div).




Top trace: received signal on emitter of Bottom trace: output of IC1b showing

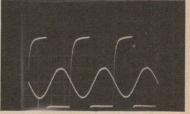composite waveform of received signal 'mixed' with a dc level. (Both traces 2 V/div, ac-coupled; time base 20 us/div).




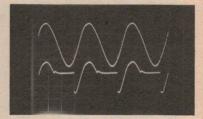As per pic (B) but with aluminium target held near search head. Note the phase delay and change in amplitude of the received signal.



Same as pic (D) but with metal target near the search head. Note the increase in average dc level from the output of IC1b. The change in this signal is much larger for non-ferrous than for ferrous metals.


DISCRIMINATE MODE

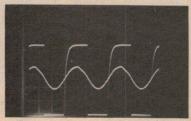

Received signal on emitter of Q2 (sine wave) superimposed on the output of IC4b. The phase difference between the two signals is adjustable through 1800 by use of the course (TR1, TR2, TR3) and fine 'discriminate' controls. (Both traces 2 V/div, ac-coupled; time base 20 us/div).



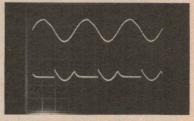As per pic (G) but brass target held near search head. Note the increase in the average dc level of the signal at the output of IC1b.



G) Top trace: received signal on emitter of Q2. Bottom trace: output of IC1b showing composite waveform of received signal 'mixed' with a dc level. Detector set to TR1 mode, discriminate control to 9. (Both traces 2 V/div, ac-coupled; time base 20 us/div).



As per pic (G) but steel target held near search head. Note the decrease in average dc level of the signal at the output of IC1b, illustrating discrimination

FEATURES

- VLF and T/R operation
- Three ranges of 'discriminate' (T/R) operation
 - Can tune out aluminium ring-pull tabs
 - Ground balance circuitry included
- Tune memory ('auto-tune') button

- High sensitivity (will detect 20¢ piece at depths over 250 mm) Pre-wound and aligned waterproof search head
- Straightforward construction, no alignment necessary
- - Low battery drain
- Uses common No. 216 transistor radio batteries
 - Costs around \$200 in kit form

HOW IT WORKS — ETI 1500

As the general principles of operation have been discussed with regard to the block diagram in the text, this description is con-

phase-lag circuitry (ground and discriminate controls) is tapped off the collector of Q3 via Commencing with the transmitter, Q3 is R17. The transmit signal to the phase-lead and C8 to the junction of R11 and R14. The ground control circuitry connects via R11 while the coil in the search head forming the nation C9 and C10. Bias is applied to Q3 via R18, D1 and R19. Emitter bias is provided by configured as a Colpitts oscillator, the trans inductance which resonates with the combi fined to the circuit alone.

gram), one CMOS gate in IC1 (IC1b), via an The signal from the receive coil is amplified emitter-following buffer stage, Q2. Note that and Q2 is not altered. Output from the emitter by Q1 and applied to gate 1 (see block dia Q1 is operated as a grounded-base amplifier The phase of the received signal through Q discriminate circuitry connects via R14. of Q2 is applied to the drain of IC1b.

derived from the transmit signal, the phase of which can be varied by either the ground or The base of IC1b is driven by a square wave discriminate controls

+100 to +400. A leading phase RC network is This signal is applied to the inverting input of an op-amp, IC4b. As this is operated at maximum gain with a high signal level at the input, it will'square up' the signal at its output In the VLF mode, the phase of the transmit signal tapped off from Q3 can be varied using RV1. This provides a phase-advanced signal that can be varied over the range from about formed by R10 and RV1 in conjunction with C7 (pin 7), which drives the gate of IC1b.

connects the transmit signal to circuitry which provides a lagging phase signal which can be nate control) and a set of 'range' resistors: R13, R15 and R16. These form a lagging The signal is then buffered by a non-inverting varied over a range set by RV2 (the discriminetwork in conjunction with C11. In the discriminate mode, switch SW1 phase RC

op-amp, IC3b, and applied to the inverting input of IC4b via SW1c.

sensitivity control, RV3. The wiper of this potentiometer goes directly to the input of add amplifier, IC3a, to which we shall return shortly. The wiper of RV3 is also connected to the sample and hold circuit, via R25, which The source of IC1b is connected to an integrator stage formed around IC3d. The output of this stage is connected directly to the involves IC5, IC1a, the tune control RV4 and the tune memory pushbutton, PB1.

The sample and hold circuit works in the R26 and R32 will be at a dc level determined by the dc level at the wiper of RV3 and the dc level at the wiper of RV4, the tune control potenliometer. The dc level at the wiper of RV3 will depend on the signal level and phase switched through to the integrator by IC1b. When the IC1a (also a CMOS switch) will apply a dc level to the input of the sample and hold circuit proportional to the dc level at the junctions of R25, R26 and R32. This will charge C13 and the output of IC5 will settle at this value. This do evel is then applied to the drain of IC1b, via following way. The junction of resistors R25 tune memory pushbutton, PB1, is pressed

the composite signal being applied to the Thus, the received signal and this dc level are 'mixed' at the input to gate 1 (i.e. IC1b)

inverting input (pin 3). This stage has a gain of C3a. The input to this op-amp comes from the sensitivity control and is applied to the nonabout 30 and a little 'smoothing' (integration) of the signal is applied around the feedback by having a capacitor (C14) connected in parallel The meter, M1, is driven by a dc amplifier with the feedback resistor, R36.

Apart from driving the meter, the output of C3a is fed to the source of IC2b which gates the audio oscillator through to the audio output stage (i.e. gate 2). The dc level from pin 1 of C3a goes via D2 and R39 to pin 11 of IC2b. A positive bias is applied to the cathode of D2 from the +5 V rail via R38. Only when the dc

level at the output of IV3a goes higher than 0.6 V above the bias applied to the cathode of D2. will IC2b be biased on.

applied to the gate of IC2b. When IC2b turns at a few hundred Hertz. The output, pin 1, is figured as an astable multivibrator operating on, the signal is applied to the input of the The audio oscillator involves IC4a, conaudio output stage.

TUNING

the input of the audio output stage. The One gate from IC2 is biased into its linear region and acts as a source-follower buffer at this stage and the output is taken from the wiper of RV5 to the base of Q4, capacitively volume control, RV5, is the source resistor for coupled via C18.

NPN/PNP transistor pair. The collector of Q4 drives the output stage, its collector load also providing bias to the output pair (R48). Both dc isolating capacitor, C20. Headphone volume is reduced by a 470 ohm resistor, R50, in series The output stage is a simple complementary and ac feedback is applied to the base of Q4 by R49 from the output. Audio output can be from an 8 ohm speaker or headphones, via a dc class-B stage employing a low power with one lead to the headphone socket, SK2.


Power supply for the circuitry is split into two parts. The audio output stage is supplied polarity protection diode, D3, and one pole of by two 9 V batteries connected in parallel (B1 and B2). These are connected via a reverse-SW2 which is a switch on RV5.

and B4, connected in series and applied to a The rest of the circuitry requires a +10 V and (0 V). This is derived from two 9 V batteries, B3 tion diode, D4, and the other pole of SW2. The a +5 V rail, with respect to the common rail regulator circuit via a reverse-polarity protecregulator is basically a conventional seriespass circuit, Q9 being the regulator transistor

reference voltage for a differential pair, Q7 and Q8, the latter controlling the base current to Q9. Resistor R54 allows a small amount of The zener diode ZD1 provides a stable current to pass to Q7/Q8 at switch-on to ensure the regulator 'starts' correctly. The base

of Q7 is biased at half the upper supply rail voltage by R51 and R52. This voltage is buffered by an op-amp, IC3c, configured as a voltage follower, and used to drive the +5 V line. Decoupling is provided by C19, C21 and C22. Note that 'battery test' facilities are provided by R44/PB2 for the 18 V supply and by R45/PB3 for the 9 V supply. During the tuning operation, when the instru-ment is being initially set up, the circuit works pushbutton operated, IC1a is gated on and a dc negative feedback loop is established from the output of the sensitivity control, back to signal applied to the integrator input, and thus a reduction in the dc level at the input of IC1a dition is established. When the dc level around the loop settles, the meter will read zero leased. The dc level at the output of IC5 (and thus at the drain of IC1b) is maintained by the tune memory button is located on the crook of in the following way: With the tune memory the input of gate 1, the drain of IC1b, via the sample and hold circuitry. A portion of the voltage from the wiper of RV3 is added to the voltage determined by the voltage divider R33, RV4 and R34. This is applied to the source of IC1a. As the tune memory button is pressed, IC1a is conducting and capacitor C13 will applied to the source of IC1a. The op-amp IC5 is a low input current device and the output, pin 6, will settle at a value equal to the composite voltage applied to its non-inverting input (pin 2). This dc level is applied to the source of IC1b and the signal output from the receive coil amplifier is mixed with it. This will bring about a reduction in the dc level of the and, within a second or two, a new dc con-(centre) and the tune memory switch is recharge on capacitor C13. In practice, it will drift very slowly, as C13 will be gradually discharged by the input current of IC5 and the capacitor's own leakage. For this reason, the the handle where it can be operated by your thumb every now and then to re-centre the charge to the value of the composite voltage

Project 1500

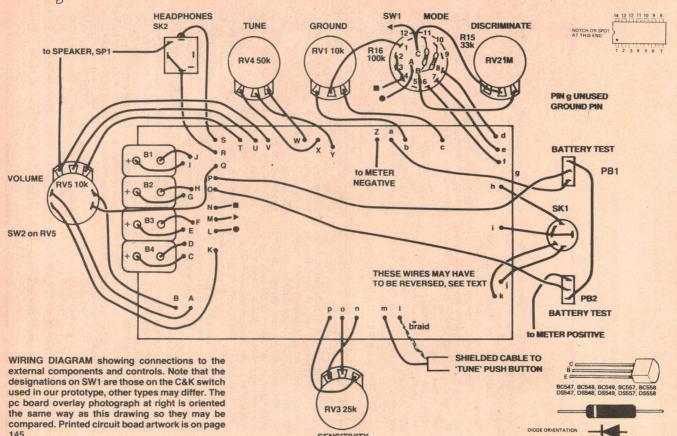

text); search coil (see text); knobs; length of

ribbon cable; two metre length of shielded

cable; double-sided sticky tape to hold batteries

in position, or a suitable clamp.

43.	SENSITIVITY
PARTS LIST	Г — ETI 1500 — — — — — — — — — — — — — — — — — —
	C10 01 00 470 16V electrol tie
Resistors all ½W, 5%.	C19, 21, 22 470 µ, 16V electrolytic
R1180k	C20 10μ , 16V electrolytic
R2, 2222k	Potentiometers
R3, 7, 8, 16, 20, 21, 30, 33, 34, 38, 40,	RV1 10k linear
42, 44 100k	RV2 1M log.
R4, 19, 35, 54 15k	RV3 25k linear
R5, 9, 48 1k	RV4 50k linear
R6, 15, 39 33k	RV5 10k log pot with
R10, 18 10k	DPST switch
R11, 172k2	Semiconductors
R1227k	
R1382k	D1, 2, 3, 4 1N914, 1N4148
R14, 55 18k	ZD1 5V6, 400mW zener diode
R23, 25, 26, 31,	Q1, 2, 4, 5, 7, 8 BC548, BC108
43, 47, 49 1M	Q3, 6, 9 BC558, BC178
R243k9	IC1, 2
R27, 36 470k	IC3 LM324
R28, 29 4k7	IC4 LM393N
R32 4M7	IC5 CA3130N
R3747k	Miscellaneous
R413k3	SW1 three-pole, four position
R45 68k	wafer switch; C&K type RA
R46120k	SW2 on RV5 (DPST switch)
R50470R	PB1, 2, 3 SPST miniature momen-
R51, 5256k	tary push buttons, push
R5312k	to make
	M1 50-0-50 μA meter,see text
Capacitors	SK15-pin DIN socket
C1, 3, 10, 14 47n greencap	SK2 shorting type jack socket
C222p styroseal	SP1 small eight ohm speaker
C4, 5, 6, 8, 12,	(75 mm dia.)
15, 18 10n greencap	B1 - B4nine volt transistor radio
C7	batteries (type 216)
C9 470n greencap	Four battery clips for No. 216 batteries; ETI-
C11 220p styroseal	1500 pc board; case (see text); handle (see
1.13 A70n nolycarbonato or	tout): accept sail (san tout) land - 1

1 and thus the dc level at the output of the integrator will change. This will be amplified and the meter will show an indication. Also, gate 2 will be operated and a tone will be heard in the speaker.

However, this method of operation will not indicate the difference between the characteristics of different targets.

In the discriminate or TR mode, the ground balance control is not used. The instrument is initially set up using the tune control to bring the meter to centrezero. The differne tTR ranges permit varying degrees of control with the discriminate potentiometer. The phaselag circuit block generates a signal which lags the phase of the transmit signal and the discriminate control provides a phase-variable signal to drive gate 1.

When a ferrous target is approached, the combined permeability and eddy current effects tend to reduce the amplitude of the signal picked up by the receive coil. This will cause a reduction in the dc level of the signal out of gate 1 and a reduction in the dc level out of the integrator. Thus, the meter will move to the negative (left hand) side of the scale. This side of the scale is marked "bad", obviously.


When a non-ferrous target is approached, the combined eddy current

C13470n polycarbonate or

..... 100n greencap

..... 1n greencap

styroseal

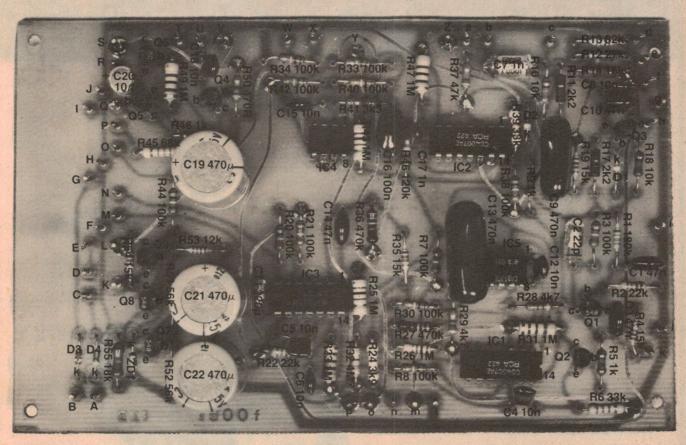

and permeability effect tends to increase the amplitude of the signal picked up by the receive coil. This will cause an increase in the dc level of the signal out of gate 1 and an increase in the dc level out of the integrator. The meter will thus move toward the positive (right hand — "good") end of the scale.

The effects we are considering are actually quite small, hence the circuit has a considerable amount of dc gain.

Gate 2 only operates when the output from the dc amp increases (goes positive) and thus the audio output is only heard in the discriminate mode when the meter shows "good".

It is unfortunate that ring-pull tabs from drink cans are aluminium and thus indicate along with other non-ferrous metals. But, the discrimination ability of the instrument can be adjusted to exclude the small effect these targets generate — along with small trinkets, the smaller gold nuggets, etc — but who wants the tiddlers anyway!

If the dc level applied to the input of gate 1 drifts — and it may do for a wide variety of reasons, operating the *tune memory* button will restore the balance of the circuit and re-centre the meter. Quite a cunning arrangement.

Search head

The most important properties of the search head are its size, the relationship between the transmit and receive coils, and the shielding against capacitive effects between the coils and the ground. Surprisingly, the actual inductance of the coils is not of primary importance.

The greater the coil diameter the greater the penetration depth but the less sensitive the detector will be to small objects. Penetration using simple, circular coils is about equal to the search coil diameter for small objects such as coins, while sensitivity is roughly proportional to the cube of the object diameter (expressed as a function of the search coil diameter). Sensitivity is also inversly proportional to the sixth power of the distance between the coil and the object.

All this means that if the object size is halved the sensitivity is reduced to one-eighth. If the depth is doubled the sensitivity is reduced to one sixty-fourth. See why metal detectors designed to pick up small objects use small coils and really only skim the surface? If the search coil is doubled in diameter for greater penetration the sensitivity to small objects falls to one eighth, apart from the coil assembly becoming mechanically less rigid. The law of

diminishing returns again or 'you don't get something for nothing'.

Our new detector improves penetration while retaining sensitivity by using a co-planar arrangement of coils in the search head which gives a slightly magnified field pattern downwards, into the ground.

We mentioned earlier that the two coils are only loosely coupled. The positioning of the receiver coil in relation to the transmitter coil is very critical and is the major factor affecting the performance of the instrument. In fact, misplacement by a millimetre or so will markedly affect the performance.

As the search head is moved around, the changing capacitance between the coils and the ground could completely mask the minute changes in the field we are looking for. To avoid this affect the coils are enclosed in a Faraday shield.

By now it should be obvious that construction of the search head is not a task to be tackled on the kitchen table on a rainy Sunday afternoon. In fact, construction and alignment of the search head would be beyond most readers' resources (anyone who has attempted our earlier induction balance metal detector knows what it's like). With this in mind we chose to use the commercially built, pre-aligned


ALL ELECTRONIC COMPONENTS

That's our name . . . that's our game!!!

MAJOR STOCKISTS OF ALL GENERAL RADIO AND ELECTRONIC COMPONENTS

JOIN THE GOLDRUSH

ETI 1500 KITSET

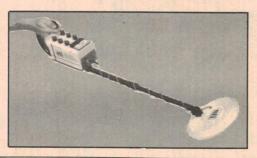

Superb unit featuring:

- Tune and discriminate.
- 4 modes of operation.
- VLF/TR design.
- Ground balance.
- Pre-wound search heads.
- Very professional unit.
- Approximately 1/3 price of many similar commercial built up locators.
- Audio and meter indication. Auto balance push buttons. Lets you know when to rejoice.

PRICE: \$200.00 plus \$7.50 P&P

ETI 549 KITSET

Features include:

- Induction balance.
- Volume and level control.
- Phone jack.
- Dual sensitivity.
- Audio and meter indication.

PRICE: \$57.86* plus \$5.00 P&P



ETI 561 KITSET



Features include:

- B.F.O. principle.
- Crystal controlled.
- Good sensitivity.
- Simple construction.
- · Low cost.

PRICE: \$33.00* plus \$5.00 P&P

EA PROSPECTOR KITSET

Features include:

- B.F.O. principle.
- Easy to build.
- Low cost.

PRICE: \$37.00* plus \$5.00 P&P



*Search heads not included.

E. D. & E. (SALES) PTY. LTD., NOW

LL ELECTRONIC COMPON

118 LONSDALE STREET, MELBOURNE, VIC. 3000. TEL: 662-3506.

Project 1500

search head made by Altek Instruments. This will be available in Australia through All Electronic Components in Melbourne who have agreed to make the unit available wholesale to other suppliers, as well as retailing parts themselves, along with hardware — the plastic extendable handle and the case for housing the electronics. See Shoparound for details, p. 85.


Construction

The mechanical components for this project — the search head, handle and case, are available through Altek's Australian agent, All Electronic Components, as mentioned earlier. We recommend you obtain these as your finished instrument will then be a professional looking piece of equipment, with the features and operation of a 'bought one' two to three times the price. However, you can suit yourself and make your own handle if you so desire and we have designed the pc board such that it will also fit in a large jiffy box. You will have to use the search head recommended though, for the reasons we have explained previously.

All the electronics mounts on a single, double-sided pc board. The Altek case has two clamps on the rear enabling it to be clipped on to the handle. The Altek



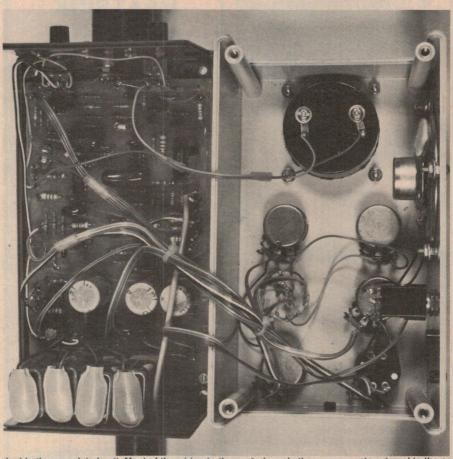A view of the front panel of the project. The Scotchcal front panel and meter escutcheon will be available from the usual suppliers. See Shoparound. p.85.



Inside the completed unit. Most of the wiring to the controls and other components external to the pc board as done using ribbon cable. The colour coding of this cable assists greatly in avoiding confusion. We suggest you place the two units as shown in this photograph to accomplish the wiring. Note how the speaker is mounted. The batteries are held in place by a strip of double-sided sticky tape.

handle has two sections, the lower section sliding inside the upper section enabling the operator to adjust the length of the handle to suit his height. Connection between the search head and the electronics is via a length of shielded cable (supplied with the head) and a five-pin DIN plug/socket arrangement. The tune memory pushbutton is mounted in the end of the 'crook' of the handle (see photographs) where it can be easily operated by the thumb. It connects to the electronics via a length of shielded cable passed through, the handle.

Construction should commence with the pc board. As it is a double-sided board (i.e. copper tracks on each side), first identify the 'front' and 'rear' side. These are marked, respectively, ETI 1500f and ETI 1500r. The rear side has the more complicated pattern of tracks. The components are mounted on the *front* of the board, where there is the less complicated set of tracks. Note that some of the resistors, IC pins and pc board pins (used for connecting external wiring to the board) must be soldered to copper tracks on *each* side of the board.

Commence with the resistors. Take

care with those that cross tracks that you don't create a short circuit where it's not wanted. Next mount the capacitors. Take care with the orientation of the electrolytics. Note that capacitors C2, C7 and C11 are styroseal types, used for their good temperature stability. Be careful when soldering them in place that you don't overheat the leads as this can cause melting of the capacitor's case, possibly damaging it. The sample and hold capacitor, C13, must be a low leakage type, preferably polycarbonate or mylar. We used a greencap successfully, but whatever you manage to obtain, make sure it's a good quality type from a well-known supplier.

Now mount the semiconductors. Take care with the orientation of these as you can destroy devices if they are incorrectly inserted when power is applied. Finally, solder the pc pins in place and the four battery clips. The latter all go along one edge of the board.

Overall assembly of the pc board is clear from the overlay picture on page 45

Once you have everything in place on the pc board and you're satisfied that all is OK, you can turn your attention to

869 George Street, Sydney, NSW. 2000. (Near Harris Street) Phone 211-0816, 211-0191.

We specialise in:

- PC Boards for ETI and EA projects.
- Scotchcal labels made under order for ETI and EA projects 1979 and onwards.
- "Kriket" model 3085. Hump Mount CB Speaker Unit. Special \$28.00.
- Small Ext. Speaker Sound Box. Model MS-03B 8 ohms 1 watt. special \$5.20.
- Microphone Model DM401 with lead and stand. Special \$4.00. Low Imp. • Horn type ext. speaker. Model S-2010.
- 8 ohms, 5 watts. Special \$6.75.

 "Uni-Board". Universal PC Boards in
- sets of one, two and six. · Car volt adaptor unit by Arlec. Model
- PS393. Logic Circuit Probes. Various types.
- · Electrical fittings, power points, plugs,
- sockets, switches, lampholders etc.

 Cables and wires for projects, radio, television and general use.
- Fuses and fuse holders in 2AG and 3AG
- Oscilloscopes, test equipment, power supplies by Hitachi, Trio, Leader and Technico.
- Wide range of heatsinks. Thermallov. Philips, Redpoint etc.

Texas Calculators

	excl. ST	incl. ST
Ti.59	\$265.00	\$299.00
Ti.58C	\$132.00	\$149.00
Ti PC 100C Printer	\$210.00	\$237.00
Ti.50	\$36.40	\$40.30
Ti.55	\$53.35	\$59.00
Ti.30 Student Pack	\$20.00	\$22.10
Little Professor	\$17.40	\$19.00
Dataman	\$23.63	\$26.15
Speak and Spell	\$68.60	\$75.95

MAIL ORDER CUSTOMERS


\$1.00 packing plus 5 percent of order value up to \$80.00, thence a flat \$4.00 for postal items. Carrier - freight on.

OPEN: Mon-Fri 8 am to 5.30 pm. Thursday night late shopping till 8.30 pm. Saturday 8 am to 11.45 am.

HEATSINK **EXTRUSION**

TYPE XA

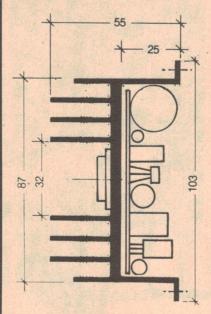CHASSIS & MOUNTING FEET INTEGRATED IN HEATSINK DESIGN.



YOU DON'T HAVE TO DESIGN OR BUY ANY OTHER METAL WORK OR CHASSIS HOUSE ASSOCIATED CIRCUITRY & COMPONENTS.

YOU SAVE -

- * MONEY
- * TIME
- * SPACE
- * STOCK HANDLING

Designed & Manufactured in Australia

WA ATKINS CARLYLE (09) 321-0101 SA PROTRONICS (08) 212-3111 **NSW** ELECTRONIC DISTRIBUTORS (02) 636-6052 QLD CW ELECTRONICS (07) 48-6601 **VIC STEWART ELECTRONICS** (03) 543-3733, ELLISTRONICS (03) 602-3282, ALL ELECTRONIC COMP. (03) 662-3506 ACT GEORGE BROWN & CO. (062) 80-4355 TAS GEO. HARVEY ELECTRIC (002) 34-2233

AUTOTRON AUSTRALIA P.O. Box 202, Glen Waverley 3150 Victoria

RPG HI-FI & MUSICAL INSTRUMENT **SPEAKERS**

Manufactured to Radio Parts Group specifications by the world's largest speaker manufacturer.

HIGH EFFICIENCY TWEETERS

Indii Lillo	PIAC	 		-		10		
H66AP45-01F	6w.					\$	5.	14
E66CP45-01F	8w					.\$	5.	14
B45DP70-01F	10w					.\$	8.9	9





HI-FI MID BANGE

B11EC80-02F 30w\$15.79
(can back) 41/2 inch
A11DP60-02F 15w\$7.37
(sealed back) 41/2 inch

MID	CHANGE			
41/2	B11EC80-01F	15w	.\$13.	49
6" A	16DC61-01FW	12w	\$8.	44
6. C	16E70-01FW 1	5w	\$13.	23
8 A2	20EP80-03FW	20w	\$15.	04
8" A2	20EC70-03FW	30w	\$14.	35





WOOFERS

0 1	420E013-01F	DUW	. 313.23
10	A25EP65-02F	20w	\$15.41
10"	C25FU90-03F	50w	\$31.47
12"	A30EU80-01F	35w	.\$29.44

12" A30FU20-01F 65w \$42.09



MUSICAL INSTRUMENT

8" B20HP14-01F 50w \$23.54 12" A30GC40-01F 100w .. \$57.92



RPG Speakers are only available from:



562 Spencer Street, West Melbourne. Phone (03) 329-7888. 1103 Dandenong Road, East Malvern. Phone (03) 211-8122.

Project 1500

the hardware. Start with the case that houses the electronics. If not pre-drilled, you'll need to mark out and drill all the holes in the case lid. The panel artwork can be used as a template. Note that we dressed up the case with a Scotchcal panel. These should be available through the usual suppliers. Centre punch holes before drilling. The cutout for the meter can be made with a hole saw or by drilling a series of 4 mm diameter holes just inside the marked edge of the hole. When you complete the circle, the centre piece can be snapped out and the edge of the hole cleaned up with a half-round file until the meter drops in neatly.

The speaker is mounted on the left hand side of the case lid (as you would normally view the unit in use). It is held in place by large washers placed under the nuts of three bolts spaced around the outer rim of the speaker. Alternatively, you can glue it in place. Be careful not to get any glue on the speaker cone or you might end up with a rather 'strangled' sound!

The pc board mounts in the bottom piece of the case, along with the DIN socket (for the search head connector) and two battery test push buttons. A small hole in the bottom passes the cable to the tune memory button. The case bottom has four integral moulded standoffs to provide support for the pc board which is held in place with screws.

Once all the mechanical work on the case is satisfactory, the Scotchcal panel may be stuck on. Take care when positioning it as it's almost impossible to move if you misalign it. Carefully smooth out all the bubbles toward the edge of the transfer.

The controls, meter etc. may be mounted next. Then you can wire all the external components to the pc board pins. We used lengths of ribbon cable where possible to simplify the wiring. The easiest way to accomplish this part of the assembly is to place the bottom of the box, with the pc board mounted in it, on your left and the lid, with the meter and controls etc. mounted, face down on your right. Follow the wiring diagram on page 44 and complete all the interconnections. You should now appreciate pc board pins!

The tune memory button mounts in a hole in the end of the 'crook' of the handle, as we explained earlier, and the shielded cable connecting to it passes through the handle, emerging through a small hole drilled in the handle near where the cable can enter the hole provided for it in the bottom of the box. This cable is best inserted before you mount

the pushbutton. Remove the handgrip. Push the cable through the hole in the handle near the case, until it appears through the end of the handle. Solder the end of the lead to the pushbutton and mount the pushbutton in the hole in the end of the hand grip (easier said than done!). Put the handgrip back and you can pass the business end of the cable into the case and terminate it. If you're lucky, kit suppliers may sell the units with this part already assembled.

Holding the batteries in place is generally left to your ingenuity. We used double-sided sticky tape (ah, that's useful stuff...). The battery life is quite good as the circuit has been designed for low current drain. Reverse polarity protection is provided on the pc board to avoid problems should you inadvertently attempt to connect a battery back to front

When all wiring is complete, push the case onto the handle and drill a small hole through one of the clamps and the stem of the handle. Insert a nail or a bolt and this will prevent the case from rotating on the handle. Mount the search head and adjust the length of the stem to suit yourself. Wrap the cable from the search head around the stem so that it is held quite rigidly and plug it into the DIN socket on the case.

You're ready to roll! ... once you've tested it.

If you wish to make the search head completely waterproof, seal the hole through which the cable passes with Silastic rubber or some similar caulking compound.

Operation

When construction is complete and you're satisfied all is well, turn the detector on and advance the *volume* control. Set all other controls to mid-



A view of the forward end of the case showing the two battery test pushbuttons and the DIN plug and socket connection to the search head. The Altek cabinet is two-tone grey plastic. The upper section is a lighter hue. Note the "GT" stripes!

to page 158

Stake your claim and win a Compass gold detector.



In the 1850s there were no fancy gadgets to help a man strike it rich.

But in December Outdoors magazine you have the chance to win a gold detector. We've 'buried' gold in an old photograph of the diggings.

You have to pick where in the photograph it's 'buried', fill in the coupon and send it to Outdoors. The first correct entry opened will win a Compass Relic Magnum gold discriminator worth \$595. The second correct entry opened will win a Compass Magnum 420 gold discriminator worth \$465.

Who knows, if you're lucky enough to win the competition you might be lucky enough to strike it rich.



MERRY XMAS TO ALL OUR READERS

NEW PRODUCTS

WELLER PRODUCTS TEMPERATURE CONTROLLED STATION **WTCPN Series**

Product Description: A transformer portoget dering station, complete with a low voltage, dering station, complete with a low voltage, dering pencil. The temperature controlled soldering pencil. The special Weller "closed loop" method of controlling maximum tip temperature is employed, thereby protecting temperature sensitive components while the grounded tip protects voltage and current sensitive components. The soldering pencil features a stainless steel heater construc-tion, a non-burning silicon rubber cord and a large selection of iron plated tips in sizes from .8mm diameter to 6mm diameter with a choice of tip temperature of 600 degrees F/315 degrees C and 800 degrees F/430 degrees C.

A redesigned transformer case features an impact resistant noryl for durability and protection against accidental damage, a quick connect/disconnect plug for the soldering iron, extra large wiping sponge, tip tray to store extra tips, plus an improved off-on switch with a long-life neon indicator light, a non-heat sinking soldering pencil holder, and a 2m flexible 3-wire power cord. The soldering iron is normally provided with a PTA-7-1.6mm screwdriver 700 degrees F/370 degrees C tip.

SPECIFICATION

o Power Input 240 volts 50Hz 60 Watts Int. o Transformer Output voltage — 24 volts (full load) o Power Unit size — 113mm x 187.3mm x 92mm. o 2 metres, 3 wire power cord. SOLDERING PENCIL

o Soldering pencil wattage - 48 watts o Tip voltage to ground .01 volts P-P o Pencil weight — 50 gram (W/0 cord) o Recovery time (from 100 degrees F drop) W/PTA7 tip equals 11 sec

Special Price Xmas only \$54.30
Please note we are now distributors for all Weller quality products.

RISTON PRE-COATED PRINTED CIRCUIT BOARD

Available ex stock in handy sizes. Write for information and prices. Single and double sided available. Tax exempt prices available through Ritronics Wholesale (03) 489-7099.

CLARE ASCII ENCODED KEYBOARDS SPECIAL \$165.00 inc. tax

Model C70/MGP microprocessor controlled.



COMPONENT

2716's	
2708's	
2114's (450ns)	
2114's (300ns)	

KITS



ETI SERIES 4000 60W STEREO AMP KIT

Complete Kit Rack Mounting	
Case	.\$199.00
Woodgrain Sided Case	.\$189.00
Parts Available Separately	
Front Panel	\$10.90
Rack Mounting Case	\$55.00
Wooden Sided Case	\$49.00
ETI 471 Preamp kit of parts	\$10.90
ETI 472 PS kit of parts (without transformer)	\$24.00
ETI 470 60 Watt kit of parts (without heatsink)	\$23.00
ETI 480 50W kit of parts	\$17.50
ETI 480 100W kit of parts	\$22.50
ETI 084 Car Alarm kit	\$11.50
EA TV CRO Adaptor kit	\$29.00
EA 300W Power Amp Module	\$63.50
ETI 466 300W Power Amp Module	\$63.50
EA Digital Capacitance Meter Kit	AFO 00
(EA March 1980)	\$52.99
MK3 Drill Speed Control	\$29.75
Capacitor Discharge Ignition	\$13.50
Musicolor MK3 kit	φ32.50 \$60.50
Disco Strobe kit	\$34.50
Leds and Ladders (EA August)	\$15.75
ETI 149 Two-Tone Generator	\$34.90
ETI 563 Nicad Fast Charger	\$54.90
Dream 6802 kit	\$109 00
Power Supply to Suit	\$29.50
Hex Keypad	\$24.90
ETI 569 Sound or Light Operated Flash Trigger	\$25.90
ETT 147 Electronic Dummy Load kit	\$99.00
Series 3000 'Mini' Stereo Amp kit	\$79.90
E11 561 Metal Detector kit	\$32.50
Playmaster 40 plus 40 Amp kit	\$129.00
Playmaster AM/FM tuner kit	\$129.00
Playmaster Graphic Equaliser	\$99.50

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE. PH (03) 489-8131. RITRONICS WHOLESALE PH (03) 489-7099, MAIL ORDERS PH (03) 481-1436.

ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE. PH (03) 489-8131

SPECIALS

 \$13.50
 \$4.50
 \$4.5U

KITS

Playmaster Graphic Analyser kit\$	99.50
EA 79SF9 Sound Flash Trigger\$	15.00
ETI 585R Ultra Sonic RX\$	15.95
ETI 585T Ultra Sonic TX	\$8.95
ETI 576 Electromyogram kit\$	89.00



ETI 147	Oct '80 Electronic Load kit parts\$75.	.00
ETI 327	Turn Hazard Unit kit parts\$22.	.00



EA Digital Engine Analyser Oct 80 80TM8a/10
Kit parts inc. front panel\$44.95



EA Car Battery Voltage Monitor Oct EA kit parts.....\$6.50
EA Bipolar Train Controller Nov 80 kit parts......\$26.00
EA Digital Storage CRO Adaptor Nov 80 kit parts \$78.00
EA Light Beam Relay Nov 80 kit of parts......\$13.00
EA RS232 Printer Interface Nov 80 kit parts......\$15.00

SPECIALS TRIO CRO'S NOW IN STOCK


130 mm DUAL-TRACE (write for full product range and price list)
15 MHz, TRIGGERED SWEEP OSCILLOSCOPE

\$555.00 plus tax.



TRIO

• Simplified circuitry improved performance and dependability have been successfully realized with the use of ICs throughout • A vertical amplifier provides as wide a bandwidth as DC to 15 MHz, as high a sensitivity as 10 mV/div, and a low input capacitance • A sweep rate extends from 0.5 µsec/div to 0.5 sec/div in 19 ranges. Further, TV vertical and horizontal syncs are available for measuring video signals and, with its x5 magnified sweep, its range of application is extremely wide • Very easy X-Y operation of high input sensitivity for Lissajous measurements • Dimensions: 260(W) x 190(H) x 385(D) mm, Weight: 8.4 kg

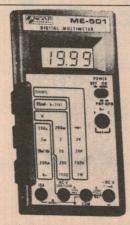

Soar Model 501A

4 digit LARGE LCD DISPLAY

Send for specs.

\$79.00

Add \$3 P&P and certified mail.

INTERSIL LCD 3½ DIGIT PANEL METER KITS. INTERSIL ICL7106 \$34.50

Build a working DPM in ½ hour with these complete evaluation kits. Test these new parts for yourself with Intersil's low-cost prototyping kits, complete with A/D converter and LCD display (for the 7106) or LED display (for the 7107). Kits provide all materials including PC board, for a functioning panel meter. ICL7106EV(LCD).

SUPER SPECIAL COMPUTER COOLING FANS 4 INCH


\$19.50



For heavier items add additional postage. Extra heavy items sent Comet freight on. Prices subject to change without notice. Send 60c and SAE for free catalogues. Minimum pack and post \$1.00. Bankcard Mail Orders welcome.

Thermatic fan controller for a vehicle

Mike Collins

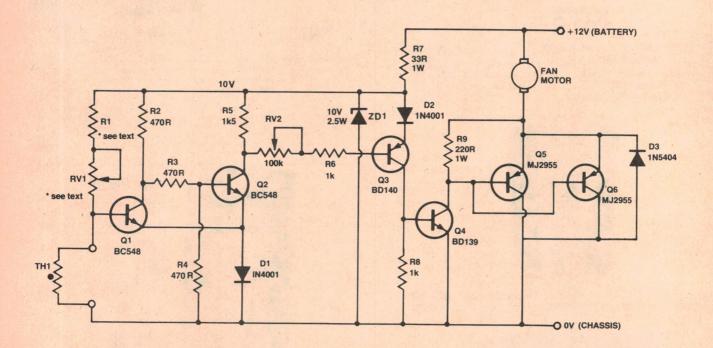

RECENTLY I decided to install a thermatic fan to my car but was dismayed to find that the price was around \$80.

This discovery sent me off to the local wreckers where I was able to purchase a fan for \$15. Unfortunately, the temperature control for this fan was unsuitable as it was fixed at the wrong temperature and was not adjustable.

I began putting together a few circuits to switch the fan on when the engine reached the desired temperature. Apart from turning the fan on at the right temperature, the circuit would have to turn it off once a predetermined lower temperature had been reached so that the engine would be maintained within its normal operating temperature range. A few circuits I tried had a

tendency to 'hang on' past this lower temperature which was definitely an undesirable situation. I eventually solved this problem by using the circuit shown here.

Circuit operation

Engine temperature is sensed by a thermistor, TH1, mounted at a convenient point on the engine block. This thermistor controls a Schmitt trigger (Q1 and Q2) which drives several power transistors (Q5 and Q6), connected in series with the fan motor, via two intermediate stages (Q3 and Q4).

So that the operating points of the Schmitt trigger remain stable despite supply voltage variations (as much as 30% in 12 V systems) the collector

supply to Q1 and Q2 is stabilised at 10 V by zener diode ZD1. This also ensures supply line spikes do not cause spurious operation of the fan.

Potentiometer RV1 sets the switch-on temperature while RV2 sets the switch-off temperature.

When the engine is below the required temperature the voltage drop across TH1 should be above 1.2 V. Thus, Q1 will be on and Q2 will be off. As no collector current flows in Q2, Q3 and Q4

SHORT CIRCUITS is a feature that lies somewhere between Ideas for Experimenters and complete Projects. Generally, the items published in Short Circuits will involve tried circuits that have not necessarily been fully developed, but fairly complete details are included as a guide to readers. Unfortunately, owing to the nature of these items, we cannot give further details other than what is provided in the article. Contributions for Short Circuits are always welcome.

will be off and no base drive will be applied to Q5/Q6. Thus, the latter transistors do not conduct and the fan will be

When the engine reaches the required temperature, the voltage drop across TH1 will fall below 1.2 V (preset using RV1) and Q1 will turn off. Q2 then turns on and base current will be supplied to Q3 via D1, Q2, RV2 and R6, turning Q3 on. This turns Q4 on which applies base drive to Q5 and Q6, turning them hard on, operating the fan.

Diode D3 prevents back-emf spikes from destroying the two MJ2955s when the unit turns them off.

There will be a certain amount of hysteresis in the operation of the Schmitt trigger. However, the collector current in Q2 will vary as Q1 will turn on gradually when the temperature drops below the preset switch-on temperature. Thus the base current to Q4 will vary. The point at which insufficient current is supplied to Q3 can be set by varying RV2.

Construction

The whole unit was constructed in a diecast aluminium box which was bolted to the vehicle chassis inside the engine compartment. The MJ2955s were mounted directly on the case, no insulation is required as the collectors are connected to 0V in any case. General construction is non-critical. However, I used a pc board and supported it by soldering the common connection copper area to the backs of the pots which were mounted on the box.

The thermistor I used had a resistance of 34 ohms at 77°C (170°F). In general, R1 and RV1 are selected such that the voltage across the thermistor TH1 is 1.2 V when the engine is at its recommended operating temperature (or in the middle of its operating temperature range). Whatever thermistor you use, you will need to know its resistance at that temperature. Knowing follows:

 $R1 = 4 \times R_{TH1}$ (at operating temp.)

 $RV1 = 6 \times R_{TH1}$ (at operating temp.)

Having calculated these values, use the component nearest in value above that calculated. The correct setting of switch-on temperature should be within the range of RV1. Values used in my unit were, R1 = 150R, RV1 = 250R.

You will need an engine temperature meter of some sort to set the on and off points correctly.

All resistors should be of the rating specified. Those used around Q1 and Q2 (R1 to R5) may be 4-watt types, but 1/2-watt or higher rated types may be more reliable. I did not find it necessary to use low value emitter resistors on the MJ2955s to assist current sharing (though it may be a good idea to match a pair for Vbe ... Ed.). The current through the fan motor when connected directly across the battery 8.6 amps. In this circuit it draws this, you can calculate R1 and RV1 as 7.7 amps but the loss did not noticeably affect the cooling.

MELBOURNE'S BEST VALUE IN COMPONENTS

	7416	74LS951.00	74LS3732.40	74412.50	741531.40	78P05
	74LS	74LS10765	7400771	744280	741541.40	78L05
	74LS0033	74LS10950	7400TTL	74471.10	741571.40	78L09
	74LS0130	74LS11350	740025	74481.10	74160 1.70	78L12
	74LS0230	74LS11475	740125	745030	74165 1.70	78L15
	74LS0440	74LS1231.50	740225	745130	741721.40	78L18
	74LS0550	74LS12570	740325	745330	74173 2.60	78L24
	74LS0830	74LS13330	740425	745430	741751.20	78CB
	74LS0930	74LS1381.10	740530	746030	741801.50	7905
	74LS1030	74LS1511.00	740660	747050	741921.80	7905K
1	74LS1155	74LS15560	740745	747255	741931.80	7906
l	74LS1230	74LS15775	740825	747355	741761.50	7908
1	74LS1480	74LS16070	740925	747435	7436780	7912
ı	74LS1575	74LS16380	741025	747545	7430700	7912K
١	74LS1660	74LS1641.40	741240	747640	748	7915
١	74LS2030	74LS1651.40	741355	74801.00		7918
ı	74LS2135	74LS1691.90	741460	74831.40	74\$0275	
۱	74LS2730	74LS17465	741660	74851.40	74S741.40	7924
ı	74LS2835	74LS17590	741765	748655	VOLT. REG.	79HG 79L03
١	74LS3030	74LS1901.60	742025	74892.90		
ı	74LS3230	74LS1911.30	742130	749040	309K1.90	79L05
١	74LS3740	74LS1921.15	742235	74911.00	317T2.90	79L12
ı	74LS3840	74LS1931.00	742560	749280	317K2.90	79L15
ı	74LS4030	74LS1941.20	742640	749350	323K8.95 723-1455	79L16
ı	74LS4245	74LS1951.00	742740	74941.15	723can95	78MGT
۱	74LS471.20	74LS1961.60	743030	74951.00		79MGT
ı	74LS7360	74LS1971.60	743230	74961.10	7805 1.00 7805K 2.10	7910101
١	74LS7440	74LS2211.50	743740	741002.00		DVM C
ı	74LS7550	74LS2471.95	743840	7410770	78121.00	74C925
۱	74LS7865	74LS25185	743950	7412170	7812K2.40	740925
١	74LS851.40	74LS25385	744030	7412385	78151.00	
١	74LS8660	74LS25775	74LS36580	741321.30	78181.00	
	74LS9060	74LS2593.30	74LS36680	741451.50	78241.00	I N
۱	74LS921.00	74LS25995		741501.50	78H059.20	
	74LS9385	74LS2901.30	74LS36790		78H127.50	
۱	7 12030	74132901.30	74LS36865	741511.40	78HG7.95	

78P05	8.00
78L05	40
·78L09	40
78L12	40
78L15	
	40
78L24	40
78CB	2.40
7905	1.60
7905K	2.95
7906	1.60
7908	1.60
7912	1.85
7912K	
	1.60
7918	1.90
7924	
79HG	

40	ITE	MS
40	XR082	1.30
40	XR084	2.30
40	XR8038	
2.40	LM331	
1.60	6800P	11.50
2.95	6810P	5.60
1.60	6821	6.50
1.60	6850	6.50
1.85	8085	22.00
2.95	Z80P10	12.00
1.60	Z80CTC	12.00
1.90	Z80CPU	12.00
1.60	1488	1.00
10.80	9368	
80	9528	
80	8T24	
80	8T26	
95	8T28	
80	81LS95	
1.80	81LS97	
1.80	93448	
1.00	2708	10.00

SELECTED

CHIP .13.50


Mail Orders, \$1.00 Min. P&P Please.

2716

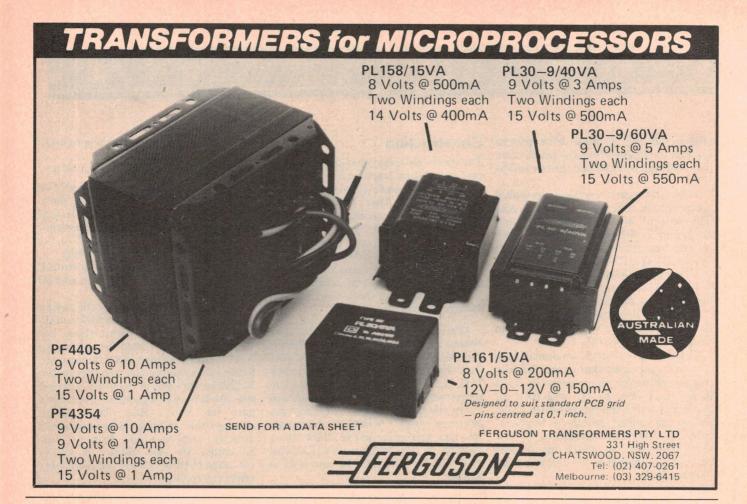29.50

ASMAN ELECTRONICS

12 Victoria Street, Coburg, VIC, 3058. Phone (03) 354-5062.





CHRISTMAS

* XMAS OUSE BOYS SELECTION OF THE STREET STR

ALARMS MENS

1.99

Also Ladies HI-FASHION model \$19.50 and UNI-SEX fashion model \$19.50

DATE, LIGHT

ALL ARE AVAILABLE IN GOLD OR STAINLESS STEEL FINISHES

12:3710

Ideal Xmas Gift! \$ 4

BUTTON PHONE SAVE \$10 Specially de

B or 14PIN 16 PIN 16 PIN 18 PIN 24 28PIN 24 28PI or 14P. 5 for \$1 4 for \$1 3 for \$1 2 for \$1 1 for \$1 14 PIN PLUG (Header) 5 for \$1

NE 555 40 LM 741 30

IN4004 400v IA rect.
IN4007 IKV IA rect.
IN5404 400v 3A rect.
IN5404 IKV 3A rect.
IN5408 JKV 3A rect.
IN54 25c 20c 16c 35c 30c 23c \$1.50 \$1.30 \$1.20 LM340T-12 \$1 EA (7812) 12V 14 REG. 10+90

NE 556 \$1 EN 100 EA DUAL TIMER LIMITED QTY, AVAIL BFX \$8 TIC 44 WA709 AY6103 TAY6103 TAY

INCREDIBLE VALUE! GOODIES

DE-SOLDER BRAID 1 metre pack\$ 1.75 INTERCOMS, 2 WAY only \$ 12 INTERCUMS, & WAT only 126
6-PCB OFFCUTS ## Handy sizes \$2
240v Light Flasher 60-580*
20-Asst MINI-POTS At new good \$2
AM Tuner Kit ## Hands ferrite Garage
AM Tuner Kit ## Hands included the ferrite Campaigners and intercess

20-Asst MINI-POIS All news, 2004 \$22

AM Tuner Kit Medick-Ferritg, Cemp. 5
100,000 UF 16 VW ELECTRO SERMS
100,000 UF 16 VW ELECTRO SERMS
25 tereo Ceramic Cartridge CP\$2.50
MOST COMMON replacement similar C-1, SC-5/Heb
20 COMPUTER BOARDS 18P\$2
Lote of diades, translators, resistors, capacitus
12 V Ni-Cad (Section 1990 Milks of 1995)
Pencell Batt. RECHARGEAGE 10 7 \$1.50 ea
FM Wireless Mike \$8-100 Mike 500 \$1
240 V to 110 V Transformer 24 cont \$1
240 V to 110 V Transformer 24 cont \$1
25 Pelescopic TV AERIALS 316 mm \$1.75
Pelescopic TV AER PL-259 (0-ax PLUG TYSHE'M 10 for 3-50
PL-259 (0-ax PLUG TYSHE'M 10 for 3-50
100 asst TAGSTRIPS all lengths \$2.50
20 asst. POTS Englishers Francis \$2
200 asst. TW Resistors Good \$2
200 asst. TW Resistors Good \$2
30 asst. Electralytic Cops \$2
6 Metres 3 (ore MAINS LEAD graft \$2
3 - 8" Ferrite Rods for antenna \$120
AY 3-2500 TW Gomes TC chis \$3

3-8 Perrite Kods for antenna 1 to Ay3-8500 TV Games II chip 8 8 "Ceiling Spkr. Grilles 508 BACK-\$2 8" 5 w SPEAKERS to suit above \$7 5 w Line Iransformer to suit 70 v line \$3 10 w Line Transformer to suit 70 v line \$4

CUE S89

THE PRO model WITH 5 BAND GRAPHIC EQUALIZER NOW ONLY



MAD'S No 2 BONANZA A VAST ASSORTMENT OF GOODIES FOR ASPIRING HOBBYISTS- All new pak



UHF AMP **BF 180**

Worth at least \$20 OVER 100 PARTS

XENON FLASH TUBE only \$ 2.50 TRIG. TRANS 90% 754 TAME

DE-LUXE METAL 105mm \$490 CABINETS 18G. Steel cover 184x \$5.45 70x \$5.45 8UY 10 +, LESS 10%. REED SWITCH 45e-

and COIL 430 15 80c MINI PCB 225 \$ 1.50 RELAY 84-15vde 10+ \$1.30 TV CIRCUIT BOARDS

BC157 7400... 15. NOW! 1999 BC158 7401...15. 7427..30. 7474.40. BC159 7404. 22. 7441...90. 7490.45. 102. 564. 2.75 7410...22. 7473. 40. 74150.90. EACH 54.35 SOLDERING IRON FAMOUS 240vs 15w or 30w mode

RESISTORSeach 4 PER 100 100 3 14 or 1/2 \$ 1.50

DE-LUXE SOLDERING SAVE \$

286 254 10+\$17 50+\$75 TRANSFORMERS SAVE \$\$\$

2N3053

20%

M-2851 6.3y-0-6.3y 150mA \$2.90 M-2155 0-6-3, 7-5, 8-5, 9-5, 12-6, 15 V 14\$5 M-6672 0-15, 17.5, 20, 24, WHILES \$ 7


GREENCAP CAPACITORS 0.001 to 0.01 uF. 10to. 50 uE 0.022 to 0.047 uF. 12to 50 uE 0.056 to 0.1 uF. 16to .22 uE 25.47 uF.40. PACK of 100 asst. (lucky-dip) ... 5.90
PCB ETCHING Kit

.99

SPEAKER KIT SALE WALNUT finish, ready-made boxes black speaker cloth 8 WOOFER+5 MID-RANGE+ 5 TWEETER + X OVERS +wire and Inner bond + SALE CAN

oCen be screws! finished in 2 hours! PER SOUND! SOUND! ASSEMBLED PR\$ 109

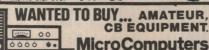Speakers Separately: 8" Woofer \$7.50 ca 5" Mid-range 500Hz-12KHz \$5.95 ca 3" Tweeter 5KHz-18KHz \$4.50 ca



000 MULTIMETERS. OSCILLOSCOPES TEST INSTRUMENTS.




PRE-PAK electronics P.O. Box 43, CROYDON 2132 1a West St. Lewisham, N.S.W. Ph: 569-9797 MPOST 10% CALLE

Phone or MAIL STORDER bankcard




Just starting out?

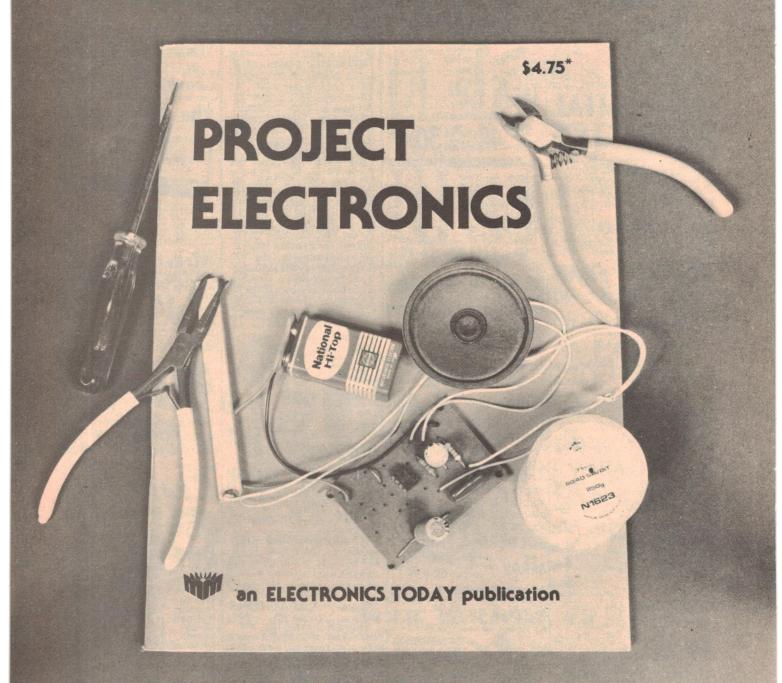

THIS BOOK has been specially designed and produced to meet the needs of newcomers to electronics. Students following the three-segment industrial Arts syllabus at high school or embarking on the Electronics & Communications or a similar certificate course, will find the projects in this book an eminently practical introduction to the 'works' in electronics. Project Electronics has been a runaway success since it was first published. There are 26 projects included, many are readily available as inexpensive kits, and the book also provides advice on tools, identifying components, troubleshooting, how to solder etc. Available from specialist electronic suppliers or direct from the ETI Subscription Department, 3rd Floor, 15 Boundary St, Rushcutters Bay NSW 2011 for \$4.75 plus 45 cents post and packing.

Emergency lighting unit

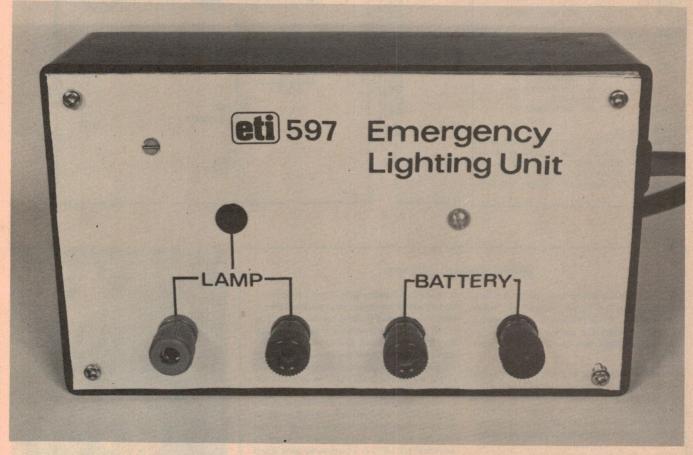If the mains power fails, you needn't be left completely in the dark. This unit automatically switches on a battery operated lamp as soon as the power goes off and keeps the battery always fully charged and ready for action.



IF YOU LIVE in an isolated country area where the mains supply is erratic, or if your local electricity authority is not too good at labour relations and its workers are always going on strike, then you'll know what it's like to be suddenly and completely without any electric power.


Being deprived of the TV and hi-fi for a while could well be good for the imagination and improve your conversational skills no end, but trying to find the toothpaste in a pitch black bathroom is simply infuriating!


In these circumstances, even a low intensity light is infinitely better than none at all. With this in mind we've designed this project, which switches on a 12 volt lamp of up to 24 watts as soon as the mains power fails. It could also be used of course to power any other 12 volt appliance with the same power rating.

The emergency lamp runs on current supplied by a 12 volt battery, which is kept fully charged when not in use by a trickle of current from the mains. We used a NiCad battery for our prototype, but there is no reason why you shouldn't use a lead/acid accumulator instead, because the charging current is kept so low there is no risk of overcharging and damaging the cells. The charging cur-

rent is determined by a current limiting resistor, which must be chosen to suit the capacity and charge characteristics of the battery you are using. On page 58 is a table which lists the necessary values of this resistor for different batteries.

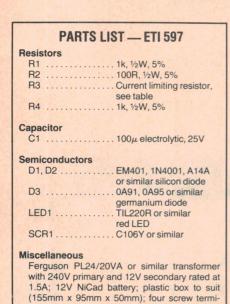We've also included a red LED on the front panel of the unit, to show when it is operating (i.e. when the battery is discharging). This may seem superfluous, because after all you can see for yourself whether a lamp is lit or not, but if you are using the unit to run a fish tank heater or suchlike, then an indication that the unit is operating will be reassuring.



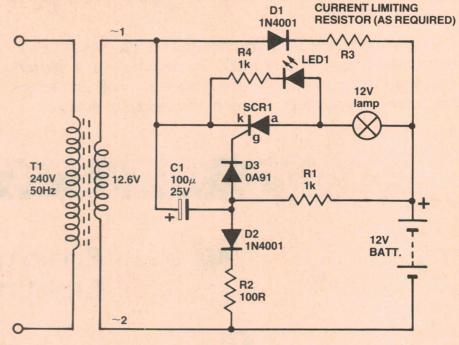


HOW IT WORKS — ETI 597

When the mains power is on, the circuit float charges a NiCad battery from a transformer and rectifier. When the mains fails, a control circuit switches the battery through to the emergency light and the LED on the front panel.

nals, two red, two black; 12V light bulb and

socket

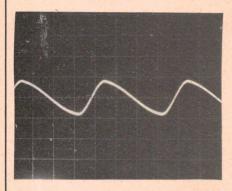WHEN POWER IS ON the NiCad battery is trickle charged through a rectifier diode D1, which supplies half wave rectified current pulses to the battery. Capacitor C1 smooths out these pulses by charging to the peak voltage from the transformer secondary through



Waveform at the positive lead of C1, showing the 50 Hz ripple.

D2 and R2 and discharging through R1 and the battery when the output from the transformer falls. The discharge time constant of C1 is much longer than its charge time constant, so that it does not have time to discharge fully during the transformer negative half cycle. So C1 stays at a high positive voltage, with some ripple, as can be seen from the oscilloscope photograph.

As C1 remains charged, the voltage on the gate of SCR1 is always lower than the voltage on its cathode and SCR1 is therefore reverse biased, so that the emergency lamp is switched off. LED1 is also reverse biased and not illuminated.

WHEN THE POWER FAILS the output from the transformer falls to zero and C1 starts to discharge through R1 and the battery. Once C1 is fully discharged it begins to charge in the reverse direction from the battery until the voltage on the gate of SCR1 is about 0.6 volts higher than the voltage on its cathode. SCR1 then switches on, lighting the emergency lamp. LED1 is now forward biased and illuminated. The voltage on C1 does not rise any further and the capacitor is not damaged by the reverse polarity because the voltage across it is less than the forming voltage of the electrolyte.


When the power returns, C1 charges again through D2 and R2, turning off SCR1 and resetting the circuit.



NiCad batteries may be used with this project and they can be obtained in ratings from 500 mAh up to 2 Ah capacity. Sealed lead-acid batteries can be obtained in higher capacities (see page 61).

BATTERY CAPACITY	VALUE OF R3 (5W, 5%)
500 mAh	82R
1.2 Ah	33R
2 Ah	22R
4 Ah	10R
6 Ah	6R8

emergency lighting unit

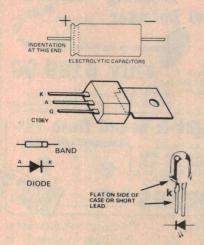

Construction


All the components are housed in a plastic case with an aluminium front panel that has terminals for the battery and lamp connections. The LED which indicates power failure is set in the panel above the lamp terminals.


As the circuit is very simple, we decided to mount the electronics on a length of twin tag strip. Mount the components as shown in the diagram on this page, being careful with the orientation of the diodes and the electrolytic capacitor.

The current limiting resistor R3 sets the charging current to the batteries and must be selected to suit the voltage and capacity of the battery. Consult the table on page 58 for the correct value. This resistor may run quite warm, so it should be mounted so that it is spaced about 5mm above the tag board for adequate ventilation.

If the emergency lamp draws 1 A or less, the SCR does not need a heatsink; if the lamp draws between 1 A and 2 A, the SCR can be mounted on the aluminium front panel with an insulating mica strip between it and the metal. For load currents over 2 A a heavier SCR with its own heatsink would have to be used, but we do not recommend drawing this much current because this is an emergency lamp and you won't want to discharge the battery too quickly.

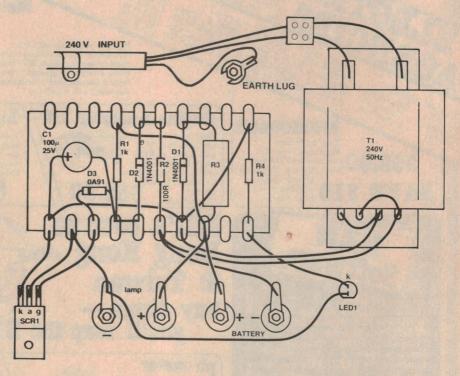Next wire the connections from the tag board to the LED, the terminals and the transformer. Be extra careful with all of these connections and use insulated hookup wire for all wiring, including connections across the tags on the tag board. The transformer is mounted in the top right corner of the box, leaving enough room for the terminals and the tag board.



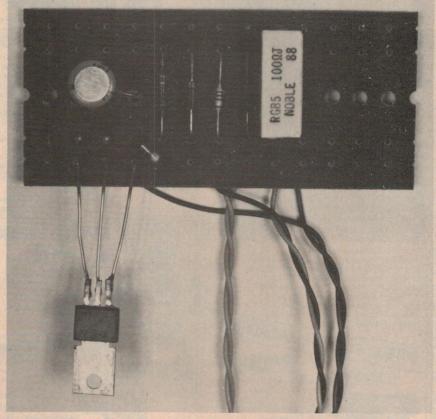

Showing the components mounted on the tagstrip.

George Ave)

Metal Detector

amazing

Join the gold rush with this incredible discriminating metal detector project from ETI. Features 4 mode operation, ground balance pre NOTE: wound search head plus incredible photos penetration & sensitivity

photograph shows unit mounted on handle which is not supplied in the kit.

MUSICOLOR

Yes! the famous Musicolor 3—now reduced to \$10 below normal price. Complete kit with deluxe metalwork and front panel

TRADING HOURS

Mon-Fri

Saturday

Sunday

_5.30pm

9am-noon 10am 2pm

Engine Analyser kit Keep your car in tune and save fuel. This unit measures RPM, dwell and battery voltage on any 4, 6 or 8 cylinder petrol engine.

& sound flash kit Light

Take spectacular action photos. Suits any flash unit—fully variable sensitivity & delay. See ETI Oct

\$26.95



Electronic Agencies is now buying direct. So

For the Sorcerer:
MUSIC: creative 4 voice music \$52.95
PIANO PLAYER: used with
MUSIC. Fully graphical \$15.95
CROSS REFERENCE: prints a
complete variable & line cross
reference voe BASIC program \$12.95 GRAPHICS: Fantastic graphic creations \$32.95 SUPER X: a great text editor \$25.95 JAIL BREAK: new modified (and cheaper) \$9.95 INVADERS: just like in the arcade \$19.95
BASEBALL: Fantastic graphics—and a great game \$15.95 CADAS: cassette base general CADAS: cassette base general purpose database system (machine code) \$32.95
HEAD ON COLLISION: You are driving clockwise, and a computer controlled car is coming the other way. \$15.95
FORTH: Serious Z80 program developers will find this program invaluable (requires program invaluable (requires Development PAC) \$32.95 Sorcerer & TRS-80/System 80 STOCK RECORD: Functions

If you're in the market for a pair of speakers, you owe it to yourself to come and look at our incredible range. Famous Philips, Coral and Foster. 10 different woofers, 6 midrange, 8 tweeters and 10 full range units means you can get a system that's perfect for your needs & budget. Write for your FREE speaker catalogue today!

include: List, Edit stock records, update prices, edit/enter items, clear all data, delete item, store

& retrieve records on cassette and print out stock list. \$45.95

FREE speaker catalogue

\$289.00 The famous FM320 at a price you'll find hard to beat. UHF 40 channel CB. Antennas to suit \$19.99 (mobile) \$95.00 (base)

Complete kit buy direct-

you'll reap the BENEFIT

you buy at a better price. Our lower overheads mean that we can offer you real value on all your electronic needs. MERRY XMAS

ph meter

3½ digit display, easy to build pH meter Ideal for pool or fish tank water testing, or

NEW wideband receiver kit

Four ranges from broadcast to 30MHz. Complete kit (see EA Nov 1980 for details)

Toroidal Transformer

Lighter, quieter, more efficient. What more could you ask for. This transformer delivers 28-0-28V @ 2A. Suits ETI \$ 480, series 4000 or other amps needing $\pm 40V$ rails.

without hum

Series 5000 FET Amp

Now you can forget about noise, distortion & hum. The fantastic new Series 5000 FET output amplifier is on its way from ETI. We are preparing a deluxe kit with our own detailed instruction manual. The price will be about \$250 (estimate only).

Please phone us for up-to-the-minute details of this kit

case?

542 wood low profile deluxe case for amplifiers etc

rack same case in a \$49 rack mount format



\$45 wood slightly deeper for those bigger projects

rack deeper case in \$55 popular rack format



prossover etc.) ETI 4000/2 3 way.

Fully assembled & veneered.

For 4000/1 per pair \$300.00 \$360 pair. For 4000/2 per pair \$200.00 Note "Freight on" only

Own a microwave?

Microwave ovens are a boon to modern living, but a leaking one is a very real danger. This simple to

build kit checks any microwave oven for harmful leaks. ETI 724. Complete kit only:

DEAR CUSTOMERS, Please phone us before coming in to check that what you're after is in stock and that the price is correct. Bill Edge and staff





emergency lighting unit


Secure the mains power lead by passing it into the box through a clamping type grommet. Connect the earth wire of the mains lead to the solder lugs on the transformer case and to the front panel. Make sure that these connections are well made and that there is slack left on the mains earth wire, so that if the cable is pulled out of the grommet the earth wire will be the last to break off.

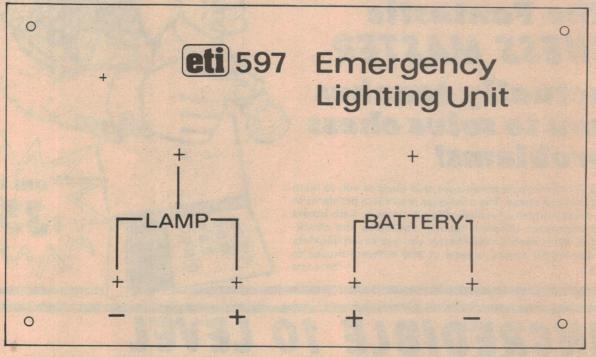Lead-acid storage batteries, such as these sealed, gel electrolyte types are ideal for use with this project and can be obtained in ratings up to 6 Ah. The two batteries on the left are 6 V types rated at 4 Ah, while the 12 V type on the right is rated at 6 Ah.





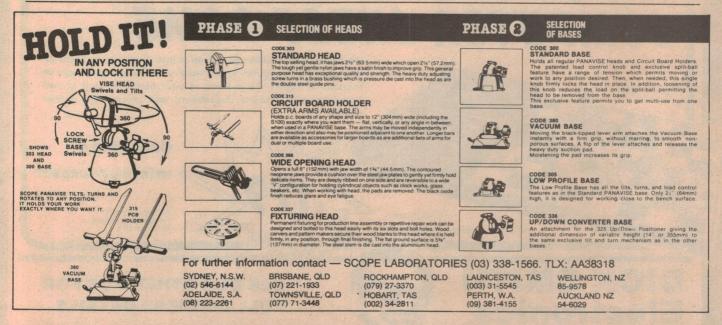

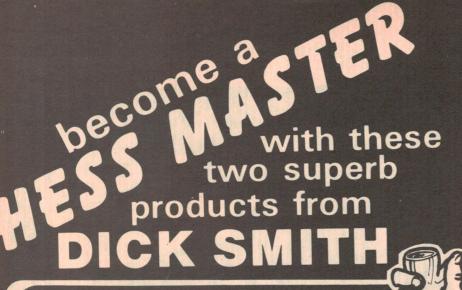

The Fantastic CHESS MASTER actually teaches you to solve chess problems!

This is the machine for all ages that enables you to learn and practise chess. The challenge is to solve problems in the least number of moves. Play it alone or with others and experience different tactics, strategies and checkmates. With each Chess Master you get seven booklets containing 50 moves, a total of 350 different moves to play.

Cat. X-1257



INCREDIBLE 10 LEVEL COMPUTER CHESS GAME

Cat. X-1255

Credit terms available to approved applicants

Whatever level of chess game you're into, this unit has them all. You play the computer at the level you select from beginner through to expert. To aid you in your game the unit comes complete with integral chessboard and pieces plus power supply.

Contains a microprocessor

\$6 below cost freight anywhere in Australia

DICK SMITH Electronics



SEE OUR OTHER ADS FOR FULL ADDRESS DETAILS

GRADUATETO

University

METERS AND INSTRUMENTS

T.D. SERIES PANEL METERS

Suitable for the hobbyist and manufacturer. Highest quality — complies with Australian Standard AS.1042. Moving coil, high torque, core magnet self shielded. Most standard ranges available ex-stock. Special scales, pointers and ranges on indent.







Available in 6 sizes


TD-48	48 x 42mm
TD-66	66 x 60mm
TD-86	86 x 78mm
TD-106	106 x 83mm
TD-118	118 x 106mm
TD-152	152 x 110mm
	TD-66 TD-86 TD-106 TD-118

TD Series meters can be rear mounted.

- TEST INSTRUMENTS
- PANEL METERS
- DIGITAL METERS
- EDUCATIONAL EQUIPMENT
- SWITCHBOARD INSTRUMENTS

MULTIMETERS

New CTi-500 "Industrial" diode protected

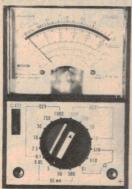

20,000 Ohms per DC AC and DC Volts DC amps to .5A Resistance and db Size 130 x 90 x 38mm An excellent general purpose unit

DIGITAL MODEL 2200A 3½ digit LCD display, 12mm high

The famous MVA-100CN
"Deluxe" now with fuse
and diode protection

100,000 Ohms per V DC AC and DC Volts to 1Kv AC or DC Amps to 10A Resistance .1 Ohms to 200M Ohms db minus 20 to plus 62 dB 4mm terminals Polarity switch Shock proof movement Size 180 x 140 x 80mm





Two input terminals
Over range indication
Overload protection
200 hours continuous operation
Auto zero and auto polarity
Low battery warning

TEST INSTRUMENTS Non Contact Voltage Indicator DEAD OR ALIVE?





The non contact EZ-Scan unit gives an immediate visual indication of voltage, with or without current flowing at distances up to 15cm from the source. Battery powered and all solid state, the unit is small enough to be carried in a pocket, and tough enough to leave in a tool box.

To find a break in a cable, a bad earth, a faulty fitting or just to know if it's live — use the EZ-Scan. For all unshielded AC electrical systems, 60V and higher.

PRICE: HIĞHEST QUALITY at the LOWEST PRICE.
GUARANTEE: 90 day, backed by University after sales service.
SERVICE: 24 hour efficient repair service.

University Graham Instruments
Ptv. Ltd.

PO Box 204, Enfield, NSW. 2136. Phone (02) 53-0644 Telex AA21398 Melbourne Phone (03) 387-6170

SICK OF SEARCHING FOR CONVERSION FACTORS?

NOW AVAILABLE

THE
COMPREHENSIVE
BOOK OF
CONVERSION
TABLES + FACTORS

FEATURES

- 54 pages of conversions.
 Alphabetically listed.
 Over 2700 individual conversions.
- All conversions simple multiplications.
- 8 pages of terminology explanations.
- 8 pages of lists of constant factors.
- All in one inexpensive pocket sized book. 110 x 195 x 4mm.
- 14 day money back guarantee.

Price: \$4.00 incl. P&P
I enclose \$cheque/m.o.
forcopy/s of the Book of Conversion Tables + Factors.
Name
Address
P'code
Mail to:

DATIV PROMOTIONS, PO BOX 201, ARMADALE, VIC, 3143.

PLESSEY COMPONENTS

NEW PRODUCT




NON VOLATILE LOGIC 256 BIT MEMORY (64 x 4)

MN9210

- Electrically alterable
- Non-volatile memory
- MNOS technology (not NMOS)
- plus 5 V minus 12 supply
- Low current programming supply minus 39 V

FEATURES

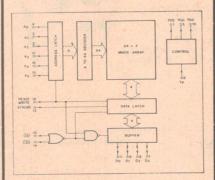- Guaranteed data retention of one year in the absence of applied power.
- Latching data and address inputs.
- Three-state outputs on data lines.
- TTL/CMOS compatibility
- Single word preprogramming facilities.
- Temperature range minus 40 degrees C plus 70 degrees C.
- 18-pin dual-in-line package.



This is a new addition to our existing range of Novol.

MN9102 — 4 bit data latch MN9105 — 4 decade BCD counter MN9106 — 6 decade UP counter MN9107 — Counter to 100 hours MN9108 — Counter to 10,000 hours.




PO BOX 2, VILLAWOOD, NSW 2163. PHONE: (02) 72-0133.

35 years young



NEW
CRYSTAL MARKER
OSCILLATOR

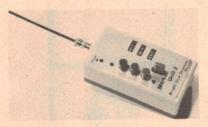

Marker frequency from 2MHz to 20MHz

Manufacturers of

PIEZO ELECTRIC CRYSTALS
Contractors to Federal and State
Government Departments.

REPRESENTATIVES:

NSW: J. E. Waters, 11 Salisbury St, Botany. 2019. Ph 666-8144.

SA: Rogers Electronics, 65 Magill Rd, Stepney. 5069. Ph (08) 42-6666.

QLD: Fred Hoe & Sons P/L, 246 Evans Rd, Salisbury North. Brisbane. Ph 277-4311.

WA: Westest Electronics, 71 Jean St, Hamilton Hill. 6161. (Mail only) Ph (09) 337-6393.

TAS: Dilmond Instruments, PO Box 219, Bellerive. Hobart. Ph 479-47-9077

Send SAE for new catalogue or quote for your requirements.



PO Box 42. Springvale. Ph (03) 546-5076 Telex AA36004

Lab Notes

Voltage regulators

— circuits and techniques

Here's a 'cookbooklet' of voltage regulator circuits and techniques covering everything from simple zeners to three-terminal regulators from UK correspondent Ray Marston, with additional material from staff.

ONE OF THE most common and mun- vided that the zener power rating is not dane tasks facing the electronics enthusiast is that of designing voltage regulator circuits, ie: circuits that produce a stable and well defined dc output voltage over a wide range of load current variations. These circuits may vary from simple zener networks, designed to provide load currents up to only a few milliamps, to fixed-voltage high current units for powering logic boards, etc, or to variable-voltage high current units designed to act as general purpose pieces of test gear.

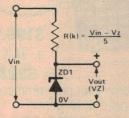


Figure 1. The simplest regulator. The zener regulator is often used to provide a fixed voltage 'reference' and supplies little or no load current. In such case a 400 mW zener of appropriate voltage is used and biased at about 5 mA. The value of R, in kilo ohms, can be calculated from the formula.

Zener based circuits

A zener diode can be used to produce a fixed reference voltage as shown in Figure 1. Often, the supply voltage (Vin) may be subject to fairly wide variations, causing the zener current to vary over a similarly large range. As long as Vin is always more than a few volts greater than the zener voltage and proexceeded this variation has only a moderate influence on the output voltage of the zener, which typically has an effective output impedance of a few tens of ohms.

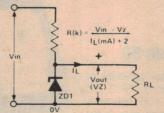


Figure 2. The basic zener regulator can be designed to supply a load current of a few milliamps to hundreds of milliamps depending on the zener power rating. Knowing the required load current, the value of R can be calculated from the formula.

A zener can be used as a very simple voltage regulator, providing load currents up to a few mA, by determining the value of 'R' as shown in Figure 2.

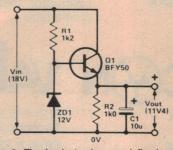


Figure 3. The basic 'series pass' fixed voltage regulator using a zener reference. This circuit can deliver up to about 100 mA at 11.4 volts. Q1 is basically an emitter follower, the base being 'clamped' at 12 V by the zener. C1 reduces the circuit's ac impedance.

In most practical voltage regulator applications the zener is simply used to apply a 'reference' voltage to a highgain non-inverting buffer amplifier, which then supplies the required output power. The simplest example of this type of circuit is shown in the seriespass regulator circuit of Figure 3.

Op-amp regulators

One way of improving the regulation of the Figure 3 circuit would be to use a Darlington or super-alpha pair of transistors in place of Q1. An even better solution is to use the op-amp plus transistor buffer stage shown in Figure 4. Choice of circuit would perhaps depend on component availability and the application.


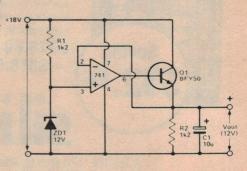


Figure 4. A considerable improvement in regulation is achieved by employing a high gain op-amp to drive the series pass transistor plus negative feedback from the dc output. This circuit will deliver up to about 100 mA and the output voltage stays within a few millivolts of the zener reference for output current variation from zero to maximum

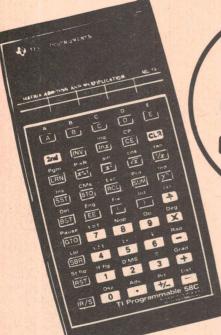

CHRISTMAS SPECIALS





Save near \$24

TI Programmable 58C

Here's a programmable calculator that offers more power, flexibility and capability and features TI's exclusive Solid State Software. With Master Library module with 25 programmes in math, statistics, and finance you can choose from 12 optional libraries. You can also programme the TI programmable 58C right from the keyboard. TI's Constant Memory feature retains data or programme information even when the calculator is turned off.

It has up to 480 programme steps or 60 memories with 4 types of display testing with independent test or "Y" register and

10 additional test registers.

Over 170 functions and operations in scientific, engineering, and statistical fields. Complete editing and error correction capabilities with single-step and back-step keys.

The TI Programmable 58C gives hard copy when used with the PC-100C thermal printer/plotter.

\$122.99 + TAX = \$141.44

The T.I. Programmable 59

A revolutionary new personal programmable calculator. 960 programme steps or 100 memories. Master library module plug in feature. 25 different programmes in key areas. Four types of display up to 10 additional test registers. 72 useful labels. Up to 6 levels of sub routines. Complete programme editing. Operates with PC-100C printer. Optional solid state software libraries.

\$276.99 + TAX = \$318.54



PC-110C

The PC-110C printer plotter turns your programmable T.I.58C or T.I.59 into a high speed quiet printer calculator that prints, lists and traces your programme.

TEXAS INSTRUMENTS

silic@n valley



ADELAIDE: 170 Sturt St, Adelaide. Telephone (08) 51 4080

BRISBANE: 22 Ross St, Newstead. Telephone (07) 52 1339

MELBOURNE: 208 Whitehorse Rd, Blackburn.

Telephone (03) 877 5311

PERTH: Unit 1, 25 Brisbane St, East Perth.

Telephone (09) 328 8091


SYDNEY: 23 Chandos St, St. Leonards.

Telephone (02) 439 2965

NOTE: Offer closes 24th December, 1980

Lab Notes

The op-amp based regulator of Figure 4 supplies 12V at currents up to 100 mA and gives excellent regulation, despite its simplicity. The op-amp and transistor (Q1) are interconnected as a unity voltage gain non-inverting dc amplifier that has an overall current gain of about one million! The output voltage will be within a few millivolts of the zener reference value and the output impedance is less than one milliohm. The safe output current driving capacity of the circuit is limited to about 100 mA by the power rating of Q1, which should have a small 'flag' or pushon heatsink attached.

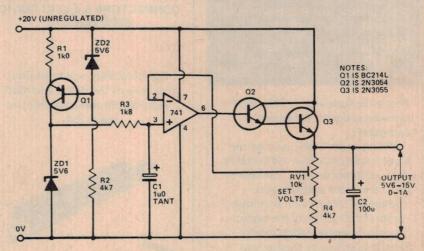

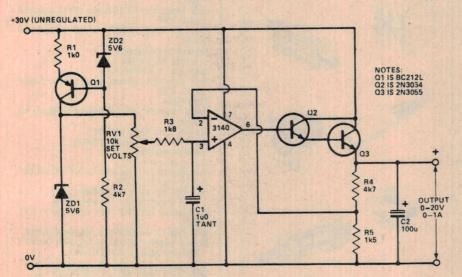


Figure 5. This circuit is a little more sophisticated and performs better than the Figure 4 circuit. This circuit will deliver up to 1 A output current, output voltage being variable between 5.6 V and 15 V. Thermal drift is near zero.

eliminated by making ZD1 a 5V6 type, with near-zero (actually about -0.2 mV/°C) temperature coefficient; the op-amp output voltage can then be set to the desired value (greater than 5V6) by using feedback components RV1-R4 to set the op-amp's voltage gain at some appropriate value.

Finally, the load current capacity of the circuit can be set to a fairly high value by using a Darlington-connected power transistor in the series pass output stage. Note that Q2 and Q3 could be replaced by a BDV65B Darlington device.

Figure 6. This variation on the Figure 5 circuit permits the output voltage to be varied between 0 V and 20 V. The 3140 op-amp has a fixed voltage gain of about four, fixed by R4/R5.

This circuit can be modified to provide greater current output by replacing Q1 with a power Darlington transistor such as the BDV65B. A suitable heatsink should be used.

The performance of the basic op-amp circuit of Figure 4 can be improved in a variety of ways, some of which are shown in Figure 5. The first improvement that can be made is to make the zener reference voltage (ZD1) independent of supply voltage variations by powering ZD1 from the output of constant-current generator Q1-R1-ZD2-R2. Next, the zener noise can be eliminated by feeding the reference voltage to the op-amp via low-pass filter R3-C1. Thermal drift effects can be

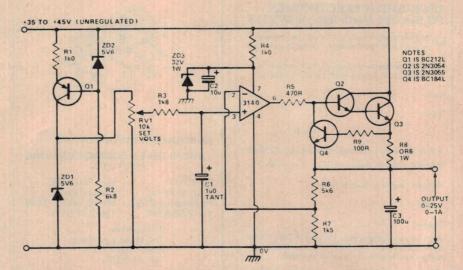


Figure 7. A further refinement is the addition of current limiting and overload protection. Q4 senses the voltage across R8 which is in series with the output. When the current exceeds 1 A, Q4

will be biased on and rob current from the base of Q2, preventing further increase in output current. The op-amp is protected against excessive supply rail voltage via R4 and ZD3.

MAGINE

A computer game that has drawn the attention of the national news media.

A computer game that has people around the world clamoring for it.

A computer game that turns your love life into a menage a trois... you, your mate, and your computer!

That's Interlude—the hottest new software program for personal computers.

But it's more than just a game. It's an experience that will tantalize you...romanticize you...fantasize you...and often surprise you.

Interlude begins with a unique computer interview of the participants to determine their mood. Then it searches its memory to select the best Interlude for the occasion. You may be referred to the instruction manual which describes most of the 106 Interludes. or your instructions may appear on your screen if you've chanced to hit upon one of the many surprise Interludes buried within the program. (When you discover secret Interlude #99, your love life may never be the same again!)

Interlude...it's fun...it's fanciful... it's fantastic. It's the computer game for adults. Are you ready for it?

DICK SMITH ELECTRONICS PO Box 321 North Ryde NSW 2113

- Yes! I want the Ultimate Experience. Please rush a copy of 'Interlude' for my System 80 or TRS-80 computer 1 am over 18 years of age
- I'm interested! But I haven't a computer Please send details of the incredible System 80 computer so I can enjoy Interlude too

Name

P'code

is enclosed

'Interlude' program and detailed instruction manual costs \$22 50 plus

\$2.00 pack & post My cheque for \$

OR Please charge to my Bankcard Exp date

No 496


(Or you can order Interlude by phone: Call Sydney (02) 888 3200 and ask for Bankcard Phone Orders Quote your Bankcard number & expiry date and Interlude will be sent to you the same day!)

ALSO AVAILABLE FROM ALL DICK SMITH STORES: Sydney, Melbourne Brisbane Adelaide Canberra Perth & Wollongong, plus re-sellers in all areas.



CONNECTORS & ELECTRONIC COMPONENTS

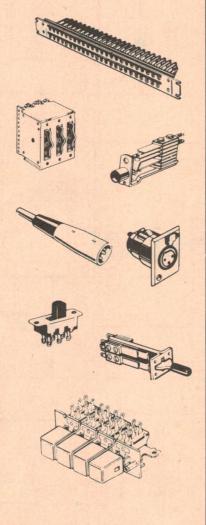Superb quality and reliability from one of the oldest and most experienced manufacturers in the U.S.A.



AUSTRALIAN DISTRIBUTORS AUDIO TELEX COMMUNICATIONS PTY. LTD.

SYDNEY 1 Little Street, Parramatta, 2150 Tel: 633 4344

MELBOURNE 7 Essex Road, Mt. Waverley, 3149 Tel: 277 5311

BRISBANE 394 Montague Road, West End, 4101 Tel: 44 6328





ELECTRONIC TRUMENTS

OSCILLOSCOPES

GOS-935 at \$199.00 (\$173.00 excl. tax). GOS-955 at \$299.00 (\$260.00 excl. tax). A laboratory quality instrument, fully solid state with 6.5 MHz useable response.

SPECIFICATIONS

Vertical Deflection

Sensitivity: 10mV/DIV

Attenuator: 1/1, 1/10, 1/100 and GND.
Bandwidth: DC: DC-5MHz(-3dB). AC: 2Hz-5MH(-

Input Impedance: 1M Ohm plus/minus 5 percent within 35PF

Max Input Voltage: 600VP-P or 300V (DC plus AC peak)

Horizontal Deflection

Sensitivity: 250mV/DIV. Bandwidth: DC-500KHz(-3dB)

Input Impedance: 1M Ohm plus/minus 10 percent within 35PF.

Time Base

Sweep Frequency: 10Hz-100KHz in 4 ranges and fine control.

Linearity: Less than 5 percent Synchronizing: Internal and external.

Synchronization

Type of sync: INT, EXT

Sync Amplitude: INT: more than 1 DIV on the screen. EXT: more than 2VP-P.

GOS-955: Internal minus and plus; external; line 0-140 degrees for line frequency sweep.

Calibration: 0.1V P-P 1KHz square wave (GOS-

CRT Type: 75mm (GOS-935, 130mm (GOS-955) Power requirements: AC110/240V 50/60Hz 10VA and approx. 20VA (GOS-955).

OTHER GW INSTRUMENTS

AUDIO GENERATOR, GAG-808A at \$189.00 (\$164.00 excl. tax). Sine/square wave, frequency range 10Hz to 1MHz in 15 ranges.

AC MILLIVOLTMETER, GVT-706 at \$169.00 (\$146.95 excl. tax). High sensitivity, RMS scale 1mV-300V in 12 ranges.

RF ATTENTUATORS

GAT-069, 0-69dB in 6 steps, 0-250MHz at \$69.50 (\$64.78 excl. tax).

GAT-872, 0-72dB in 8 steps, 0-250MHz at \$74.50 (\$64.78 excl. tax).

AVAILABLE FROM

NSW EMONA ENTERPRISES P/L (02) 212-4815. RADIO DESPATCH SERVICES (02) 211-0191. DAVID REID ELECTRONICS P/L (02) 29-6601. MARTIN de LAUNAY Newcastle (049) 24-741, W'gong (042) 28-6020.

VIC RADIO PARTS GROUP (03) 329-

SA INTERNATIONAL COMMUNICATION SYSTEMS P/L (08) 47-3688.

WA LETCO TRADING CO. (09) 387-

Lab Notes

Three terminal regulators

Three terminal regulators are remarkably easy to use, as shown in the basic circuits of Figures 8 to 10, which show the connections for making positive, negative and dual regulator circuits respectively; the ICs shown in these examples are 12 V units with current ratings of one amp. Note that a 270n or greater value disc ceramic capacitor should be connected close to the input terminal of the IC and a 10μ or greater electrolytic to the output.

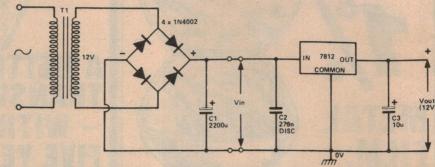


Figure 8. Circuit for the common-or-garden three-terminal fixed voltage positive regulator. Note that C2 and C3 should be mounted as close to the regulator's terminals as is physically possible.

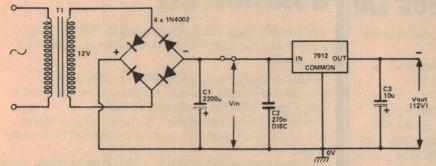


Figure 9. The negative voltage rail counterpart of Figure 8. Don't forget heatsinks.

These capacitors should be connected as close to the device's terminals as is physically possible. They can be quite good RF oscillators if this is not done correctly!

The output voltage of a three terminal regulator is referenced to the 'common' terminal of the IC, which is normally grounded. Most regulator ICs draw quiescent currents of a few mA, which flow to ground via the common terminal. The regulator output voltage can thus be 'jacked up' from the designed value by simply biasing the 'common' terminal with a suitable voltage.

There are two simple ways to do this. The first is shown in Figure 11. The required extra voltage is obtained by passing the IC's quiescent current through a trimpot (RV1). The trimpot is then set to provide the required output

voltage. Quiescent current is typically 7 mA to 11 mA. This technique is ade-

quate in most applications, although

the output voltage obviously shifts slightly with changes in the IC's quiescent current and thus regulation is degraded a little.

The output voltage of a three terminal regulator can be increased by a fixed amount by connecting a suitable value zener in series with the common terminal as shown in Figure 12. Output voltage is then the regulator voltage plus the zener voltage, in this case, 17.6 volts. Note that the quiescent current from the common terminal of the IC may not be sufficient to drive the zener and extra bias current is best provided. Here, R1 serves that purpose.

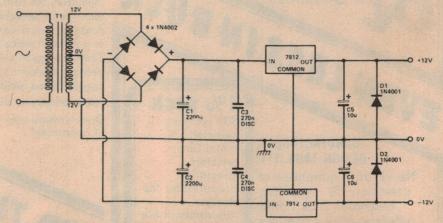


Figure 10. Circuit of a dual positive/negative power supply employing 1 A three-terminal regulators.

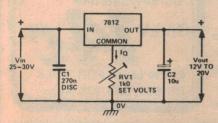


Figure 11. A very simple method of varying the output voltage of a three-terminal regulator. Regulation is slightly affected.


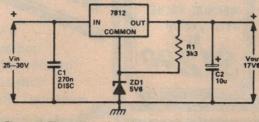


Figure 12. The output voltage can be 'jacked up' by inserting an appropriate zener in series with the regulator's common lead.

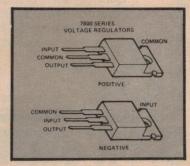



BUT THEY'RE NOT 35¢ EA!

In the past, if you wanted a 1% resistor from us you had to pay 35¢ each!

So most people settled for 5 or 10 percent resistors and circuits were designed to accommodate high variations.

Now look at the price: Dick Smith Electronics now import high stability, precision made 1% tolerance metal film resistors: and they sell for a maximum of 6 cents each (one off!) Why would you still use five or ten percent resistors in your circuits when you can use 1% metal film types for practically no more?

EVEN LESS IN BUL In One-Off

MANUFACTURERS. DESIGN LABS, ETC:

Need large quantities of precision 1% metal film resistors? Dick Smith offers special prices for quantity buyers (and there are even bigger savings for OEM quantities).



IN 100 UP

selected 1% metal film resistors. specially prepared for the design laboratory or the professional hobbyist.

NORMAL VALUE OVER \$15.00

You can buy good, old, garden variety BC548's (or their equivalents) just about anywhere. They're cheap and they are popular.

Trouble is, they're too popular. With so many different manufacturers, standards went out the window. One man's 'prime spec' BC548 is another man's reject.

We decided to change all that. We found a manufacturer who could make transistors as good as any that were on the

And if we were prepared to pay a little extra he would make them even better.

We paid a little extra - and we got a better BC548.

The good news is that you don't pay any extra. We're selling our own branded BC548's (we call them DS548 to distinguish them from the rest) at the same price - perhaps even lower than you're probably paying now.

And just to make things easy, we're even branded the leads so you won't make mistakes.

They're so good we're prepared to back them with a full five year guarantee: as long as they are used within

specifications, we'll replace any of our DS. series transistors that fail within five years

Does anyone else give you that son

of guarantee?

5 year guarantee applies only to

transistors mentioned above

DS 547/548/549 **EVEN LESS FOR BULK** DS 557/558 17¢ each



Lab Notes

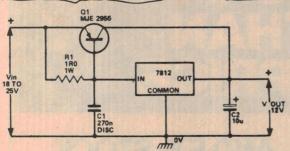


Figure 13. The output current capability of a three-terminal regulator can be boosted by using an external series pass transistor as illustrated. This circuit can deliver up to 5 A.

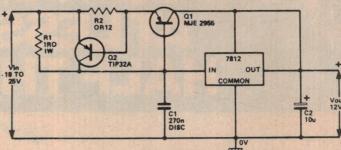


Figure 14. Adding current overload protection to the Figure 13 circuit. It's a wise idea, even though three-terminal regulators generally incorporate thermal shutdown protection.

C.12

More current

The output current capacity of a threeterminal regulator can readily be boosted via an external transistor as shown in Figure 13. This circuit, although it looks familiar, is a little unusual. At low load currents, less than 0.6 volts is developed across R1 and Q1 will not turn on. Thus, all the load current will be supplied by the 7812 regulator. When the load current is greater than about 600 mA, the voltage developed across R1 will be sufficient to turn Q1 on and Q1 will commence delivering current to the load.

This circuit can supply up to 5 A. Note that Q1 will need to be mounted on a substantial heatsink, capable of dissipating 60W.

Protection

Overcurrent or overvoltage protection for three terminal regulators can be provided relatively easily. Overcurrent protection for the Figure 13 circuit is illustrated in Figure 14. All it needs is a transistor and a resistor. When the current through R2 (a 0.12 ohm resistor) exceeds 5 A, the voltage across it will turn on Q2, robbing base current from Q1, thus current limiting the output. The 7812 will go into its switch-on/ switch-off protection mode.

from damage that may result from excessive supply line voltage, a 'preregulator' circuit is added. This is illustrated in Figure 15. You will recognise components Q1, R1, C1 and ZD1 as a simple zener-based series pass regulator (as in Figure 3).

Three terminal regulators can withstand no more than 40 V maximum between the input and common terminals, so this circuit limits the voltage applied to about 27 V. Note that Q1 should be mounted on a heatsink capable of dissipating 25 W.

The LED as a regulator

A low noise regulator can be made using a LED as the reference element. David Tilbrook used this technique in the 4000 moving-coil preamp (ETI-473, Oct '79).

The usual reference element for discrete voltage regulators is a zener. As these devices operate in the reversebiased mode, they are inherently noisy and will put noise on the regulated the circuit here are LED1 and LED2. Series regulators Q13 and Q14 regulate the incoming ±12 V. The potential dividers R21/R23 and R22/R24 divide the voltage present at the output of the regulators and drive transistors Q15 and Q16, and the LEDs. The baseemitter junction in series with each LED will drop 0.6 V; to this is added the LED forward drop of 1.65 V. Thus, whenever the voltage present at the junction of the voltage divider resistors tries to increase above 2.3 V, Q15 and Q16 will increasingly conduct, decreasing drive to the bases of Q13 and Q14 respectively.

Noise on the regulated supply rails is further reduced by the C-R networks, C12/R19 and C13/R20.

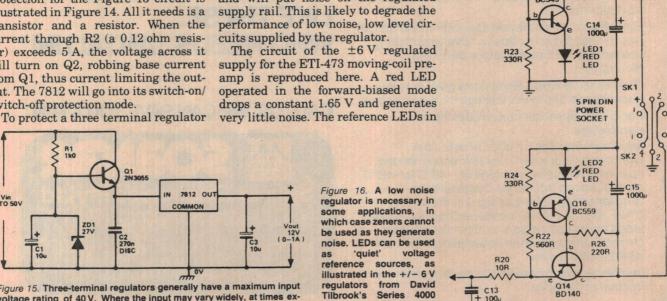


Figure 15. Three-terminal regulators generally have a maximum input voltage rating of 40 V. Where the input may vary widely, at times exceeding the device's limit, this circuit provides protection by using a 'pre-regulator'.

Tilbrook's Series 4000 Moving Preamp Coil project.

NOW! LOW LEAKAGE TANTALUM PERFORMANCE, AT LESS THAN HALF THE PRICE



Why suffer long lead times and pay the extra money for tantalum capacitors when there is a low cost alternative?

Elna, the world renowned capacitor manufacturer has developed an exclusive advanced etching technology for their miniature aluminium electrolytics.

The resulting **RBLL** Series now give you more capacitance and lower leakage than ever before. For critical applications consider these parameters:-

Maximum leakage of .002 CV or O.3u A (whichever is greater) over the recommended operating temperature range of -40°C to +85°C. plus improved frequency characteristics. Smaller space-saving designs in the range 0.1uF to 100uF than normal electrolytics, radial leads and a special seal to minimise leakage current variations when assembling PCB's with insertion machines.

In other words, tantalum-like performance — at a fraction of the price.

WITH ADVANTAGES
LIKE THESE...
WHO NEEDS TANTALUM!

CALL US. WE CAN SAVE YOU A MINT



A member of the A & R Soanar Electronics Group 30 Lexton Road, Box Hill, Vic., 3128. Australia

VICTORIA: 89 0661 QUEENSLAND: 52 5421 N.S.W. 789 6733 WEST. AUST. 381 9522 STH. AUST: 51 6981 TASMANIA: 31 6533



The one-stop Microcomputer Shop for total service to TRS-80* users

*TRS-80 is a registered Trademark of Tandy Radio-Shack

CISA

NOW AVAILABLE CISA DISK PASCAL

Executes up to 60 times faster than DISK BASIC.

HAS FULL DISK I/O FEATURES and many facilities not available on languages costing many hundreds of dollars.

DO NOT CONFUSE WITH CHEAP CASSETTE-BASED 'TINY' PASCALS.

Systems overlays and developments will be available to registered users at a nominal charge.

Includes the fastest and most powerful screen editor we have seen.

Will edit PENCIL, SCRIPSIT and ASCII files.

PASCAL is much easier to manipulate than ASSEMBLY, and is practically as efficient as it compiles into a true-optimized machine-code.

More efficient than currently available BASIC COMPILERS selling for twice the price.

We honestly believe that this Australian written PASCAL to be the fastest, most sophisticated and powerful high-level language available anywhere in the world for the TRS-80 Model I.

RELEASE 1.0 \$99.00

(numbered copies to registered single-users only)

CISA HARDWARE

HEAVY DUTY POWER LINE FILTER
Essential in most domestic situations\$65.00
CISA LIGHT PEN (again in stock)
Includes full documentation and sample prog-
ram\$19.95
CISA DATA DIGITIZER
Use this with HISPED program and you really have
a business system in LEVEL 2. Requires no system
modifications\$57.50
AUTOMATIC TELEPHONE DIALLER
Easy attachment to TRS-80. Requires no
hardware mods. Complete with softwares and
documentation\$57.50
16K UPGRADE KITS
KEYBOARD KIT\$85.00
INTERFACE KIT (yes there is a difference)\$105.00
We fit — \$20.00 plus carriage \$5.00 overnight re-
turn.
DISK DATA SEPARATOR
These are the components that TANDY forgot.
Virtually eliminates all disk I/O errors. Absolutely
essential for 77 track users. We fit\$49.95
(sorry no kits)
GREEN PHOSPHOR TUBES
Not a cheap plastic overlay. We fit a genuine pro-
fessional standard VDU tube with 1/4" armoured
low reflective front panel. (no kits)\$99.00
(fits old and new type Tandy VDU and current Dick
Smith monitor)
CISA RS232 PRINTER-DRIVER
Operate any RS232 or 20MA serial printer with this
Australian made unit. Includes software\$54.75
LOWER CASE MODIFICATION
Get video lower-case for BOTH Scripsit and Elec-
tric Pencil. Fitted\$49.95
VIDEO STABILISER CRYSTAL
Totally removes shimmer and wobble on your
video. Highly recommended for Green Tube.

Kit	\$19.95
Fitted	\$39.95
DUMMY PRINTER	
Plug this into the parallel port of the	e interface and
avoid system lockups if you acc	identally type
LLICT AND DOINT	\$14.05

TRS-80 SOFTWARE

AIR TRAFFIC CONTROLLER L2/16K
Supervise a large area of air-space in real
time\$9.95
SPACE GAMES L2/16K
Five brilliant games in the classic space
series\$14.50
STRATEGY GAMES L2/16K
Four fascinating games to test your judgement
and logic\$14.50
and logic
ADVENTURE SERIES L2/16K
Adventure-1, The Count, Voodoo Castle.
Each\$14.95
Z-CHESS
A fast and exacting opponent. 6 levels of play.
L2/16K\$19.95
Disk 32K\$24.95
DISASSEMBLER IN BASIC L2/16K only
Disassembles ROM and high memory machine
language routines\$9.95
TAPECHECK L2 16K plus
Checks and verifies every millemetre of a cassette
tape. Also useful as cassette I/O diagnostic\$9.95
RS232 DIAGNOSTIC 32K/DISK
Interrogates, tests and reports on EVERY feature
of Tandy RS232 board\$19.95
FLOPPY DOCTOR 32K/DISK
This is the most comprehensive and exacting
series of memory and disk I/O tests we have seen.
From Micro-Clinic, USA\$29.95
SIMUTEK 7 separate packages
These seven packages are excellent value for any
TRS-80 owner\$14.95 ea.

"HISPED" TAPE OPERATION

2K Baud PLUS for the TRS-80*

- Save, verify and load programs up to 4 times faster than normal
 Save, verify and load array data up to 30 times faster than PRINT
- Save, verify and load array data up to 30 times faster than PRINT
 User variable hardcopy formatting (3 output routines work with
- most printers)

 "HISPED" is a machine language program (not a hardware add-
- 2 copies plus a free basic test program supplied on high quality cassette — for level 2, 16K, 32K or 48K.

MAKES STRINGY FLOPPIES REDUNDANT

\$24.95

Available only from Cisa and authorised agents.

MICROPOLIS DRIVES FOR THE TRS-80*

For the enthusiast: 192K bytes per drive.

SINGLE 77 TRACK.........\$699.00

A professional disk drive for the business user:
TWIN 77 TRACK 385K.......\$1499.00

Both complete with heavy-duty case and inbuilt power supply and free dospatch to TRSDOS.

Requires cables — 2 drive \$30, 3 drive \$40, 4 drive \$50.

MIX 'N MATCH with any 35 or 40 track drive.

SHOP WHERE YOU CAN BE SURE OF SERVICE BACK-UP AND YOUR WARRANTIES HONOURED.

SOFTWARE FROM RACET

PHONE OR CALL AND BROWSE. TRADE ENQUIRIES INVITED

Trading Hours: 9am to 6pm Monday-Friday, 9am to 12.30pm Saturday.

Plus many, many more

All the above fine products are available at or can be ordered from:

SOFTWARE-80, Shop 11/198 Moggill Road, Taringa, Brisbane, QLD 4000. Phone: (07) 371-6996.

SOUTH COAST COMPUTING SERVICES, 90 Worrigee Street, Nowra, NSW. 2540, Phone: (044) 24967.

THE BYTE SHOP, Colbee Court, Phillip, ACT, 2606. Phone: (062) 81-5011.

H.S. ELECTRONICS, 104 Charles Street, Launceston, TAS, 7520. Phone: (003) 31-8942.

WACB RADIO CENTRE, 129 Fitzgerald Street, Perth, WA. TANDY ELECTRONCS, Springers Arcade, Bowral, NSW, 2576. Phone: (048) 91-2092.

CISA MICROCOMPUTING PTY. LTD. 159 KENT STREET, SYDNEY, NSW 2000. PHONE: (02) 241-1813.

Orders under \$100 add \$2.00 p and p. Over \$100 post free. For repairs and mods to systems — send by carrier — you pay, we pay return carriage.

Designing potcore inductors

Potcores offer many advantages when you need to use an inductor in a circuit. This article details a simplified design method for two common potcore sizes based on a nomograph.

FERRITE POTCORES are widely used in the construction of small inductors and transformers. However very few amateurs know how to choose a core appropriate to their needs, or how to wind a coil of specific inductance.

This article describes a simple method of designing coils for low frequency applications. The design of coils for high frequency applications, and of transformers, is beyond the scope of this article. Design details given apply only to the Philips 'P' series of pot cores and more particularly to the 18 mm (P18/11) and 26 mm (P26/16) diameter cores which are the most commonly available.

Each core size is available in four different ferrite materials (3H1, 3B7, 3D3, 4C6) to cover the frequency range from audio to about 20 MHz. Additionally each material, in each size, is available with a number of permeabilities to cover different inductance, stability and Q factor requirements.

There are two factors commonly used to classify ferrite cores. These are effective permeability (μe) and A_L factor.

The μ e factor is primarily determined by the permeability of the material used and its cross sectional area, and secondly by the air gap left between the centres of the two core halves. For example an 18 mm 3B7 core without any air gap (type 0 4000) has a μ e of 1750 and a tolerance on inductance of $\pm 25\%$. The use of increasingly larger air gaps in the same core size and material lowers the μ e but increases the stability and reduces the tolerance on inductance.


A second factor in common usage is A_L . This factor gives, in nanohenries, the inductance of ONE turn on the core. The inductance of N turns on the core is

 $L = N^2 A_L \times 10^{-3}$ millihenries

The selection of a core size, a core material, a permeability value, a wire size and the number of turns depends on all the following factors:-

- inductance, stability of inductance
- frequency range
- Q factor
- unbalanced dc coil current
- level of ac coil current

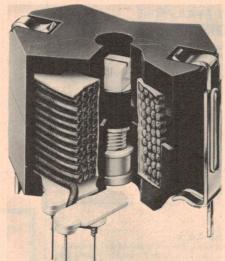Choosing the correct core taking *all* these factors into account is a difficult task indeed. However a large number of



Cutaway view of a potcore showing the winding on the internal bobbin and the inductance adjustor in the centre. The ferrite 'pot' comes in two halves, held together with a clip.

core types are eliminated by first selecting in accordance with frequency range and stability.

Frequency range

Firstly select the core material from Table 1 in accordance with the desired frequency range. To choose between 3H1 and 3B7 it is necessary to consider temperature stability.

If the tuning capacitors associated with the coil have small or varying temperature coefficients, a 3B7 core should be used as they have the lowest temperature coefficient in the range 0° - 70° C. Alternatively, if using polystrene capacitors (temp. coeff. -150 ppm/°C) a 3H1 core having an effective permeability (μ e) around 150 will give excellent temperature compensation for the temperature coefficient of these capacitors.

Inductance stability

Since the inductance of a coil is

TABLE	1
FREQUENCY RANGE	CORE
0.1 — 200 kHz	3B7, 3H1
200 kHz — 2 MHz	3D3
2 MHz — 20 MHz	4C6

proportional to core permeability, the change of effective permeability (μ e) with temperature determines the stability of inductance.

The percentage change of inductance with temperature is linearly proportional to μ e and hence low μ e cores should be used for greatest stability. Stability is therefore obtained at the expense of inductance obtainable with a given core size.

The temperature effect is not large enough to affect any but the most critical of applications and the tolerance on inductance as stated in Tables 2 and 3 will be obtained over the temperature range $+15^{\circ}$ to $+35^{\circ}$ C.

Direct current

A direct current in the winding will change the inductance value of the core and if large enough, could cause saturation. In general, large air gaps, and hence lower permeability (μ e), cores should be used where large dc currents are flowing.


Q factor

The Q of a coil is influenced by different factors at different frequenceis.

At frequencies below 10kHz it is almost completely determined by the dc resistance of the winding. The Q factor of any given coil increases linearly with frequency, and the larger the core, the larger the Q. The highest Q factors are obtainable by using gapless cores of 3H1 or 3B7 material (providing that tolerance and stability are acceptable) eg. 04000 series (P18/11) and 08000 series (P26/16).

Throughout the ultrasonic range core and winding losses affect Q, but Q factors of several hundred may still be obtained by optimum choice of wire and core, such that core and winding losses are equal. For further information, on optimum design, reference should be made to Philips Data Handbook — Components and Materials, Vol. 4.

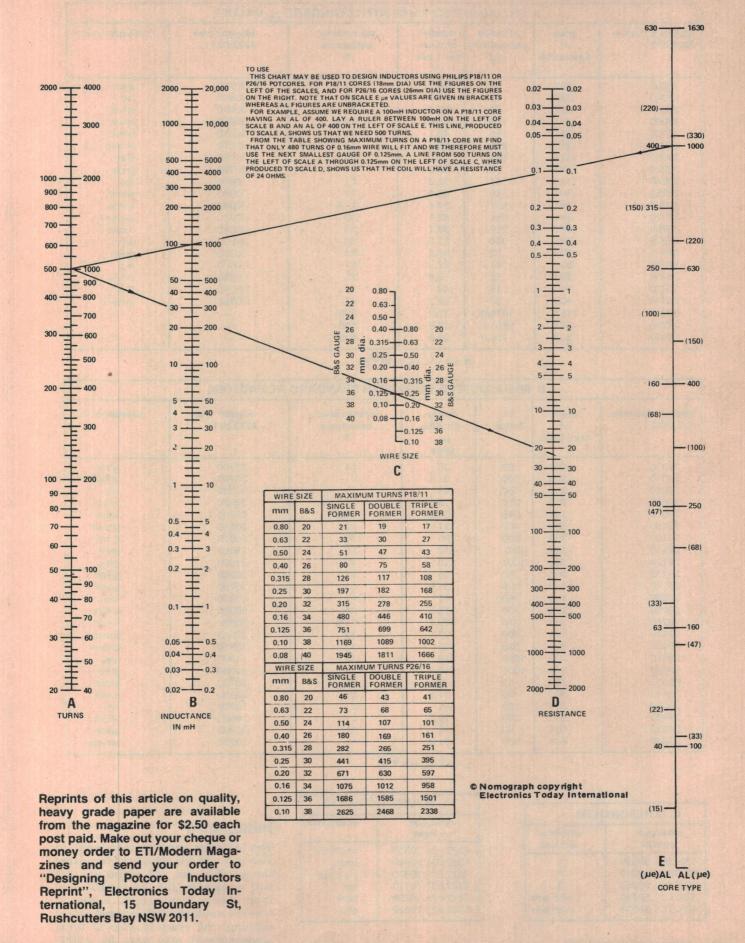At higher ultrasonic and lower radio frequencies, additional factors of dielectric and skin-effect losses and parallel winding capacitance, all affect Q, making exact design difficult. Use of Litz wires, split section formers and small cores with low μ e values will assist.



A. PRE-ADJUSTED PAIRS WITH STANDARD $\mu_{ m g}$ VALUES							
catalogue number 4322.022	grade of ferroxcube	effective permeability $(\mu_{\rm e})$	number of turns for 1 mH	tolerance on inductance %	adjustor type 4322.021	adjustor colour	
28030	387	33	98.2	±1	30780	green	
28040	3B7	47	82.3	±1	30800	red	
28050	3B7	68	68.4	±1	30980	white	
28060	3B7	100	56.4	±1.5	30980	white	
28070	3B7	150	46.1	±2	30810	brown	
28080	3B7	220	38.1	±3	30810	brown	
28090	3B7	330	31.0	±3	31090	grey	
28230	3H1	33	98.2	±1	30780	green	
28240	3H1	47	82.3	±1	30800	red	
28250	3H1	68	68.4	±i	30980	white	
28260	3H1	100	56.4	±1.5	30980	white	
28270	3H1	150	46.1	±2	30810	brown	
28280	3H1	220	38.1	±3	30810	brown	
28290	3H1	330	31.0	±3	31090	grey	
28430	3D3	33	98.2	±1	30780	green	
28440	3D3	47	82.3	±1	30800	red	
28450	3D3	68	68.4	±1	30980	white	
28810	4C6	15	146	±1	30780	green	
28830	4C6	33	98.2	±1	30790	yellow	
08000	3B7	1910.0	12.9	±25		_	
08200	3H1	1910.0	12.9	±25		_	
08400	3D3	730.0	20.8	±25		_	

 $N = \alpha \sqrt{L (L \text{ in } 10^{-3} \text{ H})}$

catalogue number 4322.022	grade of ferroxcube	AL factor	corres- ponding $\mu_{\rm e}$ value	tolerance on inductance %	adjustor type 4322.021	adjustor colou	
29030	3B7	63	20	±1	30780	green	
29040	3B6	100	31.8	±1	30780	green	
29050	3B7	160	51	±1	30800	red	
29060	3B7	250	79.5	±1	30980	white	
29070	3B7	315	100.2	±1.5	30980	white	
29080	3B7	400	127	±2	30810	brown	
29100	3B7	630	200	±3	30810	brown	
29110	3B7	1000	318	±3	31090	grey	
29120	3B7	1600	510	±3	31090	grey	
29230	3H1	63	20	±1	30780	green	
29240	3H1	100	31.8	±1	30780	green	
29280	3H1	160	51	±1	30800	red	
29260	3H1	250	79.5	±1	30980	white	
29270	3H1	315	100.2	±1.5	30980	white	
29280	3H1	400	127	±2	30810	brown	
29300	3H1	630	200	±3	30810	brown	
29310	3H1	1000	318	±3	31090	grey	
29320	3H1	1600	510	±3	31090	grey	
29430	3D3	63	20	±1	30780	green	
29440	3D3	100	31.8	±1	30780	green	
29450	3D3	160	51	±1	30800	red	
29460	3D3	250	79.5	±1	30980	white	
29830	4C6	63	20	±1	30780	green	
29840	4C6	100	31.8	±1	30790	yellow	

 $L = N^2 AL (10^{-9} H)$

C. COILFORMERS				
catalogue	number of sections			
4322.021.30330				
4322.021.30340	2			
4322.021.30350	3			
4322.021.30130	1 with pins			
4302.021,20030	1 with pins			

D. MOUNTIN	G PARTS
catalogue number	description
4322.021.30550 4322.021.30660 4322.021.30470 4322.021.30710 4322.021.30720 4302.021.20020	container spring tag plate nut bush clip

Inductance

The tolerance given on inductance, in Tables 2 and 3 is obtained when using the specified core, and a wire size that will completely fill the former close layer wound. Due to slight changes in wire diameter and different methods of winding, the exact number of turns accommodated may vary by $\pm 10\%$.

catalogue number 4322.022	grade of ferroxcube	effective permeability (μ _e)	number of turns ∝	tolerance on inductance %	adjustor type number 4322,021	adjustor colour
24030	387	33	120	±1	30760	green
24040	387	47	100.5	±1	30770	red
24050	387	68	83.6	±1	30960	yellow
24060	387	100	68.9	±1.5	30970	white
24070	387	150	56.3	±2	30730	brown
24080	387	220	46.5	±3	31080	grey
24230	3H1	33	120	±1	30760	green
24240	3H1	100.5	100.5	±1	30770	red
24250	3H1	68	83.6	±1	30960	yellow
24260	3H1	100	68.9	±1.5	30970	white
24270	3H1	150	56.3	±2	30730	brown
24280	3H1	220	46.5	±3	31080	grey
24430	3D3	33	120	±1	30760	green
24440	3D3	47	100.5	±1	30770	red
24450	3D3	68	83.6	±3	30960	yellow
24810	4C6	15	178	±1	30760	green
24820	4C6	22	147	±1	30770	red
24830	4C6	33	120	±1	30970	white
04000	3B7	1750	16.5	±25		11 45 14
04200	3H1	1750	16.5	±25		A TOTAL PROPERTY OF
04000	3D3	705	25.9	±25		

 $N = \alpha \sqrt{L (Lin 10^{-3} H)}$

Want Sales	B. PRE-ADJUSTED PAIRS WITH STANDARD AL FACTORS								
catalogue number 4322.022	grade of ferroxcube	AL factor	corres- ponding $\mu_{\rm e}$ value	tolerance on inductance	adjustor type 4322.021	`adjustor colour			
25030	3B7	63	30	±1	30760	green			
25040	3B7	100	47.5	±1	30770	red			
25050	3B7	160	76	±1	30960	yellow			
25050	3B7	250	119	±1.5	30970	white			
25070	3B7	315	149	±2	30730	brown			
25080	3B7	400	190	±2	31080	grey			
25100	3B7	630	298	±3	31080	grey			
25230	3H1	63	30	±1	30760	green			
25240	3H1	100	47.5	±1	30770	red			
25250	3H1	160	76	±1	30960	yellow			
25260	3H1	250	119	±1.5	30970	white			
25270	3H1	315	149	±2	30730	brown			
25280	3H1	400	190	±2	31080	grey			
25300	3H1	630	298	±3	31080	grey			
25420	3D3	40	19.0	±1	30760	green			
25430	3D3	63	30	±1	30760	green			
25440	3D3	100	47.5	±1	30770	red			
25450	3D3	160	76	±1	30960	yellow			
25810	4C6	25	11.9	±1	30760	green			
25820	4C6	40	19.0	±1	30770	red			
25830	4C6	63	30	±1	30970	white			

Hence it is safer, when winding experimental coils, to only try and fit 90% of the turns indicated in the maximum number of turns tables.

If the former is only partly filled, errors up to 4% may occur with the lower μe cores. However the use of an adjustor will allow a +10% adjustment range which is generally sufficient to cope with tolerances found in practical

desired to widen the adjustable range, core of low μe value.

C. COIL FOI	C. COIL FORMERS						
catalogue number	number of sections						
4322.02130270 4322.021.30280	1 2						
4322.021.30280	3						
4322.021.30090	1 with pins						
4302.021.20010	1 with pins						

When optimum stability is required at the possible expense of stability, an the type of adjustor that matches a adjustor indicated for a potcore with a certain core should be used. If it is high μe value may be used with a pot-

C. MOUNTING PARTS							
catalogue number	description						
4322.021.30530 4322.021.30640 4322.021.30450 4322.021.30710 4322.021.30720 4302.021.20000	container spring tag plate nut bush clip						

Design data for this article has been derived from the Philips publication "Ferroxcube Potcores", 1972. Nomograph copyright — Electronics Today International. This article was originally published in the October 1974 issue of ETI, Australian edition.

SIGNETICS AIM FLUKE-1 GRAPHICS — ADAPTIVE — ALPHA — LITRONICS BISHOP ADCOLA — WELLER SYNTECH JTILUX

289 LATROBE ST. MELBOURNE. 3000 PHONE (03) 602-3282, 602-3836. TELEX AA37758 LSTRON. YES! WE ACCEPT BANKCARD. All prices valid month of issue. Heavy items sent Comet freight forward. Minimum post \$3.00.

ADDITIONAL FREIGHT REQUIRED FOR HEAVY ITEMS.

OUR LOWEST PRICES EVER! RUSH FOR THESE FULL SPEC. PRIME I.C's WHILE STOCKS LAST

2716. 450ns Single 5v Supply	\$11.95 ea.	FLOPPY DISC CONTROLLERS
2716. 200ns Single 5v Supply	\$19.50 ea.	FD 1771\$37.00 ea.
2114. 450ns	\$2.95 ea.	FD 1791\$62.00 ea.
2114. 300ns	\$3.90 ea.	FD 1793\$62.00 ea.
2708. 450ns	\$6.40 ea.	8 BIT MPU's
4116. 200ns	\$4.90 ea	
		6802 \$11.80 ea. 6808 \$10.50 ea.
		6809 \$46.77 ea.
Z80 C.P.U	\$10.81 ea.	6821\$5.10 ea.
Z80A C.P.U.	\$11.14 ea.	6840
Z80 C.T.C	\$11.44 ea.	6845\$38.94 ea.
Z80 P.I.O	\$6.65 ea.	6847\$28.00 ea.
Z80A P.I.O	\$8.57 ea.	6850\$4.40 ea.
Z80 SIO/O	\$38.67 ea.	6852\$5.50 ea.
Z80A SIO/0	\$49.90 ea.	RISTON 3000 COATED FIBREGLASS BOARD
Z80 SIO/1	\$38.67 ea.	SINGLE SIDED
Z80A SIO/1	\$49.90 ea	6" x 3"\$1.60 ea.
Z80 SIO/2	\$38.67 ea	6" x 6"\$2.30 ea.
Z80A SIO/2	\$49.90 ea	9" x 6"\$3.35 ea.
Z80 SIO/9	\$38.67.00	12" x 12"\$7.95 ea.
Z80A SIO/9	\$40.00.02	DOUBLE SIDED
		6" x 3"\$2.30 ea.
		6" x 6"\$3.30 ea.
2732	\$66.00 ea.	9" x 6"\$4.10 ea.
MB 8414 (2114 CMOS 250ns)	\$21.00 ea.	12" x 12"\$9.45 ea.
65 x 08 1k x 1 CMOS	\$9.00 ea.	Full range of chemicals available.

ALL PRICES PLUS 15 PERCENT SALES TAX APPLICABLE.



JUST WRAP Tool *50 ft. ea.: blue, white, red. yellow wire *JUST WRAP Tool *Unwrapping Tool

JWK-6 \$32.15



For all the details on Hobby-Blox call or write for your free catalogue



V-151 15 MHz Single Trace

V-152 15 MHz Dual Trace V-301 30 MHz Single Trace

V-302 30 MHz Dual Trace V-550B 50 MHz Dual Trace, **Dual Time Base**

Call For

Special Intro Price Offer

NEW!



ME-501A

From \$69.00

Prices plus 15 percent sales tax.

ME-501B Same as ME-501A plus continuity checker.

SPECIAL PRICES ON PROJECT BOXES

UB1 \$1.69 plus 25c tax 150 x 90 x 50mm

UB2 \$2.56 plus 38c tax 186 x 113 x 60mm

UB3 \$1.35 plus 21c tax 130 x 68 x 41mm

UB5 81c plus 12c tax 83 x 54 x 28mm

Plus 15 percent tax.





AUSTRALIAN MADE

WELLER SP25D MARKSMAN Mains voltage constant heat 25 watt with

TAX EXEMPT

5/32 tip (lightweight 185 grams).

most imported irons. Fully

guaranteed. \$9.75 ea.

SPECIAL FOR THIS MONTH AT ONLY \$54.50 ea. TAX EXEMPT WELLER WTCPN SERIES

LOW VOLTAGE, TEMPERATURE CONTROLLED SOLDERING STATION

A transformer powered soldering station, complete with a low voltage, temperature controlled soldering pencil. The special Weller "closed loop" method of controlling maximum tip temperature is employed, thereby protecting temperature sensitive components while the grounded tip protects voltage and current sensitive components. The soldering pencil features a stainless steel heater construction, a non-burning silicon rubber election of iron plated tips in sizes from .8 mm diameter to 6 mm diameter with a choice of tip temperature of 600°F/315°C, 700°F/370°C and 800°F/430°C.

A redesigned transformer case features an impact-resistant noryl for durability and protection against accidental damage, a quick connect/disconnect plug for the soldering iron, extra large wiping sponge, tip tray to store extra tips, plus an improved off-on switch with a long-life neon indicator light, a non-heat sinking soldering pencil holder and a 2 m flexible 3-wire power cord.

The soldering iron is normally provided with a PTA7-1.6 mm screwdriver 700°F/370°C tip.

SPECIFICATIONS

Power Unit ● Power input 240 Volts 50 Hz 60 Watts Int. ● Transformer Output Voltage — 24 Volts (Full Load)
● Power Unit Size — 113mm x 187.3mm x 92mm ● 2 Metres, 3 Wire Power Cord.

Soldering Pencil ● Soldering Pencil Wattage — 48 Watts ● Tip Voltage *To Ground .01 Volts P-P ● Pencil Weight — 50 gram (W/O Cord) ● Recovery Time (From 100°F Drop) W/PTA7 Tip = 11 Sec.





\$2010 PVC weatherproof re-entrant horn/speaker. Very attractive "off white" colour. 8 ohm 5 Watt RMS. Ideal P.A. use. Individually boxed.

SPECIAL PRICE \$5.95 ea. exempt \$6.84 inc. tax

Ellistronics are direct distributors for Weller, Hitachi and Trio. For quantity discounts etc. ask for Trade



Prices plus 15 percent sales tax.

TOP QUALITY LOW COST **TRANSFORMERS**

R-2150-2851

Primary: 240V AC Secondary Voltage: 12.6 volts CT. Secondary Current: 150mA. Termination: Flying leads.

\$2.50 ea. 10 up \$2.10 ea. R-2155

Primary: 240V AC. Tapped Secondary Voltages: 6.3, 7.5, 8.5

9.5, 12.6, 15.

Secondary Current: 1 amp.

Termination: Solder lugs on transformer. \$3.90 ea. 10 up \$3.51 ea.

R-6672

Primary: 240V AC.

Tapped Secondary Voltages: 15, 17.5, 20, 24, 27.5, 30.

Secondary Current: 1 amp. Termination: Solder lugs \$6.19 ea. 10 up \$4.95 ea.

\$2000 8" (200mm) wide range general purpose. Includes transformer, mounting holes for P.A. and background use. Very smooth over-all response 45 Hz-12 KHz. Fitted to a 1.9 cubic fit vented enclosure they sound unbelievable.

8 0hm 8 wat RMS 5.6 oz magnet.
\$6.00 TRADE, \$6.95 Inc. tax



EXTRA SPECIAL

2N 3055 TRANSISTORS FULL SPEC. MOTOROLA 55c ea. plus 15c tax MJ 2955 TRANSISTORS 65c ea. plus 18c tax

TEXAS INSTRUMENTS CALCULATORS



Ti 25	\$19.04
Ti 30 SP	\$22.85
Ti 50	\$38.09
Ti 55	
Ti 58C	
Ti 59	
PC-100C	
(Printer/Plotter for Ti 5	
59)	

Speak and Spell	\$77.78
Dataman	\$24.26
Little Professor	\$17.62
AC9131 AC Adaptor/C	harger for
Ti 58C/59	

Calculators plus 15 percent sales tax if applicable. Full range of calculators and accessories in stock.

DIRECT IMPORT PANEL **METERS** AT LOW, LOW PRICES



MU-65 100uA - 1400 ohms Dimensions: Overall - 100mm(W) x

- 100mm(W) x 50mm(H) Mounting: Hole required — 63mm Bolts centres — 80mm(W) x 64mm(H) Nuts and washers provided

\$10.18 ea. plus \$1.52 tax **MU-45**



O-1MA-120 ohms O-50UA-1400 ohms O-5ADC-3 Shunt 0-30VDC-100 ohms \$6.45 ea.

plus 97c tax **MU-45 VU** METER



VU (OdB equals 1mW into 600 ohms) \$7.35 ea.

LEY

plus \$1.11 tax **MU-45 DIMENSIONS**

Overall — 58mm(W) x 52mm(H)
Scale — 58mm(W) x 31mm(H)
Hole required — 44mm
Bolt centres — 38mm(W) x 38mm(H)
Nuts and washers provided
10 or more less 10 percent

Ideas for Experimenters

These pages are intended primarily as a source of ideas. As far as reasonably possible all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory. Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details.


LED chaser

with light bulbs.

This simple circuit for a LED chaser comes from M. Spokes of Glen Iris, Vic. The circuit uses a 555 oscillator driving a 4017B counter. RV1 is used to vary the rate of the chaser by varying the oscillation frequency of the 555. The

output of the 4017 drives ten LEDs, but with a suitable interface it could be used

+9VDC

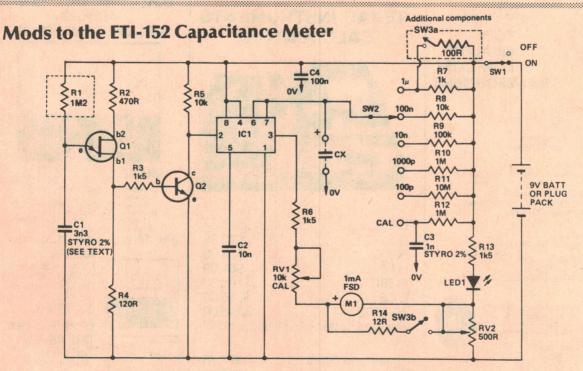

This project appeared in the February 1980 issue and was part of a short series of look-alike test instruments. Several readers pointed out that the unit did not work properly in the $1\mu/x10$ mode (i.e: 10μ full scale) as the integration time was not long enough. This problem is cured by a simple modification.

Firstly, SW3 should be changed to a double-pole, single-throw (DPST) type. Secondly, change R1 to 1M2, as shown in the new circuit diagram here. Add a 100 ohm resistor, switched across R7 by the other pole of SW3, as shown in the circuit diagram.

That should correct the problem.

Apart from that, some constructors found that RV2 (zero set control) was very close to one end of its range and difficult to adjust. This is probably brought about by LED1 having a fairly high voltage drop. To cure the problem, reduce R13 to 820 or 680 ohms.



Fantastic but true. We have purchased large stocks of the famous SANYO brand RD.5008 Stereo Cassette deck – below manufacturer's cost! This means that we can pass genuine savings on a quality cassette deck on to you. The manufacturer's loss is your gain – YOU REAP THE BENEFIT!!!

Be early – Stocks limited. Whilst we have purchased a large quantity, we expect demand to be brisk. So it you want to purchase one of these decks we suggest that you call in without delay. If, for some reason you cannot call in immediately please, please 'phone your nearest store to check the stock situation. We hate to tell customers that we have sold out after they have made a long journey only to be disappointed...

hile you're in one of our stores

Have a look around. Play with the fascinating 'gizmos' that we sell. Not only do we sell cassette decks but many interesting items including hi-fi equipment & accessories, CB & Amateur radio equipment, home computers & peripherals, home & car alarms, car accessories & hi-fi, computer games, antennas, components etc etc. In fact, we have almost everything for the electronic enthusiast - from kits to computers!

- Modern front-loading design. This allows you to stack your hi-fi as well as reduce the likelihood of dust entering the the mechanism.
- Oil-damped cassette door. This causes the lid to open & close silently without 'slamming'.
- Other features: Separate right/left level controls plus 3 digit re-settable tape counter.

terms available to approved applicants

Electronics



SEE OUR OTHER ADS FOR **FULL ADDRESS DETAILS**

THE FINEST SOPTWARE OF ITS KIND

Electronics Corporation

Reconditioned 160 Malibu New 165 Malibu with stand

\$3640 Apple Version \$3360

Complete / Manual Only K Wordstar. \$445 \$45 Mail Merge for Wordstar \$145 \$30 Wordstar with Mail Herge \$575 \$75 \$40 Data Star -\$30 word Master -SuperSort 1 -\$30 Supersort 2 -

* Manual only purchases fully credited to later software.

NASHUA FINEST QUALITY DISKS PACKED 10 PER LIBRARY BOX 54" \$45 per box] specify Soft or no of sectors \$50 per box

ALL PRICES INCLUDE SALES TAX WHERE APPLICABLE

OSBORNE & ASSOCIATES, INC.

Osbovne Software Veguires CBasic 2

OSBORNE SOFTWARE

General Ledger \$50 AIR, AIP ____ \$60] Manuals not included

Manuals - \$30 each CBasic 2 - \$100 with Hamual

SEND FOR OUR LATEST CATALOGUE Including tax Svee prices, new and used specials

archives

ARCHNES BUSINESS COMPUTED

We can supply a complete Hardware/Software package customized to your individual requirements.

MOST ITEMS IN STOCK

WE SELL MOST CP/M SOFTWARE User Group -44 Vol. \$12 ea.

THE ULTIMATE PRINT THE NEC SPINWRITER QUALITY FOR WORD PROCESSING AND BUSINESS APPLICATIONS 55 C.p.s. Bidivectional printing and paper motion Proportional spacing, Quick change print thimbles & riddons High Res. plotting and graphing R/C 5100 Version including 5100 I/o Board



notice and Subject to change without Prices FOB

N

Buy Wordstar at same time \$ Save \$ 100 - \$3,378


Ideas for Experimenters

'Endless' LED chaser

This unusual LED or lamp chaser employs a 'chain' of inverter stages connected in a ring. The portion of the circuit inside the dotted box is repeated as many times as you wish, the collector of the transistor in each stage going to the input capacitor of the following stage and so on. Finally, the circuit arrives at SW1 and SW2 and the stage involving IC1b, Q2 etc.

According to Greg Thamm of Burra North, S.A., who submitted it, the whole thing works like this: after applying power, close SW2 until all the LEDs go out. Then, open SW2 and momentarily close SW1 (a pushbutton could be used here). This starts the chaser as the collector of the transistor connected to C2 will

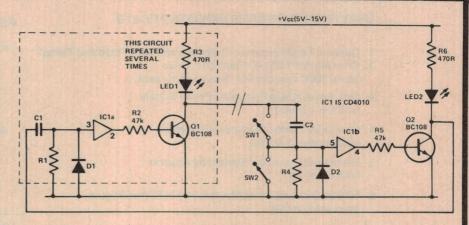
be at supply potential, Q2 will turn on and LED2 will light when you close SW1. However, C2 will charge via the LED and dropping resistor of the preceding stage until the input to IC1b goes below its



lower threshold. When it does, the output of IC1b will go low and Q2 will turn off. Then, C1 will charge via R6 and LED2, but the initial pulse will turn Q1 on via IC1a and LED1 will light. When C1 charges such that the input of IC1a goes below its lower threshold, Q1 will turn off, triggering the next inverter stage in the chain and so on, right

around the chain. The input R-C for each stage (C1, R1 etc) determines the 'on' time. The diodes (D1-D2, etc) discharge C1-C2 etc when the preceding stage transistor turns on.

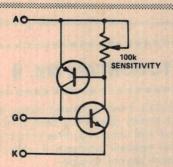By using high dissipation transistors and 12 V lamps instead of LEDs, the circuit is suitable for such applications as Christmas tree light displays, etc.



Transistors mimic SCR

This circuit, from J. da Silva of Croydon, NSW, simulates an SCR. The 'sensitivity' trimpot is useful to set the triggering voltage and prevents the circuit sefl-triggering from the leakage current of the transistors.


By reversing the polarity of the transistors the circuit becomes a PUT

(programmable unijunction transistor) and by replacing the lower transistor with a phototransistor the circuit can be light activated. Any complementary silicon transistor pairs are suitable for this circuit. (Ed. Note: whilst we are aware that this circuit is not really new or original, it is not one that is widely known amongst hobbyists).

A "no hands" organ

This simple organ is really an electronic music box. An idea from Shane Waye of Victor Harbour, SA, the circuit steps through a number of preset notes (up to 10) to play a simple tune — music box fashion.

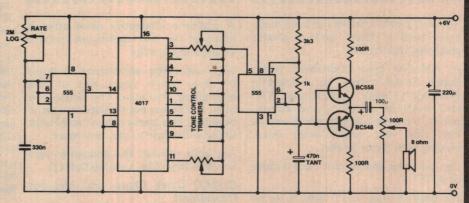A 555, used as a low frequency oscillator, clocks the 4017 — a decade divider with 10 decoded outputs. The outputs of the 4017 drive trimpots connected to a second 555 arranged as an audio oscillator. Each trimpot sets the frequency or pitch of the audio oscillator. As each output of the 4017 goes high in turn, the audio oscillator changes pitch — and you can play a tune. The output



of the audio oscillator is fed to a complementary pair of transistors which drive a speaker for the audio output.

To preset the trimpots, disable the

555 clock and jumper the end of each trimpot connected to the 4017 to the positive supply in turn, then adjust for the required note.

INTRODUCING THE \$49.00 DISC DRIVE!

ONLY FROM COMPUTER IMPORTS PTY. LTD.	RETAIL	OUR PACKAGE
1. Genuine Tandy Expansion Interface with 32K Fitted and Tested	PRICE	PRICE*
One Only MP1 B51 40 Track Disc Drive (up to 200K capacity DD. 5ms track-to-track)	\$919 \$406	\$919 \$49
Dick Smith X3234 Regulated Power Supply (will run 2 drives)	\$60	\$60
Four Drive Cable to Expansion Interface (add another 3 drives)	\$69.95	\$69.95
5. Newdos 40 Operating System by Apparat (all the extras)	\$110	\$110
6. TRS 80 Disk and Other Mysteries by H.C. Pennington (best seller in US)	\$30	\$30
	\$1594.95	\$1237.95
	Tax Paid	Tax Paid

- * 90 DAY WARRANTY
- * OFFER EXPIRES JANUARY 6TH 1981 AND MAY NEVER BE REPEATED!
- FINANCE ARRANGED FOR APPROVED CUSTOMERS THROUGH CAGA FINANCE, NOARLUNGA CENTRE.
- BANKCARD WELCOME.
- * OBVIOUSLY WE WILL BE RUSHED OFF OUR FEET WITH THIS ONE SO RUSH OFF YOUR ORDER TODAY

COMPUTER IMPORTS PTY. LTD.

P.O. BOX 7, PORT ADELAIDE, S.A., 5015

PHONE (08) 26 88065

PETER HARTLEY SOFTWARE Box 132, P.O. EASTWOOD, SOUTH AUSTRALIA 5063

SUPER SNAKE

The ever popular Snake has been made even harder, faster and a greater challenge than before.

A real-time graphics-oriented game, Super Snake offers an everlasting challenge to every Level II user. With two levels of difficulty and continuously increasing speeds, you'll always have fun, but you'll never relax, playing with Super Snake.

Can you beat the current record score of 4775?

It's possible, but you'll need a lot of practice!!!

Requires 16K, Level II.

\$9.50 incl. p&p

DALEK CHASE

A real-time interactive game offering hours of fun and excitement to both young and old alike.

With automatic adjustment to levels of play, you'll never tire of this enthralling challenge. The better you play, the harder each subsequent game becomes. Play badly enough and Dalek Chase will refuse to play any more.

Are your reflexes fast enough to save Dr. Who from the pursuing Daleks?

CLOAD Dalek Chase, and find out for yourself.

Requires 16K, Level II.

\$9.50 incl. p&p

TOUCHTYPE MK. II

Australia's most successful computerbased typing course has been further refined and improved. Now consisting of four separate programs, Touchtype can teach anyone to type.

Touchtype explains correct keyboard usage in a carefully integrated series of 22 lessons. Practice exercises are set, and marked on the screen while you watch. These exercises not only reinforce the particular skills taught in the associated lesson, but also introduce a structured revision of earlier parts of the course.

Speed and accuracy tests are used to give a realistic assessment of the student's progress, and the computer will advance a student only on the successful completion of the current learning module.

Requires 16K Level II.

\$19.95 incl. p&p

**Purchasers of the original Touchtype can upgrade to the new version by sending us their original cassatte and only \$5.00.

Shoparound

THIS PAGE is to assist readers in the continual search for components, kits and printed circuit boards for ETI projects. If you are looking for a particular component or project - check with our advertisers if it is not mentioned here. Also, for a list of suppliers who stock the ETI projects published over the last few years, our "Kits for Projects" page may generally be found on the page immediately before the DREGS page (inside the back cover).

This month's bag of projects are a little unusual and some special components are required. However, we have gone to some trouble to ensure that these components will be available by the time the magazine goes on sale. In fact, we understand they're ready as this is written, a few weeks before publication. Nevertheless, we've got our fingers crossed . . .

The pH meter

The electronics for this project employ the Intersil ICL7106 and LAD204 31/2- digit liquid crystal display. The ICL7106 is distributed in Australia by R & D Electronics. They have a 'kit', known as the RIK6017, containing the 7106 and an LAD204 31/2-digit LCD display which they advise will be available to readers for the special price of \$28.80 plus 15% sales tax. (Normal price is \$35.90 plus tax). This totals \$33.12, about 25% below normal price. Readers ordering by mail should include \$2.50 post and handling costs. R & D Electronics are located at:

Sydney: 133 Alexander St CROWS NEST 2065 Ph: (02)439-5488

Melbourne: 257 Burwood Highway BURWOOD 3125. Ph: (03)288-3232

Alternatively, many kit and component suppliers stock the Intersil Digital Panel Meter Evaluation Kit employing these ICs. It is known as the ICL7106EV kit and sells at prices varying between about \$35 and \$45.

If your usual kit or component supplier is not stocking the Ionode pH probes as mentioned in the article (pages 24, 25), they may be obtained from Starcross Scientific, P.O. Box 151 Frenchs Forest, NSW 2086. Available mail order, the G101NFE general purpose pH probes are supplied with a plastic protector cap, a wetting cap for storage and a comprehensive booklet plus two 200 ml containers of buffer solution, one of pH 6.88, the other pH 4.00. The probe itself is a "non-flow" sealed type and has a BNC plug fitted. It will have quite a long life without needing replenishment of the internal electrolyte. Total cost for the package is \$45.70, which includes sales tax and delivery. If you need any accessories, such as 100 ml plastic beakers, wash bottles etc., Starcross Scientific can assist. They also have special spear point electrodes for soil analysis.

At the time of going to press, two firms indicated they would be supplying complete kits for this project: All Electronic Components of 118 Lonsdale St. Melbourne and Electronic Agencies of 115 Parramatta Rd, Concord NSW.



Collet knobs will fit where conventional grubscrew knobs will not. They are secured to a control shaft by a split sleeve and nut arrangement. These

trols Pty Ltd, headquartered at 55 Fairford Rd, Padstow NSW. They are available in a wide range of colours and sizes and can be fitted with a collett knobs, distributed here by Associated Convariety of skirts: pointers, numbered, flange types.

Most components suppliers will be stocking pc boards and Scotchcal panels for this project: Radio Despatch Service, Electronics and Electronic Agencies in Sydney; Rod Irving Electronics, Ellistronics and All Electronic Components in Melbourne. Possibly Dick Smith stores also. The Ionode pH probes will be available we understand from Radio Despatch Service, Electronic Agencies and D.R. Electronics in Sydney.

The collet knobs we used on our prototype are distributed by Associated Controls Pty Ltd of 55 Fairford Rd Padstow NSW, and 214-224 Wellington Rd, Mulgrave Vic.

ETI-1500 metal detector

This project requires a prewound and aligned search head. This is made by Altek Instruments of the UK and All Electronic Components of Melbourne are acting as their agents in Australia. In addition, AEC will be supplying the handles and case we used to construct our prototype. All these special items are available to other suppliers at wholesale rates from All Electronic Components, as well as complete kits.

At the time of going to press we understand that, apart from All Electronic Components, Electronic Agencies in Sydney will be carrying complete kits. for this project. Printed circuit boards, Scotchcal panels etc should be available through most suppliers we have mentioned previously.

Series 3000 compact stereo

Last month's feature project is being stocked as a complete kit by All Elec-Components, Rod Irving Electronics and Tasman Electronics in Melbourne and Radio Despatch Service in Sydney (surprise, surprise!).

ETI-475 AM tuner

Featured in our September issue, this tuner is being stocked as a complete kit by All Electronic Components in Melbourne and Radio Despatch Service in Sydney. If you've gathered all the bits together for yourself, chances are you're still seeking potcores, right? Well, both these firms can supply potcores for this

Project price estimates

This information is published as a guide and a variety of factors may affect the actual price of a project, whether obtained as separate components, or as a kit.

ETI-572 pH Meter

\$80 - \$90

(inc. pH probe)

ETI-1500 Metal Detector \$200

ETI-597 Emergency Lighting Unit

\$18 - 24

(less batteries)



MENSA COMPUTERS PTYLTO.

Suite 3, 454 St. Kilda Road, Melbourne, 3004. Telephone: (03) 26-5683, 26-6150.

FINDEX — The Real Computer



THE WORLD'S FIRST PORTABLE MICROCOMPUTER Battery or mains operated

RAM 48K to 2 megabytes, bubble memory to 2MB, gas plasma display, optional audio, printer, mass storage mini floppys to 800K bytes, hard disk to 195 megabytes, acoustic coupler, S-100 bus, battery optional, CPU with real time clock. For dynamic businessmen on the move. Ideal for real estate agents, insurance brokers and accountants.

SUPERBRAIN™ SERIES

BUSINESS SYSTEMS

Priced competitively from as low as \$45.00 p.w. lease cost including sales tax and software.



Powerful, multi-purpose microcomputer systems.

TYPICAL APPLICATIONS

Debtors ledger and statements, creditors ledger and remittances, general ledger and trial balance, order entry/invoicing, sales analysis, payroll/wages, enquiry, word processing, mailing, record keeping, ledger card, doctors office, real estate, agency accounting, hotel/motel accounting, branch office accounting.

Priced from \$4995

OPAL 1000

The OPAL 1000 is an 8 slot S-100 system conforming to the new IEEE standards. A Delta Products Z80a 4 MHz CPU card, with 2 RS232c serial and 3x8 bit parallel ports, is used in conjunction with the Delta Products Disk Controller. Memory is provided by a 4MHz 64k dynamic RAM Board by Measurement Systems and Control. The memory board is fully bank selectable and is designed for upgrading to a multi-user system. Disk drives are 2x8" Shugart SA801R running at double density (480k/drive) and fitted with our exclusive Disk Saver which prolongs the life of the drives and floppy disks by turning off the AC power to the drives 14 seconds after the last drive select and thus reduces routine maintenance. The Disk Saver also reduces the risk of data loss due to power failures. The software is CP/M version 2.2 with Delta Product's utilities which include DTEST (for testing drives and floppy disks) and M2 (a comphrehensive memory test program). The Delta PROM monitor enables fault finding to be carried out independently) of the Disk Drives. The system is mounted in an attractive pressed Aluminium housing with a cast front panel fitted with reset button and key operated on/off switch.

Dealers for Opal in Victoria.
Sole Distributor for Findex, Victoria and NSW.

SUPPLIERS FOR NDKS S-4000

MATHEMATICS

$$F(w) = aT \frac{\sin wT/2}{wT/2} e^{-jwT/2}$$

$$e_{RMB}^2 = 4KTR(f_2 - f_1)$$

$$L_i = 10\log \frac{1}{80} \times S_{\bullet} (dB)$$

$$F(w) = aT \frac{\sin wT/2}{wT/2} e^{-jwT/2}$$

$$e_{\text{mes}}^2 = 4KTR(f_2 - f_1)$$

$$L_i = 10\log \frac{1}{80} \times S_{\bullet} (dB)$$

$$F(w) = aT \frac{\sin wT/2}{wT/2} e^{-JwT/2}$$

$$e_{RM}^2 = 4KTR(f_2 - f_1)$$

$$L_i = 10\log \frac{1}{80} \times S_a \text{ (dB)}$$

$$F(w) = aT \frac{\sin wT/2}{wT/2} e^{-JWT/2}$$

$$e^{2} = 4KTR(f_2 - f_1)$$


$$L_i = 10\log \frac{1}{80} \times S_{\bullet} (dB)$$

C10 DATA CASSETTES \$1.65 each!

mmmmmmmm

in packs of 20

save around 20%

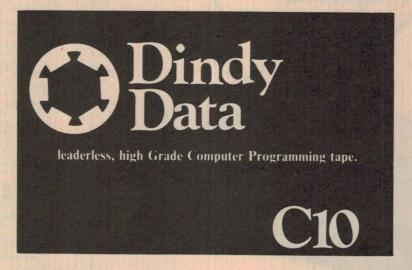

The majority of home and hobby computers employ cassette tapes for mass storage, the most common, and useful, type being the C10 cassette. Dindy Marketing has arranged to make their Dindy Data C10 cassettes available to ETI readers in packs of 20 at a special price — you can save around 20% on the price compared to similar tapes.

Dindy Data Cassettes are manufactured expressly for use in home computers. The cassettes feature 'instant-start', so no data or recording time is lost while waiting for leader tape to pass as in other cassettes. The precision housing and mechanism feature a clamped spring pressure pad to ensure good tape to head contact with no loss of data. The Dindy Data Cassette tape is certified for use on home computers and features a consistent durable coating on a tensilized base ensuring no dropouts or data loss with stretch.

Specification:

Housing — Hi Impact Hi Heat polystyrene shell, five screw type, acetal drive hubs and guide rollers, lubricated stainless steel pins, clamped phosphor bronze spring pressure pad, beryllium shield and graphite polyester slip sheets.

Tape: 12 micron tensilized base. High density acicular gamma ferric oxide coating dispersed in poly-urethane binder. These tapes come with a five year unconditional guarantee.

Money back guarantee: Dindy offer to refund the purchase price in full if you are not completely satisfied and provided you return the goods within 14 days of receipt.

NOTE: This offer is made by Dindy Marketing (Aust) Pty Ltd and ETI is acting as a clearing house only. Cheques or money orders should be made payable to 'DINDY C10 CASSETTE OFFER' and sent, together with the coupon (or a photostat or clear, handwritten copy of same), to C10 Cassette Offer, ETI Magazine, 15 Boundary St, Rushcutters Bay, NSW 2011. We will then process your order and pass it on to Dindy who will send you the goods. Please allow up to six weeks for delivery.

NOTE: Offer closes 31 January 1981

Send coupon to:

C10 Cassette Offer

ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011

2	
	Please supply: Quantity: pack(s).
	of 20 pack C10 cassettes at \$33 a pack\$
	Packing & delivery — \$2.50 per pack
	TOTAL\$
	Name
	Address
	Postcode
	Cheque or money order
	Or use your Bankcard 496
	Expiry Date/
	Signature



General Instrument's Keyboard Division has combined stateof-the-art microprocessor technology with the reliability and simplicity of capacitive keys to create a highly flexible, low cost keyboard for OEM's and hobby projects.

The C70-MGP is chock full of features like 4 level ASCII encoding, serial and parallel outputs, N-Key rollover, provision for RS232 and 20MA loop connection, cursor control and user definable keys and programmable baud rates, all-for around \$150, plus tax. At a dealer near you.

AUTHORISED DEALERS: Sydney (02) E. & M. Electronics 51-5880. A.E.D. 632-6301. Applied Technology 487-2711. G.E.S. 439-2488. Melbourne (03) Sontron Instruments 568-4022. Cottage Computers 481-1975. Ellistronics 602-3282. Stewart Electronics 543-3733.



Brisbane (07) Baltec Systems 36-5183. Zero One Electronics 371-6707. ACT (062) Ortex 82-4995. Adelaide Rogers Electronics (08) 42-6666. Perth (09) Micro Controls 325-2444. New Zealand Southmark (9) 798-078.

daneva control pty.ltd.

66Bay Road, Sandringham, Vic., 3191. Ph: 598-5622 Telex: AA34439

Ohio Scientific dealer network is Australia-wide

For more information and advice call on your local dealer to help you select the best system for your needs

AUSTRALIAN DISTRIBUTOR-TCG, 31 Hume Street, Crows Nest, N.S.W.

AUTHORISED AUSTRALIAN AGENTS

NEW SOUTH WALES

Bambach Electronics NEWCASTLE 2-4996

Compuserve Newcastle Pty. Ltd. HAMILTON 61-2579

Hi-Fi Gallery TAMWORTH 66-2525

Macalec Pty. Ltd. WOLLONGONG 29-1455

Micro Visions KINGSFORD 662-4063

Shoalhaven Communication Services NOWRA 24-444

J.G. Pearce Systems
DOVER HEIGHTS 789-4300

Unique Electronics MERRYLANDS 682 3325

VICTORIA

Ellison Hawker Education Pty. Ltd. HAMPTON 596-7444

Cypher Data Systems MELBOURNE 86-22122

Comprocessing Pty. Limited SALE 44-3399

QUEENSLAND

Dialog Pty. Ltd. BRISBANE 221-4898

SOUTH AUSTRALIA
Applied Data Control

FULLARTON 79-9211
K Tronics
ADELAIDE 212-5505

WESTERN AUSTRALIA

Datas Computer Accounting Services SUBIACO 325-5779

Micro Data Pty. Ltd. EAST PERTH 328-1179

Micro Solutions SUBIACO 328-8372

TASMANIA

Eastside Computers EAST DEVONPORT 27-8121

J. Walsh & Company HOBART 34-7511

AUSTRALIAN CAPITAL TERRITORY

Minicomputer & Electronic Services
PHILLIP 82-1774

NEW ZEALAND DISTRIBUTOR

Computer Consultants, 3 Wolfe St., Auckland N.Z. Phone: 79-8345 Computer Consultants


Queens Rd., Lower Hutt. N.Z Phone: 69-4979



OHIO SCIENTIFIC

The Challenger 4

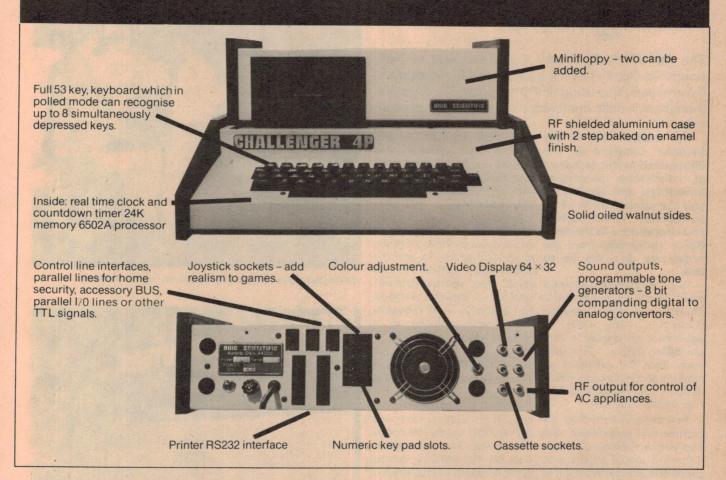Whichever way you look at it, no other computer offers so much for so little, and in colour!



You'd have to go a long way to get better value in a computer. It has execution speed that really separates the computers from the toys. We think the Challenger 4 is way ahead of anything you've seen so far, for a wide variety of uses including business, personal, educational and games, as well as a real-time operating system, word processor and a data base management system.

The Challenger 4 has a 2MHz 6502 processor, and if that's not fast enough we can supply the GT option with the 6502C processor, and 120 nanosecond memory which averages over one million instructions per second.

colours, including 8K memory in the cassette version, 24K for the minifloppy. A BUS structure allows easy plug in of extra memory or many more OHIO boards. The BUS means modularity. If you bought your vintage C2-4 in 1977 we can change the boards at a much lower cost than a new computer.

For the best surprise of all ask

A real time clock and count

down timer, a 64 x 32 display in 16

For the best surprise of all ask our opposition if they can provide all these facilities. When they can't, ask us! For the complete list of dealers, please refer to listing on opposite page.



TOWORNOWS TECHNOLOGY TODAY

OHIO SCIENTIFIC

TCG Ohio Scientific Pty. Ltd.

31 Hume Street, Crows Nest, N.S.W. 2065

Phone: 439-6477

Print-out

Dollars dominate computer

congress

The 8th World Computer Congress, held in Melbourne in October by the International Federation for Information Processing (IFIP), was more of a trade fair than the scientific conference it is officially supposed

and the advancement of in- ative memories. ternational understanding this.

equipment on display is over random access storage device. one billion dollars . . . firm sales man for the organisers.

commercial razzamatazz, this the 16 000 square metres of was also a meeting of minds. presented, along with sixty or so submitted papers (half of which dollars on their stands, although the Congress). Most of them equipment on display, just 'database problem'.

buted and constantly changing stantiated. information still awaits a this area. They suggested that a show. The highly regarded

The avowed aim of the totally new approach to data triennial congress is the storage and retrieval was dissemination and exchange needed and that the solutions of information processing appeared to lie in the areas of knowledge and techniques parallel processing and associ-

Professor Sumner emphaand cooperation in the field. sised that, "We still do not have Some statements from the an adequate method to view the organisers give the lie to process of access to, and the relationship between, data "We have made a substantial items. The various database profit" said Ashley Goldsworthy, systems - network, relational chairman of the organising and hierarchic — all eventually committee. "The value of make serial requests to a

Quite divorced from the inleads from the exhibition al-tellectual discussions at Dallas ready total one hundred million Brooks Hall was the hard sell of dollars", commented a spokes- the displays upstairs in the Exhibition Buildings. Some 170 Nevertheless, behind all the companies were spread over floor space. The big corpora-Thirty-five invited papers were tions like IBM and Data General spent hundreds of thousands of were delivered in Tokyo, the Honeywell's stand was remarkjoint venue with Melbourne for able for having virtually no were highly technical and well comfortable armchairs and beyond the comprehension of coffee tables around which the layman, but one dominant visitors were invited to "come in theme that emerged was the and relax with Honeywell". Rumours that Honeywell had This problem of how best to simply forgotten about preorganise and manage massive paring the stand until the last libraries of increasingly distri- minute have not been sub-

The 'micro sector' of the insatisfactory solution. At a press dustry, while spending much conference Frank Sumner, less on its exhibits, provided chairman of the IFIP pro- some of the main interest. The gramme committee, and Dr 'Computer Concepts' display of Simon Lavington, editor of the Apple micros on Rudi Hoess's Proceedings, agreed that very stand was perhaps the best little progress had been made in attended exhibit in the whole



ADE displayed the North Star and Compucolor microcomputers.



Mensa's stand featured the Findex portable business micro.

was perfectly timed to suit the

North Star Horizon was dis-some of these systems have played on a number of stands, matured, in the sense of offering as were the Cromenco, Com- sophisticated and proven busimodore, Compucolor and ness applications software. An Findex systems, to name but a example is the evolution of the PET personal computer into the In many ways the exhibition Commodore Business System.

On the two public exhibition distributors and vendors of days there were still a few people micro-based business systems. seeking to buy small business It is only in the past year that systems for under \$1000, but by



Mike Pratt of SME is proud of his range of peripherals and expansion boards.

and large the operators who exhibition. Of course there were peddled such dreams a year or two ago have disappeared. For the most part the vendors in Melbourne were established suppliers offering hardware, software, maintenance and support at realistic prices. They did excellent business.

A feature of the exhibition was the unprecedented number of companies supplying industrial systems. Microcon, Alfatron and Industrial Micro Systems (IMS) were notable exhibitors in this field.

By and large, however, there was nothing very exciting or systems which had not been before, but one minicomputer looks very much like another.

Prime were displaying their Office Automation System, but although their concept of administrative workstations and management workstations is interesting, one terminal is very much like another unless you can find a salesman to demonstrate the software. Persons like myself, wearing Press badges, found it rather difficult to engage the attention demonstrators who were much

dollars to spend.

puting equipment of Hemisphere.

Perhaps that wasn't such a particularly new in the whole more interested in those with bad thing. Perhaps the com-

puter world still pays too little For the businessman, the attention to the difficulties of indisplayed and demonstrated EDP manager, the potential tegrating computer systems purchaser, the exhibition was a with people. Professor Calvin unique opportunity if they had Gottlieb had this in mind when particular needs and specific he remarked that, "The comapplications in mind. For the puter technology cannot be general observer like myself, the regarded as neutral, if exvast array of competing pro- perience shows that in reality, ducts was all a bit too much to whatever its potentialities, the take in. In the end I spent more effect of introducing it is almost time talking to people in the always to favour large centraindustry than investigating the lised systems and inhibit local greatest collection of com- autonomy ... What appear to ever some as opportunities and assembled in the Southern markets, to others appear as costs and exploitations.

Christopher Speary



Get your hands on our big new PET 3008 keyboard for only \$999*

At last it's here: the Commodore PET you've been demanding! It's called the PET 3008. It boasts all the many features of our PET 2001, plus something you've been itching to get your hands on. A new, big, typewriter-style keyboard!

To celebrate the arrival of a strictly limited stock, Commodore offers you a great deal. To begin, the price is slashed to \$999*. So straight away you save \$196 on the normal price of \$1195.

Not bad for a start. And there's more...

FREE, C2N CASSETTE UNIT WITH EVERY PET 3008 SOLD

That's right.

Get your new PET 3008 with the big typewriter-style keyboard now, and we'll throw in, absolutely free, a C2N external cassette unit.

Retail value? \$126.50.

So all up on your PET 3008 purchase you save a whopping \$322.50. Naturally, it's a strictly limited offer (either that, or we go broke!)

So whatever you do, don't miss out. See your authorised Commodore Dealer very, very soon!



SAME GREAT DEAL ON THE PET 2001

We mustn't leave out the many people who fancy the PET 2001's calculator-style keyboard. So:

COMMODORE PET 2001, normally	\$1195
OUR SPECIAL PRICE NOW	\$999
YOU SAVE	\$196
PLUS FREE C2N CASSETTE UNIT, NORMALLY	\$126.50
TOTAL SAVING	\$322.50

Cz commodore

For the name of your nearest authorised Commodore Dealer, write or phone;

COMMODORE INFORMATION CENTRE

3 Campbell Street, Artarmon, NSW 2064 Telephone: (02) 437 6296

*Prices and saving may vary slightly from Dealer to Dealer. Offer ends December 30, 1980 or earlier if stocks run out.

Printout

Software contest results

A while ago ETI ran a competition in association with Computerland Australia, in which readers were invited to submit original software for microcomputers.

user, its complexity, its 'ele- Original Application. gance', the degree of human documentation.

Vic, for his HEX INFORMATION graphic display generator. RETRIEVAL SYSTEM. He wins the major prize of a Cromenco Graphics ZPU Z-80 CPU card and special goes to Kenneth Stoke of prizes for Best Documentation Hobart for his game called and Most Marketable Software. BUDGET.

Second was W.R. Hodgson of Chatswood, NSW, with his also receive free copies of ETI program for a NAVIGATION for the next two years.

Entries were assessed on COMPUTER. For this he wins a the following criteria — the Vector Graphics 8K RAM kit and value of the software to the the special prize for the Most

In third place were A. Heap engineering and the quality and R. Green of the University and presentation of the of New England, NSW, whose COMPUTER ASSESSMENT First place in the contest went OF FARM VIABILITY wins them to David Segall of Canterbury a Vector Graphics 260 x 260

> Fourth prize of a Vector PROM/RAM card

All the above prizewinners will

South Australian software

Peter Hartley, former editor of Micro-80, has established his own software house in Adelaide.

He specialises in small business applications for Z80 based microcomputers and has recently announced major agricultural and small business packages for release early next year. He will also be undertaking custom software development.

The current range of Peter Hartley software includes an interactive typing course called Touchtype, for use with TRS-80 and System 80 micros, and a number of entertaining games.

For more information contact Peter Hartley Software at P.O. Box 132, Eastwood, SA 5063. (08) 79-4061.

... and hardware

South Australian based Computer Imports Pty Ltd has announced its diversification into the small business and hobby computer market.

They will concentrate on the supply of peripheral equipment for the most popular micros. Disk drives, memory expansions and printers will be sourced from both overseas and local suppliers, and the company has announced a number of peripheral packages.

Computer Imports will operate in conjunction with Peter Hartley Software to supply composite hardware/software packages especially tailored to users' specifications.


Contact address is P.O. Box 7, Port Adelaide, SA 5015 (08)

Astrology by computer

A Sydney company is using computers to update the ancient and arcane art of astrology.

Preparing astrological charts candidate for computer autohas always been a tedious and mation. time-consuming business, in-

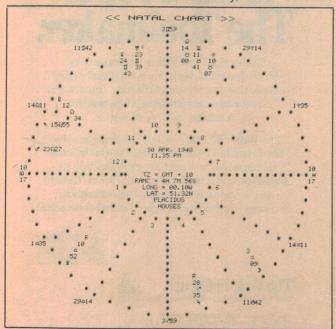Illustrated on this page is a volving a great deal of Natal Chart in the Round Wheel calculation and careful plotting format, prepared for us by of results, so it was a natural Austin Levy, head of Astrosearch



service.

The chart shows the positions of the sun, moon and planets at the birthtime of sub-editor William Fisher (the only member of staff who could remember exactly when he was

Astrosearch's charts are prepared on a 32K Commodore PET with a dual hard disk drive and a programmable printer. The programs, which are written in BASIC, have two major parts. The first part uses the equations of planetary motion to calculate the positions of the planets at the specified times; the second part, which is four times as long, output formatting.

The Round Wheel formatting program uses reflections to generate the complete design from a quarter circle basis. String variables are used in preference to numerics and the planetary symbols are plotted by

Computer Services, who say the programmable character they are only the second generator. Approximately 1500 company in the world to offer a bits are used to define the computerised chart plotting quarter circle pattern in

> The complete program uses 24K of memory. As well as Natal Charts like the one illustrated here. It can print out Progressed Charts, which are charts showing the planetary configurations at dates other than the birthdate. Biorhythm printouts are also possible.

Astrosearch are currently working on a high level program which will synthesise interpretations of the astrological data. The idea is to develop a dynamic system rather than a static text file. Other ideas which may yet materialise are computer-made synthesised music and kinetic art displays derived from the astrological

For more information contact Astrosearch at P.O. Box 1552. North Sydney, NSW 2060. (02) 913 7559.





COMPUCOLOR II ex stock

Features:

- Up to 32K user RAM
- 16K ROM
- Eight colour display
- 32 lines at 64 characters
- Inbuilt 5" disk drive
- RS-232 Port

MICROLINE 80 PRINTER ex stock

Features:

- 80 char/sec
- 40/80/132 char/line
- 9 x 7 dot matrix
- Graphics
- Long life print head (200,000,000)
- Friction, pin and tractor feeds
- Full 96 character ASCII set
- Plug compatible: TRS80, Sorcerer, Apple, Compucolor II, TI 99-4



TELEVIDEO TVI 912B (VDU) ex stock

Features:

■ 12" screen ● 24 lines at 80 characters ● 75 to 9,600 Bauds
■ RS-232 or 20MA interface ● Printer output Port ● Microprocessor controlled
■ 12" screen ● 24 lines at 80 characters ● 75 to 9,600 Bauds
■ RS-232 or 20MA interface ● Printer output Port ● Microprocessor controlled





Features:

● North Star Z80A Processor. ● North Star RAM memory board (64K). ● North Star Disk Controller Board (4 drives). ● Quad capacity drives (360K bytes per drive). ● S-100 motherboard with 12 slots and real time clock. ● Two serial and one parallel I/O interfaces. ● A power supply more than adequate to power a full complement of 12 S-100 boards. ● North Star Software — BASIC, Disk Operating System (DOS), and Monitor on diskette. ● Applications software: Debtors, Creditors, General Ledger, Inventory, Payroll, Word Processor, Mail Manager.

SPECIAL — 5½·Verbatim Diskettes \$4.00 each.

END OF YEAR SALE — Qume Print Wheels at cost.



212 High St, Prahran, VIC. 3181. Phone (03) 51-1950. 91 Regent St, Chippendale, NSW, 2008. Phone (02) 699-4919.

TRS-80 is a registered trademark of Tandy Electronics.





The Tools. from Cooper The Toolmaker.

· Weller industrial SPI non-temperature controlled soldering irons, with nickel plated copper tips, stainless steel barrels. Impact and heat resistant handles are lightweight. Available in 25 or 40 watts.

The Weller WC100 cordless soldering iron has been specifically developed for the technician. It operates from long-life nickel cadmium batteries, and it is therefore ideal for in the field applications. Special adaptor available to re-charge from cigarette lighter in motor vehicles.



The Cooper Group
CRESCENT-LUFKIN-NICHOLSON-WELLER-WISS-



The Cooper Tool Group Limited PO Box 366, Nurigong St, Albury NSW 2640 Australia. Tel: 21-5511. Telex:56995.

Printout

The personal micro goes handheld



Well, almost! The Sinclair ZX80 microcomputer is shaped to sit on a desk or table but it's easily small and light enough to hold in your hand if your prefer.

Selling in this country for market for personal com- provide shielding. puters.


People accustomed to using more sophisticated and expensive micros will probably find some of its habits a little disconcerting, but first time users are unlikely to be dismayed by any of its features.

Designed around the 780-1 microprocessor chip (a copy by NEC of the ZX80), the ZX80 QWERTY arrangement. contains a keyboard, CPU and pansion board.

One reason for this comless than \$300, the ZX80 puter's light weight is that it is looks like opening up a enclosed in a 1mm thick plastic whole new mass consumer case, metallised on the inside to

> The keyboard is made up of touch switches, completely covered by a flexible polymer sheet that protects against contamination by dust or liquids. Key symbols are printed on the underside of this sheet to prevent them rubbing off with use. Despite first impressions, the keys are easy to use. They are laid out in the standard

Sinclair have developed their I/O interface circuitry in a single own variety of BASIC for use module and can be used direct- with this machine. This has ly with any cassette recorder and some features which will defi-TV set. On board are 4K of ROM nitely make things easy for the (all on one chip) and a 1K RAM novice programmer. Key words which can be expanded to 4K like RUN, PRINT and LIST, with an optional memory ex- GOTO, GOSUB, LET and so forth can all be entered with a

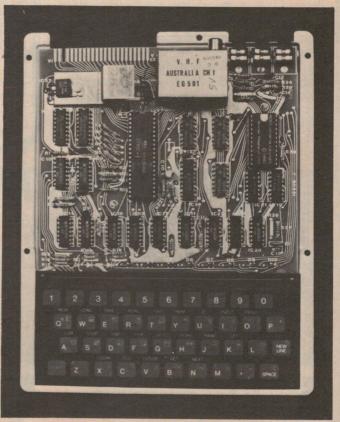

The Dick Smith Daisy Wheel

If you just

bought any
other printer
you'll eat your
heart out!

When you want letter-quality printing you are usually talking big money. If you've just bought a word processor printer you'll know what we mean.

In fact, if you've just bought a word processor printer you'd better not read any further. You might get too upset!

The new Dick Smith Word Processor Printer gives you superb print quality (even three carbons down!) at a brisk 25 characters per second. It uses standard Diablo-type daisywheels, giving you low cost replacement and a large variety of fonts. It uses standard business stationery, up to 400mm wide, prints with proportional spacing, in two directions — if you wish. It's hundreds of dollars less than its nearest competitor and thousands of dollars less than many others!

specifications:

Print speed: 25 characters per second; Carriage return speed: 1000ms; Line feed speed: 40ms (4.25mm); Characters per line: 136 (2.5mm pitch) 163 (2.0mm pitch); Resolution pitch: space 0.2mm, line feed 0.5mm; Form width: 398mm maximum; Printing width: 345mm maximum; Number of printing characters: 96; Number of copies: original plus 3 copies; Noise level: below 65db with cover; Print Wheels: Diablo-

compatible plastic; Ink ribbon: cloth or multi strike; Interface Centronics-type parallel; Operating conditions: 5-36 degrees C. 10-90% RH; Power requirements: 240v/50Hz, 70 watts; Dimensions: 625mm (w) x 380mm (d) x 258mm (h); Mass 19.5 kg including cover, power supply.

Credit terms available

to approved

applicants

All this

Cat. X-3265

We also offer outstanding value on this

DOT MATRIX PRINTER

Fantastic value for less than \$1,000!!!

This incredible dot matrix printer uses inexpensive fan fold paper Upper and lower case with 125 characters per second print speed and a one line buffer memory, plus lots more



SYSTEM 80 OWNE DON'T NEED S-100 EXPANSION?

Use this parallel printer interface if you don't need full S-100 expansion. Save a bundle! Uses similar connecting cable to S-100 interface

\$495

PRINTER CABLE

Fitted with edge connector at one end, 57N-36 plug at other: suits virtually all Centronics-type printers. Use with either S-100 interface or parallel printer interface.

Cat X-4014

DICK SMITH Electronics



SEE OUR OTHER ADS FOR FULL ADDRESS DETAILS

intout

single keystroke. The interpreter has a unique syntax checker that prevents entry of program lines with syntax errors, thereby eliminating the frustration of entering a program and only discovering the errors later on when it won't run! And there's a powerful and versatile screen editor that allows modification of existing program lines. However, given the limited capacity of the machine, all these functions have to be provided at the expense of the more powerful BASIC commands.

This deficiency of powerful commands can be eliminated by purchasing the new 8K ROM chip that Sinclair have designed for the ZX80. This is a drop-in replacement for the standard level computing, and comes with a new keyboard template and a supplementary operating manual

As well as a greatly improved range of BASIC commands, the new ROM features full floating point arithmetic with 9-digit accuracy, logarithmic and trigonometric functions and their inverses, a graph plotting capability and a facility for generating animated displays using a 'PAUSE n' command, which sends the display file to the TV screen for n frames or Europe. until a key is pressed.

The microprocessor itself. which is clocked at 3.25 MHz, peforms every single function. including the control of the cassette recorder and the TV monitor. As a result, the video display disappears whenever any operation is being carried out, returning when the operation is complete. This is one of the features that practised computer users might find offputting, but it's doubtful whether novices will find it a nuisance.

When we finally figured out how to prise open the case without completely destroying it, we discovered a single well designed and well finished printed circuit board with all the components mounted directly onto it — the ZX80 is designed to be ROM chip, designed for higher used with an external power supply.

Closer inspection revealed that Clive Sinclair has obviously shopped around for components in an effort to keep the price as low as possible. Memories from Ireland, video driver from Taiwan, regulator from El Salvador, gates from the UK and a Japanese microprocessor give the machine a truly international flavour. There's one Australian section too, the VHF modulator which replaces the UHF unit fitted to models sold in



The ZX80 was first publicly shown in Australia at the 8th World Computer Congress in Melbourne.

use the standard ASCII codes, it Maestro in Kinkumbra. is not possible to connect a consometime in the future.

Key, Vic 3101. (03) 861 6224.


Local outlets in Victoria are Esperance. Rod Irving Electronics in Northcote, Myers in Melbourne, Minit puterland in Brisbane and Computer Service in Bendigo. Scotts Audio in Townsville. NSW suppliers are Emona En- South Australian residents can terprises in Sydney, P. Hatcher obtain the ZX80 from Comin Sydney, DGE Systems in puterland and from Computer Newcastle, South Coast Com- Imports Pty Ltd. Because this micro does not puting Service in Nowra,

In Tasmania the ZX80 is ventional printer, but it is likely available from J. Walch and Son that Sinclair will be producing of Hobart, in the Northern their own compatible printer Territory from Ascom Electronics of Alice Springs, in the The ZX80 is distributed in ACT from Computer Business Australia by Sinclair Equipment Aids, in Western Australia from (Australia) Pty Ltd, 308 High St, WACB Radio Central, Radiotronics and Focus Electronics in

Queensland outlets are Com-

Elaine Ray

NorthStar Computers

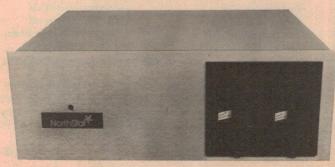

with CP/M Operating System

\$4995 plus sales tax if applicable.

30MB Hard Disk with Controller

\$9995 plus sales tax if applicable.

AMPCOMP SYSTEMS

PO BOX 214, SEVEN HILLS, NSW 2147. TELEPHONE (02) 624-3509.

Printout

For Sorcerer Apprentices

Christmas is just around the corner, so I thought you deserved a few helpful routines which can be interfaced with your BASIC programs. Thanks to Brendan J. Joyce for suggestions in his letter from which I quote:

"The column 'For Sorcerer Apprentices' in ETI is very welcome. It is frustrating as a novice to own what one has been assured is a very powerful micro and not be able to unleash its strength. There are articles in abundance on other better known machines, but there is almost a conspiracy of silence on the Sorcerer...

... There are three problems bothering me that I would like some information on:

(1) Printing a given number of lines on a page so that a space can be left above and below the perforations.

(2) A keyboard sensing routine that can detect what key has been pressed without the need for the RETURN key...

(3) A method of accessing monitor subroutines using BASIC. There must be many powerful subroutines in the monitor, but the identification of these and the method of access to them is a mystery to a non-professional such as myself

Good luck in your efforts and three cheers for A.P.F.Fry."

Thanks for your letter Brendan. The simplest way of making sure that your printer keeps track of lines per page is to do all your printing through a subroutine. This will allow you to print lines to the screen without losing track of the line count on your printer. Include the lines:

0 CLEAR 500:LP=60:CP=6

1 VE=PEEK(-4095)*256+PEEK(-4096)-47

2 IF VE > 32767 THEN VE = VE-65536

Then use this to print:

10 PR\$="HELLO":CR=0

20 GOSUB 1000

Where the subroutine is as follows:

1000 PP\$=PP\$+PR\$

1010 IF CR THEN RETURN

1020 POKE VE, 147: POKE VE+1,233

1030 PRINT PP\$:CO=CO+1

1040 IF CO LP-1 THEN FOR CO=CP TO 1

STEP-1:PRINT:NEXT

1050 PP\$="":POKE VE,240:RETURN

Of course you mustn't use the variables PP\$, PR\$, CR, CO, LP,

CP or VE for any other purpose.

In line 0 you must clear at least enough space to handle the longest line you plan to print. LP is the number of printed lines per page and CP is the number of carriage returns before page end. The total of these two should be the number of lines on your form. CR is a flag to tell the subroutine whether or not to print a carriage return at the end of the line. If CR=1 then the following line will be printed where the last left off. CR=0 terminates the line and prints a carriage return. The subfoutine will automatically switch the printer on when it needs it and return with it switched off. You never have to worry about this while the programme is running.

You'll notice that in line 1020 I poked VE + 1 with 233. This is to overcome a bug in the Monitor which may cause problems occasionally. When the Sorcerer is switched on or reset, it sets the SEND vector to E9F0 and the RECEVE vector

to EBIC. If you then use the Monitor commands SE 0=V or SE 1=K (ostensibly the same vectors), Exidy programmers see fit to stick in different vectors that do the same thing:

SE 0=V sets the SEND vector to E01B (which jumps to

SE 1=K sets the RECEVE vector to E018 (which jumps to FB1C)

The problem is that when you POKE VE,147 or POKE VE,240, you change only the LOW part of the address. If you exit BASIC and set the output, the Monitor will have changed the HIGH part when you return. To be safe, always POKE VE+1,233 when you are switching the printer on and off using this method. One can only hope Exidy takes note of all these bugs — there are lots of 'em!

In answer to Question 2, I have included a simple keyboard scanning routine which uses a modified INP(X) function:

10 POKE 318,195:POKE 320,224

20 A = 1 NP(9)

Line 20 will load the ASCII number of any key pressed into variable "A". If you want to wait for just any key, include line 30 as follows:

30 IF A=0 THEN 20

If you want to check for a specific key, (e.g. "*") change line 30 to:

30 IF A ↔ ASC("*") THEN 20

Your last question was not so easy, Brendan. I did some asking around and found that Greg Lister of Software Source could provide a solution.

BASIC MONITOR INTERFACE

Copyright (C) November 1980 Greg Lister + Claude Almer
ADDR 0 1 2 3 4 5 6 7 8 9 A B C D E F
F000: 2A B1 01 2B 7E FE 28 20 FA FD E5 D1 23 7E
F010: FE AD 20 02 3E 3D 12 13 FE 29 20 F2 1B EB36 OD
F020: FD E5 E1 CD 25 E2 CA 14 C3 DD21 12 E3 E5 DDE5
F030: 06 02 DD7E 00 BE 20 0E 23 DD23 10 F5 D1 D1 DD
F040: 6E 00 DD66 01 E9 DDE1 E1 DD23 DD 23 DD23 DD
F050: 23 DD7E 00 B7 20 D6 C3 14 C3 FA DF 47 2B 43 31

Here's how to use it. Enter the above listing from F002 (HEX) onwards. Claude warns that you shouldn't use it in conjunction with his KEYRP programmne (ETI November 1980)

It is now accessed from BASIC with the USR(X) function as follows:

10 POKE 260,2:POKE 261,240:REM initialise USR function. 20 Z=USR(COMMANDLINE)

where COMMANDLINE can be any of the standard Exidy Monitor commands, e.g.

Z=USR(DU F002 F05F)

will dump the program
you've just keyed in
you've just keyed in
will switch printer on
will switch printer off
will slow the screen down
Z=USR(SE S=10)

Z=USR(SA BASMO F002 F05F)
will save the program

An excellent use is to load a tape of predefined graphics directly from Basic.

Finally, there appears to be a lot more backup and worthwhile software than we know of. If readers or programmers would like an appraisal of their software, please send me a copy care of ETI. Of course copyright software will be treated in complete confidence.

A.P.F. Fry

HAS THE TASTE STOPPED GETTING THROUGH?

If your present tobacco just doesn't deliver the satisfaction you want, then roll a Cannon.


A rich new blend of medium dark cigarette tobacco that's just a little bit stronger.

Cannon, for the taste you're missing out on now.

CANNON.
SLIGHTLY STRONGER.



Sooner or later you'll need a Gregory's.

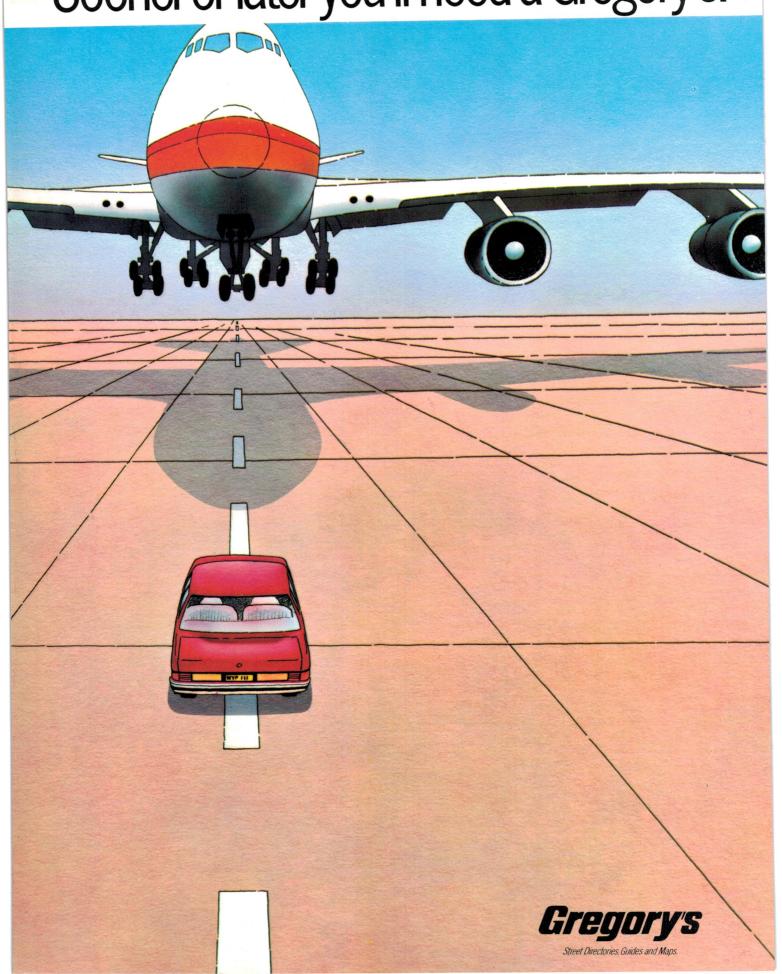

policy. Together, we have produced dual-purpose machine: - an attractive, modern, correcting typewriter which doubles as a correspondence quality Daisy-Wheel printer when used with your micro-computer.

How good is it? :- This part of our advertisement was typeset using an ET-121 driven by a TRS-80.

77 TRACK **DISK DRIVES** DOUBLE YOUR CAPACITY

DD-7S Micropolis Floppy Disk, 77 Track, 100% larger capacity than most mini-floppy drives, complete with cable, power supply, chassis, and includes NEWDOS '80.

Same as above but no cable or Newdos '80. DC-4

4 drive connector cable.

* * SPECIAL * * MPI DISK DRIVES ONLY \$339!!

40 track bare drive for TRS-80. Only requires readily available 5 volt 0.7 amp and 12 volt 1 amp power supply to be up and running. Can be mounted in simple cabinet or used bare.

DISKETTES FOR TRS-80

BASF single side/single density ... \$4.50 ea BASF double side/double density ... \$5.90 ea VERBATIM 77 track \$6.99 ea

Minimum Order 10

EXATRON STRINGY FLOPPY

\$352.50 incl p&p

15 times faster than cassette, infinitely more reliable. Completely under computer control, the stringy floppy is easier to use than disks and is a very much cheaper alternative. Will save and load any L2/16K software. Special software also available.

> Wafers for Stringy Floppy \$3.50 ea. Any Size

MICRO-80 MAGAZINE

ANNUAL SUBSCRIPTION \$24.00 Monthly Magazine dedicated to TRS-80 and System '80 users. Every issue contains at least 6 new programs, plus problem solving columns, hardware articles, readers' letters hints, etc., etc.

ANNOUNCING SYSPAND 80 FOR THE SYSTEM 80 \$119.00

SYSPAND 80 is a self-contained module which connects to the expansion port on your SYSTEM 80 and gives you a CENTRONICS parallel port to drive a printer PLUS the TRS-80 40 line bus. SYSPAND 80 allows you to connect all Tandy peripheral, including the expansion interface, disk drives, MICROTEK MT-32 memory expansion unit and the fabulous EXATRON STRINGY FLOPPY.

Price shown is for a built-up and tested unit. SYSPAND 80 is also available in kit form, call or write for details and price.

TRS-80 MEMORY EXPANSION UNIT MT-32 ... \$129.00

The MT-32 is manufactured by MICROTEK Inc., USA. It provides a CENTRONICS printer port and sockets for up to 32K of dynamic RAM. It comes complete, ready to plug into the expansion port of your Level II 16K machine. (Will also work with your SYSTEM 80 via SYSPAND 80).

MT-32A without RAM \$149.50 MT-32B with 16K RAM \$188.00 MT-32C with 32K RAM \$243.00

16K MEMORY EXPANSION KIT ONLY \$59.00 incl P&P

These are prime, branded, 200 ns (yes, 200 ns!) chips. You will pay much more elsewhere for slow, 350 ns. chips. Ours are guaranteed for 12 months. A pair of DIP shunts is also required to upgrade the CPU memory - these cost an additional \$4.00. All kits come complete with full, step-by-step instructions, no soldering is required. You don't have to be an electronic type to instal them.

FREE SOFTWARE OFFER

\$40 WORTH OF SOFTWARE FOR TRS-80 AND SYSTEM '80 WITH EVERY NEW SUBSCRIPTION TO MICRO-80!

Every new subscriber will receive on cassette, ready to load, 3 x Level I and 3 x Level II programs (includes our fabulous household budget program), with a regular retail value of at least \$40.

AUSTRALIAN SOFTWARE

BMON (L2/16K) \$19.95 plus 50c p&p The ultimate program to assist BASIC pro-

TOUCHTYPE (L2/4K) \$19.95 plus 50c p&p 22 lessons to teach you to type on your own keyboard and screen!

RPN CALCULATOR (L2/16K & 32K) \$14.95 plus 50c p&p

Turns your computer into a \$600 calculator. Ideal for Architects, Surveyors, Engineers, Teachers, Scientists, etc.

U-BOAT (L2/16K) \$7.50 plus 50c p&p

You're the Commander, read all the guages, fire the torpedoes, crash dive, get the enemy before his depth charges get you!!

MMM-1 GAMES PACK (L2/4K) \$7.50 plus 50c p&p

3 fast moving games — INDY 500, SUB-HUNT, KNIEVEL

MMM-2 GAMES PACK (L2/4K)

\$7.50 plus 50c p&p 3 more games with fast moving graphics -TANK, THIEF, SHOOTOUT

DALEK CHASE (L2/16K) \$7.50 plus 50c p&p

Save Dr. Who from the pursuing DALEKS

SHEEPDOG (L2/16K) \$7.50 plus 50c p&p

Guide your sheepdog as it rounds up the wandering sheep and drives them into the pen. But don't lose them in the bushes!!

S KEY (L2/16K and up) \$15.95 plus 50c p&p

Define shifted keys to be BASIC commands, type in graphics directly from the keyboard and see them when you LIST and much

THE FABULOUS **NEWDOS 80** IN STOCK NOW!

ND-80

The disk operating system that gives:

New basic commands that support variable record lengths up to 4095

Mix or match disk drives — supports any number of tracks from 18 to 80. Use 35, 40 or 77 track 5" mini disk drives or 8" disk drives, or any combination.

A security boot-up for basic or machine code programs. User never sees "Dosready" or "Ready" and cannot "break" clear screen or issue any direct basic statement including "List" and much, much more

ND-35+ \$99 Newdos+ for 35 track drives ND-40+ Newdos+ for 40 track drives

SCOTCH BRAND PERSONAL COMPUTING CASSETTES

C-10 pack of 10. ..\$26.00 incl. p&p ..\$28.00 incl. p&p

To: MICRO-80 P.O. Box 213, Goodwood, S.A. 5034 I Please rush me the items checked below:

12 month subscription to MICRO-80 and my free software cassette	\$24.00
12 month subscription to	

MICRO-80 and the cassette software cassette \$60.00 The lastest issue of MICRO-80

PLUS THE ITEMS LISTED BELOW					
DESCRIPTION	PRICE				
1000年 ,1000年,1000年					
	1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1				

TOTAL ENCLOSED	L		á		
Name					
Address					
Post Code		-			

bankcard No....

Please debit my Bankcard \$

Expiry date

MICRO 80 PRODUCTS


(08) 272 0966

284 GOODWOOD ROAD

CLARENCE PARK, ADELAIDE

TRS-80 and SYSTEM 80 OWNERS

\$149

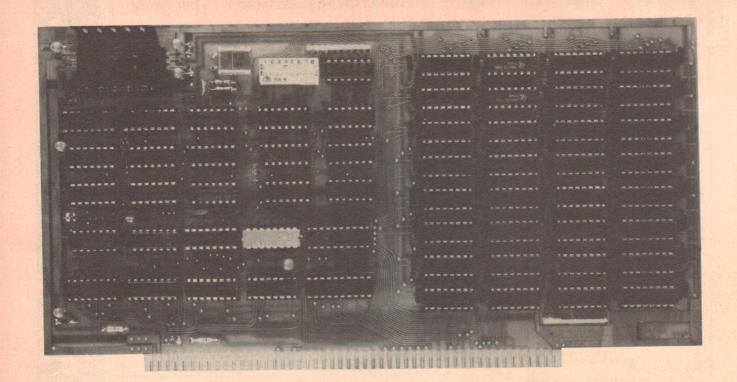

T.C.T. 64 K Dynamic Board

After years of experience with local and imported dynamic boards that simply didn't work satisfactorily, T.C.T. MICRO DESIGN decided to design a dynamic memory board that came closer than ever before to true static performance.

The resulting board will run with virtually any processor, on an S100 bus, running at any speed below 2.5MHz (Z80). A variety of disk systems and DMA devices have been tested and run perfectly.

REFRESHING:

The major difference between this board and others is the manner in which refreshes are triggered. Most current boards refresh when they are told to and when the processor is reset, halted or waited. Doing this does not avoid clashes between refreshes and processor accesses. This is the reason why some memory boards don't work properly with disk drives. Our board instead has counters that trigger a refresh whenever one hasn't been done for a certain time. This avoids sampling extra bus signals, and if a clash between a refresh and a processor access occurs it will be resolved with the special arbitration circuitry on the board. This also means that the processor may be run at as slow a speed as is desired - something that would crash nearly any other dynamic board.

This board has been tested in several systems, based on various disk systems and processors, including Z80, 2650, 8080, 6800 and 68000.

T.C.T. MICRO DESIGN PTY. LTD. Engineering excellence

FEATURES:

- * Designed for the S100 bus
- * Expandable from 16 to 64K
- Does not need halt, wait and reset status signals from bus
- Optimal arbitration between refreshes and memory accesses
- * All timing derived from 25MHz clock
- * Will run at any speed from zero to 2.5MHz (Z80)
- * Arranged as four 16K banks, with independent write protect and disable
- * Supports bank select and phantom
- Genuine S100 board size, 5.3 by 10.0 inches
- * High quality solder masked and plated through board
- * Excellent manual, including construction and setting up details and a discussion of testing and memory design techniques.

KIT PRICES:

	inc. tax	ex. tax
16K bytes	\$279	\$245
32K bytes	\$349	\$305
48K bytes	\$419	\$365
64K bytes	\$489	\$425
8 × 4116 (200ns)	\$75	\$66

Add \$60 for assembled and tested.

OEM enquires welcome.

. P.O. Box 263 Wahroonga, 2076, N.S.W.

Please add \$10 for post and packing.
Allow two weeks for delivery, we will immediately inform of any unexpected delays.



A SINCLAIR ZX80 COMPUTER

-with software

Only recently released in Australia, the Sinclair ZX80 Personal Computer is being distributed here by Consolidated Marketing at a recommended retail price of \$295, including the manual. The ZX80 owes its low price to its remarkable design; the whole system is packed onto fewer, newer, more powerful and advanced LSI chips, the makers claim. The ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer because the design packs the RAM so tightly. You can add to the memory via the expansion port, giving a maximum potential of 16K. The unit includes a cassette interface and output direct to TV antenna input.

You can win one of these remarkable computers by entering this simple contest. Only five questions to answer!

This contest is jointly sponsored by ETI and Consolidated Marketing - who have generously donated the prize.

And as a special bonus the winner will also receive six packs of innovative and imaginative software. This has been designed and donated by Peter Hartley of Peter Hartley Software in Adelaide.

Six runners-up will also win a pack of Peter Hartley software.

RULES

ated companies.

Entries should be addressed to ETI/Sinclair ZX80 Contest, Electronics

Today Int., 15 Boundary St, Rushcutters Bay, NSW 2011.

Closing date for the contest is 31 January 1981. Entries received within seven days of that date will be accepted if postmarked prior to and including 31 January

The winning entry will be drawn by the Managing Editor of ETI whose decision will be final. No correspondence can be entered into regarding the decision.

Winner will be advised by telegram the same day the result is declared. The name of the winner, together with the winning answers will be published in the next possible issue of ETI.

Contestants must enter their names and address where indicated on each entry form. Photostats or clearly written copies will be accepted but if sending copies you must cut out and include with each entry the month and page number from bottom of the page of the contest. In other words you can send in multiple entries but you will need extra copies of the magazine so that you send an original page number with each entry.

This contest is invalid in States where local laws prohibit entries

Entrants must sign the declaration, accompanying this contest, that they have read the above rules and agree to abide by their conditions

You may enter as many times as you wish but you must use a separate entry form for each entry and include the month and page number cut from the bottom right hand portion of this page. You must put your name and address on the entry form and sign it where indi-

Please read the contest rules carefully, especially if sending multiple entries.

All entries received by the due date will be placed in a barrel. First all-correct entry then drawn is the winner. Next six are the runners-up. Permit No: TC 80/1261

 What programming language is used in the ZX80?
 How many key entry strokes are required to enter words such as RUN, PRINT, LIST etc. (i.e. how many letters per word)?
 How many standard graphic symbols are included?
Can the ZX80 be programmed to play chess?
• In which country is the ZX80 made ?
Maritan Marian M
Name
Address
Postcode
I have read the rules of the contest and agree to
abide by them
Signed
Date

OGURA PRINTER

RO-136E



Basic Specifications:

- Printing speed
- Character size
- Character type
- Character spacing
- Line spacing
- Form width
- Copies
- Paper feed speed
- Data input
- Power
- Inked ribbon

120CPS bidirectional

7 (length) × 9 (width) (Standard)

ASCII 128 characters

128 (136E) or 64 (80E) special characters can

be added as an optional feature

10 characters/inch

6 or 8 lines/inch (switchable)

5-15 inches (136E)

5-9 inches (80E)

Up to five copies including the original

88m sec/line (6 lines/inch)

Paper feed mechanism Tractor feed (continuous form)

A slip may also be used

8 bit parallel Centronics compatible RS-232C I/F. TTY 20mA current loop I/F. A variety of specifications can be applied by controlling the interface.

50/60Hz 100V ±10% 160VA

13m/m (width) × 13m (length) (Black cartridge)

Graphic Data RO-136G

The printer can print graphic data by controlling printing on a dot basis of up to 960 dots across the page. Speed - 80CPS.

New Dot Printer Featuring Low Cost, High Performance, and Versatility

The OGURA RO series incorporating a microcomputer, is a low-price, high-performance serial dot printer featuring high reliability and a variety of applications.

It can be used in combination with a microcomputer, a small-scale computer, or as a CRT hardcopy device.

"Ogura RO Series" aims at dispersion of printers.

SME OLYMPIA PRINTER

Why would you want a golfball when you can now have something quieter, faster and less tiring?

The new generation electric typewriter is here! And it doesn't have a golfball. Olympia Whisperdisc. A super-quiet fully electronic typewriter with a simple, trouble-free typing disc to give you an almost perfect image.

A self corrector lets you remove up to eight characters by pressing a single key. The disc can be changed in seconds to a different typeface. The low profile keyboard reduces strain. And, being electronic, Whisperdisc is virtually trouble-free.

SME can now supply the ES100 Typewriter fitted with RS232C Serial Interface. This unit is known as a ES100P, it can interface to all standard computers via a 25-way 'D' connector.

Please contact SME for more information. \$1950.00



ELECTRONICS

Melbourne: Ph (03) 842 3666 New Tel No. January 1981 (03) 874 3666 Trading hours: 10am-6pm Mon to Fri.

6 Doncaster Rd, Doncaster East, Vic 3109. PO Box 19, Doncaster East, 3109. Telex AA37213.

DEALER Canberra — 81-5011, Sydney — 661-9237. Send 66¢ in stamps for COMPUTER PRINTOUT CATALOGUE for more details

PRODUCTS AUSTRALIAN MADE AND EX STOCK (ALMOST). DEALER ENQUIRIES WELCOME rices and specs. subject to change without notice.

All prices tax free, for retail prices add 15 per cent.



Give name, number, expiry date and signature for mail order sales





Trading Hours: 10am-6pm Mon to Fri



are on the move again

Due to an incredible increase in business, we have been forced to look for larger premises.

Consequently we will soon be moving into a new 4,500 sq. ft. air conditioned office and factory.

For our new phone number and address, watch this space in next months' issue.

Until then we are open for "BUSI-NESS AS USUAL" at the address at the bottom of this page.

S-100 VO PORT BOARD



DUAL SERIAL I/O CARD Features: dual independantly controlled serial ports with TTY and RS232 outputs and inputs. Nine programmable parallel ports, crystal controlled baud rates fully buffered and address decoded. Plated through holes & solder resist mask Price: Kit \$189. Ass. \$225.

UV EPROM ERASER



New product range. Model LEE/T 15W tube, 120 min timer, up to 40 EPROMS will erase in 10/15 mins. Model MEE/T 8W tube 120 min timer, up to 10 EPROMS will erase in 20/30 mins. Model MEE is same as MEE/T but with no timer. All erasers are fully assembled and have a safety switch. LEE/T \$125. MEE/T \$105. MEE \$85.



1096 Doncaster Rd, Doncaster East, Vic 3109. PO Box 19, Doncaster East, 3109. Telex AA37213. DEALER: Canberra — 81-5011, Sydney — 661-9237.

Send 66c in stamps for COMPUTER PRINTOUT CATALOGUE for more deta

PRODUCTS AUSTRALIAN MADE AND EX STOCK (ALMOST). DEALER ENQUIRIES WELCOME.

Prices and specs. subject to change without notice

All prices tax free, for retail prices add 15 percent.

NEW COMPUTER **DEMONSTRATION** CENTRE **NOW OPEN!**



117a Henley Beach Rd., Mile End S.A. 5031. 43-7981 - 43-8324

Two Adelaide men have formed the new company - Graham Stallard and Jim Pope. Their combined knowledge and experience introduces a more complete service to customers.

Authorised Distributor for:

Commodore

Computer Systems and Peripherals.

Full range of business software --- excellent after sales service - operator training available.

PERSONAL COMPUTER

The completely integrated, low cost, versatile, personal computer for the home.

JUST RELEASED 8000 SERIES 8032 PROFESSIONAL **COMPUTER SYSTEM**

Basic 4.0; 32K. RAM; with larger 80 column screen.

8050 MINI-FLOPPY

Disc drive with capacity of 1 Megabyte (one million characters).



117a Henley Beach Rd.. Mile End S.A. 5031 43-7981 - 43-8324

MILEVILOVI

PROGRAMS

- **ODEBTORS**
- CREDITORS
- INVOICING
- **GENERAL LEDGER**

MAINTENANCE

Repair and maintenance of boards, drives and printers.

SALE OF CENTRONICS 779 PRINTERS

60 CHARACTERS PER SECOND FULL 132 COLUMN PRINT ABILITY 96 CHARACTER ASCII SET





Back door into BASIC

This is the first in a series of four articles that will explain BASIC programming from first principles, using the familiar pocket calculator as a starting point.

I GUESS all of you have used a pocket calculator? Well, you'd be surprised how much it has in common with a computer. The only major difference is that a computer is much more flexible — it does the same things, but more of them.

One thing a computer can do that most calculators can't is repeat a sequence of 'key presses' any number of times. Such a sequence is called a program and writing a program is simply the process of deciding what the sequence of key presses is to be.

Calculators

Let's take a closer look at a simple pocket calculator. It has ten keys with numbers on them and others with 'functions' like +, -, x and =. When you press the keys, complicated electronic circuits inside the machine respond by performing certain actions.



Figure 1. Block diagram of a simple four function calculator.

Figure 1 is a simplified diagram of how the calculator is organised inside. The block in the middle labelled 'clever bits' represents a lot of sophisticated hardware, but it's not necessary to understand how the hardware works to be able to use the calculator.

This simple kind of calculator has no 'memory' facility where you can store numbers for future use. For example, suppose you have a set of numbers and you want to multiply them all by 0.123949. On this kind of calculator you have to key in 0.123949 for every calculator.

lation, which is time-consuming and boring.

Phil Cohen

Calculators with memory

The next step towards a computer is the calculator with memory, which saves you the tedium of entering the same number over and over again. You can just enter the number once into memory and then pull it out with one keystroke at the relevant part of each calculation.

Figure 2 is a block diagram of a calculator with memory. Its memory can only store one number at a time.

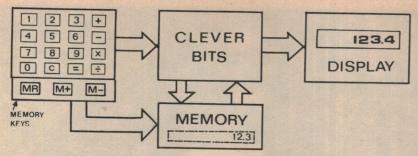


Figure 2. A calculator with memory is a little more complicated.

The memory control keys allow the user to control what the memory does. For example to put the number 0.123949 into memory all you have to do is key in 0.123949 so that it appears on the display, then press the M+ key, which enters the contents of the display in the memory. To 'recall' or 'read' the memory contents at any time during a calculation, you press the MR (Memory Recall) key. This is probably all very familiar to most of you, but it's worth going through it all because it ties in with what I'm going to say later about computer memory.


Some calculators have more than one memory, allowing different numbers to be stored in different places. In fact, some calculators have *hundreds* of memories, each of which can be independently 'written to' or 'read from'.

Programmable calculators

Although I said earlier that one of the differences between a calculator and a computer is that the computer can repeat a sequence of steps any number of times, there are in fact many calculators on the market which can also perform this feat.

So how do you tell a computer from a calculator? The answer is, "These days it's not easy." In fact, in a number of cases, the two terms overlap.

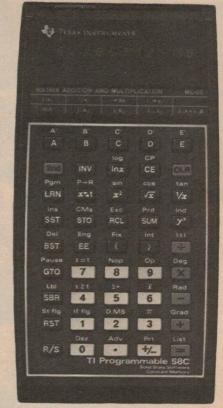We saw how a calculator with memory is useful when multiplying a whole set of numbers by a constant value. Well, what if you wanted to take the same set of numbers and *for each one* multiply by 15.698, subtract 34.697 and find the square root of the answer? You could start by putting 15.698 and 34.697 into two memories in the machine, but



Today's programmable calculators can do jobs which once needed a large computer.

you would still be left with a formidable number of key presses to get the answer.


To get away from all the repetition involved in such a calculation, the solution is to use a programmable calculator. This is a machine which can 'remember' a sequence of steps (such as x $15.698-34.697\sqrt$). You program the calculator with the sequence of steps you want it to carry out, then for each number in the set, key in its value and press the RUN key.

Pressing the RUN key will cause the calculator to go through the programmed sequence once. The great thing about this system is that, having got the answer for the first number in the set, you simply key in the next number and press RUN again. The calculator will then apply the same sequence of calculation steps to the new number

The program is fed into the calculator in much the same way as a value is fed into a memory — you press the PROGRAM key, which tells the machine you are about to program it, then simply press the desired key sequence. This enters the steps into a special group of memories in the calculator and when the RUN key is pressed this 'program memory' is read out, one step at a time, starting at the beginning and working through to the end of the sequence you originally keyed in.



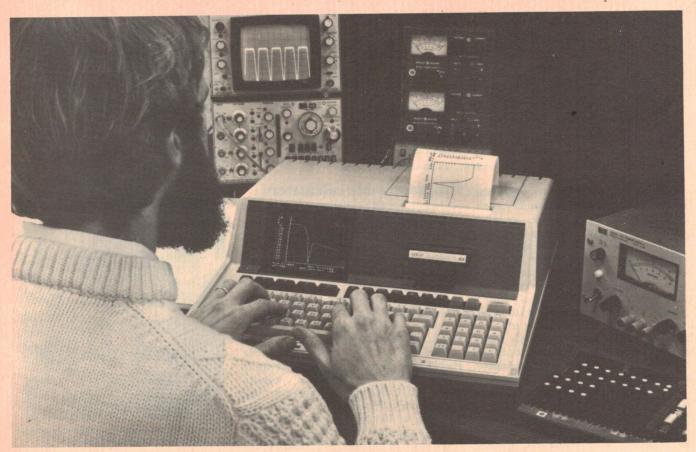The humble office calculator has several features in common with a computer.



A high powered professional microcomputer like this Hewlett-Packard HP85 is basically similar to the simplest home computer.

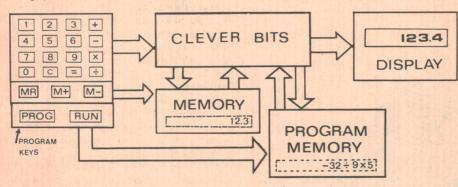


Figure 3 shows a simplified block diagram of a programmable calculator. By now we're getting close to a computer.

Computers

Figure 4 is a much simplified block diagram of the inside of a computer. As you can see, the program memory and the number memories have been lumped together into one area, which can be used for both purposes. In fact the computer will, at any given time, be using part of the memory for program storage and part for number storage. This is a very useful flexibility because some applications need a lot of program storage and very little number (or 'data') storage, while others need the opposite.

Figure 3. Programmable calculators have two distinct types of memory.

Programming a computer is exactly the same as programming a calculator. You fill up part of the memory with a sequence of steps (the program) which you want the machine to carry out.

The keyboard of a computer is a bit different to that of a calculator. Because the number of functions which a computer can perform is literally without limit, most computers use a keyboard more like that on a typewriter. For example, rather than pressing a key marked RUN, you press R, then U, then N. All the functions of the computer can

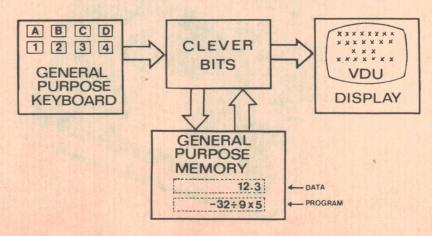


Figure 4. A computer has one large and versatile memory for both program and data.

now be designated by different 'keywords' or 'reserved words', instead of using one key per function like a calculator.

This sort of keyboard has other advantages too. The computer can not only store numbers and programs in its memory, it can also store letters - and these can be entered through the keyboard. This means that the machine can be used as a word processor - a machine that allows text to be typed in and then edited while still on the machine, so that it can be printed out free of errors and arranged in all sorts of different formats.

A computer display is different too. In general it's on a screen like a TV, which is usually called a Visual Display Unit (or VDU). This shows letters, numbers and symbols and usually has some sort of 'graphics' capability to enable the user to draw lines on the screen for tables, graphs and so forth. One of the problems with a programmable calculator is that you can't see the whole program at one time. With a VDU display, you can see whole pages of the program.

Languages

Naturally if you type the wrong word into the computer it won't do what you want it to do. For example, if instead of typing RUN you typed START, the machine would be confused. Computers can only understand certain words, just as a calculator only has so many keys. The vocabulary of a particular computer depends on what 'language' it uses. A language in computer terms means almost exactly the same as in human terms - it's an agreed way of writing things, which means the same to everyone.

The grammar of a computer language defines what order the words can be put in. For example, you can put 3 + 4 =into your calculator and get the right answer, but you can't put in = 3 + 4. Grammar is known as 'syntax' in computer jargon. Each different computer language has its own syntax rules, which govern the way the computer will interpret what is typed into it.

The three remaining articles in this series will deal with the syntax of BASIC, which is currently the commonest language for home computers.

Computer physiology

Before we get into talking about how to write programs, it's a good idea to say

something about what the average home computer consists of and how it works. It's not necessary to understand the 'anatomy' or detailed internal workings of a computer to be able to recognise the major functions, which we might call the computer's 'physiology'.

First of all, every computer has some kind of keyboard. These come in a variety of shapes, sizes and styles, but most of them look very much like typewriter keyboards. One difference that is easily noticed is the RETURN key. This corresponds to the carriage return on a typewriter and is usually found at the right hand end of the keyboard. Pressing the RETURN key has the effect of making the computer read what the user has just typed in. This allows you to

COMPUTER LANGUAGES

Various different computer languages are in common use for different purposes. The table below lists the principal languages and what they are used for.

LANGUAGE	EASE OF LEARNING	SPECIAL USES	COMMENTS
ALGOL	Medium	Scientific	Needs a fairly large machine
APL	Difficult	Scientific	Uses many special characters — most machines can't handle it
BASIC	Easy	Learners	Very common in home computers
COBOL	Medium	Accounting	Designed for efficiency, not ease of use
FORTRAN	Medium	Engineering	Very common in large machines
PASCAL	Fairly easy	General purpose	BASIC's only rival in home computers — but BASIC is easier to use

The California DC range of switching regulated power supplies is now available in Australia. The LR Series of open frame supplies provide size and weight savings over linear, series regulated supplies. Conservatively rated for long life, the LR Series was designed for use in computers, computer peripherals and industrial controls. They provide power for floppies, tape drives, memories and microprocessors. The range includes versions with up to four independant output voltages.

The power supplies range in price from \$170 to \$330.





Standard features include:

- Plus/Minus 20 percent line tolerance
- Inrush limiting on turn-on Individual output regulation of 1 percent
- Individual output current limiting with foldback
- Thermal protection
- 50 millivolt P-P output ripple and
- 0-40 degrees C convection cooling without derating • 70 percent minimum efficiency at

MicroPro Design Pty.Ltd.

PO Box 153, North Sydney, NSW 2060. Phone (02) 438-1220.



With Sinclair ZX80, for just \$295 you get everything you need including leads for direct connection to your own cassette recorder and television. The ZX80 really is a complete, powerful full-facility computer matching or surpassing other personal computers costing much more.

Two unique and valuable components of the Sinclair ZX80: the Sinclair BASIC interpreter and the Sinclair teach-yourself BASIC man-

The ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer because the ZX80's brilliant design packs the RAM so much more tightly. (Key words occupy just a single byte). You can add to the memory via the expansion port, giving a maximum potential of 16K.

Now available from:

EMONA ENTERPRISES PTY. LTD. CBC Bank Bldg., 661 George Street, Haymarket, Sydney. (02) 212-4815.

EMTRONICS

649 George Street, Sydney.

Order Form: Emona Enterprises P/L, PO Box 188, Coogee, NSW, 2034.
Ready-assembled Sinclair ZX80 Personal Computer, excl. mains adaptor\$295.00
Mains Adaptor \$16.00
Memory Expansion Board(s) takes up to 3K bytes\$28.50
RAM Memory chips — standard 1K byte capacity (6 IC's)\$10.00 ea. TOTAL\$
Please send further information and prices:
Sinclair Measuring Instruments SEW Test Instruments SEW Panel Meters Goodwill Test Instruments Oscilloscopes Audio Generators AC Millivoltmeters RF Attenuators
I enclose cheque/Bankcard. Total \$
© conicard unicome have
Name
AddressP'code

them off the screen to make sure that they are correct before committing yourself by pressing RETURN.

Some computers have a second keypad to the right of the typewriter-style one. This second keypad looks like a calculator keypad — it contains the numbers from 0 to 9. It's there because the standard typewriter layout is not ideal for keying in numbers - all of the number keys are in a row along the top of the keyboard.

When it comes to displays, the market is split between the more expensive machines, which have their own video screen built in, and the cheaper ones which plug into the back of a domestic


A normal screen layout is something like twenty rows, each containing about sixty characters (a character is a letter, a number, a symbol or a space). All but the very cheapest computers have some

type a full line of instructions, then read method of storing programs so that they can be recalled when you want to use them again.

For example, suppose you spent a whole afternoon writing a program to calculate compound interest. If you knew that you were going to need it again a week later you could go to the trouble of writing it down line by line so that you could type it in again the next week. But this would be timeconsuming and there would always be the possibility of making a mistake.

A much easier way is to design the machine so that it can take a program which is stored in it and convert it into a sequence of musical notes that can be recorded on a domestic cassette recorder. When you play back the cassette, the computer will listen to the notes and reconstruct the program from them. Some machines have cassette recorders built in, while others require the use of an external recorder.

> XXXXXX TV SET

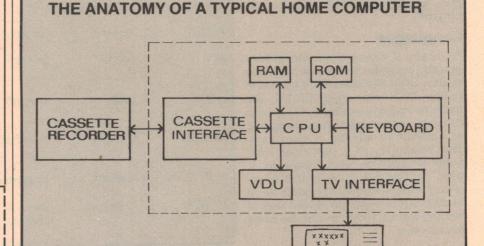

CPU stands for Central Processing Unit, home of the famous microprocessor. This part of the machine does all the thinking and corresponds to the 'clever bits' in a calculator.

RAM or Random Access Memory is where the computer stores all the numbers and programs that the user enters.

ROM means Read Only Memory. This is where the language is kept, in the form of an interpreter program that translates BASIC into a 'machine code' that the computer can understand. Data in ROM is permanently stored — it does not disappear when the power goes off, and it cannot be altered.


VDU stands for Visual Display Unit, a screen on which information is displayed in a form that humans can read. On most computers the VDU is fairly autonomous - it does not need to be refreshed all the time by the CPU, but can store a string of characters in its own memory and display them until the CPU tells it to change.

The Cassette Interface translates messages from the CPU into a code of audio tones suitable for recording on a cassette. It can also translate these tones back into machine code when the CPU needs the information again.

E-X-P-A-N-D YOUR SYSTEM



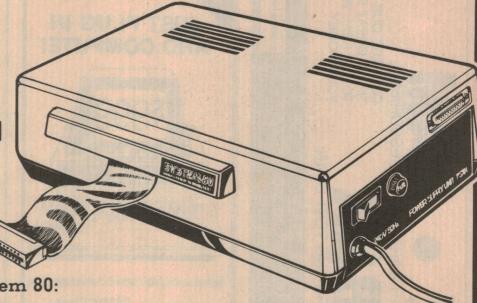AT LAST! THE **NEW SYSTEM 80** S-100 EXPANSION INTERFACE



Here's what it can do for your System 80:

- Give you a standard Centronics parallel printer port. (Suits most printers including our Dot Matrix (X-3255) and Daisy Wheel (X-3265) printers.
- Give you an RS-232C port with full 'handshaking' logic for connection to modems, etc.
- Give you the option of fitting extra memory: fit a RAM CARD with another 16K or 32K (available separately) — plus you can still fit another S-100 add-on board
- Give you a floppy disk controller (up to four drives) with external data separator for improved reliability
- Gives you the ability to use a cheap teleprinter instead of a parallel printer. Save a bundle!
- Gives you S-100 compatibility: so you can use many of the peripherals from hundreds of manufacturers: why be tied to one source of supply?

AND IT'S \$\$\$\$ CHEAPER THAN TANDY!

Apart from the massive savings on the computer itself, our expansion unit is over \$119 less than Tandy's (theirs is \$618.95 including RS-22C interface). And it offers you much more!

Cat X-4010

Freight \$6 Below cost anywhere in Australia

ONLY

Terms available to approved applicants

16K RAM CARDS TO SUIT S-100 INTERFACE

Comes with 16K fitted; with room for another 16K. You can have a 48K computer! And the savings can be massive!

Card (including 16K RAM) X-4016 \$199.00 (Tandy charge \$220.00!)

Second 16K RAM (Tandy charge \$220.00!!)

X-1186 \$59.95

IF ALL YOU WANT IS A PRINTER INTERFACE ...

We've got this economical parallel interface allowing you to run any Centronics-type printer direct from the System-80 — no expansion interface needed. And again, the price is a big saving over Tandy's!

Printer Interface: Cat X-4013



Connecting Cable: (suits Printer Inteface or S-100 Interface)

Cat X-4014

Electronics



L ADDRESS DETAILS

COMPARE OUR PRICES ON THESE GREAT PRODUCTS TO GET REAL VALUE FOR YOUR MONEY ETONE We also handle TRENDCOM

GENERATORS

50 PARK STREET, ABBOTSFORD, VIC, 3067. PHONE (03) 41-5708.

19 William Street, Alexandria, NSW 2015. Phone (02) 699-4334 JUST PLUG IN AND COMPUTE!

> **PERSONAL** COMPUTER

> > **USER 8K USER RAM** CASSETTE MONITOR

complete

Call in and see our

Microcomputer House

- Specialised custom software for all your business applications
- Software development
- Conversion from 16K to 32K
- Sound units
- · Exciting range of executive furniture for microcomputers from \$285.00
- Extensive range of technical publications
- All microcomputer supplies

Sole NSW agents for DATASOFT

- Business programmes covering a wide variety of standard business applications accounts, estate agent pack, hotel database, portfolio management, Wordpro II and III
- Games and simulations fast moving, quick thinking, exciting. See our extensive

TEACH YOUR PET NEW TRICKS Select your software and try now

Computer Country

"THE **MICROCOMPUTER** PROFESSIONALS"

Thinking of purchasing a microcomputer system or adding to the one you already have? Make a good investment - invest a little bit of time to talk to the professionals at Computer Country. Remember the quality of the aftersales hardware service and continual after-sales software and hardware advice you get is just as important as the price of the system you buy. Come and have a chat with the professionals of Computer Country just once and you'll realise how much help we can be in enabling you to get the most out of your microcomputer

Computer Country stocks a wide range of microcomputer hardware including the Apple, Northstar, Commodore, Texas Instruments, NEC, Impact Data and many more. We carry a wide range of software for many systems including the TRS-80. We can also help you in customising software for your specific application.

Our service department not only completely backs up all hardware purchased from us, but invites enquiries from those who have purchased elsewhere and have hard-to-fix problems.

MAKE A SMART MOVE - COME TO

Computer

Country

Pty. Ltd.


338 QUEEN STREET. **MELBOURNE, VIC 3000** (03) 329-7533

NEW!

"THE BIG BOARD" OEM - INDUSTRIAL - BUSINESS - SCIENTIFIC

SINGLE BOARD COMPUTER KIT!



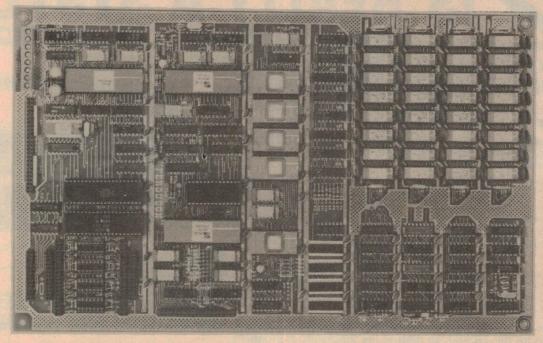

THE FERGUSON PROJECT: Three years in the works, and maybe too good to be true. A tribute to hard headed, no compromise, high performance, American engineering! The Big Board gives you all the most needed computing features on one board at a very reasonable cost. The Big Board was designed from scratch to run the latest version of CP/M*. Just imagine all the off-the-shelf software that can be run on the Big Board without any modifications needed! Take a Big Board, add a couple of 8 inch disc drives, power supply, and an enclosure; and you have a total Business System for about 1/3 the cost you might expect to pay.

\$695 · 00 (64K KIT BASIC 1/0)

SIZE: 8½ x 13¾ IN.

SAME AS AN 8 IN. DRIVE.

REQUIRES: •5V @ 3 AMPS

• - 12V @ .5 AMPS.

FEATURES: (Remember, all this on one board!)

64K RAM

Uses industry standard 4116 RAM'S. All 64K is available to the user, our VIDEO and EPROM sections do not make holes in system RAM. Also, very special care was taken in the RAM array PC layout to eliminate potential noise and glitches.

Z-80 CPU

Running at 2.5 MHZ. Handles all 4116 RAM refresh and supports Mode 2 INTERUPTS. Fully buffered and runs 8080 software.

SERIAL I/O (OPTIONAL)

Full 2 channels using the Z80 SIO and the SMC 8116 Baud Rate Generator. FULL RS232! For synchronous or asynchronous communication. In synchronous mode, the clocks can be transmitted or received by a modern. Both channels can be set up for either data-communication or data-terminals. Supports mode 2 Int. Price for all parts and connectors: \$95

BASIC I/O

Consists of a separate parallel port (Z80 PIO) for use with an ASCII encoded keyboard for input. Output would be on the 80 x 24 Video Display.

24 x 80 CHARACTER VIDEO

With a crisp, flicker-free display that looks extremely sharp even on small monitors. Hardware scroll and full cursor control. Composite video or split video and sync. Character set is supplied on a 2716 style ROM, making customized fonts easy. Sync pulses can be any desired length or polarity. Video may be inverted or true.

FLOPPY DISC CONTROLLER

Uses WD1771 controller chip with a TTL Data Separator for enhanced reliability. IBM 3740 compatible. Supports up to four 8 inch disc drives. Directly compatible with standard Shugart drives such as the SA800 or SA801. Drives can be configured for remote AC off-on. Runs CP/M* 2.2.

FOUR PORT PARALLEL I/O (OPTIONAL)

Uses Z-80 PIO. Full 16 bits, fully buffered, bi-directional. User selectable hand shake polarity. Set of all parts and connectors for parallel I/O \$45

REAL TIME CLOCK (OPTIONAL)

Uses Z-80 CTC. Can be configured as a Counter on Real Time Clock. Set of all parts: \$25

PFM 3.0 2K SYSTEM MONITOR

The real power of the Big Board lies in its PFM 3.0 on board monitor. PFM commands include: Dump Memory, Boot CP/M*, Copy, Examine, Fill Memory, Test Memory, Go To. Read and Write I/O Ports, Disc Read (Drive, Track, Sector), and Search. PFM occupies one of the four 2716 EPROM locations provided. It does not occupy any of the 64K of system RAM!

CP/M* 2.2 FOR BIG BOARD

The popular CP/M* D.O.S. modified by MICRONIX SYSTEMS to run on Big Board is available for \$150.00.

REGISTERED PACK & POST \$5.00 DELIVERY

TERMS CASH CHEQUE OR BANKCARD (MIN \$100 DEP)

ALL PRICES PLUS TAX IF APP
DELIVERY 3-8 WEEKS ON ORDER

¥

RITRONICS WHOLESALE

425 HIGH ST., NORTHCOTE VIC 481 1923 489 7099 PO BOX 235

Bankcard Mail Orders Welcome
Please debit my Bankcard
Bankcard No
Expiry Date
Name
Signature

AT LAST. THE SYSTEM 8 IS REALLY A SYSTE

NOW YOU CAN BUILD YOUR SYSTEM 80 INTO A SUPERB COMPUTER SYSTEM.

This is Australia's fastest selling microcomputer: the superb System 80 available only through Dick Smith Electronics (& authorised re-sellers).

However, until now, there has been a problem. The System 80 hasn't really been a system at all. Like a car without a tow-bar: useful, but limited in what you could do with it.


Now all that has changed: we're proud to announce the release of the System 80 Expansion Interface. The System 80, through its S-100 expansion interface, now has the potential to be used with hardware and software devices from over 200 manufacturers. S-100 is fast becoming the industry standard, which means you aren't tied to any single one supplier for add-ons. A single supply source means that prices can — and usually are - sky-high because there is no competition.

So now we expect the System 80 to really boom - not just to hobbyists, who've had it all their own way until now - but to businesses, to students, to housewives, to industry ... There are virtually no limits to the System 80 system. All it takes is imagination.

And don't forget: software requirements for the System 80 are virtually the same as for the TRS-80: so most of the thousands of programs written for it will also run on your System 80 system!

(4K RAM. LEVEL II Cat X-4003)

16K RAM, LEVEL II MODEL (Cat X-4005)

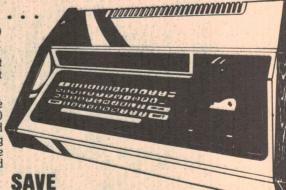

INDREDS OF LLARS OVER EQUIVALENT **COMPUTERS AND HARDWAR**

The System 80 will run with any TV set: but in case you need a monitor, check this one out! P.S. This monitor will also work with most other microcomputers. Compare our prices and \$ Cat X-1196

USE WITH COMPUTER!



NEW SYSTEM 80 SOFTWARE -

FOR FUN & EDUCATION

Here are five recently released software tapes for the System 80 (also suitable for the TRS-80 Level II). They're fun to play and they're educational, too.

X-3688 "DEATH TRAP"

In this fast-moving realtime graphics game you have to control the motion of a constantly-moving point on the video screen and avoid randomly-appearing "mines" until an "escape window" appears. You can't cross your own trail, or hit the sides of the screen either. If you escape, you get further tries

only it gets tougher! Has
sound effects. Requires 16K.

X-3692 "SPEED READING COURSE

A set of programs supplied on two cassettes, designed to help readers of all-ages to improve their reading skills. The programs have been developed from the West Australian Reading Development Scheme. Requires 16K.



\$9.95

SPEED READING

\$19.95

X-3694 "LEARNING FUN 1: SCURVE INVADERS"

Combines basic maths drill with the ever-popular "Space Invaders" game. Before being able to take each shot the player feeds in the "correct data". Sound effects, three levels of difficulty. Requires



\$9.95

X-3696 "LEARNING FUN 2: HANGMAN/CONCENTRATION"

Two programs. Hangman is complete with animated graphics "man" getting hung. The words chosen by either the program or a second player. Concentration: two players or teams have to match prizes behind numbers on the screen, then try to guess the mystery food word. Requires 16K.



\$9.95

X-3698 "LEARNING FUN 3: ALPHABET COUNTDOWN/RHYME TIME"

In Countdown sets of words taken at random from a large group must be placed in alphabetic order. Rhyme Time displays a series of unfinished displays a series of unfinished thymes, and the player has to type in the missing word from the clues given in the rhyme itself. Requires 16K.



\$9.95

BARGAIN PRICED MINI DISK DRIVE

\$200 less than Tandy's equivalent You'd pay over \$1000 more from Tandy for a 4drive system! This incredible drive is worldfamous Pertec brand; offers higher capacity than Tandy drive and will work with System 80 or TRS-80. Ask for more info. at your nearest Dick Smith store X-3230

Unbelievable prices for either hard or soft sectored mini diskettes. Suit virtually all disk drives available. Buy from Dick and save a

Hard Sector (X-3505) Soft Sector (X-3510)

Trade enquiries

WERE \$5.95 EAI NOW:

1 - 10: \$4.95 10 - 100: \$3.95 100 UP: \$3.50

ITOH 8300P BUDGET PRINTER

For budget printing, you can't go past this one! Uses standard tractor-feed paper, gives high quality print from its 7x5 dot matrix. Up to 240mm paper, prints 125 chars/sec. For either System 80 or TRS-80. Cat X-3255.

40/80/132 CHAR/LINE

Uses Printer interface and cable below



FAN-FORM COMPUTER PAPER TO SUIT ABOVE PRINTER. 2000 SHEETS

Cat X-1189

\$35.00

LETTER QUALITY

For top quality print, try this: it's over \$300 cheaper than Tandy's daisywheel, and is capable of proportional printing! Limited stocks



PROGRAM CASSETTES

16K MEMORY EXPANSION KIT

.\$7.90 ea.

Popular C-10 computer cassettes (just the right size for programs!) with computer-quality tape. Suitable for all 'compact cassette' type units (which everyone uses!) Cat X-3500



Were almost \$100 more twelve months ago! Fast 250nS 4116

RAMs, for up-grading your 4K

Cat X-1186 5095

Cat Z-9310

Also available individually:

DON'T NEED FULL S-100 **EXPANSION?**

Use this parallel printer interface if you don't need full S-100 expansion. Save a bundle! Uses similar connecting cable to S-100 interface

PRINTER CABLE Cat X-4013



Fitted with edge connector at one end, 57N-36 plug at other: suits virtually all Centronics-type printers. Use with either S-100 interface or parallel printer interface.

Cat X-4014

SOUND OFF

Add sound to your System 80 programs! Includes amp, programs and full instructions You can add sound to existing programs too! Also suits TRS-80.

Cat X-3648

EDITOR/ASSEM-**BLER PLUS!**

Editing, assembling & debugging power you've never had before! Equivalent of Tandy's Editor/ assembler and T-bug products but in one package and at less than half the price! And t's far more powerful! System 80 & TRS-80.

MICROSOFT



LIGHT PEN BARGAIN! Cat X-3645

The best value around Gives your System 80 or TRS-80 an eye. Easy to use, has simple programs



Cat X-3680

OMPUTER HOT

SOFTWARE for System 80 or TRS-80

GAMES AND EDUCATIONAL SOFTWARE CURRENTLY AVAILABLE

TIME TREK \$17.95

You're boldly going where no man has gone before ... Mind you, those pesky Klingons attack you from time to time, so you'll need fast reflexes as well as sharp wits. Nine levels of difficulty. Cat X-3650

STIMULATING SIMULATIONS

No less than 10 different games: all fascinating and original. Art Auction, Forest Fire, Monster Chase, Nautical Navigation, Lost Treasure, Business Management, Gone Fishing, Rare Birds, Space Flight and Diamond Thief. Cat X-3652

ELECTRIC PAINTBRUSH \$17.95

This is a special machine language 'graphics interpreter' program, which lets you program dazzling graphics displays using simple high-level commands. Easy—and fun! Cat X-3654

BRIDGE CHALLENGER

Keen on Bridge? This game never gets tired of playing with you. Ideal for practising and improving your level of play – whether you're an expert or just a beginner. Needs a 16K machine. Cat X-3656

MICROCHESS

Think you're a wizz at chess? This program will put you to the test! But think out your moves carefully: the computer is out to beat you! One of the top selling chess programs in the USA. Cat X-3658

You'll need fast reflexes and good co-ordination for this one. It's written in machine language so it can give really high speed graphics. Try to force your opponent into a collision with a moving wall: without running into a wall yourself!

Cat X-3659 PUNTER'S DREAM PUNIER S DREAM S12.50
Place your bets, please the race is about to start! Study the form of the various horses before placing your bets. Then the race is on! The program looks after the betting accounts of up to nine punters, and can even cream off a percentage for the house! You get a realistic simulation of racetrack probabilities. Use it for fun: or to improve your strategies! Needs a 16K machine. Cat X-3660

Like playing the one-arm bandits down at the club? Here's one you can play seated at your friendly System 801 Tell the machine how much you want to spend, and it will feed it through. Watch the handle go down, the reels spin, and your money go! Then experience that familiar thrill when you hit a jackpot. Needs a 16K machine. Cat X-3661

MATHS/SPELLING Here's a great way to coach spelling and maths: imagine how much mo interesting the lessons are if the computer is giving the problems! Help stamp out illiteracy and poor spelling – this great program can help, you do it! Cat X-3662

AIRMAIL PILOT You're back in the early days of aviation. You must get the mail through in the shortest possible time. Your cloth-covered bi-plane must take you through unpredictable winds and electrical storms — can you make it? Cat X-3663

INTERLUDE

This is the adults-only game for your computer. After the kids have gone to sleep, let the computer give you ideas for the rest of the night! It comes with a 'comprehensive instruction manual! (Note: this program is NOT available to any person under 18 years of age). Do not purchase this program if you are easily offended. Needs a 16K machine. Cat X-3675

SIMUTEK 1 Not just one, but FIVE superb space fantasy games. Includes Graphic-Trek 2000 (try to dock the Enterprise with the space station without being shot down!), Invasion Worg (protect the Earth), Star Wars (get in to the Death Star, plant a Bomb and get out again!) Space Target (a battle game) and Saucers (an action graphics game). Complete with instruction book. Needs 16K. Cat X-3685

Like a game of poker? He's a pretty shrewd player – hard to beat, although it ca be done. Has really intriguing graphics; needs 16K machine. Cat X-3664

NOW AVAILABLE SYSTEM 80

48 pages of data, technical information, service data, minor modifications, etc. etc. Great for technically minded people with their own computer.

MANUAL



Cat B-6210

DICK SMITH ELECT



SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS

Matrox video boards reviewed

Craig Barratt

This article looks at two stackable S-100 video graphics boards, the ALT 256 and the ALT 512, both from Canadian manufacturers Matrox.

THE PRICE OF video display units is falling all the time and their high speed and flexibility are making them the most popular output device. But their vast potential cannot be properly realised without a fairly sophisticated board to drive them. At the high end of the video board market are a range of boards from a Canadian company, Matrox. Their Australian distributors are Measuring and Control Equipment Company, of Epping in New South Wales.

Matrox's range of boards may be broadly divided into two categories, alphanumeric and graphic displays. Both of these display types are available in a variety of bus structures, including S-100, Multibus (the SBC-80 bus from Intel), LSI-11 and a variety of stand alone modules.

The alphanumeric boards have display formats starting with eight lines by sixteen characters, right through to boards with 24 lines by 80 characters. Character fonts vary between 5 by 7 upper case only and 7 by 9 upper and lower case. One board has its characters sitting in a 12 by 14 matrix and is intended for a public information environment. Some boards have special features such as software programmed display formats, colour, character blanking, inverse video and variable intensity. All the boards are memory mapped, which means the microprocessor simply writes into certain memory locations to make characters appear on the screen.

The range of graphics boards is just as extensive. Display formats include 256 by 256 dots, 256 by 512, 512 by 512 and even a 256 by 1024! These boards are

I/O mapped and the features on some boards include colour, variable intensity and software programmed display formats.

Stacking boards

This seems all very well, but two problems become evident. Firstly these boards are obviously designed for the American market with a 60 Hz frame frequency and would seem unsuitable for use in Australia. This however is not a problem since Matrox have provided a series of jumper options which may be arranged to provide 50 Hz/312 line operation.

Secondly it would seem that a graphics board would need its own monitor, or you may need to switch either the alphanumeric or graphic video line through to your monitor. Matrox have overcome this problem by making their boards stackable. This means that a graphic and alphanumeric board may be combined to produce graphics and alphanumerics simultaneously on your monitor.

The only special requirement for stacking boards like this is that all boards derive their timing from one source, in other words one board must be a master and the others slaves. Most of the graphics boards and some of the alphanumeric boards have jumpers to select master/slave operation and these boards have 16 pin connectors with all the relevant signals.

Another more useful but not so obvious application for stacking boards is to have several graphics boards in a system and use each of the boards to provide grey level, colour, flashing or some other information particular to


each bit on the screen. Thus if you want a display with 256 by 256 bits, four grey levels, four colours, and a flashing bit for each dot on the screen you simply plug together five 256 by 256 by 1 Matrox graphics boards and add some of your own electronics, to give a 256 by 256 by 5 display. Now you know what to do when you win the pools!

The ALT-256

You wouldn't have guessed it, but the purpose of this article is to review an S100 graphics board from Matrox, the ALT-256. This board has only one bit per pixel (dot on the screen), in other words each of the 256 by 256 pixels may only be switched on or off. If you want colour or several grey levels you will have to stack two or more of these boards together as explained above.

The board occupies four output ports and one input port. The base address of these I/O ports is set to any multiple of four using wire jumpers on the board, and a functional breakdown of these I/O ports is provided on page 115.

As shown in figure 1 pixels are addressed with x and y coordinates. The x value for a pixel is the column number of that pixel, with the left column having x = 0, and the y value is the row number of that pixel, with the top row having y = 0. This means that the top left pixel has coordinates (0,0), and the bottom right pixel has coordinates (255,255). So to address a given pixel we simply write its x coordinate to port b+1, and its y coordinate to port b+1, and its y coordinate to port b+2, where b is the base address of the I/O ports. Having set up the x and y registers of the graphics port we may now set

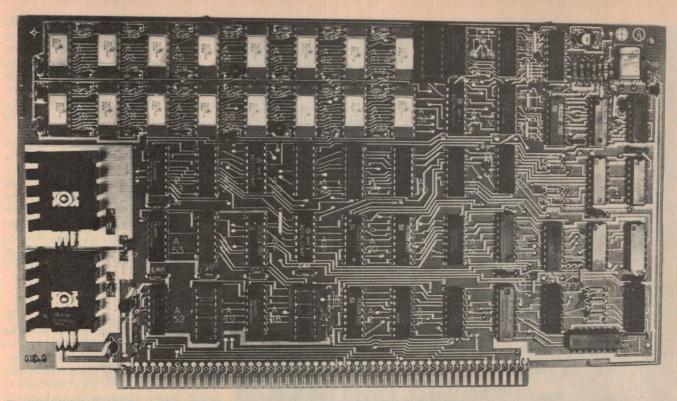

The ALT-256 video board provides a rock steady 256 x 256 pixel display with no flickers during screen accesses.

or reset that pixel. To reset that pixel we write a 0 to port b+0 and to set it we write a 1 to port b+0.

We may also erase the screen by writing to port b+3. Writing a 0 will clear all pixels and writing a 1 will set all pixels. Erasing the screen obviously isn't instantaneous, and in fact takes between 20 and 40 milliseconds (one and two frame times) and new commands issued during erase time will have undefined effects. To avoid this an input port has been provided with two status bits. The bottom bit (bit 0) is high if the display is busy (being erased) and low if the display is ready to accept commands. Bit 1 is low if the video portion of the screen is currently being scanned, and is high during vertical blank. Although setting and clearing

bits doesn't put flickers on the screen, this bit is useful for things like animation, where it wouldn't be desirable even for one TV frame to have half of a new image and half of an old image on the screen. The idea is that the processor should do all its screen manipulations during the vertical blank period.

Software interface

Obviously most programs that use graphics output will not use the graphics board at such a low level. Such an approach would be very clumsy, and all programs would have to be modified if a new and different graphics board was required for some reason. There are two good software solutions, one from an American company called Sublogic and another courtesy of myself.

Sublogic have written what they have called a Universal Graphics Interpreter. The idea is that programs produce a file of data for the interpreter, and the interpreter then looks at this data and draws the corresponding lines and pictures on the screen. This has the advantage that if your hardware changes, you only need a new interpreter while all your programs and data files need not change.

Interpreter commands include drawing lines, dots, polygons (shaded or unshaded), ellipses, moving the cursor or origin and setting various display modes. Things may be done single precision (8 bit) or double precision (16 bit) and the interpreter does its best to fit what you want done onto the display for which it was written.

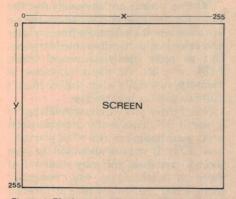


Figure 1. Pixels are addressed with x and y coordinates.

TABLE OF I/O PORTS

Write ports:

b+0 Dot intensity

b+1 X address


b+2 Y address

b+3 Erase


Read port:

b+0 Status

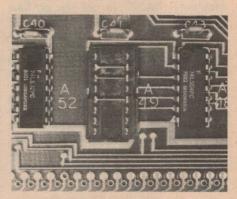b is the base address of these ports and is any multiple of 4.



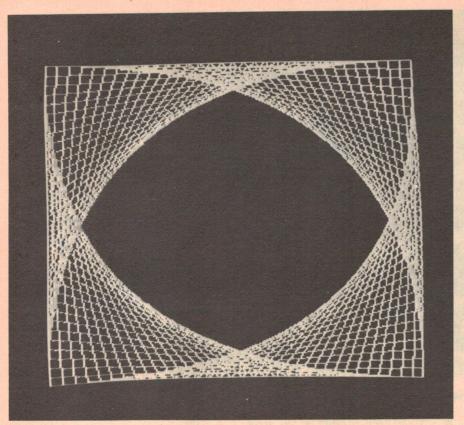Jumpers convert the board from 60 Hz to 50 Hz operation.



Writing the program to generate a pattern like this is very difficult if you use BASIC. It's relatively simple in PASCAL. A related pattern is shown on the facing page, together with the program used to generate it.

While this approach is a good one you would really need at least one disk drive and a good operating system to use the software package effectively.

Unfortunately the wrong Sublogic interpreter was given to us with the board, so we never got a chance to use it. Obviously we needed some method of drawing pictures for the photos you can see in this article.

All we wanted was three functions: clear the screen, set or reset a dot and draw a line between two points. These individual functions should really be written in assembly code for speed and should be linked into some higher level language. BASIC is not the obvious choice, and is about the worst choice we could make for this task. The juggling of variables required and the difficulty in interfacing assembly code subroutines (let alone passing parameters to them) ruled out BASIC. In fact a good langauge to choose is PASCAL and the above assembly code routines were quite easy to link in as procedure calls, with parameters passed in the usual fashion.

The PASCAL program that produced the triangle pattern is shown on page 117.

The hardware

Having covered the software aspects of the ALT-256, it would be a good idea to look at its hardware, and our impressions of it.

On the plus side the boards are stackable, and may be selected for 50 or 60 Hz operations, as explained above. Besides these there are only two other nice aspects of the hardware that deserve mention. These are that there are no screen flickers during processor accesses, and the picture on the screen is rock stable.

In the category of "nasties" there are more than just trivial things, which isn't very satisfactory. The major shortcoming of the board we feel is that you cannot test a bit on the screen. In other words the board has write only memory (or WOM). This may not seem to be a problem if you are using Sublogic's interpreter but if you are writing interactive software, games or simply drawing pictures with a joystick you have to maintain a duplicate copy of the screen in system memory. This slows down screen accesses, because the duplicate copy has to be updated as well, and complicates programs quite unnecessarily. We cannot understand why such a feature on a supposedly very good board was omitted.

The second non-trivial shortcoming is that the position of the video data with respect to the vertical and horizontal synch pulses is fixed, in other words you cannot move the picture up and down or left and right to centre it on your monitor screen. Although on our monitor the whole picture was visible, it certainly wasn't centred, and it is quite possible that with some monitors it would be necessary rather than just nice to be able to move the picture.

The only trivial hardware "nasty" of the board is that it is 145 mm high—even though Matrox's catalogue specifies that the ALT-256 is a 135 mm board. This is only a minor detail but if the accepted thing is to have 135 mm cards, why make one that is 145 mm high? Anyhow, just be careful if you want to plug this card into a close fitting card cage—you may not be able to get the lid on!

The ALT-512


This board is the big brother of the ALT-256, and is the only other S100 graphics board that Matrox makes. There are no prizes for guessing that its display format is 256 by 512 by 1, but that is only half true. The ALT-512 allows you to select under program control one of eight display modes, including 256 by 512 by 1, 256 by 256 by 2 (4 grey levels) and 256 by 256 by 1. In the last mode the processor may write into one 256 by 256 by 1 plane while the other plane is being displayed, which is ideal for applications in animation.

The price

Both the ALT-256 and ALT-512 are available from Measuring & Control Equipment Co Pty Ltd. Their postal address is P.O. Box 78, Epping, NSW 2121, and their phone number is (02) 86-4060. These two boards are available only in assembled and tested form, and come with a three month warranty. Now for the bit that hurts; the ALT-256 will cost you \$474 and the ALT-512 considerably more at \$695. Neither of these prices include sales tax, so you will have to add another 15% if you have to pay tax.

Matrox boards are obviously just the thing for the OEM market where people are after assembled hassle free modules and price is a more minor consideration. But as most hobbyists would think, \$474 is a lot for eight kilobytes of memory, especially when the board isn't quite as good as it should be.

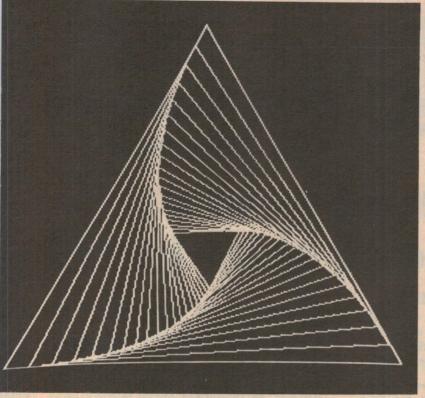Now I think you will be wondering "Is it worth it?". This really depends upon what your budget is and what you may need it for. If you are about to buy your second hard disk, you may want one of these to brighten up your computer room, but if you have to save up for each month's ETI, you needn't think about buying a Matrox board yet.



```
program triangle;
   uses drawline;
   const ratio = 0.06;
   var new, old: array [1..6] of real;
       count, count1: integer;
procedure newpt(var x1,y1 : real; x2,y2 : real);
var m, b : real;
begin
    line(round(x1),round(y1),round(x2),round(y2),1);
    if x1<>x2 then begin
         m := (y2 - y1)/(x2 - x1);
         b := y1 - m * x1;
         x1 := x1 + ratio * (x2 - x1);
         y1 := m * x1 + b
    end
    else y1 := y1 + ratio * (y2 - y1)
end:
begin
    clrscr;
    new[1]:=128;new[2]:=0;new[3]:=0;new[4]:=255;
    new[5]:=255;new[6]:=255;
    for count := 1 to 20 do begin
       for count1 := 1 to 6 do
          old[count1] := new[count1];
       newpt(new[1],new[2],old[3],old[4]);
       newpt(new[3],new[4],old[5],old[6]);
       newpt(new[5],new[6],old[1],old[2]).
    end
end.
```


Micro Computers From INDUSTRIAL MICRO SYSTEMS SERIES 8000: SYSTEMS WITH TIME PROVEN COMPONENTS

SERIES 8000

Regardless of the size of machine you choose, there's room inside for up to 256k of IMS RAM with memory management. And the integrated floppy disk capacity is pretty impressive too — more than a million bytes per drive! You can start with a single 8" drive, then install one or two more when you need it — all in the same cabinet. The Series 8000 System's power supply and disk controller are made with this kind of expansion in mind so growing is simple. And our Z-80 computers have features like serial parallel 1/0's, clocks, PROMS on board so that less slots are used on the S-100 12 slot motherboard, giving more space for extra RAM or special purpose boards.

Because the system is S-100 and CP/M based you can run all of the programs written for use with CP/M systems. (Like CBASIC, FORTRAN, COBOL, PASCAL, C, ALGOL, WORDSTAR etc). And you can go multi-user as well!

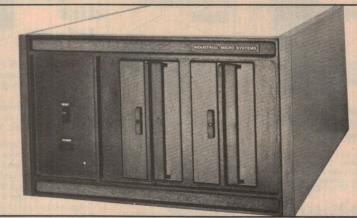CALL US FOR MORE INFORMATION ABOUT THIS SYSTEM OR IT'S LITTLE BROTHER WITH THE 5" DISKS — THE SERIES 5000.



S.I. MICROCOMPUTER PRODUCTS PTY LTD

GPO BOX 72 SYDNEY 2001 92 PITT ST SYDNEY (02) 2314091 2326804

Distributors: Mark Dewhirst, 428 St Kilda Road, Melbourne, VIC 3004. Tel (03) 26-5522.

Bruce Lipscombe Computer World, 98 Main Road, Moonah, Tas. 7009. Tel (002) 28-6288.

The Rolls Royce of persona computers or the basis usiness system

Yet the Sorcerer will still cost you less!

Looking for a really serious small computer? Feature for feature, dollar for dollar, the Sorcerer is way out in front. When you've finished playing with the others, move up to the Sorcerer.

FROM S. ONLY Credit terms

available to approved applicants

Cat. X-3000 Cat. X-3001

\$1340

8k Memory 16k Memory \$1395

P&P \$5.50 per unit

- Up to 48K RAM on board with full S-100 expansion for a huge number of peripherals, etc.
- User-definable graphics and full upper & lower case character set as standard; also special character set.
- Plug-in ROM PACS™ give you instant changeover for special applications: Word processing, software development, etc. Or your own custom programs, using the EPROM PAC.
- Numeric keypad as well as full 63 key ASCII set.
- Centronics-type printer interface & RS-232C communications port built-in as STANDARD!

look at our prices for peripherals

Video Monitor



Suits Sorcerer, Tandy TRS-80. Apple etc.

Why waste money on overpriced monitors? This unit has large 30cm diag, screen plus it simply connects to your computer via an RCA socket. 240V AC or 12V DC operation.

14950 X-1196 PAP \$5.50

S-100 Expansion



Use other manufacturer's peripherals with your Sorcerer & S-100

For the serious computer owner Contains powerful computer power supply plus buffer/interface circuit to protect the computer in case of damage to the S-100. Plus many more benefits

X-3010 P&P \$5.50 Floppy disc drives



Need more storage? Floppies are the way to go. Quality Micropolis disk drives added on to your system can give up to 1260K bytes capacity!

Start with the Micropolis 1043 - it comes with the controller board to plug into your S-100 expansion unit. This gives you 315K.

If you want more capacity, use the Micropolis 1023 drive: it uses the 1043 controller board, so it's cheaper - much cheaper (\$600 to be precise!) You can add up to three 1023 drives, bringing your total capacity to over one and a quarter megabytes! Compare the cost of our 1.26M system with others - and be pleasantly surprised.

X-3205 \$1350.00 X-3208 \$750.00

ROMPACS"

Just plug them in they instantly re-program the Sorcerer for specific uses. No problems!

WORD PROCESSOR PACT

Want professional quality Word processing at a fraction of the cost of commercial systems? Your Sorcerer, Word Processor Pac and our daisywheel printer . . and you Cat. X-3085 \$275.00 you're there!

DEVELOPMENT PACT

If you're serious about developing your own software, this is a MUST! turns the Sorcerer into a powerful, dedicated development system for Z-80 assembly language programming. Cat. X-3090 \$139.50

EPROM PAC"

The Sorcere is ideal for dedicated uses: this PAC allows an EPROM to be used to control the computer. Ideal for all types of control. systems, etc. Cat. X-3095 \$75.00

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS





per pack Including postage & packing

PROGRAMS ON CASSETTE WITH FULL DOCUMENTATION ALL PROGRAMS RUN ON BASIC ZX80 SYSTEM UNLESS OTHERWISE STATED.

ZX80 COMPANION 87 PAGE BOOK

Book is arranged so that the intending user of the ZX80 entering computing may start using the system and gradually gain a better appreciation of the machine and facilities. The informed computer user will find the later sections useful in applying his knowledge to the ZX80 which has brought a breath of fresh air to the personal computer

Linsac Software comes on C12 Cassettes with Full Documentation including Program Listing
 User Instructions
 List of Variables with Meanings Program Description
 Sample Program Run

GAMES PACK ONE CONTAINS

G001 Three Towers

Rearrange the rings to build a new tower

G002 Number Guessing

Find the hidden number with hints from the ZX80

G003 Mastermind

Break the four digit code.

G004 Sketcher

Draw patterns of your choice with memory mapping.

G005 Hurkle

Hunt the horrible hurkle in the 15×15 grid.

G006 Nim

The familiar game of skill.

G007 Symbol Simon

Try and match the complex increasing pattern.

GAMES PACK TWO CONTAINS

G008 Nine Lives

A word game for two players — possibly fatal.

G009 The Maze Game

Find the treasure as the maze grows around

G010 Plain Sailing

Steer a yacht against dangerous currents.

G012 Noughts & Crosses

The ZX80 plays an excellent strategic game.

G013 Chinese Puzzle

Can you rearrange the blocks in the right way?

G014 Tower of Hanoi

The game of antiquity.

G015 Battleship

Realistic naval artillery action.

GAMES PACK THREE CONTAINS

G011 Fruit Machine (2-4K)

The ZX80 as a one-armed bandit.

G016 Four in a Line (4K)

A 2 player game arranging patterns of counters.

G017 Zombies

You are surrounded by zombies on a desert island

EDUCATION PACK ONE CONTAINS

E001 Maths Drill

Two levels of aifficulty included.

E002 Dot recognition

Recognise the number of a random dot pattern.

E011. Musical Notes

Teaches children notes on the scale.

E004 Spelling Quiz

The teacher sets five words to be tested.

E007 Day Finder

Gives the day of the week for a date.

EDUCATION PACK TWO CONTAINS

E005 Graph Plotter

Plots quadratic equations.

E006 Prime Factors

Calculates prime factors of given numbers.

E008 Number Bases

Conversions and calculations in different

E009 Bar Charts

Plots bar charts from supplied data.

E010 Statistics

A collection of statistical routines.

UTILITY PACK ONE CONTAINS

U001 Memory Display
Displays 80-byte blocks of memory (char/hex).

U002 Hex Code Monitor

Handles machine code routines.

U003 Renumber

A full renumber routine

U004 Memory Search

Finds and displays byte patterns. C-12 CASSETTE ORDER FORM SINCLAIR EQUIPMENT (AUSTRALASIA) PTY. LTD. 308 High St., Kew 3101, Vic. Tel. 861 6224

Item	Quantity	Total
Games Pack One		
Games Pack Two		
Games Pack Three	300,000	O TO SE
Education Pack One		
Education Pack Two		Sitta hay
Utility Pack One		
ZX80 Book		
	Total	
	AND DESCRIPTION OF	

Postcode



Discover the exciting world of microcomputers, profit from programming and applying these technological wonders. With the Applied Technology MICROMODULE family you can learn as you build these affordable, versatile and powerful kits. Based on the popular Z80 microprocessor and the industry standard S100 bus, MICRO-MODULES can be built up to any configuration from a simple 2 board system (INSTRUCTOR 80) to 64K systems with floppy disks, high speed printer suitable for process control, word processing and business systems.

INSTRUCTOR 80

The ideal starter system comprises DGZ80 kit with 1 K RAM and DGOS ROM operating system, DG640 VDU kit, full function ASCII keyboard, 3 slot mother board and 2 x S100 sockets. Full assembly manuals are included, together with a simple programming course and sample programs to run. You add a simple power supply (8V) and a modified TV set and you have a complete computer system.

INSTRUCTOR 80 KIT

\$399.00.

COETWARE

Microworld 12K Basic for Z80. If purchased with DGZ80. Microworld Editor/Assembler. Games Pack 1. (Target, Trek). Utility Pack 1.	\$14.75. \$14.75. \$14.75. \$14.75. \$5.50.
PCG Chess (If purchased with PCG).	\$5.50.


NOTE. PRICES INCLUDE SALES TAX. Specifications and prices subject to change without notice.

MICROMODULE FAMILY.

HAKUW	AKE.	
DGZ80	CPU	Kit v

HAKUWAKE.	
DGZ80 CPU Kit with 1K RAM	\$199.25.
DG640 VDU Kit - 64 characters x 16 line format,	
upper/lower case and graphics	\$149.50.
TCT 16K EXPANDA RAM using static RAMS.	
- with 4K RAM.	\$139.50.
- with 8K RAM.	\$179.50.
- with 16K RAM.	\$259.00.
TCT PCG (ETI June 1980) adds fine graphics to DG640	\$140.00.
SCVT-100 (EA Oct 1980) Serial Terminal.	\$189.50.
2650-S100 2650 on the S100 bus.	P. O. A.
JC100 9 slot mother board plated through holes and	
provision for power supply.	\$49.50.
JC200 Card Frame for JC100 mother board.	\$49.50.
JC300 S100 Power Supply 8V/8A, 15V/15V 2A with	
computer grade components.	\$67.50.
SECI Cassette Interface.	\$24.50.
SEUI GASSELLE IIILEITAGE.	45 11001

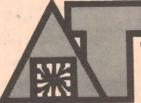EA/MODEM 300 BD Modem Kit (See EA September 1980) Clare C70 Keyboard.



SECI Cassette Interface.

\$69.50.

\$165.00.

MAIL ORDERS TO:

PO Box 311, Hornsby 2077

Please add \$2.00 per order towards cost of post and packing.

OFFICE/SHOWROOM

1a Pattison Avenue, Waitara 2077 Hours: 9-5 Monday to Saturday Telephone: 487 2711

AND NOW AT GOSFORD -

1 Debenham Road, West Gosford (behind the Pizza Hut)



Micros invade the communications world

Microprocessor technology has begun to change the style of radio communications equipment, making it lighter, more effective and easier to operate and service.

F.E. Phillips

THE INCREASING use of large scale integration and particularly the microprocessor has had a major influence on product design to the extent that modern radio communications equipment is becoming rather like the snack bar menu, 'chips with everything'. Almost no area of communications is escaping the relentless onslaught of the increasingly powerful microprocessor and other associated LSI products.

Chips are finding applications in control and display functions as well as providing memory and computing functions. In the near future we can expect that they will be used for improved fault location and diagnosis; circuit operations like frequency synthesis and automatic gain control; demodulating, decoding, handling and printing of data; and as the controlling link between synthesisers and preselectors.

An added benefit of the use of LSI is the general reduction in both size and weight over the modules that they replace. This is particularly apparent in the military field, where reduction in size and weight of manpack equipment, the simplification of controls, and the growing need to be able to handle data efficiently are the predominant issues.

Ease of operation

But the services have one problem that they share with industry. They too find it increasingly difficult to recruit and train personnel of consistently high calibre. Consequently, unless the new equipment can be operated and serviced effectively — the advantages in performance will be largely lost. This problem has been closely studied by communications equipment designers. The solution has been to incorporate microprocessors into communications



The Redifon R1006 receiver can control up to 99 remote receivers over any distance by ordinary telephone lines or radio links as appropriate.

equipment; thus the intelligent receiver has been developed. Such a receiver clearly opens up a number of interesting possibilities.

For example, if the receiver can be arranged to have its own channel information storage, the frequency, mode, bandwidth and other parameters for a particular operating state can be stored against a particular channel number. This enables the user to preprogram the channels he most frequently uses. Change of data can be effected quickly whenever required and without affecting the receiver's current operating status.

Having given the receiver storage for

channel information and mode of operation, it is a simple matter to instruct it to scan through a number of channels for traffic. To achieve this, the number of each channel to be scanned and the dwell time required can be fed into the receiver.

If the receiver has the software for a scan capability it is easy to program it to sweep between two frequencies. In this instance, the only information required is the upper and lower frequencies of the sweep, the sweep increment and the dwell time on each increment.

These examples show just a few of the possible functions which can be delegated to the receiver to reduce the load

on the operator simply by changing its software. Obviously many other automatic functions can be programmed in to suit given operational requirements.

For instance, Redifon has just arranged to fit R1000M marine receivers to three British Post Office cable ships. Programmed with the channel information for shore stations and linked to a telex machine, the receivers will scan pre-determined channels for traffic, enabling telex messages to be passed virtually automatically and without time delays. This will remove from the operator the need to listen through long traffic lists broadcast by the shore stations and then have to set up the necessary links.

It will be readily appreciated that an intelligent receiver can be used not only for local, but also for extended and remote control applications. The problems that hitherto faced the designer of computerised control systems for remote installations were principally tied up with the sheer volume of data involved. There was no feedback of information from the remote installation, which meant that the overall level of confidence in the system was low. Furthermore, it was not possible to separate the control facility by much more than 1km without prejudice to system reliability.

The high data rates involved meant that digital control over either telephone or radio links was not possible without interface problems. In fact, the use of high speed serial data of nonstandard format would have involved the design of special interfaces for the control computer and also special equipment to test the complete system compatibility between civil and military networks.

Control simplicity

Again, the microprocessor has changed all this. These control limitations have been overcome in a positive way which has extended the system flexibility without increasing the complexity of the control system and without recourse to special interfaces.

Such a receiver for local or remote control applications could, for example, incorporate a microprocessor with 6K of ROM, a 1K RAM and two serial input/ output ports. This overcomes the problems described previously because the volume of data that is sent to each receiver is greatly reduced by sending only those parameters which need to be changed. If it were desired to alter the bandwidth of a receiver then all that need be sent is a label, saying that the

	REDIFON CETAC SYSTEM	14.02 6MT
poct 00 H E	SYSTEM STATUS	SP, 2.182
	4267 KHZ; MD A1 ; CD I; MRX 2; AFI	
		1. WS SIM. I. READY
		1. WS DUP. I. READY
		2, WS DUP, I, READY
	12006 KHZ, MD A3J, CO D, MRX 1, AFI	
		2. WS SIM: 1: READY
RX 1: CH 03: FF		BF V10, R6 V10, MT 5
RX 2+ CH 08+ FF		
RX 3, CH 12, FF		BF V 4, R6 VIO, MT -
RX 4: CH 23: FF		
RX 5: CH 13: FF	1412 KHZ, MO F1 , BW .3 KHZ, R6C L6,	BF F, R6 V10, MT 3
RX 6: CH 24: FI	500 KHZ, MD A2J, BW 8 KHZ, A6C SH,	BF F, R6 V 5, MT -
RX 7: CH 09: FI	22349 KHZ, MD A3H, BW 6 KHZ, A6C SH,	BF F, R6 V10, MT 4
RX 8, CH 18, FI		
RX 9, CH 12, FI		
RX10, CH 25, FI RX11, CH 01, F		
RX11, CH 01, F	₹ 25887 KHZ, MO A3J, BW 8 KHZ, A6C L6; ₹ 12788 KHZ, MO A2 , BW 3 KHZ, A6C SH;	
	₹ 12788 KHZ, MO A2 , BW 3 KHZ, A6C SH, ₹ 16974 KHZ, MO A1 , BW`.3 KHZ, A6C SH,	DC C. DG V 9. MT -
RX14, CH 17, F		
RXEM, CH 09, F	2182 KHZ, MO A3 , BW 8 KHZ, ASC SH	BF F, R6 VIO, MIEM
TXEM, CH 09, F	R 2182 KHZ, MD A3 , CD I, MRX EM, AFI	2, WS SIM, I, READY

A typical CETAC page readout immediately identifies current operational status which can be preprogrammed and amended by simple keyboard operations.

data is bandwidth data, and then provide the new bandwidth instructions. By this means, the data rate can be kept down to 600 baud yet still retain an adequately fast response time under manual control. This latter requirement is important as it gives the operator the same 'feel' as is achieved with local control.

Secondly, once the microprocessor in the receiver has received the data, it then retransmits it back down the line. So a revertive data capability now exists, which allows for built-in self-checking and enhances operational confidence.

Thirdly, such a system can be de-- clearly not a desirable situation in signed to use asynchronous ASCII the light of current trends to achieve characters for its data format. The big advantage of this is that any device which can produce ASCII characters can now control the receivers. Therefore, control can be derived from any standard serial input/output board, whether this be a computer, VDU, teletype or any other similar device. This really is what distributed processing is all about!

Furthermore, the data format can be designed so that error correcting modems can be used in the transmission path, thus enabling control to be achieved over less than perfect paths. Full control is therefore possible over virtually any distance by line or data link. The need for special interfaces is eliminated and consequently, it becomes much simpler to test the complete system. Of course, as the volume and rate of data are low the receiver can be used for remote control applications over ordinary telephone lines, as well as for local systems.

A particular application would be in the area of frequency synthesis, where the basic synthesiser can now be made by LSI technology, but where a large number of discrete peripheral ICs are still required for interface with control display and other interdependent functions. The microprocessor can sweep some of these ICs out of the way.

Digital AGC

A persistent problem in HF receivers has been the AGC. Here the microprocessor can easily out perform analogue systems.

Microprocessors can also be used for a host of other applications such as diversity analysis and diversity combining. Methods can be used which are quite unlike currently available analogue combiners and a reduction in error rates by a factor of ten is possible.

There is yet another complete area where the microprocessor will be used. This is in the demodulation, decoding, handling and printing of data. Whilst this may not actually be done in the receiver itself, it may be carried out by a very compact unit.

All the above applications really come under one heading — signal processing. The sheer complexity of functions per chip have now made digital filtering a reality. In the past, the accuracy of analogue filtering was determined by the quality of the component parts used. Now the only really critical component is the crystal reference and the practical limitations to accuracy are the number of bits per word and the processing speed.

Last but not least, a microprocessor

can test its own systems and diagnose any fault in them. A particularly important tool for achieving self-test is signature analysis. The elegance of a system based on signature analysis is that the signature print can be stored in the processor memory itself, thus simplifying test procedures.

In the longer term microprocessors may well take over most of the signal processing of an HF receiver. Most of the data or information that is handled by such a receiver is at a relatively low information rate and, therefore, if the information can be processed at the actual information rate as opposed to the RF frequency, it is quite possible that microprocessors could do a large proportion of the signal processing. This is likely to lead to a receiver comprising an RF filter and first mixer followed by a microprocessor which would perform the remaining functions. Such a receiver would have no filters, no crystals except for a very accurate clock – and very little analogue circuitry.

The real bonus however, arises from the nature of digital processing. So far the tendency has been to think more in terms of the accuracy and reliability of digital versus analogue systems. The advantage of translating communications intelligence into a digital format is that it can easily be stored and processed according to need, i.e. signal processing need no longer mean adhering to a fixed format for processing but can be designed for adaptive processing.

Systems applications

Having discussed the application of microprocessors to equipment, it is worth looking at their applications in the management of complete communication systems. With the complexity of modern communications, experience has shown that at times of high activity or stress operational errors can and will arise. The incorrect selection of frequency, channel, mode or even equipment could, in a military context, result in catastrophic loss of communications. In addition faults or breakdowns in hardware require valuable time to locate and repair. However, these problems can be overcome by centrally controlling the system with a minicomputer and its associated equipment to exercise control over distributed processing built into the system.

One such system is the Redifon CETAC. Originally designed for the management of fighting ships communications, it is equally applicable to land-based civil and military communications. The heart of the

system is a central control unit employing a mini-computer with VDU and keyboard. This controls a range of standard, digitally-controllable communications equipment (HF/VHF/UHF), transferring the control data along data highways using conventional multiplexing techniques. These data highways carry the command and tuning data to the transmitters, receivers and ancillary units.

The system memory allows for the programming of several separate action states. This gives the operator the facility to recall on the VDU at a single keystroke the operational modes of all equipment needed in any particular action state for status verification.


New generations of equipment will probably feature a greater degree of module commonality so that modules fulfilling roughly similar functions in different equipment will tend to become standardised in the same way that the motor industry has adopted a common approach to such things as door handles, alternators and ignition systems.

This article has been reprinted from the March 1980 issue of Communications International. Communications International is published at 40/50 Hatton Garden, London ECIN 8XS, England by Northwood Publications Limited, trade and technical publishing division of the Thomson Organisation Ltd. We are indebted to Vicom International for supplying us with the article and photographs.



INTRODUCING AUSTRALIA'S BEST VALUE IN RAM

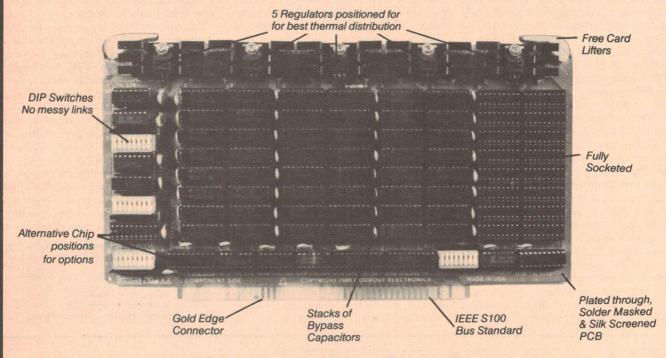THE GODBOUT ECONORAM XX IEEE S100 STATIC RAM CARD



- 16, 24 or 32K 4 MHz STATIC RAM TO IEEE S100
- BANK SELECT/24 BIT ADDRESSING AND PHANTOM
- STATIC RELIABILITY AT NEAR DYNAMIC PRICES

Populated to 16K — Unkit \$335.......\$319*

Populated to 24K — Unkit \$450.50....\$429*

Assembled \$587.50 \$539*

Populated 32K — Unkit \$587......\$559*

Assembled \$734.....\$699*

*SPECIAL INTRODUCTORY PRICES FOR DECEMBER

Plus sales tax if applicable.

Definition: "Unkit" — name applied by Godbout Electronics to products that are not fully assembled, but do have all IC sockets, dip switches, bypass caps and most other discrete components pre-installed and precision flow soldered.

Use 2 cards for 48, 52, 56, 60 or 64K system with page selectivity for further expansion.

- See us for details on the incredible VB3 80 x 24 video cards
 a display card that will make you forget all about serial terminals.
- We are the S100 specialists cards and complete systems.



Trading hours Monday to Saturday 9am - 6pm

MICROCOM PRODUCTS

130 Military Road, Guildford, NSW 2161. Phone (02) 632-6301, (02) 632-4966. Telex AA25958.

archives

the price breakthrough in performance business computers.

Success in today's business world demands efficiency and financial accuracy. But the ever-increasing cost and comlexities of doing business are forcing you to find new ways to cut labour cost as well as gain tighter control over your business.

The ARCHIVES BUSINESS COMPUTER can give you the control you need to be successful, all in one economical desk-top cabinet.

The ARCHIVES BUSINESS COMPUTER can do your daily business functions such as accounts receivables and payables, general ledger and inventory control. It can keep track of stock on hand, stock on order, and supplies to be ordered. As a Word Processor the ARCHIVES BUSINESS COMPUTER can do your correspondence, text editing of manuals, contracts and proposals. The ARCHIVES BUSINESS COMPUTER can do virtually any information handling or record keeping operation you are presently doing plus many desirable operations that cannot economically be performed by manual methods

The Archives disk storage can reduce entire filing cabinets to convenient 5½ inch disks and instantly retrieve any information that you may need when you need it.

Sound incredible? The ARCHIVES BUS NESS COMPUTER is that and more!

It's a business assistant. One that never forgets, never loses reports, makes efficient use of its time and is completely trustworthy.

The ARCHIVES BUSINESS COMPUTER is also easy to work with. So easy in fact, it's no more difficult to operate than any other office machine. While the ARCHIVES BUSINESS COMPUTER is handling the extra work load, you can have more time to develop new business in the field.

There is no question that the major area restricting your business growth is in the office. This is one place where employee efficiency is still in the dark ages -requiring the handling of paper, forms and files. What you really need is not the physical presence of obsolete forms and letters, but the information and data they contain. You need the Archives Business Computer.

The Archives Business Computer offers you an economical way to individualised computing power. You can take it anywhere there's work to be done. Plug it in, turn it on, and it's working for you giving you instant access to the information you need.

Designed especially for a small business or single department in a large company, the Archives Business Computer is a system you can understand and use with a high degree of efficiency without being a computer specialist.

Incorporating quality and reliability the Archives Business Computer provides you with today's and tomorrow's best value in a computer system. The Archives Business Computer is a system to help your business grow.

The Archives Business Computer is backed by competent and qualified technical support for both equipment maintenance and software aid as well as continuing personalised service.

One of the best investments you can make in this inflationary economy is the Archives Business Computer. In fact, virtually every business enterprise can benefit in some practical way from business computing.

A full scale demonstration of the Archives Business Computer will help you draw positive conclusions about how your business can improve its cash flow, reduce costs and risks, improve customer service, increase sales, and improve your employee productivity.

It's time to make a move for the future.
It's time to contact Computerland
Melbourne your Archives dealer.

FEATURES
Z80 4MHz Processor
64 K RAM Standard
744K Bytes Storage (Standard)
1½ Megabytes Storage (Optional)
12" Green Phosphor Monitor
25 Lines x 80 Display
CP/M Operating System
Selectric Style Keyboard
S100 Expansion Inbuilt
Microprocessor Keyboard
240 x 100 Graphics Format

Numeric Keypad and Function Keys.

ComputerLand[®]
in Melbourne

Microsoft Fortran
Microsoft Basic
Microsoft Cobol
General Ledger
Stock Control
Mail List
CBasic 2
Accounts Payable
Accounts Receivable
Property Management
Word Processing System
Microsoft Basic Compiler



555 Collins St. •Melbourne, Vic. •Australia 3000 Phone 62 5581 •62 6737 •Telex AA37007

BUMUMBATUMS

Six metres "buried"

— but it ain't dead and gone!

Two days after multicultural ("ethnic") TV went to air on channel 0 at the end of October, a group of Sydney amateurs "buried" the six metre band.

The mock funeral was held tain interest in the band. on 26 October outside the Gore Hill studios of ABC TV as a protest against the use, "temporary as it might be". of channel 0.

A group of some 15 people carried a coffin from the ABC studios to Gore Park where they buried their beloved six metre rigs. Quite a bit of media coverage was obtained, news teams from channels 2, 7 and 10 attended as well as several radio stations and newspaper re-

The Sydney Morning Herald carried a small piece on the event the following day.

A "Sydney Channel O Action Group" was formed subsequently with the aim of (1) educating the public about the interference-prone channel 0 and its alternative, channel 28; and (2) promoting the utilisaband as a portable/mobile/ yet to come! handheld band. The group feels that aim (2) is imperative to sus-

Frankly, we disagree. Any TVI that arises from operating on six metres is the fault of (a) the TV set, (b) antenna deficiencies or (c) antenna/feedline problems - that is, apart from straight front-end overload. In any event, the onus is on the TV set owner to have the problem rectified. not the amateur.

Your scribe once lived in a valley in one of Melbourne's eastern suburbs - and operated AM on six metres (those were the days ...) following the introduction of channel 0 there. The RI had in excess of 120 TVI reports to 'cure'. He made the points I just made. If you operate six metres, as I do, and intend to 'pack up and go on some other band', as I don't, then you should re-think your position carefully.

They may have "buried" six tion of the amateur six metre metres, but "the awakening" is

Roger Harrison VK2ZTB

Requiem for six metres, Gore Hill, Sydney (pix: Sam Voron VK2BVS)

National VHF Field Day

For many years there has been much discussion about a nationally-coordinated VHF field day.

Many VHF field days have scoring been held over the years, but purposes. they have generally suffered from being only state-wide

The Geelong Amateur Radio Club from Victoria has decided to accept the challenge to coordinate a national VHF field day weekend.

It was decided to hold the contest when interest is highest - during the annual Ross Hull contest period - hopefully giving added impetus to the event. The Ross Hull rules and scoring have been adopted for the National VHF Field Day to keep the two contests compatible for

log-keeping

The contest period is any 24 hours within the first 48 hours of the Ross Hull contest. Only entries from portable stations will be accepted. A station is deemed portable when more than 2 km from his home QTH. No equipment may be set up more than 24 hours prior to the start of the contest. Power may be derived from any source available. A scoring contact may be made with the same station on the same band repeatedly provided at least four hours elapse between successive contacts. Each entry must include a front sheet giving details of station, location and score claimed.

All entries will be acknowledged and certificates will be awarded to the overall winner plus the highest scorer in each call area. All entries to "Contest Manager", Geelong Amateur Radio Club, P.O. Box

VK2DTE on the air!

A new callsign — so what ? This one's different — it belongs to the Modern Magazines Electronics and Communications Club!

That's us folks!

or less on staff - Roger call. VK2ZTB, Phil VK2DKN, David Simon VK2YAZ plus a number of correspondents and close thought it a good idea one night, the regulations!).


over a few synergistic beers, to There being five hams more form a club and apply for a club

VK2DTE is the result. So, if VK2YMI, Jonathan VK2YBN, you recognise the callsign on the air, you're welcome to break in and say hi!, or whatever takes associates with callsigns, we your fancy (and complies with

The Gosford Convention

Yes folks, it's on again. The 24th annual field day (convention, really) of the Central Coast Amateur Radio Club will be held on Sunday 22 February 1981.

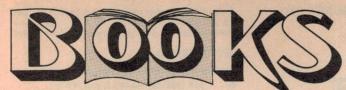All the familiar goodies and events are planned: scrambles, foxhunts, disposals, trade displays, outings etc. Read all about it in next year's first issue!



Just some of the books from the biggest range of radio and electronics books in Australia. If the book you require is not listed below, it can be

NEW - NEW	- NEW	Latest	editions	of	some	of	the most	1
popular book	s on th	e subie	ect:					

NEW - NEW - NEW Latest editions of some of the	
popular books on the subject:	
The Master IC Cookbook (Clayton L. Hallmark)	12.50
Amateur Operator's Handhook (Revised Dec. 78)	10.00
(Postal & Telecommunication Dept.)	\$3.60
ARRL Handbook 1980	14.95
R.S.G.B. Handbook — Volume 1	18 90
Tile Master It Cookbook (Walter C. Jung)	27.75
ADAM OSBORNE BOOKS:	
An Introduction to Microcomputers — Volume 0 —	
The Beginner's Book	13.50
An Introduction to Microcomputers — Volume 1 —	
The Beginner's Book An Introduction to Microcomputers — Volume 1 — Basic Concepts. An Introduction to Microcomputers — Volume 2 — Some Real Microprocessors	\$19.20
Some Real Microprocessors	29 00
An Introduction to Microcomputers — Volume 3 — Some Real Support Devices	
Some Real Support Devices	21.20
Some Common Basic Programs Accounts Payable and Accounts Receivable Payroll with Cost Accounting in Basic Z80 Assembly Language Programming	23.00
Payroll with Cost Accounting in Basic	23.00
Z80 Assembly Language Programming	19.20
Z80 Programming for Logic Design 8080A/8085 Assembly Language Programming 6800 Programming for Logic Design 6800 Assembly Language Programming 6800 Assembly Language Programming	16.20
6800 Programming for Logic Design	15.50
6800 Assembly Language Programming	519.20
6502 Assembly Language Programming	19.20
Z8000 Assembly Language Programming	19.20
The 8086 Book includes the 8088	\$22.50
AMERICAN RADIO RELAY LEAGUE PUBLICATIONS:	
8080 Programming for Logic Design. 6502 Assembly Language Programming. 28000 Assembly Language Programming. 28000 Assembly Language Programming. The 8086 Book includes the 8088 AMERICAN RADIO RELAY LEAGUE PUBLICATIONS: All New A.R.R.L. Code Kit Hints and Kinks for the Radio Amateur.	\$14.50
The Radio Amateur's VHF Manual	\$7.20
Understanding Amateur Radio The Radio Amateur's License Manual.	.\$8.80
The Radio Amateur's License Manual	\$7.20
Specialized Communications Techniques for the Radio Amateur	\$7.20
Specialized Communications Techniques for the Radio Amateur FM & Repeaters for the Radio Amateur Single Sideband for the Radio Amateur	.\$8.80
Single Sideband for the Radio Amateur Ham Radio Operating Guide	\$7.20
Flectronics Data Book Solid State Design Design for the Radio Amateur	\$7.20
Solid State Design Design for the Radio Amateur	£12 80
Cond Ctate Boolgii Boolgii for the Hadio Milatour	\$12.00
BUILDE COOLUMN TERRO MAIOR OPPOSITOR DO	
BUILDE COCKETIFE DO MAIODODD COPOCODO DOCUM	
BUILDE COCKETIFE DO MAIODODD COPOCODO DOCUM	
BUILDE COCKETIFE DO MAIODODD COPOCODO DOCUM	
BUILDE COCKETIFE DO MAIODODD COPOCODO DOCUM	
BUILDE COCKETIFE DO MAIODODD COPOCODO DOCUM	
BUILDE COCKETIFE DO MAIODODD COPOCODO DOCUM	
MICROCOMPUTERS/MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H. C. Pennington).	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80
MICROCOMPUTERS/MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H. C. Pennington).	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80
MICROCOMPUTERS/MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H. C. Pennington).	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80
MICROCOMPUTERS/MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H. C. Pennington).	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80
MICROCOMPUTERS/MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H. C. Pennington).	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80
MICROCOMPUTERS/MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H. C. Pennington).	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80
MICROCOMPUTERS/MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H. C. Pennington).	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80
MICROCOMPUTERS/MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H. C. Pennington).	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80
MICROCOMPUTERS/MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H. C. Pennington).	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H. C. Pennington) Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Z80 Microprocessor Programming and Interfacing Book 2 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputers for Business Applications (Barden).	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Z80 Microprocessor Programming and Interfacing Book 2 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi) How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputer Primer (Waite & Pardee). OTHER TITI FS:	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80 .\$9.95 \$17.50 \$17.50 \$17.80 \$12.70 \$16.80 .\$8.50 \$10.75 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Z80 Microprocessor Programming and Interfacing Book 2 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi) How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputer Primer (Waite & Pardee). OTHER TITI FS:	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80 .\$9.95 \$17.50 \$17.50 \$17.80 \$12.70 \$16.80 .\$8.50 \$10.75 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Z80 Microprocessor Programming and Interfacing Book 2 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi) How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputer Primer (Waite & Pardee). OTHER TITI FS:	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80 .\$9.95 \$17.50 \$17.50 \$17.80 \$12.70 \$16.80 .\$8.50 \$10.75 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Z80 Microprocessor Programming and Interfacing Book 2 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi) How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputer Primer (Waite & Pardee). OTHER TITI FS:	.\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$20.00 \$19.80 .\$9.95 \$17.50 \$17.50 \$17.80 \$12.70 \$16.80 .\$8.50 \$10.75 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost IC Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin).	\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$22.00 \$19.80 \$19.80 \$19.80 \$14.75 \$17.50 \$14.75 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost IC Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin).	\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$22.00 \$19.80 \$19.80 \$19.80 \$14.75 \$17.50 \$14.75 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost IC Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin).	\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$22.00 \$19.80 \$19.80 \$19.80 \$14.75 \$17.50 \$14.75 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost IC Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin).	\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$22.00 \$19.80 \$19.80 \$19.80 \$14.75 \$17.50 \$14.75 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost IC Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin).	\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$22.00 \$19.80 \$19.80 \$19.80 \$14.75 \$17.50 \$14.75 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost IC Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin).	\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$22.00 \$19.80 \$19.80 \$19.80 \$14.75 \$17.50 \$14.75 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony). Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Primer (Waite & Pardee). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost IC Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin).	\$6.00 \$19.95 \$17.50 \$12.50 \$11.95 \$10.00 \$22.00 \$19.80 \$19.80 \$19.80 \$14.75 \$17.50 \$14.75 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS-80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony) Z80 Microprocessor Programming and Interfacing Book 2 (Nichols /Nichols /Rony) Bost of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Frimer (Waite & Pardee). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost IC Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin). Video User's Handkbook (Peter Utz). Music and the Synthesiser (Bruce Graham). The S-100 and other Micro Buses (Elmer C. Poe & James C. Goodwin). TV Antennas and Signal Distribution Systems (M. J. Salvati). Building Hi-Fi Speaker Systems (Philips). Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendal Webster Sessions).	.\$6.00 \$19.95 \$17.50 \$17.50 \$17.50 \$11.95 \$11.95 \$11.95 \$19.80 \$20.00 \$20.00 \$21.00 \$19.80 \$17.80 \$17.80 \$17.80 \$17.80 \$17.80 \$11.95 \$1
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS-80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony) Z80 Microprocessor Programming and Interfacing Book 2 (Nichols /Nichols /Rony) Bost of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Frimer (Waite & Pardee). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost IC Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin). Video User's Handkbook (Peter Utz). Music and the Synthesiser (Bruce Graham). The S-100 and other Micro Buses (Elmer C. Poe & James C. Goodwin). TV Antennas and Signal Distribution Systems (M. J. Salvati). Building Hi-Fi Speaker Systems (Philips). Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendal Webster Sessions).	.\$6.00 \$19.95 \$17.50 \$17.50 \$17.50 \$11.95 \$11.95 \$11.95 \$19.80 \$20.00 \$20.00 \$21.00 \$19.80 \$17.80 \$17.80 \$17.80 \$17.80 \$17.80 \$11.95 \$1
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS-80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony) Z80 Microprocessor Programming and Interfacing Book 2 (Nichols /Nichols /Rony) Bost of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Frimer (Waite & Pardee). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost IC Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin). Video User's Handkbook (Peter Utz). Music and the Synthesiser (Bruce Graham). The S-100 and other Micro Buses (Elmer C. Poe & James C. Goodwin). TV Antennas and Signal Distribution Systems (M. J. Salvati). Building Hi-Fi Speaker Systems (Philips). Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendal Webster Sessions).	.\$6.00 \$19.95 \$17.50 \$17.50 \$17.50 \$11.95 \$11.95 \$11.95 \$19.80 \$20.00 \$20.00 \$21.00 \$19.80 \$17.80 \$17.80 \$17.80 \$17.80 \$17.80 \$11.95 \$1
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). 280 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). 280 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony) Book 2 (Nichols /Nichols /Rony) Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi) How to Build Your Own Working Robot Pet (DaCosta). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost (C Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin). Video User's Handkbook (Peter Utz). Music and the Synthesiser (Bruce Graham). The S-100 and other Micro Buses (Elmer C. Poe & James C. Goodwin). TV Antennas and Signal Distribution Systems (M.J. Salvatti). Building H-Is Speaker Systems (Philips). Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendal Webster Sessions). Getting Acquainted with the IC (Rufus P. Turner). Practical Antennas for the Radio Amateur (Scelbi). CO P-AMP Cookbook (Lancaster) 1 TV Typewriter Cookbook (Lancaster) 1 St Edition 1977.	\$6.00 \$19.95 \$17.50 \$117.50 \$12.50 \$11.95 \$12.50 \$20.00 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$10.75 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). 280 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). 280 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony) Book 2 (Nichols /Nichols /Rony) Best of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi) How to Build Your Own Working Robot Pet (DaCosta). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost (C Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin). Video User's Handkbook (Peter Utz). Music and the Synthesiser (Bruce Graham). The S-100 and other Micro Buses (Elmer C. Poe & James C. Goodwin). TV Antennas and Signal Distribution Systems (M.J. Salvatti). Building H-Is Speaker Systems (Philips). Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendal Webster Sessions). Getting Acquainted with the IC (Rufus P. Turner). Practical Antennas for the Radio Amateur (Scelbi). CO P-AMP Cookbook (Lancaster) 1 TV Typewriter Cookbook (Lancaster) 1 St Edition 1977.	\$6.00 \$19.95 \$17.50 \$117.50 \$12.50 \$11.95 \$12.50 \$20.00 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$10.75 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95
MICROCOMPUTERS / MICROPROCESSORS BOOKS: Stimulating Simulations — 2nd Edition (Engel). NCR EDP Concepts Course (NCR Corporation). Computer Graphics Primer (Mitchell Waite). The Complete Microcomputer Systems Handbook (Edward L. Safford, Jr.). TRS-80 Interfacing — Book 1 (Jonathan A. Titus). Z80 and 8080 Assembly Language Programming (Kathe Spracklen). Australian Microcomputer Handbook (Prepared by Computer Reference Guide). TRS-80 Disk and Other Mysteries (H.C. Pennington). Computer Programming for the Complete Idiot (Donald McCunn). Z80 Microprocessor Programming and Interfacing Book 1 (Nichols /Nichols /Rony) Z80 Microprocessor Programming and Interfacing Book 2 (Nichols /Nichols /Rony) Bost of Interface Age: Volume 1 — Software in Basic (Ed. Carl D. Warren). Best of Interface Age: Volume 2 — General Purpose Software (Ed. Interface Age). 6502 Software Gourmet Guide & Cookbook (Scelbi). How to Build Your Own Working Robot Pet (DaCosta). Microcomputer Frimer (Waite & Pardee). Microcomputers for Business Applications (Barden). OTHER TITLES: Solid State Power Electronics (Irving M. Gottlieb). So You Want to be a Ham (Robert Hertzberg). Practical Low-cost IC Projects (Herbert Friedman). Introduction to Miomedical Electronics (Edward J. Bukstein). Design of Active Filters, with Experiments (Howard M. Berlin). Video User's Handkbook (Peter Utz). Music and the Synthesiser (Bruce Graham). The S-100 and other Micro Buses (Elmer C. Poe & James C. Goodwin). TV Antennas and Signal Distribution Systems (M. J. Salvati). Building Hi-Fi Speaker Systems (Philips). Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendal Webster Sessions).	\$6.00 \$19.95 \$17.50 \$117.50 \$12.50 \$11.95 \$12.50 \$20.00 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$19.80 \$10.75 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95 \$11.95

For mail orders please add: \$1.40 Local \$1.75 Interstate

McGILL'S AUTHORISED NEWSAGENCY PTY. LTD.

187 Elizabeth Street, Melbourne. Phone: 60-1475-6-7 Prices Subject to Alteration

AUSTRALIA'S ONLY

ONE STOP RADIO COMMUNICATIONS AND SWL CENTRE

INTRODUCES

THE NEW NO COMPROMISE JRC NRD-515



Communications Receiver.

Versatile high quality.

- Covers 100KHz to 30MHz using PLL and photo type rotary encoder to determine frequency setting.
- Continuous coverage. Optional 24 channel memory unit. Effective passband tuning and electronic switching.
- All solid state chassis completely modular construction. All components mounted on plug-in circuit boards for easy servicing
- Excellence and quality for professional and commercial services, sophisticated SWL and ham users.

NEW YAESU FRG-7700



- 150KHz 30MHz. CW, SSB, AM, FM.
- Three AM selectivity positions.
- 12 channel memory.
- · Noise blanker.
- · Digital clock and timer.
- And many other features.

KENWOOD R-1000 Communications Receiver

Analog dial, digital clock, automatic timer, three selectivity positions and many other features



INFO-TECH M-200F

RTTY, CW, ASCII, VIDEO CONVERTER



This fantastic machine, together with a good communications receiver and your own TV set or CCTV monitor, provides the most sophisticated SWL SYSTEM, that until recently could only be dreamt about. M-200F will reveal the secrets of RTTY, CW and ASCII transmissions from all over the world. Listen to embassy, commercial, military, world news serivce and amateur transmissions.

We also stock Australia's largest selection of scanning receivers. You can listen to aircraft, marine, police and other transmissions

BEARCAT 210, BEARCAT 220, BEARCAT 250, BEARCAT POCKET SCANNERS and SX-200.

SWL ACCESSORIES: antenna tuners, indoor/outdoor active antennas, active audio filters, preselectors, headphones. Best selection of best brands of ham radio transceivers.

WRITE OR CALL FOR FURTHER SPECS.



CITY & SHOWROOM: 649 George St. Sydney. NSW. (02) 211-0531. POSTAL: PO Box K21, Haymarket, NSW 2000. Cable: Emtron Sydney.

Covering 3 MHz to 40 or 60 MHz, these predictions show the times radio contact is possible between the areas designated beneath each graph, as well as the possible 'mode' and reliability. Vertical columns indicate time — commencing at 0000 UT on the left, to 2300 UT at right. For reliable predictions follow the times and frequencies indicated by the F character.

Complete information on using these predictions can be obtained by sending a stamped, self-addressed envelope to:-




JANUARY 1981

These GRAFEX style computer generated predictions are provided courtesy of the Australian Ionospheric Prediction Service, Dept. of Science & the Environment.

KEY TO SYMBOLS

A blank area means no normal propagation is possible.

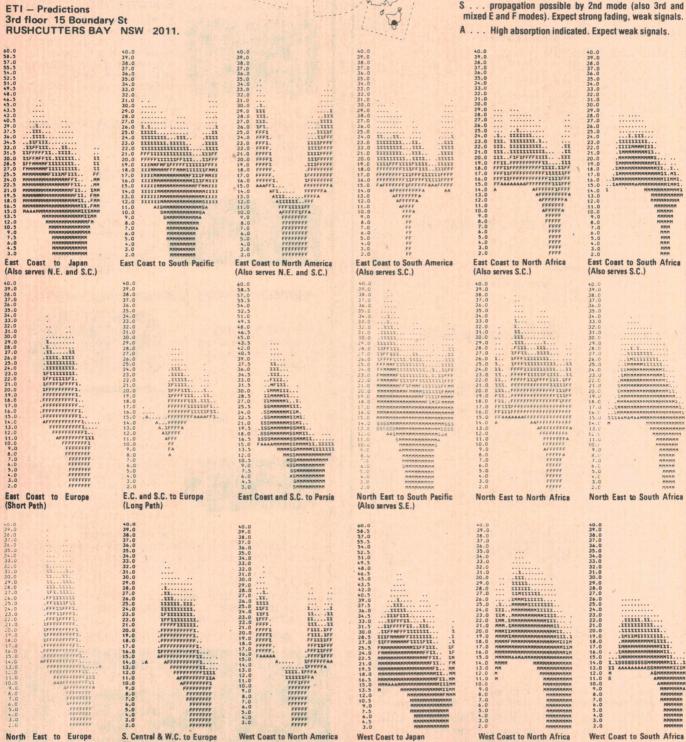- . . . path open less than 50% of days in month.
- % . . . path open 50-90% of days in month.
- F . . . path open at least 90% of days in month.
- X . . . complex mixture of modes. Expect abnormal propagation.
- propagation possible by both 1st and 2nd F-layer modes. Expect strong fading.



(Short Path)

(Short Path)

THE RECEIVER

NEW YAESUFRG 7700 MORE FEATURES THAN THE 7000 -

and it's CHEAPEI

First the incredibly popular FRG-7. Then the FRG-7000.

Now a brilliant new all mode, general coverage receiver with all the features the keen amateur or short wave listener really needs.

Digital Display - reading from 150kHz to 30MHz! This also doubles as a highly accurate crystal controlled clock.

Wide dynamic range. Selectable AGC. All mode (including FM and 3 widths of AM). Optional twelve memory channels with backup. A remarkable piece of solid state engineering — and it is actually cheaper than the FRG-7000 (and many other 'similar' receivers on the market). Ask to see one soon at your nearest Dick Smith store or reseller.......Magnificent!



Below cost anywhere in Aust.

Freight \$6

OR FROM \$55 DEPOSIT AND \$25.74/MONTH (24 MONTHS)

Memory Unit extra



NEW FT480

- All mode 2 metre SSB/CW/FM!
- Microprocessor controlled
- Digital display!
- 30 watts PEP

This is the one they're all talking about: the fabulous new 2 metre allmode transceiver from Yaesu. Offering outstanding performance and ease of controls, it must be the transceiver of the eighties! Cat D-2887



We've knocked an incredible \$100 off the price of these popular allmode 6 metre rigs. There's still plenty of good DX out there on 6 and the FT-625 is just the transceiver to get it! Cat D-2886

SAVE ON FT625 ALL MODE 6M

WAS \$795.00 . . **NOW ONLY**

OR FROM \$75 DEPOSIT AND \$20.48/MONTH (48 MONTHS)



OR FROM \$63 DEPOSIT

AND \$26.28/MONTH

(24 MONTHS)

- All HF bands!AM/SSB/CW!
- Tiny Size!
- True digital displayNew WARC bands!

They've been pretty hard to get: and small wonder! The superb FT-707 packs a huge punch from its tiny size: 240W DC! It's the ideal rig for mobile, base or portable work. Cat D-2869

SUPERB FT-207

- Microprocessor controlled hand held giving full 144-148 band!
- Digital display.

For today's active ham. this is the set to take with you. Takes up virtually no room, but really gets out! Make contacts wherever you go with the FT-207R.

Cat D-2888

OR FROM \$38 DEPOSIT AND \$17.52/MONTH (24 MONTHS)





OR FROM S85 DEPOSIT AND

OR FROM \$138 DEPOSIT AND \$38.32/MONTH (48 MONTHS)

NEW FT107M

- The ultimate!
- **WARC** bands
- All solid state
- Variable IF
- bandwidth! • Speech proc.

It must be every amateur's dream to own one of these! You can: and take full control of the bands. Whatever you want from your transceiver, the FT-107 offers it! Cat D-2871

DGET FT-101Z

We throw in a digital display kit worth over \$100! This turns the FT-101Z into an FT-101ZD!

More hams have 'cut their teeth' on one of the famous '101 series than any other rig! Rugged and reliable, with all the features you really need. Cat D-2862

OR FROM \$85 DEPOSIT AND \$23.19/MONTH (48 MONTHS)



WITH BONUS DIGITAL **DISPLAY WORTH \$139!!**

ANY TERMS OFFERED ARE TO APPROVED, PERSONAL APPLICANTS ONLY.ORDER BY MAIL: USE YOUR BANKCARD!

125 York Street. 818 George Street 162 Pacific Hwy,

30 Grose Street. 613 Princes Hwy. 147 Hume Hwy. 531 Pittwater Road

BROADWAY GORE HILL PARRAMATTA 683 1133 BLAKEHURST 642 8922 93 0441 CHULLORA BROOKVALE

SYDNEY

439 5311 546 7744

656 Bridge Road QLD Logan Road 842 Gympie Road. 96 Gladstone Street 60 Wright Street.

WOLLONGONG 28 3800 MELBOURNE 67 9834 RICHMOND 428 1614 BURANDA CHERMSIDE 391 6233 59 6255 FYSHWICK ADELAIDE 80 4944 212 1962

welcome here SHOPS OPEN 9AM to 5.30PM

bankcard

(Saturday 9am till 12 noon) BRISBANE Half hour earlier ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY



SAWA 648 0558 MAIL ORDER CENTRE: PO Box 321, NORTH RYDE NSW 2113 Ph 888 3200 PACK & POST EXTRA

RE-SELLERS OF DICK SMITH PRODUCTS IN MOST AREAS OF AUSTRALIA

shortwave loggings



New Indian amme for DXers

All India Radio has joined the growing ranks of international radio stations which have a weekly programme specifically for shortwave DXers and shortwave listeners.

The new DX programme was introduced during Oct- well-known Calcutta DXer, Alok ober, and goes to air every das Gupta, will include each week during the Monday week a phone-in report detailing English programmes.

New Zealand, best reception is bands. during the service beamed our on air a few days in advance.

The programme, scripted by the very latest available news of For listeners in Australia and happenings on the shortwave

With All India Radio and way from 1000 to 1100 each Trans World Radio on Guam evening. Current frequencies for recently introducing DX prothe nightly Australia and New grammes, Radio Australia is left Zealand service from Delhi are: as the odd station out, in that 17 875, 15 285 and 15 205. Australia's overseas service is Keep in mind that frequencies one of the very few international are subject to change at short broadcasters in the Asia/Pacific notice. Any frequency modifi- area not to have a programme cations are usually announced in English for DXers and shortwave enthusiasts.

Hot summer nights bring Africa

Summer nights often make for good listening on the higher frequency bands as far as signals from Africa are concerned.

Signals from eastern and southern Africa usually start to become audible from about 1330 on the 31 metre band. Watch for Mozambique on 9618, which is usually one of the first signals to become audible, and Tanzania on 9685 and 9750. Zambia operates an Overseas Service in English Malawi Broadcasting Corpora-

mitters, each of 250 kilowatts, problem in city locations.

Late night or very early and one of these broadcasts morning listening can some- from the northern town of Soroti times reveal strong signals from with the English service on many countries which at other 6030 from 1430 to 1530. Probtimes of the year may be hard to ably the strongest African signals at this time would be from Addis Ababa in Ethiopia, from their station known as "Voice of Revolutionary Ethiopia", operating the English service from 1500 to 1600 on both 9560 and the parallel outlet of 7165.

Most of these stations will reply to correct reception reports with a verification card from 1500 on 9580 and the or letter, and these early morning broadcasts present the DXer tion operates from Blantyre on with good opportunities to verify 7130 from 1600 with English some of the countries of Africa which otherwise only operate on the low frequency or "tropical" Radio Uganda has recently bands below 5900 kHz where fired up its two powerful trans- noise levels are an increasing

All India Radio would welcome listeners' comments and suggestions concerning the new DX programme, and any Box 500, New Delhi.

letters should be addressed to: The Director, External Services Division, All India Radio, Post

Lesotho boosts signals

With the addition of new 50 kilowatt shortwave transmitters, the Lesotho National Broadcasting Service at Maseru has considerably increased the strength of their 4800 signal during our early mornings.

recently purchased by the occasional programmes in Lesotho government in Britain, English are also heard, notably and installed at their transmit- between 2000 and 2100 every ting centre at Lancer's Gap near Sunday (early Monday morning Maseru. The station now pro- in Australia) when the LNBS vides good to very good carries a religious programme reception on 4800 (Lesotho's produced in Pennsylvania, USA. shortwave frequency) 2030.

Lesotho National Broadcasting 552, Maseru.

The two new transmitters were Service are in SeSotho, but

The Lesotho station generally between about 1900 and sign verifies correct reception reoff at 2110. Sign-off does vary ports with a QSL card showing and sometimes is as early as the national flag, and reports can be sent to: Lesotho National Most programmes of the Broadcasting Service, PO Box

Iceland coming in well!

As mentioned in our column a couple of months ago, Reykjavik Radio's recent time shift for their Home Service relay on shortwave brought this rarely heard country within reach for Australian listeners.

fairly regularly on 12 175 during from overseas listeners. These our early mornings from 1955 reports should be sent to: to 2000 with Home Service Iceland State Broadcast Service landic seamen and Icelandic Reykjavik. workers in Scandinavia. Programmes are in Icelandic and consist of news, comment, NOTE! All times are given in Greenwich mean time (GMT). To conmusic and magazine features.

The programmes are relayed directly from the Home Service Daylight Saving Time, November to programming which is usually only broadcast on medium wave. The transmitter used on 12 175 for the Home Service relay from 1855 to 2000 is at other Bunn on behalf of the Australian Radio times used for utility broadcasting purposes.

reputation of being a good veri- 22¢ stamp.

Reykjavik Radio is now heard fier of correct reception reports programming beamed for Ice- Rikisutvarpid, P.O. Box 120

> vert to Australian Eastern Standard Time, add 10 hours (11 hours during February). To convert to Central Standard Time, add 9.5 hours and Western Time add 8 hours.

All frequencies are given in kHz. These notes are compiled by Peter DX Club (ARDXC). Further information on DXing or the activities of the ARDXC may be obtained from P.O. The Iceland station has the Box 79, Narrabeen, NSW 2101, for a



Let your fingers travel the world.

Sony proudly presents an exciting world receiver with FM & AM that gives you the best value in its class. Frequency synthesized "calculator-type" tuning of the LW/MW/SW bands offers unprecedented convenience, versatility and wide frequency coverage.

We call it the ICF-2001. It captures broadcasts with a push of a button from virtually every source on the globe including marine, amateur radio and other fascinating short wave transmissions. Even citizen band.

Now world travelers can hear where they've been and where they're going. Or "practice" another language. Or literally share another culture. But you don't have to be versed in complicated radio lore to enjoy your foreign adventures because our world traveler is marvelously easy to use.

Sophisticated technology such as a frequency synthesizer for extreme stability as well as a microcomputer gives you four different tuning methods for fast, easy operation. Direct Access, Memory, Auto Scan and Manual tune in the exact frequency you're searching for. They're push-button easy and only Sony gives you the communication spectrum at your fingertips.

Sony's ICF-2001 brings home the world.

Bon voyage.





FEATURES: • THE CRAFT OF THE SPEAKER BOX MAKER 150

REVIEWS: • MARANTZ ST500

COMPUTER STEREO TUNER

• G.R.D. PAS 30 SPEAKERS


1.00

156

168



The world's fastest integrated amplifier

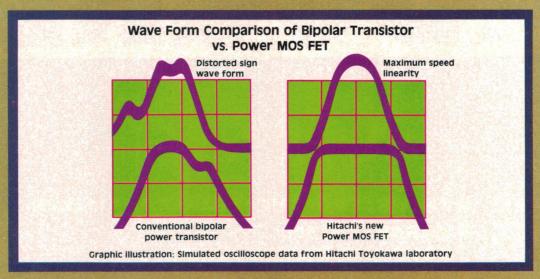

Hitachi Power MOS FET

The HA-7700 Stereo Integrated Amplifier brings you stunning sound reproduction. The Hitachi Power MOS FET offers ultra-high switching speed for dramatically reduced distortion and outstanding transient response. It features the same incredible technology that went into our renowned HMA-7500 Stereo Power Amplifier and HA-8700 Stereo Integrated Amplifier.

Power output is 70 watts per channel with no more than 0.008% total harmonic distortion from 20 to 20,000 Hz. And all stages are direct coupled, so you get the purest waveform reproduction fidelity from input to output.

The RIAA phono equalizer is a top-precision design employing only the highest-quality components for low-distortion and true-to-life disc playback. There's a full complement of control and convenience features for maximum system flexibility.

The HA-7700. True purity in waveform reproduction is here.



HA-7700





Forward thinking by Sansui

Sansui claim that their new Super Feedforward system completely eliminates all kinds of distortion in the power stage of amplifiers.

years ago by the same amplifiers, the AU-D9 and the American scientist, H.S. AU-D11. These have output transformer. Black, who later developed negative feedback approach currently adopted in all hi-fi amplifiers.

In principle feedforward involves taking a fraction of the amplifier output (actually 1/a times the output, where a is the open loop gain) and comparing it with the input signal to derive a difference signal which is fed to the output to cancel the distortion. The system has been successfully applied in communications equipment, but it has not so far been effectively used in hi-fi amps.


Sansui's feedback system combines feedforward in the power amp stage with a relatively low level of negative feedback applied to both preamp and power amp. In a manner they don't explain, they have arranged things so that the NFB operates mainly at lower frequencies and the feedforward at higher frequencies.

The first of Sansui's amplifiers in which the new

power ratings of 95 watts and tively.

Both have a built-in moving Feedforward techniques Super Feedforward system has coil head amp, both are direct were actually invented 52 been adopted are two integrated coupled and both feature the variation of no more than 3 dB

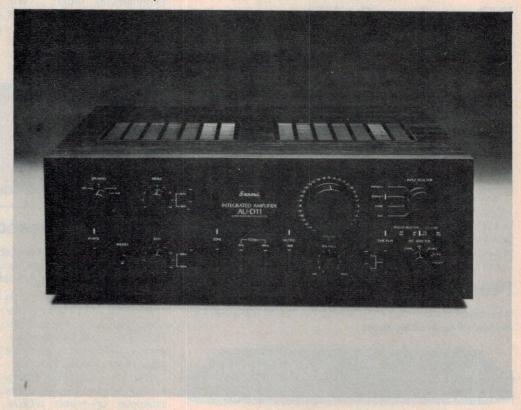Total harmonic distortion 120 watts per channel respec- does not exceed 0.005% for either of these amplifiers and the quoted frequency response is the same for each, showing a newly developed 'C1' core power over the entire range from dc to 300 kHz.



Audio level meter

Signal levels down to -72 dB can be measured by a small analogue meter recently available from Soundex.


The calibrated range of the enough to hold in the hand. It's 100 kilohms, balanced, switch- to have only one function. able to 600 ohms and the protected headphone output has an impedance of approxi- tact the distributors the specs.

adaptor and is small and light 2089; (02) 909-2388.

AMM100 is from -72 dB to described as a multimeter, +22 dB. Input impedance is which is odd because it appears

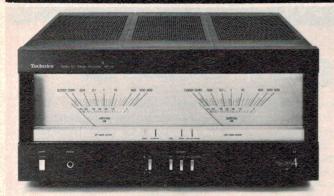For more information, conmately 50 ohms, according to Cunningham Pty Ltd, P.O. Box 4533, Melbourne, Vic 3001; The meter comes in a tough (03) 329-9633 or P.O. Box 214, plastic case with a built-in mains Neutral Bay Junction, NSW





DC amp is really AB

Technics describe their new SE-A3 200 W per channel power amp as Class A, but we at ETI maintain it's really Class AB.

The reason for the dis- with the amp running at its full agreement is its 'synchro-bias' rated power into eight ohms. At circuitry that samples the input 1 kHz, THD is only 0.001%. of the output transistors so that tortion is said they are never quite cut off. This immeasurably small. arrangement allows the efficiency of Class B operation without switching distortion.

We don't want to knock this amplifier though - its specifications are certainly impressive. Total harmonic 20 Hz to 20 kHz is only 0.002% 'em you read about it in ETI.

waveform and adjusts the bias Transient intermodulation dis-

Independent left and right channel power supplies keep the channel separation up to 70 dB and signal to noise ratio is extremely high at 123 dB.

Brochures available from distortion over the range from your local Technics dealer. Tell

Plus Series Tuners

Two tuners are included in Sanyo's recently released 'Plus Series' of hi-fi components.



The slightly more expensive fied by the provision of a LED model T55 has a quartz crystal reference oscillator. Frequencies of this and the controlled oscillator are digitally divided by different whole numbers and the divided signals are phase locked together with a correction signal to keep them precisely in phase.

A two-position IF bandwidth switch allows selection of a narrow bandwidth for 80 dB alternate channel rejection when FM stations are closely spaced.

The Plus T35 AM/FM tuner has a sampling quartz locked \$470 for the T55 and \$399 for tuning system. Tuning is simpli-the T35.

bar graph signal strength indicator and a 'centre of signal' position indicator. Both these displays use high gain dccoupled voltage comparators.

For correct balancing levels when recording from the FM tuner onto tape, the T35 has a record level calibrator with adjustable output level. This provides a 400 Hz tone at a level equal to the level of the tone produced by an FM signal with 50% modulation.

Suggested retail prices are

A new approach to noise

Phase Linear's new noise reduction system is claimed to reduce noise by 10 dB even on recordings that have already been Dolby or dbx processed.

is based on what Phase Linear claim is the principle that "The human ear doesn't hear noise when accompanied by music." It incorporates circuitry that recognises harmonic relation-What the ships. circuit recognises as 'music' is sent direct to the output stage; what it thinks is 'noise' is expunged.

But not all music nowadays consists entirely of harmonious mixtures of tones that an elec-

The 1300 Series Two system tronic circuit can recognise.

Much avant-garde serious and popular music uses some sounds that in other contexts would be considered noise.

Phase Linear's circuitry probably not capable of sensing when this is happening and lovers of such music would perhaps be better off not spending \$349 on a machine which is likely to impose a kind of aesthetic censorship on them.



Planar 2 released in Australia


The Rega Planar 2 turntable, once described by UK magazine Hi-Fi Answers as at least the third best in the world, is now available in Australia.

Intended as a 'budget' version is somewhat thinner, the mat is arm is \$445 and a cartridge stead of laminate. adds a further \$45 to the price.

The Planar 2 is fundamentally a very similar design to its made in the UK and distributed illustrious up-market relative, in Australia by Concept Audio with a few modifications to re- Pty Ltd, P.O. Box 422, Dee Why, duce the cost. The glass platter NSW 2099. (02) 938-3700.

of the renowned Planar 3, the also thinner and rubber backed Planar 2 turntable alone sells for instead of being all felt and the \$335. Price with its own tone- base is made of chipboard in-

Rega Planar turntables are

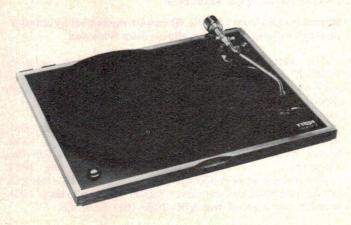



Heavy.

Introducing another Sony only. The MDR series open-air headphones. The smallest, lightest stereo headphones available today. Or tomorrow.

With our lightest at 40 grams, you will barely know you're

wearing them. Yet the sound is dynamite.

Through a remarkable new audio breakthrough, our engineers have succeeded in reducing big-headphone technology down to the size of your listening channels.

The MDR series headphones' airy spaciousness delivers absolute clarity through an ultra-small driver


unit that produces more than three times the energy of conventional circuits. And a new high-compliance diaphragm accurately reproduces the 20 to 20,000Hz bandwidth and improves low-range response.

That means you can listen to the heaviest of music for hours. Lightly. And know that you're hearing every nuance of the original recording from deep bass to the highest treble.

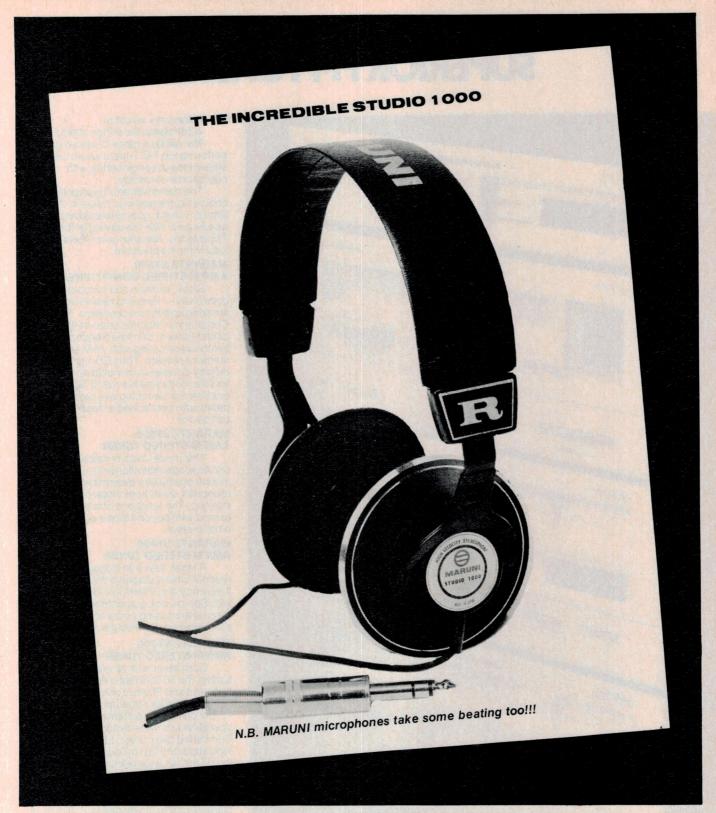Listen to our new MDR series headphones.
They're light.
And heavy.







MARUNI

SUPERLATIVE HEADPHONES AND MICROPHONES

THE MARUNI CORPORATION

297 WILLIAMSTOWN ROAD, PORT MELBOURNE, 3207 • TELEPHONE, 645 2079 • TELEX 32571

RARE ADDITIONS FROM MARANTZ. SUPERIOR FM TUNERS.



Rare: very valuable.
Addi'tions: the things added.
Ma'rantz: a range of ultra-high
performance FM Tuners which blend
state-of-the-art engineering with
operational versatility.

The name Marantz guarantees your choice from a superior range of AM/FM Stereo Tuners, guarantees exceptional quality and, with the advent of more FM stations, Marantz guarantees your

total listening pleasure.

MARANTZ ST500 AM/FM STEREO COMPUTUNER

Sleek, slimline and microprocessor controlled — tune and recall stations with amazing speed and precision. The Computuner features state-of-the-art, quartz-locked, drift free frequency synthesised tuning with 7AM and 7FM memory presets. The LED signal strength display doubles as a multipath indicator and the Wide and Narrow IF Selector enables the switching of a tuning bandwidth best suited to reception area conditions.

MARANTZ ST600 AM/FM STEREO TUNER

This model incorporates a built-in oscilloscope that affords the most precise means possible to determine optimum reception, even from weak or distant stations. The functions of the oscilloscope extend well beyond those of conventional tuner meters.

MARANTZ ST400 AM/FM STEREO TUNER

A large, fuss-free Vacuum Fluorescent readout clearly displays the selected frequency and Electronic Gyro-Touch with Servo-Lock guarantees drift-free, razor-sharp tuning every time. Uncompromising quality through and through.

MARANTZ ST300 AM/FM STEREO TUNER

Consistent with all quality Marantz tuners, the ST300 features MOSFET FM front end and Phase Lock Loop demodulator for superlative performance — low distortion, extremely linear operation and wide dynamic range. Illuminated dial cursor, LED function indicators and Gyro-Touch tuning make the ST300 an exceptionally sophisticated buy at a modest price.

Your Marantz stockist will be pleased to demonstrate the complete range of Marantz tuners. If you see your hi-fi as an investment and, if you demand critical performance standards as well as the best value for money, listen to the future.

Listen to Marantz.

Now you're listening.

Distributed by: MARANTZ (AUST.) PTY, LTD. 32 Cross Street, Brookvale, N.S.W. 2100 Telephone: (02) 939 1900 Telex AA 24121 Melbourne (03) 329 7655 Brisbane (07) 48 8882 Adelaide (08) 223 2699 Perth (09) 328 3874

TEAC breaks away from tape.

The introduction of a new amplifier system marks a break with TEAC's former policy of specialising in tape recorders.

The PA-7 preamplifier and its complementary MA-7 power amp are both direct coupled designs with exceptionally high slew rates. The MA-7 is claimed to have no more than 0.003% distortion from 10 Hz to 20 kHz and the PA-7's distortion is said to be less than 0.005% over the same range. TEAC neglect to say at what output power these figures were obtained.

To avoid damage caused by dc voltages appearing on the signal path (which can be very dangerous for a DC amp), the cuit prevents the popping noise PA-7 incorporates special pro- that would otherwise appear betection circuitry and muting cause of power surge when the relays that shut off the output if unit is switched on and also any signal below 2 Hz and above prevents clicks when switching 60 mV appears. This same cir- phono inputs.



The PA-7 has a moving coil input. headamp built in. Input sensitivity on the moving coil input is 5 mV at 1 kHz and the frequency response is better than 20 to 20 000 Hz at ±0.2 dB for any

The MA-7 power amplifier can deliver 150 W per channel into eight ohms. It has completely separate power supplies for left and right channels.

Arena for A & R

The highly-regarded products of the UK company A & R will soon be marketed in Australia by Arena Distributors.

A & R's reputation is based on relatively small number of units their A60 amplifier, a slimline unit with a nominal rating of 35 watts into eight ohms, whose success is largely due to its reliability and ability to cope with a wide variety of input sources without distortion. The company also make an FM stereo tuner and have recently introduced a moving coil head amplifier in response to demand from audiophiles.

The company is still basically a cottage industry, producing a WA 6101. (09) 361-5422.

which are all subjected to rigorous checks before they are released from the factory.

example, to test the overload protection, all amplifier circuit boards are given a short circuit on the output terminals for ten seconds at full power.

For more information on A & R products contact Arena Distributors Australasia Pty Ltd, P.O. Box 178, East Victoria Park,

Audible demagnetisation

A tape head demagnetisation device just introduced into this country from the USA emits an audible tone that rises in pitch as the demagnetisation proceeds.

The Whistle Stop demag- increases with frequency the well over 20 kHz in the course of six seconds after the 'Play' switch on the tape recorder is pressed. The oscillator output is applied to a built-in demagnetising coil that produces an alternating magnetic field of gradually increasing frequency.

The oscillator output has a constant amplitude, but because the reluctance of the coil 3700.


netising cassette contains an amplitude of the alternating oscillator whose frequency in- magnetic field at the heads creases from below 60 Hz to steadily diminishes as the frequency increases. This results in effective demagnetisation of the


> The Whistle Stop comes in a standard size cassette case, equipped with its own batteries, and retails for \$19.95. It is distributed in Australia by Concept Audio Pty Ltd, P.O. Box 422, Dee Why, NSW 2099. (02) 938-

Scaling the peaks


The Soundex division of Bulgin Electronics recently released a full range of audio peak programme meters.

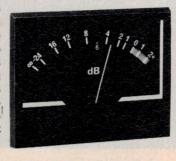They are available in three different standards in both single channel and stereo. The Series 100 was designed to meet the exacting requirements of the British Broadcasting Corporation, the Series 300 is designed to DIN 45406 and BS 5428 (Type 1) and the Series 400 is an economy version that closely resembles the BBC style



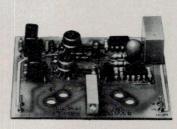

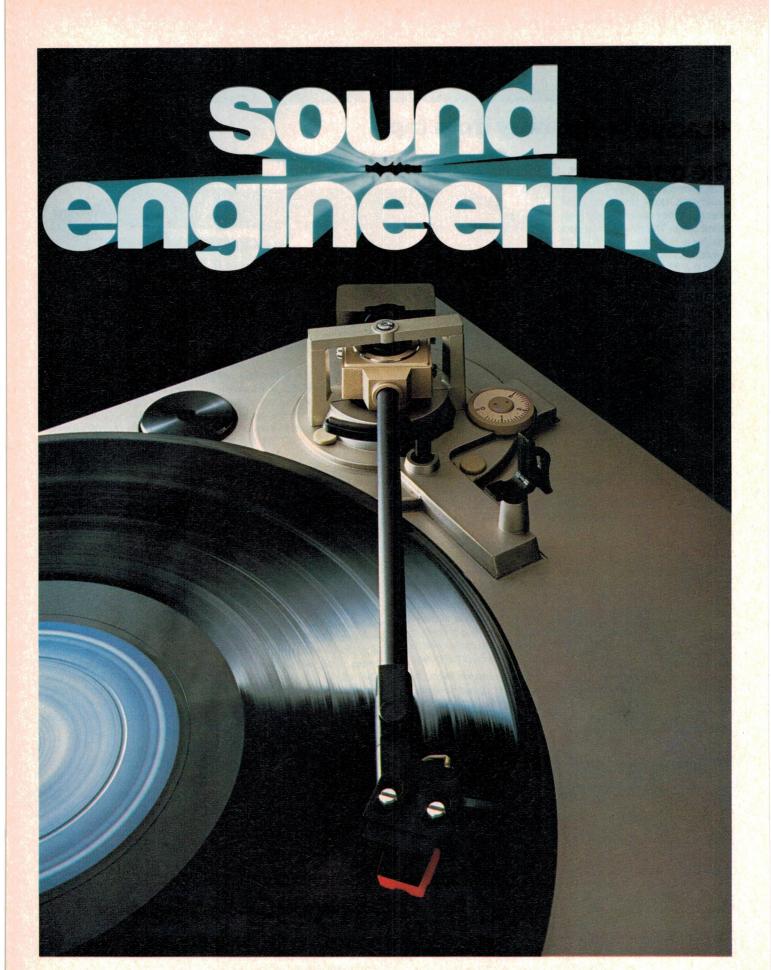The meters comprise a sophisticated meter movement with fast ballistics and an amplifier with a high input impedance and low thermal drift. More information from the distributors, R.H. Cunningham Pty Ltd at P.O. Box 4533, Melbourne, Vic. 3001. (03) 329-9633 or P.O. Box 214, Neutral Bay Junction, NSW 2089. (02) 909-2388.





Hitachi's Photo Sensing Straight Tonearm

The optically-activated straight tonearm eliminates side force and reduces mass to keep the HT-60S Turntable in line with excellence.

The photo sensing straight tonearm is sound engineering. Precision engineering. Optical activation does away with the side force that's common to conventional systems. And the straight tonearm is significantly lower in mass, so sound quality is greatly improved. In the HT-60S Turntable these two design advances are joined by

Mechanical side force

a Quartz-locked Unitorque motor. It makes every revolution of the platter exceptionally smooth. Wow and flutter is just 0.025% WRMS.

The benefits of non-contact switching are readily apparent — every time you play a record. Distortion-producing mechanical parts have been replaced by a light beam and a photo sensitive cell. There's no drag, less required tracking pressure and it's very reliable.

The straight arm is a responsive design that cuts resonance way down and resists oscillation. And it can be used with a variety of high-performance, low-compliance cartridges.

(B) Hitachi photo sensor tone arm return system with LED

The HT-60S Turntable is fully automatic, of course. But all auto functions are independently powered, so there's no drain on the main drive motor. And the

controls for those functions are right up front. You never have to lift the dust cover to get to them.

Hitachi technology is at work to bring you greater turntable accuracy through advanced design and electronics. The HT-60S Turntable with photo sensing straight tonearm and Unitorque with Quartz is the result of those efforts. Listen to the soundness of Hitachi engineering today.

(A) Conventional mechanical sensor tone arm return system Graphic illustrations are reconstructed from Hitachi Toyokawa audio laboratory data.


Professional sound through sound engineering

best sound reproduction






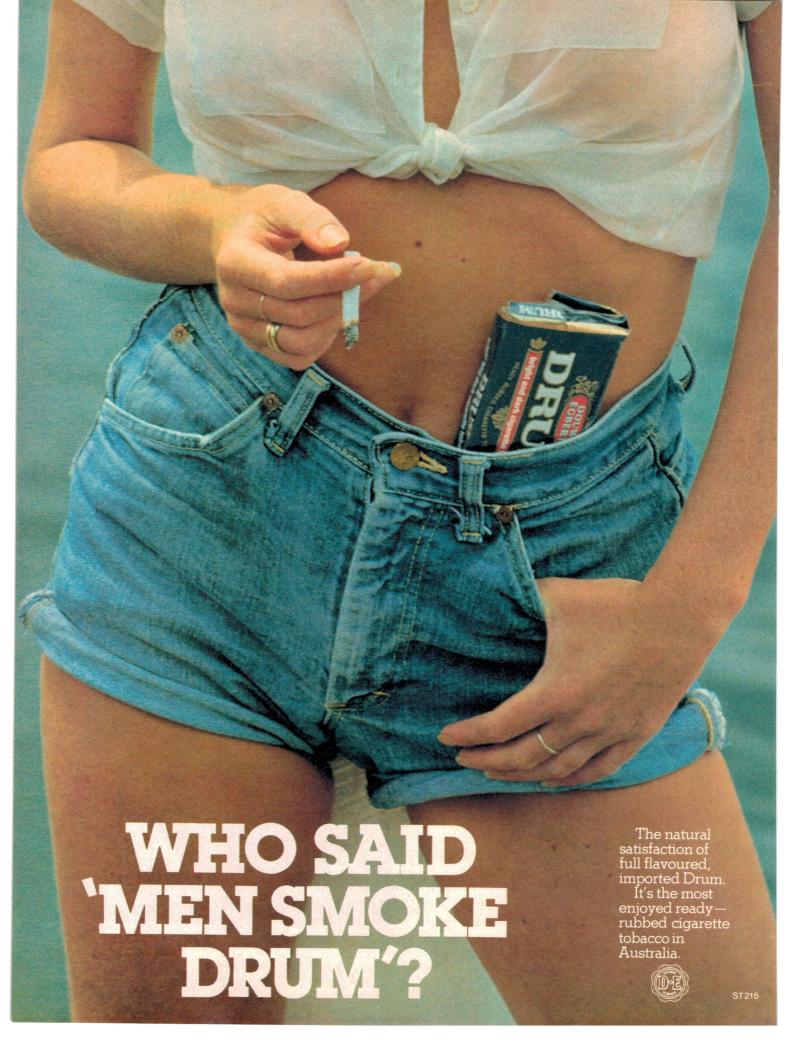
Hitachi Sales Australia Ptv Ltd. 153 Keys Road, Moorabbin, Victoria 3189 Tel: 95 8722



PCB's

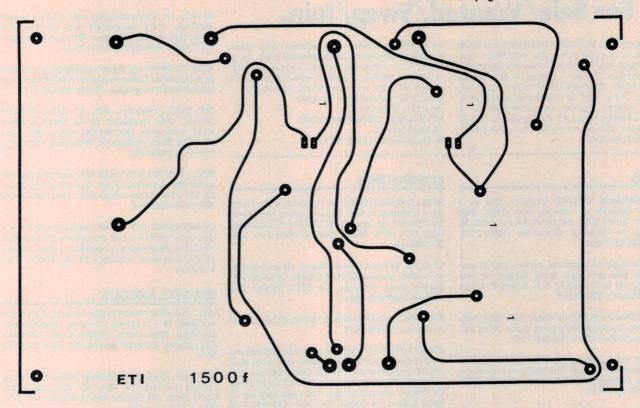Instructions on how to make your own pc boards using the Scotchcal method and exposing through this page may be found on page 113 of the March '80 issue.



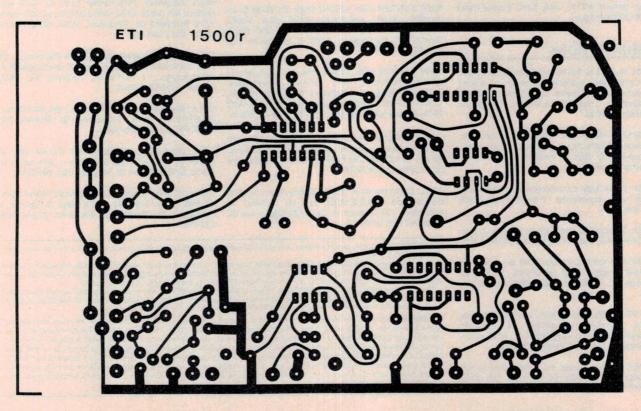

WIND-WART

Where readers can advertise — For Sale/Wanted/Swap/Join.

• We'll publish up to 24 words (maximum) totally free of charge for you, your club or your association. Copy must be with us by the 1st of the month preceding the month of issue. Please — please — print or type adverts clearly, otherwise it may not turn out as you intended! Every effort will be made to publish all adverts received however, no responsibility for so doing is accepted or implied. Private adverts only will be accepted. We reserve the right to refuse adverts considered unsuitable

• Conditions: Name and address plus phone number (if required) must be included within the 24 words. Reasonable abbreviations, such as 25 W RMS or 240 Vac, count as one word. Adverts must relate to electronics, audio, communications, computing etc general adverts cannot be accepted.

Send your advert to: **ETI Mini-Mart, Modern Magazines** 15 Boundary St, **Rushcutters Bay NSW 2011**

AUDIO

SELL: Kenwood KSQ-400 amplifier. Use as 4 channel decoder or stereo amp \$100. Pair speakers 2-way 25W, excellent sound \$100. M. Johnson, 31 Hazel St, Girraween, NSW 2145. Phone (02) 631-2092.

The Tape Club of Australia invites you to join others in this new club. Make friends all over Australia and New Zealand. Full details P.O. Box 118, Wellington, NSW 2820.

Acoustic Research XB1 turntable. Exc cond, new Shure mag. cartridge. Very good specs. Must sell. \$180 o.n.o. Phone Chris (02) 939-7141.

QUAD 22 valve preamplifier \$85. Dynaco Mark 3 mono valve power amps 60W RMS, mint condition \$400 pair. G. Page, 17 Elm St, Unley Park, SA 5061. Phone (08) 271-9191.

AMPLIFIER wanted. Phase Linear 400. Must be in good original condition.

For sale. Sansui AU717, only \$440. Phone Peter (08) 31-5220 after 6 p.m.

COMMUNICATIONS

WANTED: R.1155-N, Ex-R(A)AF communications receiver, preferably working but other condition/model acceptable. I have appropriate manual. John Lavender, 3 Raw Place, Farrer, ACT 2609. Phone (062) 86-4029.

AUSTRALIAN Radio DX club for shortwave, mediumwave DXers. For a sample copy send one 22c stamp to P.O. Box 79, Narrabeen, NSW 2101 mentioning this ad.

WANTED: Valve type communications receivers. All ages and conditions. Phone Peter (042) 29-5047 a.h.

WANTED: Teleprinter, mod 15 or similar. J. Lee, MS 30, Chinchilla, Qld 4413. Phone (074) 65-8183.

SELL: SX-190 extra crystals \$165 or exchange for Barlow Wadley MKII or DR-28. N. Glaros, 11 Norman St, Underdale, SA 5032. Phone (08) 43-4981.

YAESU FT-7 SSB transceiver. Ideal for novice. 80m-10m, excellent condition, all manuals, accessories and mounting bracket. \$429 o.n.o. Phone Stephen Dennis (02) 630-5552 a.h.

TELETYPE ASR-33 good condition \$550 o.n.o. John Delforno, 4 Argyle St, Glenroy, Vic 3046. Phone (03) 306-1464.

COMPUTERS

SELL: OSI(6502) 8K BASIC in ROM (4 x 2k chips). I have changed to disk and no longer need them. \$80 the set of four. Geoff Cohen, 72 Spofforth, Holt, ACT 2615. Phone (062) 54-7608 b.h., (062) 49-2688 a.h.

SYSTEM 80 owner would like to swap programs with other owners. Mark Fairbairn, 8 Shelley St, Spring Gully, Bendigo, Vic 3550. Phone (054) 42-4450 weekend only.

S100 16K static RAM Board, 450 ns, ETI-642. \$280. Alan Peek (02) 89-1450.

Z80 STARTER KIT: Hex key pad, hex address and data displays, 2 x S100 sockets, wire wrap area, PROM programmer, parallel port, Kansas City cassette interface, timer chip (Z80 CTC), 2K moni tor PROM, monitor listing, 120 page manual, 2K RAM. \$250 o.n.o. Phone Paul Forte (03) 615-4183 b.h., (03) 543-5451 a.h.

S100 SYSTEM sale, DG640 \$120, 8K RAM \$150, monitor \$150, mainframe \$120 plus VDMII. modem, keyboard, 2650, SCMP IO, 466 North Rocks Rd, Carlingford, NSW 2118. Phone (02) 871-2858.

JOIN OMEGA (OSI Microcomputer Enthusiasts Group Australia) and receive newsletters, hardware mods and software exchange details. Contact Geoff Cohen, 72 Spofforth St, Holt, ACT 2615. Phone (062) 54-7608 a.h., (062) 49-2688 b.h.

OSI C2/4/8 owners, join 540-Board Mutual Benefit Society. Resources all areas. Need members. Please send S.A.E. to Peter Meulman, 4 Halsmere St., Geebung, Qld 4034.

SELL: Crystals, new 12MHz, divide down to MPU frequencies (6,4,3,2,1MHz are all factors) 12 available - \$4.50 each. N. Cook, 22 Brightman St, Flagstaff Hill, SA 5159.

SELL: Dream 6802 with H/D power supply, cassette recorder, tapes, spare ICs, no bugs. \$200. P.O. Box 283, Carnarvon, WA 6701.

WANTED: Documentation for Polymorphics CPU card 101031, and VIDEO card (Especially I/O pinouts, jumpers and monitor commands). Xerox or original. Ken Grimes, 51 Dudley St, Sherwood, Qld 4075. Phone (07) 379-3895.

EA2650 1K microcomputer with CUTS cassette interface. Fully assembled and working \$100 o.n.o. Roy Anton, P.O. Box 333, Coonabarabran, NSW 2857. Phone (068) 42-1470 a.h.

WISH TO SWAP my Sargon computer chess book or program for Eddie Paay level II ROM map. Cash adjustment if necessary. Phone (02) 337-2317.

Z80 S100 computer. 48K. 5" Drive, Selectric printer, VDU, keyboard. CP/M, Macro assemb, word processor, disk BASIC, chess and more. \$2500. A. Peek, 10 Gale St., Woolwich, NSW 2110. Phone (02) 89-1450.

SELL: TRS 80 Level II with 32K, numeric pad and expansion interface. Also disk drive and Axiom EX 801 microprinter. Best offer. Max Hooper (02) 399-5158 evenings.

COMMODORE PET — 16K business version and Decwriter printer — full documentation, software including diagnostics, assembler, editor, listings, circuit diagrams, manuals \$1400. Phone Chris 419-4424

MISCELLANEOUS

SELL: Schober theatre organ, kit-built. 2 x 61 note manuals, 16' - 1' voicing, pre sets, couplers, percussions, tape-reverb, amplifiers etc. Complete and playing. Bargain opportunity. Gary (03) 233-

WANTED: Wireless World May 1972 or data of advanced preamplifier. Pay \$5. Very desperate. Louis Ziras, 144 Beavers Rd, Northcote, Vic 3070. Phone (03) 481-1209.

SELL: Amplifier, Playmaster Twin 40, built and tested. Kit costs \$129, will sacrifice at \$80 cash. 7/14 Burtfield Dr, Chiswick, NSW 2046. Phone Chris (02) 712-1460.

FOR SALE: Automatic telephone equipment. 25 pos. switches 200 relays. Sell or exchange. E.A. Whatmough, 14 Heriot St, Lismore, Vic 3524. Phone (03) 055-962145.

SELL: Magazines. ETI 72-79 inc., EA 69-79 inc., PE 69-78 inc. Greg, 12 Coombell St. Jindalee, Qld 4074. Phone (07) 376-1484.

SELL: Wire wrap sockets, new, 14 pin DIL, in boxes of 7. Ten boxes available — 50¢ each. N. Cook, 22 Brightman St, Flagstaff Hill, SA 5159.

CAPACITORS: Tants 220uF 10vw \$3 100uF 25vw \$2 Met. Poly. 3uF3 \$1 + 40c pep. R. Barratt, 2 Davidson Av, Parkholme, SA 5043. Phone (08) 277-2982.

COPYRIGHT: The contents of Electronics Today International and associated publications is fully protected by the Commonwealth

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards. Although any form of copyright extends to all written material, protographs, drawings, circuit diagrams and printed circuit poards. Authorigh any form or reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold, in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Modern Magazines (Holdings) Ltd or from the copyright holders.

LIABILITY: Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any components parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid. The Publisher accepts no responsibility for unsolicited manuscripts, illustrations or photographic mater



PHILIPS LOUDSPEAKERS

PROFESSIONALLY DESIGNED SPEAKER KITS

If you are in the market for a \$2000 set of speakers with only a few hundred dollars in your pocket, we could have just what you want. The ETI 4000 Series Speakers - using Philips Drivers compare very favourably with speakers costing twice to three times as much. If you are on a really tight budget you could consider the Philips AD12K12 kit - a 70 watts r.m.s. per channel 12" 3-way system - which you assemble completely in about 2 hours. A steal at under \$300 per pair. You can buy all components with or without boxes, any way you like. We have both the ETI 4000-I and II on display, as well as other Philips Kits. Come in for an audition, or write for further information.



Price per box of 10 OPUS UD \$19.00 **AMPEX PROFESSIONAL** \$16.90 **AMPEX 20/20** \$21.30 AMPEX GRAND MASTER I \$36.00

Mail order charges:

Up to 20: \$2.75 20 to 50: \$3.50 Over 50: \$5.00

northpoint hi-fi 100 Miller St, North Sydney. Ph 922-7780.



380 SUSSEX STREET, SYDNEY, NSW P.O. BOX K39, HAYMARKET 2000 **Telephone 264-6688**

AUDIO SPECTRUM ANALYSER



The 489 Analyser can be used in conjunction with a Graphic Equaliser to accurately equalise systems for room acoustics

Features:

- Ten octave spaced displays
- LED readout in 3 dB steps.
- Input sensitivity control.
- Inbuilt pink noise generator.

Complete kit includes matched LEDs, polarised plastic display, complete metalwork, etc.

ONLY \$142 plus \$3 freight.

100 WATT POWER SLAVE

This rugged, compact amplifier is ideal for PA, disco, foldback or guitar amp use. 2-input Preamp with tone controls or 10-way Equaliser can be built into the same cabinet

Features:

- Robust construction.
- Handles for portability
- · Cannon mains input, quick connect speaker terminals.
- Attractive finish in light

Complete kit ONLY \$105 plus \$3.50 freight. 2-input Preamp with front panel \$25.



Introducing a totally new concept in stereophones.

The new Koss HV/X high velocity stereophone represents a remarkable breakthrough in hear-thru stereophone design and performance. For the first time, Koss engineers have been able to create a lightweight, hear-thru stereophone that combines the transparency of high velocity phones with the superior bass performance of closed-type phones. The result is a breathtaking musical experience.

CONTOURED VARIABLE-DENSITY EARCUSHIONS

While most lightweight, hear-thru stereophones have earcushions that fit against the ear, the new Koss HV/X features a unique, contoured, variable-density cushion that fits around the ear. Not only does this unique earcushion design create

earcusnion of a far more comfortable stereophone but it has also allowed Koss engineers to create a dramati-



SECTION OF THE PARTY.

design as well. These new variabledensity earcushions are made up of a very porous material that is acoustically transparent at the perimeter of the earcushion yet compressed toward the center region. This varies the pattern of acoustic resistance over portions of the earcushions creating the proper seal for specific bass frequencies while allowing the flow of middle and high frequencies at the perimeter of the earcushions.



The uniqueness of the new variable-density ear-cushions made it possible

for Koss engineers to design a lightweight element that reproduces a Sound of Koss you have to hear to believe. Incredibly, even though the overall weight of the element was reduced, Koss engineers were able to develop a magnet with enough magnetic density to drive an extra large diaphragm. With a response range of 15 to 35,000 Hz, the new Koss HV/X will drive you into ecstacy and our competitors nuts.

HEARING IS BELIEVING.

Slip into the new Koss HV/X or HV/XLC with volume/balance controls at your audio dealer soon. You'll like the best of both worlds: the open, airy, upfront sound of hear-thru stereophones and the deep, rich bass performance of closed-type stereophones.

For more information on the HV/X and our full line of stereophones write to



ELECTRO-VOICE AUSTRALIA PTY. LTD.

© 1980 Koss Corp.

©KOSS*stereophones/loudspeakers hearing is believing™

ELECTRO-VOICE AUSTRALIA PTY. LTD. 174 Taren Point Road, Taren Point, NSW, 2229. Phone (02) 525-8588.

cally better element

Not Hazardous To Your Head.

Cleaning a video cassette recorder is one thing, not hurting the heads is another. The new Allsop VHS Video Cassette Cleaner completely cleans the (1) Audio Head, (2) Video Head, (3) Pinch Roller and (4) Capstan. It saves your head because: 1. It's a healthy alternative to the abrasive continuous


loop tape cleaner. Push play button to start; it stops automatically. 2. Uses a soft, absorbent cleaning chamois to clean video and audio heads in about 4 seconds flat. 3. Uses non-abrasive felt pad to wipe pinch roller and

capstan clean. Saves you money. You can use the original Allsop Video Cleaner forever. Cassettes should be cleaned every 30 to 50 hours of playing time and replaced after one year — with a replaceable cleaning cartridge supplied with solution. This eliminates the necessity of purchasing another

complete cassette.

Available at all leading retailers of video products

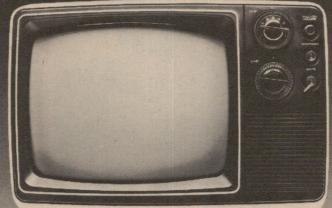Sole Australian distributor: Communications Power Inc. (Aust) Pty Ltd P.O. Box 246, Double Bay NSW 2028. (02) 357-2022 Telex AA23381





The craft of the speaker box maker

There's more to making a speaker box than first meets the eye. Despite automated woodworking machinery, or more likely, with its assistance, the manufacture of speaker boxes is still more a craft than an assembly job.

NEXT TIME you walk into a hi-fi store, have a look at the loudspeakers on display. Chances are that, despite the Japanese, European or even American 'brand name', it has been assembled here, using a locally-made box. It's a big industry, in terms of quantity, and competition is tough at both the so-called 'budget' end of the market as well as the 'top-line' end. At each year's annual Consumer Electronics Show we have never failed to be staggered at the array of speakers, both in kit form and readymade, on display. Quite apart from the number of 'all-Australian' speakers available, we were recently surprised to learn the extent to which overseas companies have their speakers locally assembled.

So, when Chadwick Audio Furnishings Pty Ltd offered to show us their factory, we jumped at the opportunity. We found the whole operation fascinating and thought readers might like to see 'behind the scenes' too. Our photographer, Ivy Hansen, followed the proceedings and recorded the 'evolution' of a speaker box from blank board to the finished article.

The company

Chadwick Audio Furnishings was started in 1972 by Wayne Chadwick. The venture began life as virtually a 'hobby' business which Wayne conducted from his home (as all good hobby businesses start ...). Business progressed apace and an associate, David Crabtree, bought into it in 1974. In 1978, the firm became a proprietary limited company with David Crabtree at the helm and in mid-1978 he bought factory premises in the Sydney industrial suburb of Silverwater and installed some quite sophisticated woodwork production machinery.



David Crabtree

Apart from doing a considerable amount of OEM work, Chadwick produce a small range of locally designed loudspeakers, dubbed their "Executive" range. Top of the line is the Executive Monitor, a four-way system, then the Executive 12, followed by the Executive 10. All are finished in wood veneer — in which the company specialises.

Okay, okay — we can hear readers clamouring already for us to review a pair from the Executive range, especially as they're Australian designed and manufactured (see November editorial). All in good time. Apart from speaker boxes, Chadwick make speaker stands and equipment cabinets.

What happens

The pictures tell the story, for the most part. Great sheets of veneered and plain particle board provide the raw material. Particle board is ideal for speaker box material as it's dense, has generally uniform characteristics, is easier to 'work' than timber and boxes generally suffer from fewer resonance problems compared to timber. It's less expensive, too. The sheets are cut into appropriate strips, calculated so that the least waste is produced.

The cabinet top and sides are formed from a single strip, grooved and chamfered so that it can be folded around the front and rear panels. That edge of the strip which is to appear to the front of the cabinet is specially grooved so that it can be 'rolled back' on itself and glued, the veneer then continuing around the front lip of the cabinet right to the front panel. Very cunning — and a precision job.

The panels then have the corner chamfers cut in them. Power driven circular blades cut two slots at 45° to the plane of the panel right to the veneer, without cutting the veneer! The veneer then acts as a hinge when the panel is assembled. It's quite a precision job, too.

At the same time, the front and rear panels have the appropriate holes cut in them and all the pieces are brought together for assembly. Glue is run in the grooves in which the front and rear panels sit, the panels inserted and the cabinet literally folded together around the front and rear panels. The box is then put in a jig for setting. Small strengthening 'chocks' are glued in at this stage. When ready, the cabinet is cleaned up and sent for oiling or spraying and final finishing work. If drivers and crossover etc. are to be assembled in the box, then it goes to a final assembly line, otherwise it's packed and shipped to the customer. Assembled speakers are tested before despatch. There you have it! The 'evolution' of a speaker box, from blank board to finished article.



fact: there's a Shure microphone that's right for your application & equipment...



rugged and superb sound.


SM59

You've seen it on TV musical shows where sound quality is a must. Unidirectional, dynamic with exceptionally flat response, extremely low handling noise; mellow, smooth, and accurate



The most widely used "on-stage hand-held dynamic cardioid

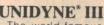microphone—the world standard noted for its distinctive, crisp sound



The world-famous UNIDYNE® III family offers top value per dollar. Uniform car-

dioid pattern helps control off-axis coloration, background noise, and

SM61

Omnidirectional dynamic. Outstanding low handling noise.

Handsome, smooth looks with new VERAFLEX® dentresistant grille—a favorite on-camera mic with soundmen and entertainers.


342 Kent Street 2A Hill Street 51A Castlemaine Street SYDNEY 2000 N.S.W. THORNBURY 3071 Vic. MILTON 4064 Qld.

AUDIO ENGINEERS P/L AUDIO ENGINEERS (Vic.) AUDIO ENGINEERS (QId.)

lick Jagger

NOMIS ELECTRONICS P/L 33 Wittenoom Street 689 South Road EAST PERTH 6000 W.A. BLACK FOREST 5035 S.A.

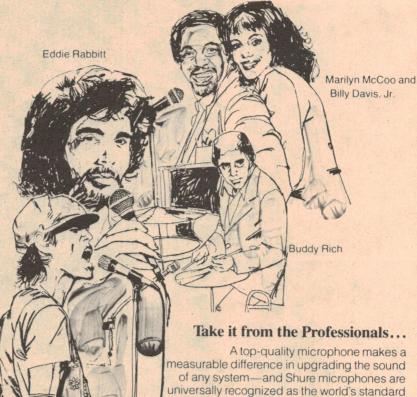fact: the microphone is your link with your audience



A top-quality microphone makes a measurable difference in upgrading the sound of any system—and Shure microphones are universally recognized as the world's standard of quality. Wherever sound quality, reliability, uniformity, and intelligibility are prerequisites, you'll find that professionals choose, and use, Shure. You'll find more Shure microphones than any other single brand in applications as

diverse as live entertainment, radio and TV. hotel and auditorium sound reinforcement, churches and temples; Congress, legislatures and the White House, and public safetyanywhere that sound excellence is a prime consideration. They are the reliable,

professional connection between you and the people you're trying to reach. Send for complete literature. Please let us know your microphone application.

The Sound of the Professionals



MHY YOU ARE



Up to now, if you wanted a terrific pair of loudspeakers you had to hassle with wasted Saturday mornings and Thursday nights listening to a myriad of salesmen when you should have been listening to the loudspeakers they were standing in front of. Did they have something to hide?

Hassle no more. Because we have developed a pair of loudspeakers with enough unique features to place them far beyond **brand X, Y** and **Z**. And place you beside your phone ringing Chadwick to find out where you can get a pair.

To build the pair, we began with two terrific 245 Erone 300mm bass drivers, which we made even better with a unique modification.

Then we added two Audax 160mm full range Bextrene cone drivers,

which we loaded in a transmission line enclosure, vented at the rear.

Next we added two Audax 25mm domes and two 50mm aluminium

cone super tweeters.

Finally we linked them all together with a crossover especially designed

for this particular configuration. The sound that emerged from the completed pair was amazing. Just

what you would expect from Chadwick.

But being the perfectionists that we are, we further added mirror

matched baffles for very tight stereo imaging.

We called the pair "Executive Monitor". Even the name sounds

If you can't afford the "Executive Monitor" (\$990 a pair), we have two

other "Executive" models that have also been meticulously developed and engineered:
"Executive 12" (8499 a pair) and "Executive 10" (8449 a pair).

If you have already listened to Brand X, Y and Z, when you listen to a
Chadwick lousdspeaker pair you will wonder why it wasn't your first choice.


For more information phone Chadwick today on (02),647 1103.



GM + ASSOC/Eti/12/80

- Low Noise
- 4 Stereo Program Inputs
- 2 Microphone Inputs
- 5 Channel Stereo Equaliser
- Full Cueing Facility

STUDIO DISCO MIXER

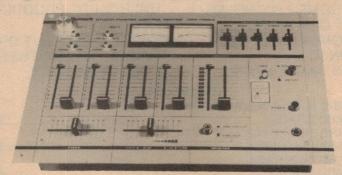

SPECIFICATIONS

Hum And Noise

Input Sensitivity	MIC	0.5mV 3mV	
Input Impedance	MIC PHONO	150mV 10K ohms 50K ohms	
Maximum Input Level	LINE MIC PHONO	50K ohms 45mV 140mV	
Rated Output	LINE AMP REC	35V 1V 1V	
Output Impedance	100 ohms		
Harmonic Distortion	At Rated Output 0.2%		

MIC PHONO LINE -52dB -62dB -65dB MIC PHONO LINE 30 to 16000Hz (-1dB) 30 to 20000Hz (RIAA±2dB) 20 to 30000Hz (-1dB) Frequency Response Equaliser Section Control Frequencies Control Range Control Type Headphone Output (CUE) Talk Switch Power Consumption 60Hz, 250Hz, 1kHz, 3.5kHz, 12kHz ±12dB, Boost or Cut Slide Centre Detent for "Flat" setting 50mW at 75 ohms at 0.5% THD 14dB at Phono or Line at TALK Position AC 240V 50/60Hz 8 Watts 15.3" (W) x 3.7" (H) x 10.2" (D) Dimensions Shipping Weight

*Trade Enquiries Welcome


Distributed by 89-91A LIVERPOOL ROAD, SUMMER HILL, NSW 2130

MANUFACTURERS . IMPORTERS . WHOLESALERS SALES AND SERVICE TO ALL SOUND EQUIPMENT TELEPHONE (02) 797 9941, 797 0986

ENTER THE 80's NOW WITH

UNI-BOARD

THE "UNIVERSAL" CIRCUIT BOARD

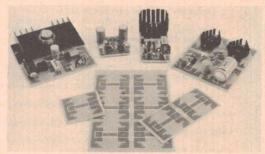

BUILD ALMOST ANY CIRCUIT

- AMPLIFIERS
- REGULATED POWER SUPPLIES
- LINEAR IC CIRCUITS
- DIGITAL IC CIRCUITS
- PRE-AMPS, TONE CONTROLS
- STANDARD 6 PACK UNI-BOARD (41" x 6½") HAS SOME 2,800 HOLES SO IT CAN EASILY ACCOMMODATE EVEN 40 PIN IC's
- MANY, MANY MORE!

ECONOMY PLUS!

UNIBOARD WILL SAVE YOU MONEY.

- NO WASTE SURPLUS BOARD CAN BE USED ON ANOTHER PROJECT
- USE AGAIN & AGAIN
- LOW COST "BREAD BOARDING"
- PROTOTYPE LAYOUTS CAN ALSO BE USED FOR YOUR "UNI-BOARD" PRODUCTION RUN
- BOARD EASILY CUT OR TRIMMED TO SUIT THE SIZE OF YOUR PROJECT.

PRICE LIST

I MOL LIST	
UNI-BOARD SINGLE MODULE PACK	
(STANDARD GRADE)	\$2.20
UNI-BOARD SINGLE MODULE PACK	
(PROFESSIONAL GRADE — F/GLASS)	\$2.60
LINI-BOARD TWIN PACK	
(STANDARD GRADE)	\$3.20
UNI-BOARD TWIN PACK	
(PROFESSIONAL GRADE — F/GLASS)	\$3.80
UNI-BOARD SIX PACK	
(STANDARD GRADE)	\$7.97
UNI-BOARD SIX PACK	
(PROFESSIONAL GRADE — F/GLASS)	\$9.90
	40.00
TO: ADVANCED ELECTRONIC SYSTEMS PTY LTD	
3 STANILAND GROVE, ELSTERNWICK 3185	
DI FACE CURRILY	

BAD T.V. RECEPTION

IMPROVE YOUR PICTURES BY FITTING AN AMPLIFIER, PLUS A GOOD QUALITY CABLE.
SUCH AS:

ECRAFT Double Screened Coaxial cable 2045 3.5 dB loss at 216 Mhz per: 30 M 47c per metre.


2063 2.05 loss at 216 Mhz per: 30 M 1.08 per metre. Open-wire feeder 1.5 dB loss at 200 Mhz per 30 M 70c per metre.

FIERS		
Output	Gain	Ratio
300	10 dB	3.1
75	20 dB	10.1
300/75	25 dB	17.1
own on Ch	's 3-4-5A	
75	20 dB	10.1
75	20 dB	10.1
75	28 dB	25.1
75		
	0-6	
	Output 300 75 300/75 own on Ch 75 75 75	Output Gain 300 10 dB 75 20 dB 300/75 25 dB own on Ch's 3-4-5A 75 20 dB 75 20 dB 75 28 dB

ECRAFT Line Amplifiers VHF-UHF

ECRAFT	Line Amplifiers VHF-	UHF
Туре	Outlets	Gain per Outlet
175D16	1	16 dB
275D12	2	12 dB
375D10	3	10 dB
475D10	4	10 dB
175D25	1	25 dB
275D21	2	21 dB
375D19	3	19 dB
475D19	4	19 dB

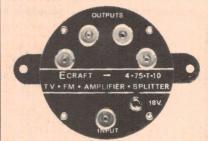These Amplifiers are suitable for installation of extra points in your home. Please phone for prices.





ELECTROCRAFT TH

68 Whiting Street, Artarmon NSW Telephone 438-4308 ext. 6 or 438-3266 ext. 6

WE ARE SPECIALISTS
30 years in the antenna business.
Hours: 8am to 5pm

Prices subject to alteration without notice.

SANSUI DRAMATIZES ITS TECHNOLOGICAL LEADERSHIP AGAIN!



The superb sound quality of the top-of-the-line SUPER COMPO System will impress the most dedicated audiophile. And the unique visual displays combined with easy operation create new pleasures for music lovers. Only Sansui's finely honed advanced technology offers such multi-dimensional benefits.

Take a good look at the C-77 control center preamplifier with its built-in auto/manual fader. The colorful display shows you how smoothly one sound source is fading out while another is coming in. The fact is this is the first time in audio history that such a function has been offered in a quality stereo system.

Now look at the "Linear A" DC-Servo power amplifier. You'll see a large spectrum analyzer display and detailed peak power display. But what you can't see is the Linear A design which eliminates switching distortion for exceptional pure sound you will clearly hear. Combined with DC-Servo circuitry, the B-77 outperforms any other amplifier in its class.

Look at other audio systems and now examine the front of the T-77 Digital Quartz PLL Synthesizer tuner. It allows you to "program in" eight of your favorite AM or FM stations for instant pushbutton recall. In addition, an auto search feature scans either up or down the band until it locks on a good quality station.

The more you look, the more you listen, the more will the tangible advantages of Sansui's special technology impress you and your listeners. Superior musical quality is what SUPER COMPO is all about.



50000 review

Marantz ST500 computer stereo tuner

Louis Challis found this tuner delightfully convenient to operate and praises its "faultless quality of reception".



LARGE SCALE integration, generally in the form of the microprocessor, means that today's electronic equipment can be provided with features that not so long ago were only wild and impractical ideas in the minds of designers. The sophisticated tuning, preset and display features of the Marantz Computer Stereo Tuner are examples of the kind of elaboration that is now feasible.


Design

The external appearance of this tuner is remarkably neat, with black lettering anodised into the brushed satin aluminium escutcheon. The panel is divided into three sections. At the left is a five digit frequency display with green gas plasma digits. In the top left hand corner the words "FM Stereo" are displayed when the signal strength is sufficient and below this is an "ME" display which indicates when the memory is active and the station is stored.

To the right of the digital display is a signal strength and multipath indicator with five rectangular light emitting diodes. These are clear and effective in their operation and normally indicate relative signal strength on both AM and FM. When the multipath switch is depressed, this five-LED array provides (in the FM mode only) an indication of the extent to which there are multipath reflections present on the received signal. These reflections, which occur when radio waves from the transmitter bounce off mountains and tall buildings, arrive at the receiver slightly out of phase with the direct signal and are responsible for much of the sibilance and distortion which characterise poor FM reception. In the owner's manual which accompanies the tuner, Marantz give advice on installing directional antennas to minimise multipath problems.

Immediately below the signal strength and multipath indicators are seven small LEDs which indicate that a preset station has been selected and is actually recorded in the microprocessor's memory. The centre of the escutcheon contains seven rectangular switches numbered 1 to 7 and a "memory" switch. To enter a station frequency in the memory, you tune to that station and press the "memory" switch followed by one of the numbered switches. Many receivers contain batteries to maintain this kind of memory function, but Marantz have designed in storage capacitors to supply power to retain the data for up to ten days. Obviously if you go away for more than ten days you have to rewrite the memory.

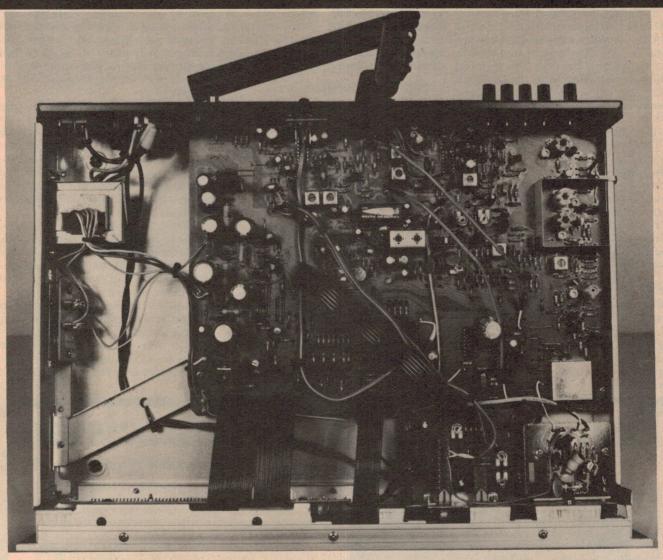To the right of the preset controls are four selector buttons for FM/AM, wide or narrow band on the FM, multipath indication and stereo/mono. The wide/narrow band facility enables the FM bandwidth and frequency response to be narrowed and cut off more steeply to minimise adjacent channel interference where this occurs. In Australia this is not a problem on FM as we do not have



the same station density as Japan and America, but it is a pity that the makers did not provide this facility with the AM tuner as well.

On the extreme right of the escutcheon is a wide switch bar for tuning and scanning. Pressing the right hand side of this bar causes the tuner to scan upwards automatically; pressing on the left makes it scan downwards in frequency. It can be set to scan continuously or to lock onto the nearest station with sufficient signal strength. If it approaches the end of the band without finding a station it switches to the other end of the band and continues the search.

The cabinet is made of neatly pressed and folded steel, finished with a black matt plastic coating. The tuner would be equally at home mounted in a rack or stacked on top of other equipment on a shelf.

At the rear of the receiver are five terminals for 75 ohm and 300 ohm aerial cable termination, a ground connection and an AM antenna connection. The centre of the panel is fitted with a neat plastic encapsulated universal AM loopstick antenna which is attractive and effective, and a scan step control with increments of 9 kHz or 10 kHz for AM and 50 kHz or 200 kHz for FM. The unit supplied to us was adjusted for 9 kHz and 50 kHz steps to suit Australian conditions. Also at the rear are a pair of coaxial sockets for left and right channel outputs, a mains voltage selector and an unusual mains socket which accepts the two-pin plug moulded onto the mains lead.

The inside of the unit is every bit as

neat as the outside and features one large printed circuit mother board, neatly labelled with component numbers and stencilled on top with the track lying underneath. Four minor boards immediately behind the front panel contain the frequency indication, selector switch connections and the tuning search control. All these boards are connected to the mother board in a neat and professional manner.

The mains power transformer and fuses are separately located on the side of the chassis, but the rest of the power supply and all the other components are on the main board. The connections to the input and output sockets are all made directly onto the board and the general impression is of a unit designed for the minimum number of wiring connections.

Project 1500

from page 49

range and switch the *mode selector* to *VLF*. Hold the search head up in the air and well away from metal objects, press the *tune memory* button and rotate the *tune* control. The meter should swing either side of the centre position. Set the pointer to centre scale and release the tune button. The meter should remain at this position but may drift slightly, which it will tend to do immediately after switch on. Pressing the *tune memory* button at any time should return the meter to centre position, set by the *tune* control.

The next step is to determine that the polarity of the receive coil is correct. After tuning the detector as described, bring a piece of iron near the search head. If the meter swings to the right your circuit is correct, if it swings to the left you will have to reverse the two wires on the DIN socket that connect to the receiver section on the pc board. The meter should now swing to the right.

Ground balance

With the detector tuned, lower the search head to the ground. The meter may swing off scale. If it swings to the right turn the *ground* control to the left, if it swings to the left turn the *ground* control to the right. Raise the search head from the ground, press the tune

button and the meter will return to centre scale. Lower the search head again and repeat the procedure until there is little difference in the meter reading when the search head is lowered. Setting the ground control is quite critical and may take some time to achieve the first time around. The detector can now be used in the VLF mode.

Sensitivity control

The sensitivity control sets the gain of the dc amplifiers in the detector and will generally give best results at midrange. If the control is set fully clockwise the tuning will tend to drift, requiring more frequent operation of the tune memory button.

Discriminate controls

The mode switch selects one of three discriminate ranges: TR1, TR2 or TR3, while a vernier action is provided by the discriminate control. The discrimination ability of this circuit is extremely effective and it is possible to discriminate between an aluminium ring pull tab and a gold ring. Remember that discrimination depends on the resistivity of the target object.

When set to TR1, discriminate control at mid-range, the meter should show 'bad' for ferrous objects and 'good'

for non-ferrous objects along with a tone from the speaker. As the discrimination controls are advanced, some non-ferrous objects such as brass will start to give a 'bad' reading, while gold and silver will give a 'good' reading. As the controls are advanced further aluminium will start to give a 'bad' reading, and so on. As you use the detector you will become familiar with its operation.

The best way of setting the discrimination controls is to carry around a few sample objects of the type you want to discriminate against just for this purpose. One thing to remember is that a corroded object will require a different setting of the controls to a non-corroded one so carry samples typical of what you are likely to dig up.

By careful setting of the controls, unwanted objects can be tuned out, giving no meter movement at all so the detector can be used to reject particular objects and at the same time discriminate between others.

Well, it's now up to you. Remember, the secret of success in metal detecting is more knowing where to look than the type of detector you have. There are many books available on the subject which could help put you on the right track.



You spent thousands of dollars getting hi-fi. Keep it that way for a few dollars more.

To maintain the best performance from your cassette, reel to reel recorders and decks. video tape recorders and record playing equipment use Philips Maintenance Products.

Philips manufacture a very large range of maintenance aids to assist you to keep your valuable equipment in good order.

All these and many more products are available from your Philips Service Centre or dealer outlets.




Drop In Cleaning Cassette

Philips Drop In Cleaning Cassette is a complete kit for cleaning, tape head guides and capstan. \$4.20* Code 38920015

Philips RC3000

Hi Fi Record and Stylus Cleaner. Length pivot to pad 200 mm, arm overhang 35 mm. Complete with 2 pads, stylus brush, cleaning fluid. \$25.46*

Code 39590159

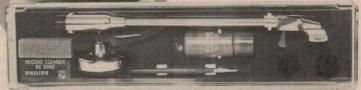

Other popular Philips Service Products.





Philips Disco Combi Set Gets down deep into the recorded grooves with a long lasting velvet pile, complete with special cleaning fluid.\$3.89 Code 39590157

Philips Hi Fi Stereo Headphones

Hi Fi Stereo Headphones with twelve extra membranes for spatial sound. \$96.00*

Technical Data (Subject to modification without notice) Frequency response 16-20000 HZ (±3.5 DB); Impedance (nominal) 2 x 600 ohm; Sensitivity 94 DB 2 x 600 onm; Sensitivity 94 DB S.P.L. at 1 MW; Nominal power input 2 x 1 MW; Maximal power input 2 x 200 MW; Distortion <1%; Weight 390 g approx. Code 242 47017





Philips V.C.R. Cleaning

Maintains highest quality of picture and sound. removes deposits from video, audio heads and tape guides. Use every 30 hours for maximum results. \$19.20* Code 39590102

Head Renovator Cassette

All recorders eventually lose performance through their heads becoming gradually magnetized Thanks to the new SBC 137 you can effectively clean and demagnetize recorder heads all in one easy operation. \$4.85*

Code 39590165

*Recommended retail price

All Philips audio and video service products are available through your nearest Philips Service Centre or selected dealers.

Sydney: 443 Concord Road, Rhodes, N.S.W. 2138. Telephone: (02) 73 0231. Philips Building, 2 Blue Street, North Sydney, 2060. Telephone: (02) 922 0181.

Newcastle: 190 Parry Street, Newcastle West, 2302. Telephone: (049) 61 1631. Canberra: 86 Wentworth Avenue, Kingston, A.C.T. Telephone: (062) 95 0321.

Melbourne: Cnr. Miles & Dodds Street, South Melbourne, 3205. Telephone: (03) 699 2711. Hobart: 2A Pierce Street, Moonah, Tasmania, 7009. Telephone: (002) 28 0121. Brisbane: 55 Forbes Street, West End, Brisbane, 4101. Telephone: (07) 44 8121. Townsville: 38 Punari Street, Currajong, 4812. Telephone: (07) 79 7422. Adelaide: 81-97 Flinders Street, Adelaide, 5000. Telephone: (08) 223 2999. Perth: 875 Wellington Street, West Perth, 6005. Telephone:

Service Service Service



AHEARN PSI

review

In the lab

The objective testing of this unit was unusual in that the first parameter that most people are interested in, the usable sensitivity, was a little complicated to evaluate. In the stereo mode the inbuilt muting, which cannot be disconnected. makes it impossible to measure the sensitivity in the normal manner. At 26 microvolts into 75 ohms the receiver mutes and that's it! In the mono mode things are a little better. A signal to noise ratio of 26 dB (commonly regarded as the lower limit of acceptability) occurs at 1.3 microvolts input, which is slightly higher than the maker's specification but nevertheless a good performance.

A plot of the signal to noise ratio against input signal power is shown on this page. Performance on mono is particularly good — for signals above the 68 dBf level the S/N ratio is 68 dB. When the stereo muting takes place the S/N ratio is still 58 dB so it is apparent that the designers intend that you should receive premium quality reception in the stereo mode and revert to mono where less adequate signals are received. The surprising thing about

this receiver is that the unweighted signal to noise ratios in the stereo mode are superior to those in the mono mode, being 70 dB for narrow band stereo and 65 dB in mono.

The FM frequency response extends from 24 Hz to 16 kHz but it is not the smoothest we have ever seen. However, the channel separation is particularly good, exceeding 35 dB from 40 Hz to 2 kHz. Image rejection, IF rejection, channel balance and subcarrier rejection are all excellent.

By contrast the AM tuner has only a mediocre sensitivity of 25 microvolts for 26 dB signal to noise ratio with 30% modulation. This is suitable for local reception only and has been designed for that purpose. The AM bandwidth, in the usual Japanese fashion, is 50 Hz to 3.2 kHz — only slightly better than the norm

Subjectively

Subjective evaluation of this tuner was a real delight. Of all the tuners I have ever used this is without doubt one of the easiest and most pleasant to operate. The computuner circuitry has been very well conceived and in conjunction with the automatic tune and search facility produces the sort of results and convenience I believe most listeners really want.

The quality of reception is faultless. Especially noteworthy is the freedom from distortion on both the FM stereo and mono reception. Distortion is less than 0.25% under any operating conditions and that is a remarkably good performance.


The Marantz ST500 is not the cheapest or the most expensive tuner on the market; it is not the biggest or the smallest. It is, however, one of the nicest and easiest to use and frankly I liked it.

MARANTZ STEREO COMPUTER TUNER MODEL ST500


Dimensions: 416 mm wide x 73 mm high x 300 mm deep


Weight: 4 kg Price: \$399 Manufactured by: Marantz in Japan

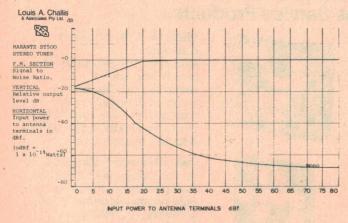Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.





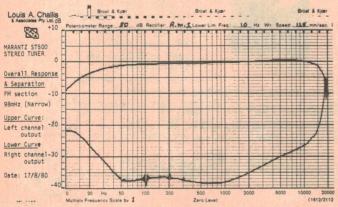

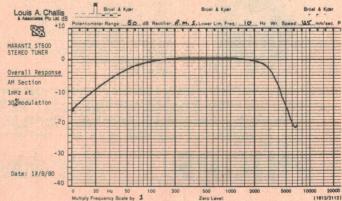

OF THE BEST SPEAKERS ARE IN POLITICS.

But many of them depend on our speakers to make themselves heard. Because we're specialists in the manufacture of loudspeakers for just about any application — P.A. systems, car stereo, hi-fidelity, radio, TV and communications.

Whatever your loudspeaker requirements are the specialists at

Magnavox can help.

Just send in the attached coupon for details of our complete range or

contact your nearest Magnavox distributor.

Qld. R.A. Venn Pty. Ltd. 67 Doggett Street, Fortitude Valley Qld. 4006 Ph: 525421. N.S.W. Standard Components Pty. Ltd. 10 Hill Street, Leichhardt N.S.W. 2040 Ph: 6606066. VIC TV Tuner Service Pty. Ltd. 469 St. Georges Road, Thornbury Vic. 3071 Ph: 446179. S.A. Gladiola Company 11 Laurel Avenue, Linden Park S.A. 5065 Ph: 513700. Protronics Pty. Ltd. 180 Wright Street, Adelaide S.A. 5000 Ph: 2123111. W.A. Everett International Pty. Ltd. 17 Northwood Street, West Leederville W.A. 6007 Ph: 3815500.

To: Magnavox Australia Pty. Ltd. PO Box M345. Sydney Mail Exchange. N.S.W. 2012. Please send me information on Magnavox □ High fidelity range □ General purpose range.

Name

Address

Postcode

Australia Ptv. Ltd.



Now your newsagent can solve your urgent parcel problems.

This TNT Courier Overnight Satchel has just turned your friendly newsagent into an air freight depot. For \$8.75 you can send anything that fits inside to almost anywhere in Australia. Overnight. You don't have to wrap a thing. The bag is tough, waterproof and tear resistant.

bag is tough, waterproof and tear resistant.
You can buy TNT Satchels at most newsagents throughout Australia. (At present in N.S.W., they are

available only in Sydney, Newcastle, Wollongong, Gosford and A.C.T.). Just address the satchel and leave it with your newsagent. TNT Courier collect it, air freight it overnight and deliver the next morning.

The TNT Courier Suburban Satchel is for overnight local deliveries in all mainland capitals (and

soon Hobart) for just \$5.00.

TNT Courier Overnight Satchels.*Anything, anywhere, overnight.

A Speedy Communications product. *Anything which fits inside the satchel may be sent almost anywhere in Australia, overnight.







Is your music still in the box?

You took your loudspeakers out of their cartons, but you may have left your music in a box.

Conventional loudspeakers project sound only from the front of the speaker cabinet. So you hear music coming from a very small area. Boxed in. Confined.

Direct/Reflecting loudspeakers radiate *reflected* as well as direct sound, like live music. You hear music coming from a wide area behind and to the sides, as well as from the front of the loudspeakers.

Direct/Reflecting loudspeakers release the spacious feeling of live music from your recordings. It's like sitting in front of a stage instead of a box.



Direct/Reflecting® Loudspeakers are made only by...

Better sound through research.

Australasian Distributors: Bose Australia, 11 Muriel Avenue, Rydalmere 2116, Sydney, NSW. Phone 684-1022.

Covered by patent rights issued and pending.

ither filology for the filology for the

S & Electronics Books

RNARD BABANI (publishing) LTD

160: COIL DESIGN &
CONSTRUCTION MANUAL
B.B. Babani

 Complete book on how to design and make RF, IF, audio and power coils, chokes and transformers. Every type is discussed and calculations given. Covers AM and FM radio and TV.

96 pages

Price \$2.75

202: HANDBOOK OF ICS EQUIVALENTS AND SUBSTITUTES. B.B.Babani

 One of the most complete IC equivalent and substitute guides yet published. Full data on over 9500 ICs. Covers digital and linears of all types from UK, USA, Japan, Germany, France, Czechoslovakia etc.

128 pages

Price \$3.70

221: 28 TESTED TRANSISTOR
PROJECTS
R.Torrens

 Some circuits are completely new — others are more familiar designs. The projects can be split into simple building blocks to enable readers to combine circuits for specialised needs.

96 pages

Price \$4.60

224: 50 CMOS IC PROJECTS R.A.Penfold

 CMOS ICs are suitable for an extraordinarily wide range of applications, are cheap and easy to obtain. Here are a number of interesting and useful projects in four general categories: (1) Multivibrators, (2) Amplifiers and oscillators, (3) Trigger devices, (4) Special devices.

112 pages

Price \$3.50

225: PRACTICAL INTRO TO DIGITAL ICS D.W.Easterling

 This book introduces the reader to digital ICs (mainly TTL 7400 series). Besides a number of simple projects, contents include details of a Logic Test Set which enables constructors to identify and test digital ICs. Also includes digital counter-timer.

80 pages

Price \$4.60





227: BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS R.A.Penfold

 Enables total beginners to tackle practical electronic so he or she can confidently build electronics projects such as published in ETI and other magazines and books. Subjects include component identification, tools, soldering, various building methods, cases, legends etc. Practical basic projects are also included.

112 pages

Price \$4.60

BP1: 1ST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES B.B.Babani

Complete transistor equivalents guide. More than 25 000 transistors with alternatives and equivalents. Covers devices made in UK, USA, Japan, Germany, Europe, Hong Kong etc. See also BP 14 (below).

80 pages

Price \$2.25

BP 14: 2ND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES B.B.Babani

 The second book contains data on devices not included in the first. This book supplements BP1, no data is duplicated.

208 pages

BP 24: 52 PROJECTS USING IC 741 Rudi & Uwe Redmer

 Originally published in German, this book achieved huge European sales. Now translated into English with copious notes, data and circuits, this book is a must for those interested in any way in this inexpensive and most versatile IC.

90 pages

Price \$3.50

Price \$4.05

BP 33: ELECTRONIC CALCULATOR USERS HANDBOOK M.H.Babani

 An invaluable book for all calculator users. Presents formulae, data, methods of calculation, conversion factors etc, often with examples. Includes way to use simple fourfunction calculator for Trig functions (sin,cos,tan); Hyperbolic functions (sinh,cosh,tanh), Logs, Square Roots & Powers.

& Powers.
Comprehensive conversion factors incorporated, including length, area, volume & weight through specialised conversions such as viscocity, illumination, cargo shipping measures etc. Also formulae for discounts and mark-up, currency conversions, interest, solutions of equations, binary and octal numbers, areas and volumes, stats and maths etc.

208 pages

Price \$3.50

BP 36: 50 CIRCUITS USING GERMANIUM, SILICON, ZENER DIODES R.N.Soar

Contains 50 interesting and useful circuits and applications in many different branches of electronics.

64 pages

Price \$2.75

BP 37: 50 PROJECTS USING RELAYS,SCRs & TRIACS F.G.Rayer

 Relays, SCRs and Triacs have a wide range of applications — from motor speed control, dimming, heating, timers, light-sensitive circuits, warning devices, light modulators, priority indicators, circuit breakers etc. Book gives tried and proven circuits which will tolerate wide latitude of components and values allowing easy modification to suit special needs.

112 Pages

Price \$4.60

BP 39: 50 (FET) FIELD EFFECT TRANSISTOR PROJECTS F.G.Rayer

• Field effect transistors are used in many circuits. The projects here include amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers and tone controls, plus miscellaneous devices. The FET used is not critical and many other types will work as well. This book will be of interest to all enthusiasts, shortwave listener, radio amateur, hi-fi buff or general electronics experimenter.

112 pages


Price \$4.60


BP 40: DIGITAL ICS AND PIN CONNECTIONS Adrian Michaels

 Equivalents and pin connections of a popular userorientated selection of digital ICs. Shows details of packaging, families, functions, manufacturer and country of origin. Includes devices by Fairchild, Ferranti, Harris, ITT, Motorola, National, Philips, RCA, Signetics, Sescocem, SGS-Ates, Siemens, SSSI, Stewart Warner, AEG-Telefunken, Texas, Teledyne. Companion volume to BP 41 — Linear ICs.

320 pages

Price \$9.00

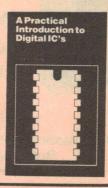

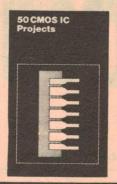





BP 41: LINEAR IC EQUIVALENTS AND PIN CONNECTIONS Adrian Michaels

• Essentially similar in concept to above but deals with linear integrated circuits.

320 pages

Price \$10.00

BP 42: 50 SIMPLE LED CIRCUITS R.N.Soar

 50 interesting and useful circuits and applications using LEDs. A useful book for beginner and advanced enthusiast alike

64 pages

Price \$3.50

BP 44: IC 555 PROJECTS E.A.Parr

 Every so often a device is made that is so useful one wonders how life went on before it! The 555 IC is one such.
 Frist made by Signetics it is now manufactured by almost everyone in the business. It is very cheap and readily obtainable.

Included in this book are basic and general circuits, motor car and model railway circuits, alarms and noise makers plus a section on the subsequent 556,558 and 559 devices.

160 pages

Price \$6.4

BP 45: PROJECTS IN OPTO-ELECTRONICS R.A.Penfold

 Opto-electronic projects of interest to all electronics enthusiasts. Included are simple circuits using ordinary LEDs as well as more sophisticated designs such as infrared transmitters and receivers, modulated light transmission and photographic projects.

112 pages

Price \$4.95

BP 47: MOBILE DISCO HANDBOOK Colin Carson

 Most people who start mobile discos know little about equipment or what to buy. This book assumes no preliminary knowledge and gives enough info to enable you to have a reasonable understanding of disco gear.

128 pages

Price \$4.95

BP 48: ELECTRONIC PROJECTS FOR BEGINNERS F.G.Rayer

 This book gives the newcomer to electronics a wide range of easily built projects. Actual component and wiring layouts aid the beginner. Some of the projects may be built without using soldering techniques.

128 pages

Price \$4.95

BP 49: POPULAR ELECTRONIC PROJECTS R.A.Penfold

 A collection of the most popular types of circuits and projects covering radio, audio, household and test equipment.

144 pages

Price \$5.35

BP 51: ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING M.K.Berry

 This book shows how electronic music can be made at home with simple and inexpensive equipment. It describes how sounds are created and recorded to build up a final composition. It shows how to build a small studio including mixer and various sound effects units.

96 pages

Price \$4.60

BP 53: PRACTICAL ELECTRONIC CALCULATIONS AND FORMULAE F A Wilson

 This book is for the practical person's workshop bench. It bridges the gap between technical theory and cut-and-tried methods which may work but leave the experimenter unfulfilled. There's a strong practical bias. Tedious and higher maths has been avoided where possible. Many tables are included. This one's a beauty!

256 pages

Price \$8.25

BP 56: ELECTRONIC SECURITY DEVICES

R.A.Penfold

 Simple and more sophisticated burglar alarms using light, infra-red and ultrasonics; also other types of alarm such as gas and smoke detectors, flood alarms, doorphone and baby alarms etc.

112 pages

Price \$5.35

ELEMENTS OF ELECTRONICS F.A.Wilaon

BP 62 - Book 1

BP 63 - Book 2

BP 64 — Book 3

 This series provides an inexpensive intro to modern electronics. Although written for readers with no more than basic arithmetic skills, the use of maths is not avoided — all the maths is taught as the reader progresses.

the maths is taught as the reader progresses.

The course concentrates on the understanding of concepts central to electronics rather than continually digressing over the whole field — on the basis that once the fundamentals are mastered, the workings of most other things are soon revealed. The author anticipates where the difficulties lie and quides the reader through them.

Book 1 . . . All the fundamental theory necessary to a full understanding of simple electronic circuits and main components.

Book 2 . . . Alternating current theory.

Book 3 . . . Semiconductor technology leading to transistors and ICs.

These three books constitute a complete, inexpensive electronics theory course of inestimable value in either hobby or career.

224 pages

Price \$8.25 (each volume)

BP 65: SINGLE IC PROJECTS R.A.Penfold

 All projects in this book are simple to build and are based on a single IC. A few projects use one or two transistors in addition. A strip board layout is provided for each project together with special constructional points and setting up info. The five chapters are: Low level audio, Audio power amps, Timers, Op-amps, Miscellaneous circuits.

128 pages

Price \$5.50

BP 66: BEGINNERS GUIDE TO MICROPROCESSORS AND COMPUTING E.F.Scott

 An introduction to basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. The only prior knowledge assumed is very basic arithmetic and an understanding of indices.

128 pages

Price \$6.45

BABANI BOOKS - MAIL ORDER, DIRECT FROM ETI!

Please sen	d me:		PRINT MARKET	Post & handling:
Book	Qty.	BP41		1 - 4 books: \$1.35
160	1918年197日	BP42	COLUMN THE NAME OF	5 - 10 books: <i>\$2.70</i>
202		BP44		11 - 20 books: \$3.50
221		BP45		over 20 books: \$5.00
224	Table 1	BP47		I enclose \$ (inc. p & h.)
225		BP48		
227		BP49		Name
BP1	PORTUGE STATE	BP51		
BP14		BP53		Address
BP24		BP56		postcode
BP33		BP62		
BP36		BP63		Send to: ETI 'Book Sales', 3rd Floor,
BP37		BP64		15 Boundary St, Rushcutters Bay NSW 2011.
BP39		BP65		Please allow 4 - 5 weeks for delivery.
BP40		BP66		WE REGRET WE CANNOT SUPPLY NEW ZEALAND READE

AUSTRALIAIS MOSTPOPULAR AMPLIFIERRIT OVER 7,000 BUILT!

NEW MPROVED MODEL — NOW OVER 20% OFF!





Universal Stereo **Amplifier kits**

EST 'BI-FET'

Yes! Here's your opportunity to join over 7,000 Australians who have sucessfully built their own quality stereo amplifier: the Playmaster Twin 25 or Playmaster 40/40.

Now the Playmaster amplifiers have been up-graded to the very latest 'bi-fet' operational amplifier input circuitry for outstanding performance at a realistic price.

And just look at our new low, low price: only \$89.50 for the twin 25, or \$99.50 for the 40/40: a saving of over \$25!

Here's what you get:

- A kit of parts absolutely complete to the last nut and bolt, including the case, pcb, components. - even solder!
- A step-by-step instruction manual which shows you how to build this amplifier even if you've never built anything before!
- Your choice of transformers: the 40/40 has the superb 'C-core' transformer which not only gives high power output, it actually results in a quieter amplifier! (The Twin 25 has a standard transformer).
- Attractive dress panel with matching quality imported knobs to give your amplifier a true professional appearance.
- And our exclusive 'Sorry Dick, it doesn't work' coupon: in the unlikely event that you can't get your amplifier working, you can send it to us. For a small fee, our technicians will correct any wiring errors and get your amplifier working perfectly!

NEW LOW, LOW PRICES Twin 25 NOW ONLY Forty/Forty NOW ONLY

EXCLUSIVE:

Fibreglass printed circuit board with component positions marked on the top side

You cannot go wrong! Every component position is clearly printed onto the top side of the PCB. All you do is select the component, place it in position and solder: what could be simpler? And the printed circuit board is made of professional quality fibreglass, which means that it is much more tolerant to heat: so even if you've never soldered a circuit board before, the chances of damaging it are pretty small!

EXCLUSIVE:

New BI-FET Operational amplifier input circuitry for lowest noise and optimum signal handling characteristics.

EXCLUSIVE:

Step-by-step instruction manual


Our exclusive instruction manual contains far more than comprehensive step-by-step constructional data: it also shows you how to solder, how to recognise components, how to place them in the printed circuit board . . . plus trouble-shooting information just in case you run into trouble.

EXCLUSIVE:

*Optional timber sleeve to give your amplifier that "commercially made" look. It looks so good your friends will never believe you built it yourself.

Timber sleeve: Cat. H-3113 \$8.50

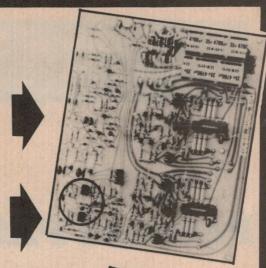Even if you've never built anything before you can build a Playmaster amplifier





EXCLUSIVE TO DICK SMITH WITHA 7-DAY SATISFACTION GUARANTEE

Not quite convinced you can build your own amplifier? Use our 7-day satisfaction guarantee. Buy the kit, and take it home. Examine it, and the instructions carefully. If you still think it is beyond you, return the kit in original condition (i.e. before construction is commenced) and we'll refund your purchase price in full. What could be fairer than that?

105	seven days. If I'm not completely happy with i	olifier kit. I understand that I may examine the kit for it or if I think the kit construction is beyond me, I may and I will receive a full refund of my purchase price.
40	Please send me Standard Twin 25 Playmaster amplifier with normal	l enclose (cheque, postal order etc
	transformer. (\$89.50 pack and post free)	do not send cash) for the sum of \$ OR Please charge my Bankcard
	Deluxe Forty Forty Playmaster amplifier with low-	
	noise 'C-core' transformer (\$99.50 pack and post free)	A/c No:496 Exp. date:
Name:	Address:	Bankcard Account name:
		(Signed)

SEND TO: DICK SMITH MAIL ORDER CENTRE

P.O. Box 321 North Ryde, N.S.W. 2113 OR call into your nearest branch



SEE OUR OTHER ADS IN THIS ISSUE FOR STORES & RE-SELLERS ADDRESSES

for the second s

Peerless PAS 30 speaker system

Locally manufactured enclosures keep the price of these speakers below that of comparable fully-imported systems. Louis Challis tried them out and found them good value.

ONE OF THE questions I am most often asked by friends and associates is, "What loudspeakers should I buy for my new system?" When I reply by asking, "How much do you want to spend?", the most common answer is \$500. Likewise, most retailers will tell you that \$500 seems to be the current 'watershed price' for loudspeakers that separates the serious from the less serious audiophiles.

So when I receive a set of speakers with a recommended retail price of \$498 I tend to sit up and take notice. Are the speakers priced to just pip the intending purchaser's budget or do they have other merits and offer a performance that matches their price?

The Peerless Company of Denmark has always been one of the most respected manufacturers of loudspeakers in Europe. I have used many of their speakers and have found that they offer competitive performance and are usually well designed, with construction apparently based on sound research and good manufacturing techniques. The GRD group of Melbourne

have been able to keep the cost of the PAS 30 speakers in this country down to below the magical \$500 by making the enclosures locally, thereby avoiding most of the freight costs and duty which usually add so much to the price of imported systems.

The manufacturers rate the PAS 30 system as having a 100 watt capability with an eight ohm impedance. They're three way speakers incorporating a 200 mm diameter bass driver with a rolled polyethylene foam surround, a 100 mm diameter midrange driver with a conventional 25 mm diameter voice coil and a 25 mm soft dome tweeter to provide the extended high frequency response.

The enclosure is made out of 18 mm chipboard veneered on the sides and front edges with Australian walnut. The fascia is a black ply panel covered with an open weave artificial fibre and attached to the enclosure by strips of Velcro at the corners and sides.


All the drivers are mounted from the front of the fascia to facilitate construction and repair and the unit


incorporates infill in the form of low density fibreglass to provide internal resonance control and balanced output. In keeping with current thinking about reduction of phase differences, the drivers are aligned vertically with the woofer at the bottom and the tweeter at the top. The back of the cabinet contains two spring-loaded colour coded terminals for the speaker leads. These are set into a recessed circular plastic well on the lower rear face of the unit.


In the lab

Objective testing of these units showed they have a frequency response that extends from 70 Hz to 20 kHz (+/- 6 dB). Hence they match the normal concept of a 'bookshelf' speaker system, which in most cases is expected to have a lower cutoff frequency between 50 and 70 Hz. The frequency response curve is remarkably flat and although there are interactions between the various drivers, whose individual characteristics are not perfect, the resulting response is still particularly good.


The off-axis response is flatter than

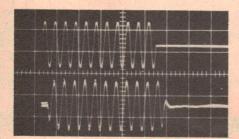

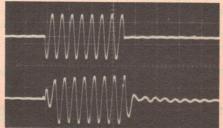

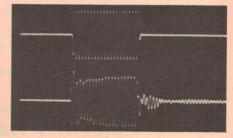

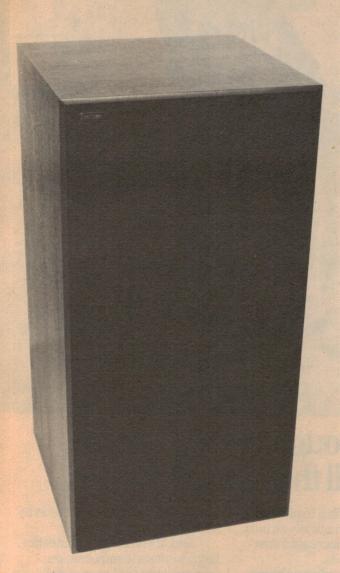Tone burst response: left, at 100 Hz; centre, at 1 kHz; right, at 6.3 kHz.





the on-axis response and the general frequency response characteristics are above average. The individual responses of the three drivers have been very well selected and the crossover frequencies are well chosen. This is borne out by the phase response of the unit, which is exceptionally flat and shows how effective the design is in reducing phase differences.

The impedance curve shows a sharply rising response at the fundamental resonance of 55 Hz and a ripple whose lowest level is seven ohms. This impedance curve is quite acceptable and would allow these speakers to be paralleled with any other nominal eight ohm speaker system without risk of excessively low impedance.

The distortion characteristics are particularly good. At the 90 dB level at two metres on-axis the total harmonic distortion at the test frequencies of 100 Hz, 1 kHz and 6.3 kHz never exceeds 0.8% — a very satisfactory performance. At higher levels the distortion starts to rise and at sound pressure levels exceeding 100 dB it begins to become unacceptable.

The speakers are moderately efficient, requiring 8.2 watts to achieve 90 dB on-axis, from which it can be seen that the manufacturer's 100 watt rating is fairly realistic. The tone burst response proved to be good, with only a slight trace of ringing being apparent in the 4, 7, 8 and 10 kHz regions. This ringing was not particularly pronounced

and was indicative of an acceptable transient performance.

To the ear

The subjective evaluation of the units gave, in many respects, a better impression than the objective testing. Unlike many of the other speakers we have recently reviewed, the PAS 30 system imposes a remarkably low level of colouration and offers a performance similar to the AR6s, which used to be one of my favourite systems a decade ago. Unlike the AR6s, whose frequency response was still excellent at 50 Hz, the PAS 30s do not perform so well at the bottom end of the register. Fortunately they do not exhibit gross frequency doubling or excessive dis-



Because it's hard enough getting a home together, we've put all this cover together.

Six insurance covers in one. It's called the AGC Insurance Executive policy for homeowners and householders.

And it saves you dealing with six different insurance companies and worrying about six different policies.

You get one simple policy.
Up to six kinds of cover.
It's a policy that's never been

beaten.

Your home itself.

AGC provides insurance cover for your home. Even garages, out buildings and swimming pools.

And we also offer you the New Rebuilding Cover alternative.

These days there is generally a big difference between the current value of your home and what it would cost if you had to rebuild.

AGC's Rebuilding Insurance protects you automatically against inflation. And the increased cost of building materials.

The contents of your home.

We'll cover household goods and personal effects of every description.

No depreciation on goods or articles less than 5 years old. (Excluding linen and clothing.)

Specified personal property anywhere in Australia

We'll also cover the special things you value.

Very valuable objects such as furs, jewellery, paintings and the like.

Other essential protection.

Your AGC Executive policy can also give you cover against Personal Legal Liability Death of nominated person by accident.

And, if you employ domestic help, workers' compensation (not applicable in Queensland).

With AGC's Executive policy you're not only covered by up to six different types of insurance.

You're covered by a big name -

AGC Insurances.

Sydney: Phillip & Hunter Streets. Melbourne: 31 Spring Street. Brisbane: Tank Street & North Quay. Adelaide: 10 Pulteney Street. Perth: 165 Adelaide Terrace. Hobart: 161 Collins Street, and offices throughout Australia.

AGC (Insurances) Limited. A division of Australian Guarantee Corporation Limited in which the Bank of New South Wales is the major shareholder.

AGC 994 FCB



Among the many reasons for the wide acceptance of these programs is their simplicity. Each learning program is simply and logically arranged for easy, step-by-step 'programmed' learning. Progressing at your own established pace, you learn in an unhurried environment free from pressure. No facet of the material is omitted and nothing is assumed. Each program includes everything you need for a high degree of understanding. Audio records (or optional cassettes) reinforce the text material and an optional final examination lets you test your overall comprehension.

The Continuing Education Programs are economical too. The first four programs use the same trainer so you can get a complete education in fundamental electronics at substantial savings. The advanced programs, Digital Techniques and Microprocessors, require separate trainers, but they still cost less than competitive courses.

Get 'Hands-on' experience for a better understanding of electronics. Learning electronics and being able to apply what you've learned are, of course, the goals you seek to achieve with

the Heathkit Continuing Education Series. For that reason, we have spared no effort in assuring your complete comprehension. Our optional Electronic Trainers, designed for use with each program, perfectly illustrate the Heath approach to learning. These trainers give you actual 'hands-on' experience with electronic components and circuitry. It's an acknowledged fact that you learn best by doing and the trainers let you do exactly that. You get a better grasp of circuit concepts and perform the program projects quicker and easier as well. Solderless connectors on the trainer panel make hookup of the components supplied with the program quick and neat. Built-in power supplies and signal sources provide convenient operation. The trainers are available in both kit and assembled form.

When you've finished the program, the trainer still serves as the ideal device for breadboarding circuits of your own design. We highly recommend these trainers as supplements to the Heathkit Individual Learning Programs. A record (or cassette) player is needed to play the audio portion of the material. A VOM for measuring voltages is also needed, and an oscilloscope is required for some of the experiments in the Electronic Circuits and Digital Techniques Programs.

to find
out more
send for your
FREE CATALOG
today!

Recommended Order

The Heathkit Self-Instruction Programs are Designed to let you Progress from DC Electronics to AC Electronics to Semiconductor Devices to Electronic Circuits. These are the Four Basic Programs. For Optional Advanced Study, The Digital Techniques Program Provides the Background for the Microprocessor Program.

There are many courses in the HEATHKIT Continuing Education Program designed to effectively expand your electronic horizons including:—

EE 3101	DC Electronics	\$76.00
EE 3102	AC Electronics	\$84.00
EE 3103	Semiconductors	\$84.00
EE3104	Electronic Circuits	\$99.00
EE 3201	Digital Techniques	\$125.00
EE 3401	Microprocessor Program	\$168.00
ET3100	Experimenter/Trainer	\$131.00
ET 3200	Electronic Trainer	\$157.00
ET 3400	Computer Trainer	\$347.00

Appendix of the second	MICROPROCESSORS
(\$20 (
1941	MICROPROCESSORS

ORDER BY COUPON NOW OR COME TO OUR SHOWROOM

Please rush me the Heathkit of my choice. My cheque for \$..... is enclosed plus \$7.00 for package and post.

Name P/Code

Send to: W. F. Heathkit Centre 220 Park St., South Melb. 3205. Phone 699 4999.

□EE 3101	
□ EE 3102	
□ EE 3103	
□ EE 3104	

□ EE 3201

□ EE 3401

□ ET 3100 □ ET 3200

□ET 3400

 Please rush me my Free catalog containing full details on the complete range of Heathkit Learning Programs.

	Cree	dit C	Card	No							
Bankcard	Exp	iry [Date			Sig	gnat	ure			

review

tortion either, so I was only aware of a general reduction of low frequency response in comparison with our reference speaker system.

The most striking attribute of this speaker system is that it can reproduce speech with reasonable fidelity, an ability which I regard as very important and which so many speakers lack. On orchestral music the speakers perform admirably on all string, brass and woodwind instruments, but not on drums. On soft rock they give an acceptable performance but hard rock recordings with electric guitar sounds in the 40 to 80 Hz region cannot be

played satisfactorily at high levels.

By contrast with many other speaker systems we have evaluated, the PAS 30s achieve a reasonable degree of attenuation of those frequencies below their range and thereby reduce what could otherwise be distress for the listener.

Summary

The Peerless/GRD PAS 30 is undoubtedly one of the better small speaker systems available, offering lower distortion and a flatter frequency response than most. It constitutes good value in the hotly contested 'under \$500 stakes'.

PEERLESS PAS 30 SPEAKER SYSTEM


Dimensions: 580 mm high x 291 mm wide x 290 mm


Weight: 15kg each unit

Price: \$498

Manufactured by: GRD Group, Melbourne.

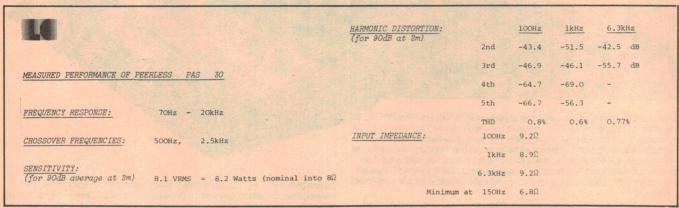Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.



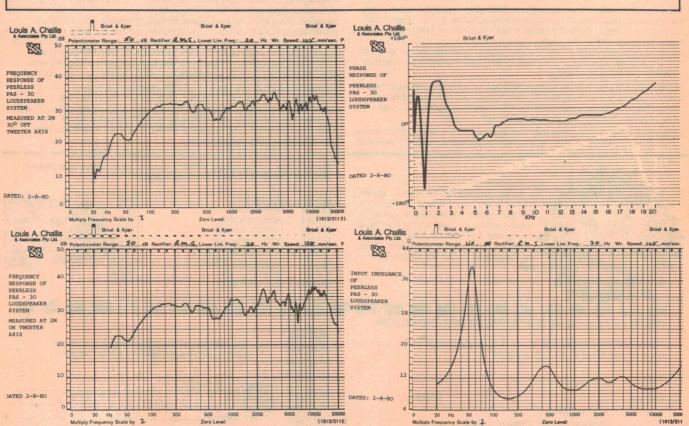

ELECTRONICS COURSES

FULL OR PART TIME

- Post Trade
- Technician
- Certificate of Technology
 - Computer Service

COLOUR TV AMATEUR - HOBBY RADIO COMPUTERS COMMUNICATIONS INDUSTRIAL CONTROL **MICROPROCESSORS** MOTOR SPEED CONTROL DIGITAL



991 Whitehorse Rd Box Hill 88 0691

SORCERER OWNERS!

A BETTER BASIC

The new Software Source Mod 1.01 makes your Basic into a Superbasic with capabilities that outstrip even some Disk

- Full input checking to eliminate syntax errors and line over-
- Redo from start if type mismatch in input statements.
 Save numeric arrays with confidence.
 Full selective renumbering move your subroutines around; make a hole to insert more text.
- Bollete any block of lines.

 Full recovery of programme after accidental reset.

 Available only for Exidy Standard Basic Version 1.0.

 Basic Mod 1.01 (include Rompac with order)......\$125.00

USE YOUR SORCERER'S GRAPHICS CAPABILITIES!!

Just released! This tape-based machine-language programme allows instant definition of graphic characters. Powerful macro command allows you to define 24 characters as a block. Numeric keypad becomes a special keypad for drawing lines and curves. Inverse, flip rotate, tilt, mirror or translate characters. Study the makeup of any character. Easy-to-read 17-page booklet explains exactly how Sorcerer Graphics work and how to define your own shapes.

SPELLBINDER

The super disk wordprocessor that talks directly to your disks. No drivers to install. Automatically centres titles. View right-justified printing on the screen just as it will be printed. Alternating left and right margins! And much more. Simple to

Specially configured for Sorcerer (requires CP/M) .\$299.00 We have an extensive range of hardware and software for the Sorcerer. We can offer memory expansions and disk expansion at reasonable rates. We are experts on Sorcerer, and offer full advice on compatability of peripherals. Write for free

SOFTWARE SOURCE, PO Box 364, Edgecliff, 2027 All prices inclusive. For free catalogue send SAE Need specialised software? — call us, we can help

SOFTWARE SOURCE

Phone (02) 33-4536

Give your Sorcerer or any other micro some real support in the New Year. The support of a custom made operating desk also ideal for amateur radio.



Features vinyl leather inlay, plenty of space for cassettes, disk drives, \$100 or any other busses. Feed slot for printer paper, two deep spacious drawers for convenience. Put an end to those backaches from hours of out of position programming.

Send cheque or money order to the value of \$170.00 to:

D. J. GILLIN. 170 Moore Street, Warrnambool, VIC, 3280. Phone (055) 62-4376.

Delivery free in Victoria. Subsidised freight interstate. An ideal Christmas gift. Chair and equipment not included

TRY THIS EXCITING HOBBY!

Build your own Organ, at half the cost of a ready-built Organ.

WITH WERSI ORGAN KITS

Wide range of models: COMBO to large CHURCH ORGANS



AISO


- . STRING ORCHESTRA
- . BASS SYNTHESIZER e ELECTRIC PIANO
- and the famous WERSIVOICE **ROTATION SOUND**

All available from

CLEFTRONICS PTY. LTD.

9 Florence St., Burwood, Vic. 3125 Phone: (03) 288-7899

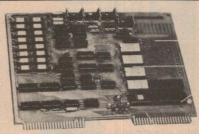Catalogue 104 pages in colour — \$3.00 (incl. postage). Klaus Wunderlich Demonstration Record, music only with jacket notes — \$7.00 (incl. postage).



DRAM PLUS for AIM-SYM

KIM4 bus. 16K of 4116's provided with expansion to 32K; 16K ROM/EPROM space accommodates XX16 and XX32's in four sockets, EPROM Programmer for XX16 and XX32 SV types, 2 x 6552's for 40 1/0 lines, 5V, 12V, 24V Regulators and -12V DC-DC converter. 50 x 70 mm WW area. Memory Test and EPROM Programming Software on cassette, 5V 1A, 12V, 0.15K (Solder masks and silk screen). 12V 0.15A. (Solder mask and silk screen). A&T

PROTO PLUS II. KIM4 bus Universal 2.54mm pattern with pattern provisions for transistors, regulators, rotary switches, connectors etc. Includes address decoding and selection by DIP switch for 8K boundaries, address line buffering and bi-directional tristate data line buffers. A&T \$64.

ASK I/O. Provides a low cost method of interfacing to the AIM, SYM application connector. Includes I/O jacks, remote control relays for cassette read/write control, audio input LED 8 x switches and 8 x LED's for I/O control and demonstration. Female 44 way connector. A&T \$59.



PO BOX 6502, GOODNA 4300 PHONE (07) 288-2757

Prices subject to change without notice

SAF for

Hi-Energy Cassettes

C90's

1-5	\$1.95
6-24	
25 plus	\$1.79

NO POST AND PACKAGING CHARGES

- Low noise/hi output.
- Screwed cases, not glued.
- Fully guaranteed.

Just send a cheque or money order in an envelope, with the number required and your address on the back and address it to:

T.A.A.R.C. 68 Wellington Street, Longford, Tas. 7301.

Now you can breathe easier!

NEGATIVE IONS.

For more than 20 years Medical research has been demonstrating the amazing benefits of negative air ions. They clear the air of smoke and dust, reduce fatigue and increase alertness. reduce up to 75% of airborne bacteria and much more.

In natural surroundings they are abundant but in stale or polluted air they quickly become depleted. Now an inexpensive device to alleviate this condition is being manufactured in Australia.

The "Aironic" negative ion generator electrically produces safe, natural levels of negative ions. Stale odours and smoke are removed from the room and the air becomes fresh and invigorating once more.



See your health food shop or natural therapist or post coupon to:

BELLE LUMIERE PTY. LTD.

SYDNEY: P.O. BOX 216, Lane Cove. NSW. 2066. Tel: (02) 428 1334 MELBOURNE: 5/47 Fitzroy St., St. Kilda. Vic. 3182. Tel: (03) 534 7493 BRISBANE: P.O. BOX 184, Toowong. Qld. 4066. Tel: (07) 371 3645

Home/office model. \$85 each.
Deluxe wood casing. \$95 each.
Add \$2.00 for postage and packing. I enclose cheque/money order for
NAME
ADDRESS
POSTCODE
Bankcard Mail Orders Welcome.
Expiry Date
Signature



Mail Order Drivers & Kits

CERTIFIED MAIL DELIVERY THROUGHOUT AUSTRALIA & NEW ZEALAND Bankcard accepted



...the no-compromise approach to uncoloured sound

For full information, write to: **AUDIOKITS** PO BOX 553 **BROOKVALE NSW 2100**



The Digital Age has begun . . .



DINAUDIO Authentic Fidelity

YOU are into moving coil pickups, direct cut discs, fast amplifiers and gold cables. BUT are your vocalists touchably real?¹ Do you instinctively react at a rim shot?2 Are you elated by orchestral dynamics3 or the lyrical clarity of a Bosendorfer Imperial Concert grand?4 CAN your speakers cope with a 19th century cannon?5

DINAUDIO high fidelity loudspeaker systems are precision engineered to the highest standards. The craftsman-built cabinets utilize sectionally braced, double layered high density walls. The Model 25-90 uses optimally tuned reflex loading in a time differential compensated three-way system. Its performance exceeds that of highly acclaimed professional monitors.

DINAUDIO drivers use hexagonal wire, ferrofluidics, and dynamic transient linearity for fast rise time and low IM distortion.

For information on DINAUDIO high fidelity speaker systems, models 30-90, 25-90 and 20-55, contact:

VIC: The Sound Craftsman, 61 Kooyong Rd, Nth Caulfield, 509 2444. 654 Glenferrie Rd Hawthorn, 818 8637. Mr Audio, 121 Denmark St, Kew, 861 9888

NSW: Leisure Sound, 401 Pacific Hwy, Artarmon, 438 4166 & 38 York St, Sydney, 29 1364.

- Discs Referenced Above

 1 Three Blind Mice TBM5005 "No Tears"
 2 East Wind EW1001, "The Three"
 3 Telarc DG10039 "The Firebird"
 4 Terlarc DG 10040 "Malcolm Frager Plays Chopin"
 5 Telarc DG10041 "1812"

DYNAUDIO (AUST) PTY LTD, PO Box 2 Hawthorn Vic 3122

negative ions.

Send SAE for further literature on

HRISTHAS SPECIAL **DECEMBER 25, 1980** ING THE AUSTRALIAN FINANCIAL TIM

What other present says so much?

Politics, finance, current affairs and the arts in 52 weekly episodes, written by the cream of Australia's journalists. Alan Reid, Trevor Sykes, Peter Samuel, Robert Drewe, David McNicoll, Phillip Adams, Max Harris.

What more could you say? What better way of saying it?

Fill in coupon, complete with credit card details if applicable, and send to: The Bulletin, Box 4088 GPO, Sydney 2001 or Box 486 CPO, Auckland, New Zealand. Send Gift to

Address Indicate your choice by placing a tick in the appropriate boxes 26 Weeks Also send me 52 Weeks American Express Credit Card No Card Expiry Date.

Signature of Cardholder (Unsigned orders cannot be accepted)

Australia and New Guinea: 26 weeks A\$21.00, 52 weeks A\$39.00
New Zealand: 26 weeks A\$21.00 — (NZ\$24.50) 52 weeks A\$39.00 —
(NZ\$46.00) Singapore, Malaysia and Hong Kong: 26 weeks A\$24.75
52 weeks A\$46.50 Other overseas countries: 26 weeks A\$24.55
52 weeks A\$55.00 — Piease Note: The cost of a subscription to The Bulletin includes air freight to Australian capitals; also Auckland.
Christchurch, Wellington, Port Moresby, Singapore and Hong Kong.
Subscriptions to other overseas countries are sent by surface mail.
Direct airmail rates to other countries available on application.

MNAC/BLN/2704

KITS for projects

WE GET MANY enquiries from readers wanting to know where they can get kits for the projects we publish. This list is a guide to suppliers of kits and components for ETI projects.

We have listed here most of the projects published over the last few years which are either available as kits or can still be made up by shopping around for components. Suppliers listed against a particular project will either stock it as a kit or stock the pc board plus the other components.

Printed circuit boards

Those suppliers listed against specific projects here are able to supply pc boards for those projects. Printed circuit boards for every project ever published in ETI are available through the following companies (to the best of our knowledge):

RCS Radio Radio Despatch Service
651 Forest Rd 869 George St
Bexley NSW Sydney NSW 2000

For current projects and a more comprehensive list of pc board suppliers refer to the Shoparound page in this and previous issues. This list will be updated roughly every four months.

Key to Companies

- A Applied Technology Pty Ltd. 1A Paterson Avenue. Waitara. NSW 2077. Ph. (02) 487-2711.
- B Bill Edge Electronic Agencies. 115 Parramatta Road. Concord (PO Box 1005, Burwood North 2134). Ph. (02) 747-6472.
- C J.R. Components, PO Box 128, Eastwood, NSW 2122. Ph. (02) 85-3385.
- D Dick Smith Electronics P/L. Cnr Waterloo & Lane Cove Roads. North Ryde, 2113. Ph. (02) 888-3200.
- E All Electronic Components, 118 Lonsdale Street, Melbourne. Vic 3000. Ph. (03) 662-3506.
- F Tasman Electronics. 12 Victoria Street. Coburg. Vic 3058 Ph. (03) 354-5062.
- J Jaycar Pty Ltd. PO Box K39. Haymarket. NSW 2000. Ph. (02) 211-5077.
- K SM Electronics, 1096 Doncaster Rd, Doncaster East Vic 3109. Ph. (03) 842-3666.
- L Ellistronics. 289 Latrobe Street, Melbourne, Vic 3000 Ph. (03) 602-3282.
- M Mode Electronics, PO Box 365, Mascot. NSW 2020. Ph. (02) 666-6324.
- N Nebula Electronics Pty Ltd. 15 Boundary Street. Rushcutters Bay, NSW 2011. Ph. (02) 33-5850.
- O Orbit Electronics. PO Box 7176, Auckland, New Zealand
- P Pre-Pak Electronics, 718 Parramatta Road, Croydon, NSW 2132, Ph. (02) 797-6144.
- R Rod Irving, PO Box 135, Northcote, Vic 3070 Ph. (03) 489-8131.
- V Silicon Valley, 23 Chandos Street, St. Leonards, NSW 2065. Ph. (02) 439-4655.
- W Willis Electronics, 993 Hay Street, Perth, WA 6000. Ph. (09) 321-7609.
- Y Trilogy, 40 Princes Highway, Fairy Meadow, NSW 2519.

Proj	ect Electronics			
041	Continuity Tester W.R.D.B.Y.L			
042	Soil Moisture Indicator			
043	Two Tone Door Bell (Oct 76) . W.R.D.E.A.F.B.Y.L			
045	500 Second Timer			
047	Morse Practice Set W.D.O.A.B.Y.L			
048	Buzz Board			
061	Simple Amplifier (Oct 76) W.R.D.E.A.B.Y.L			
063	Simple AM Tuner (Mar 77) W.D.E.B.Y Electronic Bongos R.D.A.B.Y.L			
064	Simple Intercom (Nov 76) W.A.			
065	Electronic Siren WRDFOABYL			
066	Temperature Alarm (Dec 76) W.D.E.A.B.Y.L Singing Moisture Meter D.B.Y			
067	Singing Moisture Meter			
068	LED Dice Circuit (Oct 76) W.R.D.E.A.B.L. Electronic Tie Breaker (Jan 77)			
071	Tape Noise Limiter (Jun 78)			
072	Two-Octave Organ (Jun 78) W.D.B.Y			
081	Tachometer (Mar 77) W.E.O			
082/ 528	Intruder Alarm W.R.E.A			
083	Train Controller W.R.E.L			
084	Car Alarm W.R.D.E.A.B.Y.L			
085	Over-rev Alarm W			
086	FM Antenna W			
087	Over-LED W.E			
088	Hi-Fi Speaker			
	Equipment			
132	Experimenter's Power Supply (Feb 77) E.O			
133	Phase Meter (Apr 77) E			
134	True RMS Voltmeter (Aug77) E Digital Panel Meter (Oct 77)			
136	Linear Scale Capacitance Meter (Mar 78)			
137	Audio Oscillator (May 78) W.D.E			
138	Audio Wattmeter (Nov 78) E.B			
139	SWR/Power Meter (May 78)			
140	1GHz Frequency Meter-timer (Mar 78)			
142	Logic Trigger (Jan 79) E High Current Power Supply (Feb 79) W.E			
143	Curve Tracer (Jan 79)			
144	Expanded-scale RMS Voltmeter (Jun 79) E			
148	Versatile Logic Test Probe (Jul 79) E.L			
Sim	ple Projects			
243	Bip Beacon (Apr 77)			
244	Alarm Alarm (Feb 77) F			
245	White Line Follower (Nov 77) F			
246	Rain Alarm (Apr 78)			
248	Simple 12V to 22V Converter (Jul 78) W Electronic Combination Lock (Apr 79) E			
252	The Passionmeter (Aug 79)			
253	Electronic Grenade (Hot Potato) (May 79)			
254	Egg Timer (Jun 79) W			
Moto	orists' Projects			
316	Transistor Assisted Ignition (May 77) W.E.O.K			
317	Rev. Monitor Counter (Jul 77)			
318	Digital Car Tacho (Jul 78) W.E.K			
319	Variwiper MK II (Sep 78) W F O			
320	Battery Condition Indicator (Apr 79) E.L			
	io Projects			
448	Disco Mixer (Nov 76)			
449 450	Balanced Microphone Amp (Nov 76) W.D.E.J.F.Y			
451	Bucket Brigade Audio Delay Line (Dec 77) W.E Hum Filter (Jul 79) D.E.F			
470	60 W Amp Module (May 79) W.R.E,F.B,P.L.A,V			
471	High Performance Stereo Preamp Control			
470	Unit (Jun 79) W,R,E,F,B,P,A,V,L			
472	Power Supply — the Series 4000 Stereo Amp (Jul 79)			
473	Series 4000 Moving-coil Cartridge			
	Preamplifier			
480	50-100 Watt Amp			
481	Modules (Dec 76)			
481	High Power PA/Guitar Amp (Jun 77) W			
482	Stereo Amp (Jan 77) O,E			
482	Stereo Amp Part 2 (Feb 77) O.E			
483	Sound Level Meter (Feb 78) E			
484 485	Simple Compressor Expander (Jul 77) A.E. Graphic Equaliser (Jun 77) W.E.J.O			
486	Howl-round Stabiliser (Nov 77)			
487	Audio Spectrum Analyser (Feb 78) E			
489	Audio Spectrum Analyser 2 (Apr 78) E.J			
490 491	Audio Compressor (Dec 78) Simple Graphic Equaliser (Mar 79) W.E			
495	Transmission Line Speakers (Aug 77)			

Miscellaneous				
546	GSR Monitor (Mar 77)	W.E		
547	Telephone Bell Extender (Jun 77)			
548	Photographic Strobe (May 77)	W.E		
549	Induction Balance Metal			
7	Detector (May 77)	W.D.E.L		
550	Digital Dial (Aug 78)	E.O		
551	Light Chaser (Sep 78) LED Pendant (Sep 78)	W.E.O		
552 553	Tape/Slide Synchroniser (Oct 78)	E		
556	Wind Speed/Direction Indicator (Dec 78)			
557	Reaction Timer (Feb 79)	F		
558	Mast-head Strobe (Feb 79)			
559	Cable Tester (Mar 79)			
575	Portable Fluorescent Light Wand for			
	Car. Camping (Aug 79)	W		
577	General Purpose Power Supply	J		
581	Dual Power Supply (Jan 77)	W.E.Y		
582	House Alarm (Jul 77)	W.E.O.A.		
	House Alarm —			
	Installation Instructions (Aug 77)			
583	Marine Gas Alarm (Aug 77)	D.E.M		
585	Ultrasonic Switch (Sep 77)	H.D.E.O.F		
586 587	Shutter Speed Timer (Oct 77) UFO Detector (May 78)	MAN E		
588	Theatrical Lighting Controller			
300	(Nov & Dec 77 Jan & Mar 78)	N		
589	Digital Temperature			
	Meter (PCB135) (Dec 77)	E		
590	LCD Stopwatch (Oct 78)			
591	Up/Down Presettable Counter (Jul 78)	D.E		
592	Light Show Controller (Aug 78)			
593	Colour Sequencer (Dec 78)			
594	Development Timer (Apr 79)	E		
595	Aquarium Lamp Controller (May 79)			
Floor				
	tronic Music			
602	Mini Organ (Aug 76)			
603	Sequencer (Aug 77)	W		
604	Accentuated Beat Metronome (Sep 77)	E		
605	Temp Stabilized Log-exponential			
	Converter (Sep 78)			
Com	puter Projects			
630	Hex Display (Dec 76)	. EA		
631	ASCII Keyboard (Dec 76)	W.E.O.A		
631	Keyboard Encoder (Apr 77)	. W.E.O.A		
632	Video Display Unit (Jan 77)	AFO		
633	TV Sync Generator (Jan 77)	A.E		
634	8080 Educational/Prototyping			
635	Interface (Jul. Aug 78)			
637	Microcomputer Power Supply (Sep 77)			
638	Cuts Cassette Interface (Jun 78)	V.E.A		
639	Eprom Programmer (Jul 78)	VV.E.A		
640	S100 VDU (Apr. May. Jun 78)	WOAV		
641	S100 Printer (Sep 78)	. W.O.A.V		
642	\$100 Printer (Sep 78)	K		
650	STAC Timer (Nov 78)	AEL		
651	Binary to Hex Number Converter (Jun 79)	E		
Radi	o Projects			
712	CB Power Supply (Jun 77)	W.E		
713	Add-on FM Tuner (Sep 77)			
714	VHF-Log-Periodic Antenna (Feb. Mar 78)			
715	VHF Power Amplifiers (Nov 77)			
716	VHF Power Amplifiers (Jan. Feb 78)			
717	Crosshatch Generator (May 78)	W.D.E.A.Y		
718	SW Radio (Oct 78)	=		
719	RF Field Strength Indicator (Nov 78) 2m VMOS Power Amp (Jan 79)			
721	Aircraft Band Converter (Mar 79)	WE		
722	Antenna for Aircraft Band			
	Converter (May 79)			
724	Microwave Oven Leak Detector (Jul 79)	D.E.B		
725	Simple SSB Generator employs Polyphase			
	Network using Standard Components (Aug	79) . E.L		
730	Get Going on Radioteletype (Aug 79)			
FI				
	ronic Games			
804	Selectagame (Nov 76) Selectagame (Rifle Project) (Mar 77)	0		
804	Selectagame (Rifle Project) (Mar 77)	0		
805	ruzzie of the Drunken Sailor (Oct 77)			
806	Skeet (Jan 78)	0		
810	Stuff Cycle TV Game (Jun 78)	DO		
811	IV Tank Game (Oct 78)	0		
812 813	vyneel of Fortune (Dec 78)			
814	Race Track Game (Jan 79) The 'Dinky-Die' (Aug 79)	0		
	The Diliky Die (Aug 79)	10		
		10		



Editor Roger Harrison VK2ZTB

Technical Editor David Tilbrook VK2YMI

Project Manager **Phil Wait VK2DKN**

Editorial Staff

William Fisher B.Sc. (Hons) J.B. Scott B.Sc./B.E. (Hons) VK2YBN

Jan Vernon B.A.

Art Direction and technical photography Ivy Hansen

Layout **Bill Crump**

Reader Services Jan Collins

Managing Editor Collyn Rivers

Acoustical Consultants Louis Challis & Associates

Editorial and Sales Office 4th Floor, 15 Boundary St **Rushcutters Bay NSW 2011** Ph: 33-4282; Tlx: 27243

Sales Manager: Bob Taylor Sales Admin: Jan Collins (address as above)

Melbourne Bill Philpott 150 Lonsdale St Melbourne Vic 3000 Ph: 662-1222; Tlx AA34543 Auckland NZ

New Zealand P.O. Box 39163

Adelaide Admedia Group 24 Kensington Rd Rose Park SA 5067 Ph: 332-8144; Tlx AA82182 **United Kingdom** Australian Consolidated Press Ludgate House 107 Fleet St London EC4A 2AL Ph: 353-1040; Tlx: 267163

Brisbane Geoff Horne Agencies 60 Montanus Drive Bellbowrie QLD 4070 Ph: 202-6229

Genzo Uchida Bancho Media Services 15 Sanyeicho Shin juku-Ku Tokyo 160 Ph: 359-8866 Cable: Elbanchorito

Aubrey Barker 133 St Georges Terrace Perth WA 6000

USA Peter Samuel Australian Consolidated Press 444 Madison Avenue New York NY 10022 Ph: 322-3184; Tlx: AA93810 Ph: 751-3383; Tlx: 620892


Electronics Today International is published by Modern Magazines (Holdings) Ltd, 15 Boundary St, Rushcutters Bay, NSW 2011. It is printed (in 1980) by Wilke & Co, Browns Rd, Clayton, Victoria and distributed by Gordon and Gotch. Recommended retail price only.

Reader Enquiries

By Mail: There is no charge for replies but a foolscap-size stamped addressed envelope must be enclosed. Queries relating to projects can only be answered if related to the item as published. We cannot advise on modifications to projects, other than errata or addenda, nor if a project has been modified or if components are otherwise than specified. We try to answer letters as soon as possible. Difficult questions may take time to answer.

By phone: We can only answer readers' technical enquiries by telephone after 4.30 pm. In enquiring by telephone about back issues or photostats. please ask for the "Subscriptions Department" 33-4282

ORDER FORM				
I enclose \$	for (tick appropriate box/es):			
NAME				
ADDRESS	A Deputation of the second	and a state of the		
	POSTCODE	bladara av		
Subscriptions	\$21.50 per year within Australia	\$		
t to conflict 81 of	\$27.00 overseas (surface mail) Airmail rates on application.	\$		
	(\$2.50 from April 1977 on) (\$2.50 per article per issue)			
or photocopies	(\$2.50 per article per issue)			
Project No	Month Year	\$		
Project No	Month Year	\$		
Project No				
Project No	Month Year	\$		
* Please attach a list if more than four required.				
ACTOR STREET, N				
Binders	No @ \$6.10 each in NSW	\$		
DAN MERCHANIA	No @ \$7.50 each other states	\$		
ALL PRICES INCLUDE POSTAGE				
The state of the s				
Send orders to: ETI, 4th Floor, 15 Boundary St,				
RUSHCUTTERS BAY NSW 2011 Phone: (02)33-4282				

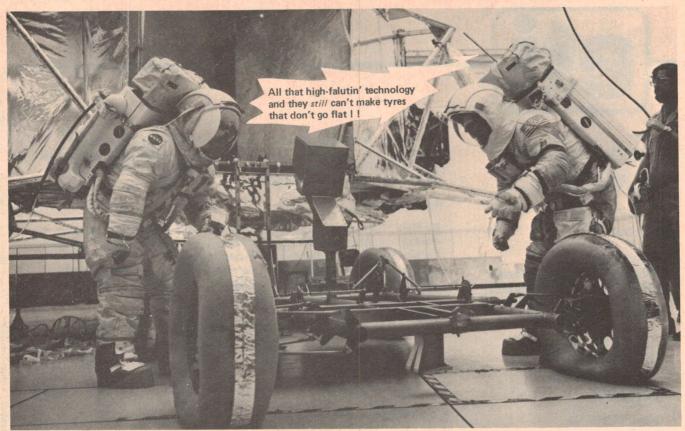

Direct current from the sun?

The idea of using the sun's energy to generate electric power is nothing new. Silicon cells and artificial photosynthesis are probably the best known ideas for harnessing some of the 1.35 kilowatts of radiant energy our local star throws at every square meter of our atmosphere. However, these are really small beer compared to some of the exotic suggestions that have been put forward.

The Australian astronomer, V.A. Bailey, calculated some twenty years ago that the electric potential of the sun relative to the Earth may be around 10¹⁹ volts (give or take an order or two of magnitude). With this kind of potential difference, even a very small current flowing from the sun to the Earth would deliver a lot of power!

But how could such a current be initiated and kept going? In the movies of course, this would be no problem you'd use a laser, just as you do for everything else in sci-fi these days. And would you believe that an American by the name of John Krepak has seriously suggested that a high energy laser fired There were some clever ones this time at the sun could in fact initiate a current around, the standard of puns is getting

space'?

The photons in such a laser would of course need to be guite energetic, so an ultraviolet laser seems the best possibility. Except that there are rumours that the US military (or the CIA, or somebody) is working to develop a gamma ray laser (also known as a 'graser') to use for non-benevolent purposes (naughty, naughty...). The graser seems to be ideal for ionising atoms in space. Coherent gamma rays would probably not only free the orbiting electrons, they might very well smash up the nucleus into fundamental particles.

John Krepak suggests putting a graser on the moon and aiming it at the sun, then using the current from the sun to generate microwave radiation which is beamed to Earth. Remember, you read about it first in Dregs!

More puns

by ionising molecules in the very low noticeably better (or worse, depending density gas that we normally call on your point of view!). Young Chris

Hoffman of Riverstone NSW came up with several, his best being about interfacing a camera to the S100 buss to get a photographic memory! G. Hansper of Tullamarine in Victoria also had several, his best being about boasting of "record-breaking turntable sales". lan Compton of SA had an amusing tale about polylingual puns being punishable and Chris Price of Brookvale NSW had this poem:

"The readers of Dregs got together To think of new ways to make weather Instead of less sun

They each made a pun

Their first (and their last!) get together"

Very good!, but this month's prize goes to Jim McBeath of East Doncaster, Vic, with the following tale:

"Early in World War I, electronic equipment was very heavy and horses were used where portability was needed. The Australian Wireless Corps had only one unit operating at Gallipoli, Morse Cpl. Murphy and his tatty old roan horse. The Turks had no portable units at all. One day Cpl. Murphy was shot and the horse captured. The Turks tried to use the roan and the wireless to intercept the allied morse communication, but the horse proved most unco-operative, killed two Turks and was shot. The moral of this story is: A stolen roan gathers no morse."

UNTILWE DEVELOPED THE STEREO GROOVE, HI-FI WAS PRETTY HO-HUM!



The world of hi-fi owes a lot to the original and continuing innovation of JVC. Few companies, if any, have done as much to help turn records and record-players into the virtual musical instruments they are today . . . or to lead the way in developing so many *firsts* in the more recent concepts of sound amplifiers, cassette decks and computer-designed speaker

systems. Hi-fi, as we know it today, had its beginnings in 1956, with JVC's development of the 45°/45° groove for stereo records. The fact that this system still remains as the world standard is, in itself, outstanding testimony to the technology of JVC. The development revolutionised not only the record-*making* industry, in which we've been involved since 1930; it also paved the way for enormous advancement in the design and engineering of record-playing equipment. Now, hi-fi has expanded to



R-S77. Super-A FM/AM Stereo receiver

embrace a wealth of highly-sophisticated electronic equipment; and it's not surprising that JVC has continued to play a leading role in so much of its development.



HR-3660 EA. VHS Colour Video Cassette recorder

THAT WASN'T OUR ONLY FIRST, EITHER.

We also pioneered Japan's television industry, introducing their first TV receiver just over 40 years ago. A more recent innovation is VHS, the home video recording system now gaining world-wide acceptance as *the* system for such equipment. In the course of staying ahead, we've introduced a number of world *firsts* of radical importance: the Quartz Lock turntable is one of them.

THE QUARTZ LOCK TURNTABLE. MANY TIMES MORE ACCURATE.

It stands to reason that if your equipment is at the top end of the range, then your turntable must be capable of comparable performance. Only Quartz Lock ensures this, tying the speed of the turntable to the unvarying pulse of the atom, and providing a level of accuracy far in excess of conventional turntables.



MORE MILESTONES IN HI-FI.

To match the superb quality of Quartz Lock, we produced the S.E.A. graphic equalizer system. Then we refined it to such a degree it even compensates for the effect your furniture has on sound when it leaves the speakers! To expand the capabilities of tape, we designed ANRS and



SEA-80. Stereo Graphic Equalizer

Super ANRS — automatic noise reduction systems which not only reduce distortion and 'hiss' but actually extend the dynamic range of the tape. Similarly, with speakers: at JVC we employ computers in their design to help provide the ultimate in sound reproduction.

AND NOW, SUPER-A.

In its own way, as significant a hi-fi development as the stereo groove. Imagine an amplifier which combines the *best* features of the two recognised amplifier classes (A and B) ... an amp which combines the *efficiency* of one with the *low distortion* of the other. Some engineers said it couldn't be done; but not those at JVC. Enter the Super-A amplifier ... the *latest* JVC *first!*





THE FUTURE.

It's already with us. For instance, we were so far ahead in the new metal tape technology that our cassette decks were metal-compatible before the tapes were generally available. And now there's the JVC Electro-Dynamic Servo Tonearm, damping tonearm resonance by means of a purely electronic system and two 'thinking' linear motors. Who was it who dubbed JVC, 'the innovators'?



Technics new Class 'A' amp. eliminates 'switching and cross-over distortion' with Class 'B' efficiency.



New Class A circuitry with synchro bias.

Straight DC circuitry for direct coupling between DC power amp section and high-level input signals.

Concentrated power block prevents distortion from electromagnetic induction. ICL phono EQ circuit with ultra-low noise FET's permits use of MC cartridge without pre-preamp or step-up transformer. Independent right and left power supplies using 2 transformers.

105 watts per channel power output at 8 Ohms from 20Hz – 20kHz. 0.007% THDF. Super bass brings the deepest bass sounds to life. Recording selector with 2-way dubbing. Remote action switches.

Technics